

ISCAS Monday 7th May 2001

## All-MOS Subthreshold Log Filters

Francisco Serra-Graells

[paco.serra@cnm.es](mailto:paco.serra@cnm.es)


### Index

- Introduction
- Principle of Operation
- Generalization to Non-Linear Capacitors
- All-MOS Implementation
- Design Examples
- Conclusions



Centro Nacional de Microelectrónica-IMB, Campus UAB, 08193 Bellaterra, Spain


## ► Instantaneous Companding Processing

 

$y \equiv$  Current       $x \equiv$  Voltage

► Log Companding law:  $y = F(x) = e^x$

## ► Subthreshold MOSFET Implementation

 

► EKV model in weak inversion:  $V_{S,DB} > \frac{V_{GB}-V_{TO}}{n}$

$$I_D = I_S e^{\frac{V_{GB}-V_{TO}}{nU_t}} \left( e^{-\frac{V_{SB}}{U_t}} - e^{-\frac{V_{DB}}{U_t}} \right)$$

$$I_S = 2n\beta U_t^2$$

► Application environments:

- High-frequency
- Low-voltage
- **Non-linear capacitive elements?**

► Saturated and non-saturated cells from the author:

- Low-frequency (up to 100KHz)
- Very low-voltage (down to 1V)
- **All-MOS proposal?**

## ► State-Space description of the filter:

$$\begin{cases} \frac{dI}{dt} = AI + BI_{in} \\ I_{out} = CI + DI_{in} \\ \frac{dI_i}{dt} = \sum_{j=1}^N A_{ij} I_j + \sum_{j=1}^M B_{ij} I_{inj} \quad \text{for } i=1 \text{ to } N \end{cases}$$

► Monolithic integration through linear capacitors:

$$\underbrace{C_i \frac{dV_i}{dt}}_{I_{capi}} = \begin{cases} \sum_{j=1}^N I_{tunAij} e^{\frac{V_j - V_i}{nU_t}} + \dots & \text{GD} \\ - \sum_{j=1}^N I_{tunAij} e^{\frac{V_i - V_j}{U_t}} - \dots & \text{SD} \end{cases}$$


## ► Gate- (GD) and Source-Driven (SD) Log functions:

$$I = F(V) = \begin{cases} I_S e^{-\frac{V_{TO} + nV_{bias}}{nU_t}} e^{\frac{V}{nU_t}} & \text{GD} \\ I_S e^{\frac{V_{bias} - V_{TO}}{nU_t}} e^{-\frac{V}{U_t}} & \text{SD} \end{cases}$$

$$I_{tunAij} = \begin{cases} nU_t C_i A_{ij} & \text{GD} \\ U_t C_i A_{ij} & \text{SD} \end{cases}$$

► Equivalent processing in the compressed  $V$ -domain:
 
$$\frac{dV_i}{dt} = \begin{cases} \sum_{j=1}^N nU_t A_{ij} e^{\frac{V_j - V_i}{nU_t}} + \dots & \text{GD} \\ - \sum_{j=1}^N U_t A_{ij} e^{\frac{V_i - V_j}{U_t}} - \dots & \text{SD} \end{cases}$$



► Actual State-Space variable to be controlled:

$$I_{cap i} = \frac{dQ_i}{dt} = C_i \frac{dV_i}{dt} + \frac{dC_i}{dt} V_i = \underbrace{\left( C_i + \frac{dC_i}{dV_i} V_i \right)}_{\text{versus}} \frac{dV_i}{dt}$$

versus


$$C_i \frac{dV_i}{dt} = \begin{cases} \sum_{j=1}^N I_{tunAij} e^{\frac{V_j - V_i}{nU_t}} + \dots & \text{GD} \\ - \sum_{j=1}^N I_{tunAij} e^{\frac{V_i - V_j}{U_t}} - \dots & \text{SD} \end{cases}$$

► Causes of signal distortion:

- Variation of capacitance ( $\frac{dC_i}{dV_i} \neq 0$ )
- Signal range itself ( $V_i$ ) ↳ Minimized in Log Companding!


► Two general approaches:

 - Capacitance compensation ( $C_i$ )
- Tuning-current compensation ( $I_{tunAij}$ )


 
## ► Capacitance Compensation:

$$C_i \doteq C_{oi} \left( 1 + \frac{V_{oi}}{V_i} \right)$$



$$\left( C_i + \frac{dC_i}{dV_i} V_i \right) \equiv C_{oi} \neq f(V_i)$$

Difficult to synthesize in VLSI technologies!

## ► Tuning-Current Compensation:

$$I_{tunAij} = I_{tunoAij} \left( \frac{C_i}{C_{oi}} + \frac{dC_i}{dV_i} \frac{V_i}{C_{oi}} \right)$$

$$I_{tunoAij} \doteq \begin{cases} nU_t C_i A_{ij} & \text{GD} \\ U_t C_i A_{ij} & \text{SD} \end{cases}$$

## ► Non-linear re-shaping:

- Depends on the  $C/V$  law of the capacitor. . .
- . . . but limited to a window of  $< 5U_t$

Available capacitors in digital VLSI technologies?



The MOSFET itself!

► NMOS capacitor proposal:

$$C_i \doteq C_{GG} \equiv C_{GB} + C_{GS} + C_{GD}$$


► Unified EKV model for all regions of inversion:

$$C_i = C_{oxi} \frac{\frac{n-1}{n} + 2\sqrt{IC} \left(1 - e^{-\sqrt{IC}}\right)}{1 + 2\sqrt{IC} \left(1 - e^{-\sqrt{IC}}\right)}$$

$$IC = \ln^2 \left( 1 + e^{\frac{V_i - V_{TO}}{2nU_t}} \right)$$

► Flat regions of capacitance:
 
$$C_i \simeq \begin{cases} \frac{n-1}{n} C_{oxi} & IC \ll 1 \text{ deep weak inv.} \\ C_{oxi} & IC \gg 1 \text{ deep strong inv.} \end{cases}$$



Sweep of  $\pm 20U_t$  around Threshold Voltage


$V_{TO} = 0.5V$  and  $V_{DD} = 1V$  at Room Temperature

► Tuning-current compensation for NMOS capacitance:



$$I_{tunAij} \simeq \begin{cases} \frac{n-1}{n} I_{tunoAij} & IC \ll 1 \\ I_{tunoAij} & IC \gg 1 \end{cases}$$

► Topological compatibility with GD and SD Log functions:
 
$$I_{tunAij} \simeq \begin{cases} \frac{n-1}{n} U_t C_{oxi} A_{ij} & SD \\ n U_t C_{oxi} A_{ij} & GD \end{cases}$$




► Third-order cascaded filter:

  


$$I_{tuno} = U_t C_{ox} 2\pi f_c$$

► Common circuit specifications:

Parameter	Value	Units
Supply Voltage	1.0	V
$(V_{TON} +  V_{TOP} )_{max}$	1.3	V
Full-Scale ( $I_{max}$ )	4	$\mu A_{pp}$
Corner Frequencies @-3dB ( $f_c$ )	500-5000	Hz
Oxide Capacitance per Pole ( $C_{ox}$ )	10	pF
Tuning Currents ( $I_{tuno}$ )	1-10	nA
Technology	1.2	$\mu m$

 

First to third order selection

 

Example for  $K = 10$


Design of the compressed operating point in the  $V$ -domain

- 1V supply voltage
- Third-order selection


}

External linearity in the  $I$ -domain

► MOS-Capacitance Model Requirements:

 

 BSIM1 for a  $1.2\mu\text{m}$  VLSI technology



BSIM3 for a  $0.35\mu\text{m}$  VLSI technology

► Currently working on an analytical approximation of  $C_i$  for GD cells ◀

► Si Area Savings or Dynamic Range Improvements:

Parameter	Process A	Process B	Units
$\lambda$	1.2	0.35	$\mu\text{m}$
$t_{oxgate}$	18.5	7.5	nm
$C_{gate}$	1.87	4.6	$\text{fF}/\mu\text{m}^2$
$t_{oxpoly}$	50	40	nm
$C_{poly}$	0.69	0.86	$\text{fF}/\mu\text{m}^2$
$C_{gate}/C_{poly}$	2.7	<b>5.4</b>	-

► Constant Power:

$$A_{gate} < \frac{A_{poly}}{5} \quad I_{tun, gate} \equiv I_{tun, poly}$$

► Constant Si Area:

$$A_{gate} \equiv A_{poly} \quad I_{tun, gate} > 5I_{tun, poly}$$

$$SNR_{thermal} \propto 20 \log \sqrt{I_{tun}}$$

$$DR_{gate} > DR_{poly} + 7\text{dB}(1\text{bit})$$



$$C_{poly} = 45\text{pF} \quad C_{gate} = 243\text{pF!!}$$

- ▶ Non-linear capacitance  $\equiv$  local tuning-current compensation
- ▶ NMOS capacitors compatible with existing CMOS cells
- ▶ Distortion strongly related to compressed operating point
- ▶ Important Si area savings or Dynamic Range improvements
- ▶ Suitable for 1V analog circuits in digital VLSI technologies