

**1V sub-100 $\mu$ W 12b all-MOS  
 $\Sigma\Delta$  A/D Converters  
in the Log-Domain**

**Francisco Serra-Graells**

paco.serra@cnm.es


Wednesday 20th Nov 2002

- ▶ Introduction to  $\Sigma\Delta$  ADC
- ▶ All-MOS Log-Domain Proposal
- ▶ Low-Voltage Basic Building Blocks
- ▶ Second-Order Effects
- ▶ Design Examples
- ▶ Conclusions

- ▶ Portable and mixed SoCs
- ▶ Digital CMOS technologies

↓  
low-power  $\Sigma\Delta$  ADCs

↓  
low-voltage all-MOS

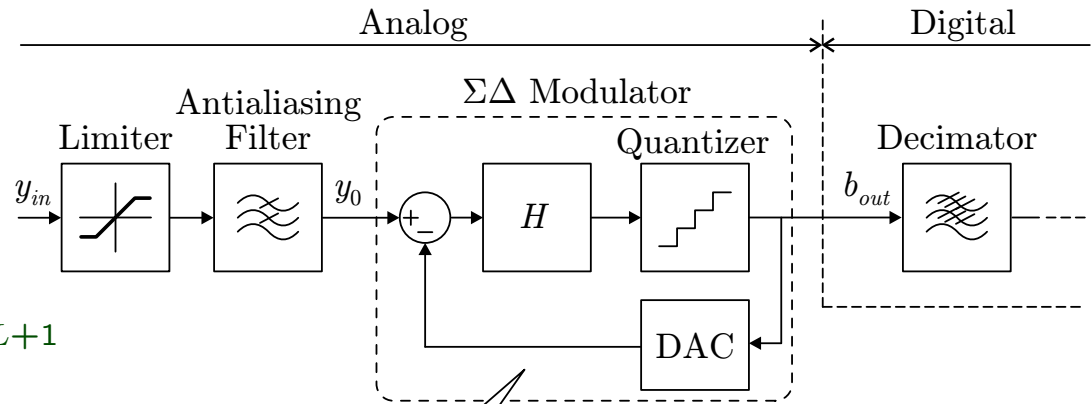


$$DR_{ideal} = \frac{3\pi}{2} (2^N - 1)^2 (2L + 1) \left(\frac{M}{\pi}\right)^{2L+1}$$

$M$ -oversampling ratio

$L$ -order frequency selective  $H$ -stage

$N$ -bit quantization

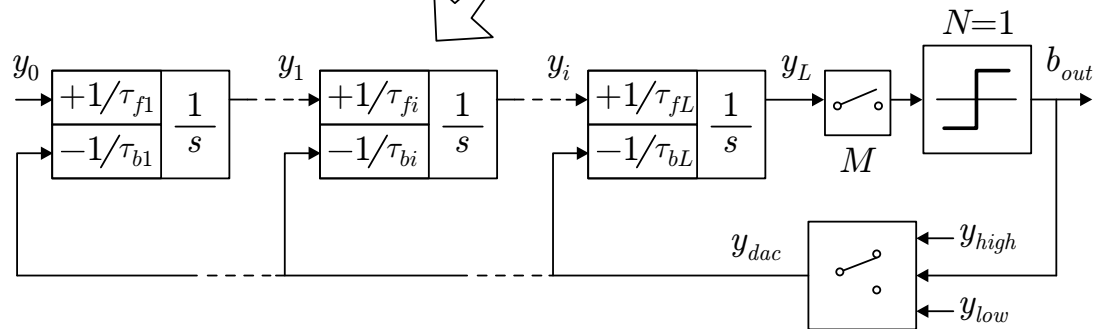

- ▶ 1bit → no linearity problems at Quantizer/DAC



- ▶ Single-stage → compact circuits

$$\frac{d\bar{Y}_{ss}}{dt} = \begin{bmatrix} 0 & 0 & 0 \\ \frac{1}{\tau_{f1}} & 0 & 0 \\ 0 & \frac{1}{\tau_{fL}} & 0 \end{bmatrix} \bar{Y}_{ss} + \begin{bmatrix} \frac{1}{\tau_{f1}} \\ 0 \\ 0 \end{bmatrix} y_0 + \begin{bmatrix} -\frac{1}{\tau_{b1}} \\ -\frac{1}{\tau_{bi}} \\ -\frac{1}{\tau_{bL}} \end{bmatrix} y_{dac}$$

- ▶ Introduction to  $\Sigma\Delta$  ADC
- ▶ All-MOS Log-Domain Proposal
- ▶ Low-Voltage Basic Building Blocks
- ▶ Second-Order Effects
- ▶ Design Examples
- ▶ Conclusions

► Instantaneous Comanding theory

► MOSFET operating in subthreshold

  

weak inversion  
 $V_{SB,DB} \gg \frac{V_{GB}-V_{T0}}{n}$   
 forward saturation  
 $V_{DB} - V_{SB} \gg U_t$

$$y = F(x) = e^x$$

$$I_D = I_S e^{\frac{V_{GB}-V_{T0}}{nU_t}} e^{-\frac{V_{SB}}{U_t}} \quad I_S = 2n\beta U_t^2$$

$$\frac{dy_i}{dt} = \frac{1}{\tau_{fi}} y_{i-1} \xleftrightarrow{F} \frac{dx_i}{dt} = \frac{1}{\tau_{fi}} e^{x_{i-1}-x_i}$$

GD, SD or BD Comanding:

$$y_i = \frac{I_{Di}}{I_S} \xleftrightarrow{F} x_i = \frac{V_{GBi}}{nU_t}$$



► Pros & cons:

- Internal  $DR_V$  compression → True low-voltage operation ✓  
 Compatible with non-linear caps (e.g.MOS) ✓
- Subthreshold operation → Low-power consumption ✓  
 Low-frequency applications (typ.<1MHz) ×

- ▶ Introduction to  $\Sigma\Delta$  ADC
- ▶ All-MOS Log-Domain Proposal
- ▶ **Low-Voltage Basic Building Blocks**
- ▶ Second-Order Effects
- ▶ Design Examples
- ▶ Conclusions

► CMOS circuit techniques for:

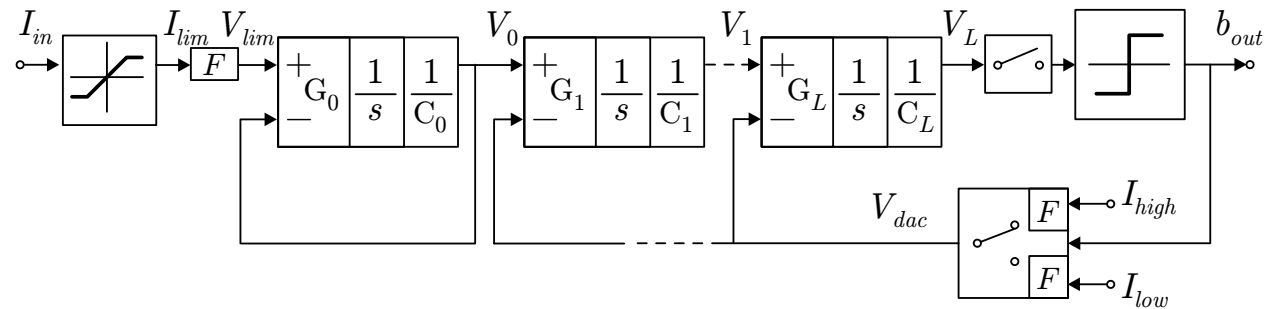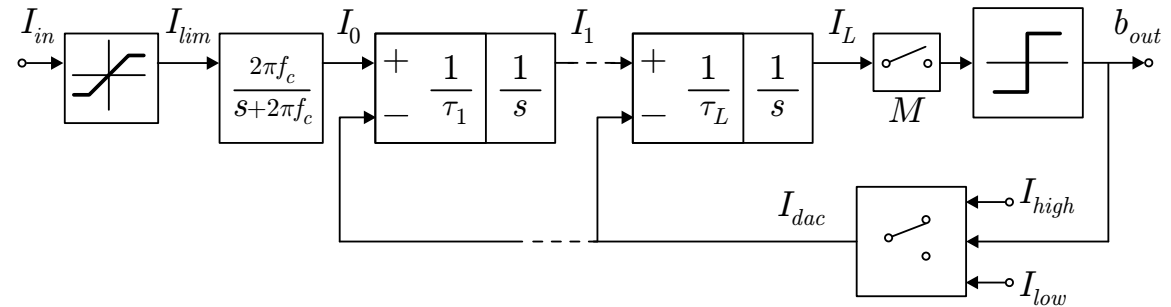- Input compressor and limiter
- Anti-aliasing filter
- Modulator integrator
- Modulator quantizer
- Modulator DAC



► Target specs:

- Very low-voltage (1V)
- Digital Technology (MOS-only)
- Audio bandwidth
- Low-power (sub-100μW)

► Application example: Hearing Aids

## ► Input compressor


$$I = F(V) = I_{ref} e^{\frac{V - V_{ref}}{nU_t}} \quad I > 0$$

Class-A operation:

$$V_{in} = V_{ref} + nU_t \ln \left( \frac{I_{in}}{I_{ref}} + 1 \right) \quad |I_{in}| < I_{ref}$$

Simple frequency compensation:
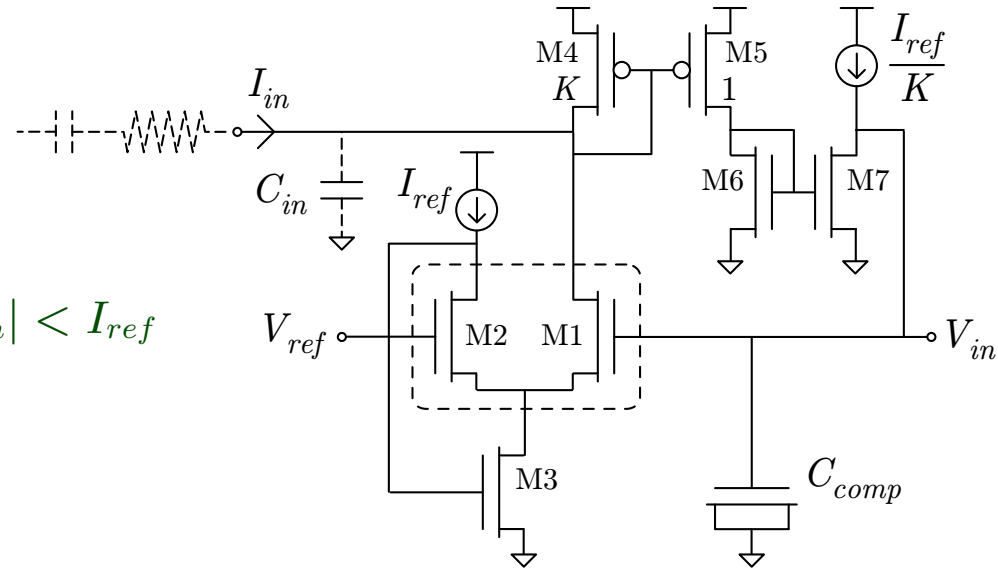
$$\zeta = \frac{1}{2} \sqrt{\frac{KC_{comp}}{C_{in}}}$$





- $I_{ref}$  defines full-scale in Class-A
- $V_{ref}$  optimizes low-voltage operation
- Low input impedance ( $< 1K\Omega$ ) for optional linear  $V \rightarrow I$  conversion at input



► Input compressor with limiter

$$I_{lim} = \begin{cases} I_{ref} + I_{in} & |I_{in}| \leq I_{knee} \\ I_{ref} + \frac{I_{in} \pm PI_{knee}}{1+P} & |I_{in}| > I_{knee} \end{cases}$$

piece-wise transfer function:

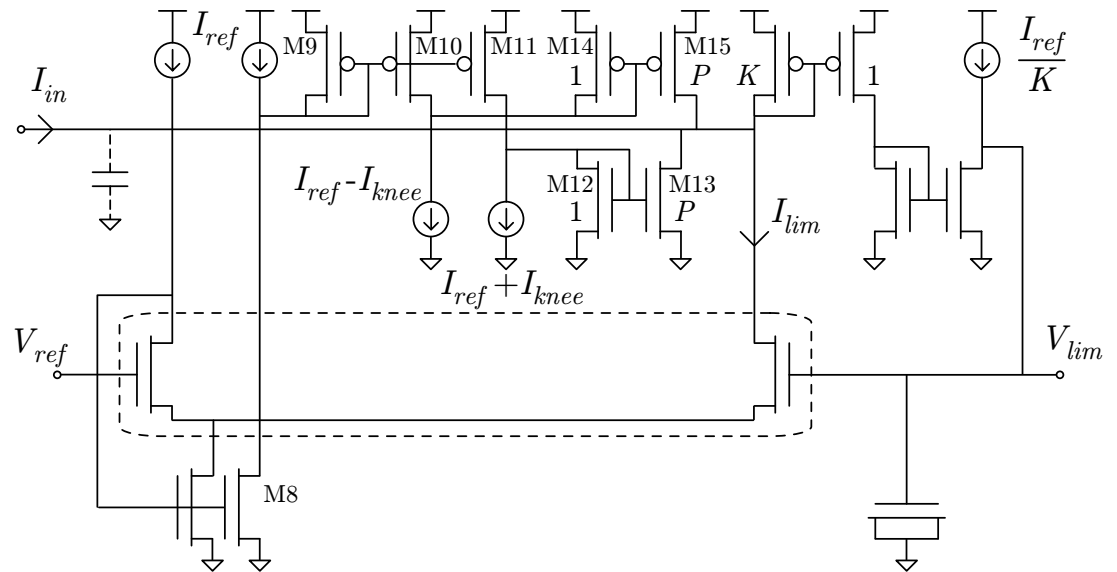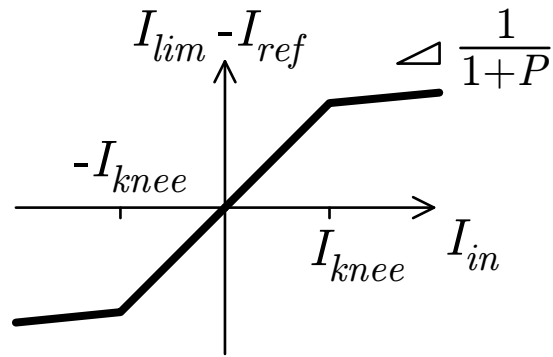

- $I_{knee}$  selects the input threshold
- $P$  defines compression ratio

► Anti-aliasing filter

*I*-domain 1st-order low-pass ODE:

$$\frac{dI_0}{dt} = -2\pi f_c I_0 + 2\pi f_c I_{lim}$$


*V*-domain non-linear ODE:

$$\frac{dV_0}{dt} = -2\pi f_c n U_t + 2\pi f_c n U_t e^{\frac{V_{lim} - V_0}{n U_t}}$$

*Q*-domain circuit ODE:

$$\frac{dQ_0}{dt} = \underbrace{C_0}_{I_{cap0}} \frac{dV_0}{dt} = -I_{tun0} + I_{tun0} e^{\frac{V_{in} - V_0}{n U_t}}$$
 
$$f_c = \frac{1}{2\pi} \frac{I_{tun0}}{n U_t C_0}$$



- Tuning parameter  $I_{tun0}$
- Thermal cancellation for  $f_c$  through PTAT  $I_{tun0}$
- Non-linear NMOS capacitor  $C_0$

## ► Modulator Integrator

$I$ -domain ODE for the  $\tau_{fi}$  case:

$$\frac{dI_i}{dt} = \frac{1}{\tau_{fi}} I_{i-1}$$

$V$ -domain non-linear ODE:


$$\frac{dV_i}{dt} = \frac{nU_t}{\tau_{fi}} e^{\frac{V_{i-1}-V_i}{nU_t}}$$

$Q$ -domain circuit ODE:

$$\frac{dQ_i}{dt} = \underbrace{C_i \frac{dV_i}{dt}}_{I_{capi}} = I_{tunfi} e^{\frac{V_{i-1}-V_i}{nU_t}}$$

$$\tau_{fi} = \frac{nU_t C_i}{I_{tunfi}}$$

positive  $\tau_{fi}$  case:

 

- Tuning parameter  $I_{tunfi}$
- Thermal cancellation for  $\tau_{fi}$  through PTAT  $I_{tunfi}$
- Non-linear NMOS capacitor  $C_i$


Log-mapping (i.e.  $I > 0$ ) → coefficients only charge xor discharge caps!

► Modulator Integrator

$\Sigma\Delta$  modulator case ( $\tau_{fi} > 0$   $\tau_{bi} < 0$ ):

OP designed at SS-matrix level:
 
$$\frac{d\bar{I}_{ss}}{dt} = \begin{bmatrix} 0 & 0 & 0 \\ \frac{1}{\tau_{fi}} & 0 & 0 \\ 0 & \frac{1}{\tau_{fL}} & 0 \end{bmatrix} \bar{I}_{ss} + \begin{bmatrix} \frac{1}{\tau_{f1}} \\ 0 \\ 0 \end{bmatrix} I_0 + \begin{bmatrix} -\frac{1}{\tau_{b1}} \\ -\frac{1}{\tau_{bi}} \\ -\frac{1}{\tau_{bL}} \end{bmatrix} I_{dac}$$



In general, matrix transformation may be required to ensure DC solution for  $I > 0 \dots$


Differential integrator:

Coefficients of the same row can share half circuitry

$$\frac{dQ_i}{dt} = \underbrace{C_i \frac{dV_i}{dt}}_{I_{capi}} = \boxed{I_{tunfi} e^{\frac{-V_i}{nU_t}}} \left( e^{\frac{V_{i-1}}{nU_t}} - \frac{\tau_{fi}}{\tau_{bi}} e^{\frac{V_{dac}}{nU_t}} \right)$$
 
## ► Modulator Quantizer


$$b_{out} = \begin{cases} 1 & \text{for } V_L > V_{ref} \\ 0 & \text{for } V_L < V_{ref} \end{cases}$$




## ► Modulator DAC

$$V_{dac} = V_{ref} + \begin{cases} nU_t \ln \left( \frac{I_{high}}{I_{ref}} \right) & \text{for } b_{out} = 1 \\ nU_t \ln \left( \frac{I_{low}}{I_{ref}} \right) & \text{for } b_{out} = 0 \end{cases}$$

## I-domain switching scheme:

 


## V-domain switching scheme:

 

- ▶ Introduction to  $\Sigma\Delta$  ADC
- ▶ All-MOS Log-Domain Proposal
- ▶ Low-Voltage Basic Building Blocks
- ▶ **Second-Order Effects**
- ▶ Design Examples
- ▶ Conclusions


## ► Moderate Inversion

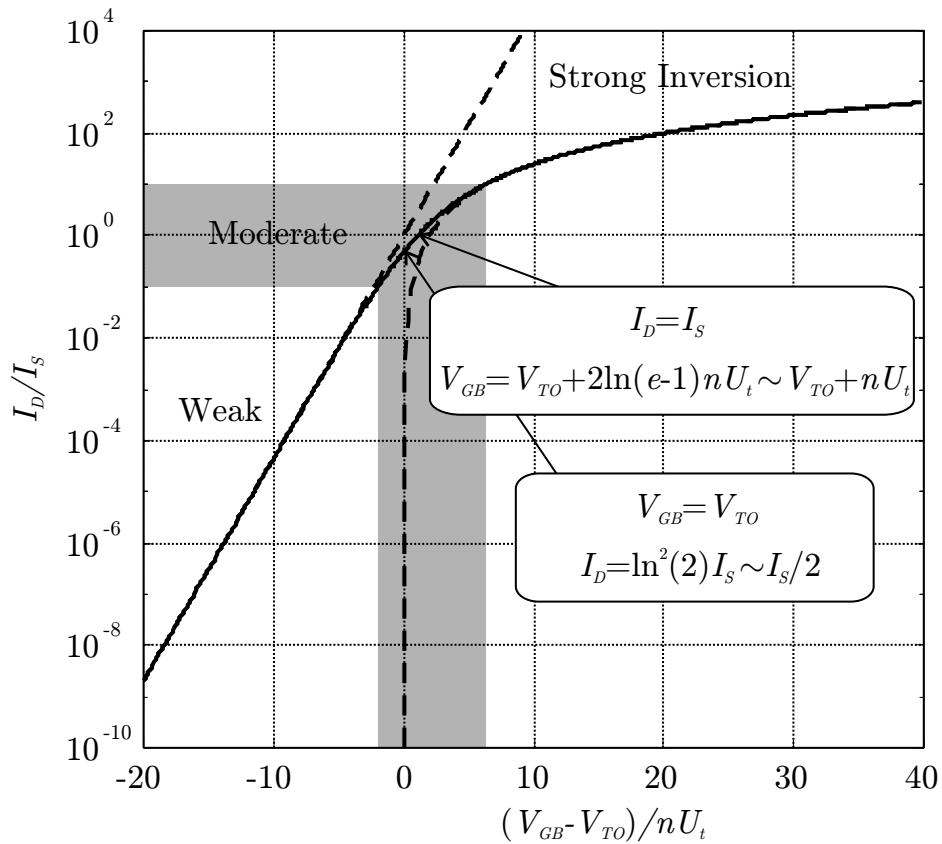

$$I_D = I_S e^{\frac{V_{GB} - V_{TO}}{nU_t}} e^{-\frac{V_{SB}}{U_t}} \quad IC = \frac{I_D}{I_S} \ll 1$$

$$I_D = I_S \ln^2 \left( 1 + e^{\frac{V_{GB} - V_{TO}}{2nU_t}} e^{-\frac{V_{SB}}{2U_t}} \right)$$

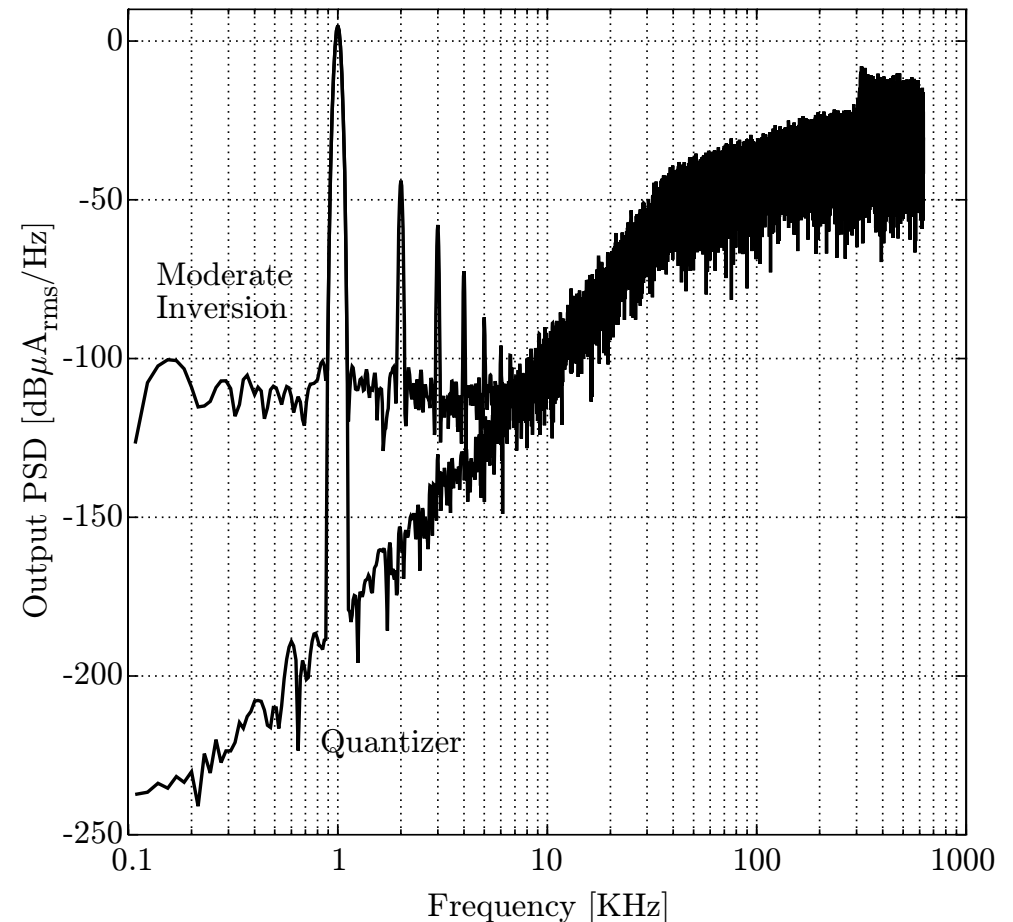- $e^x$  degradation causes signal distortion
- Wide ( $W/L$ ) to keep devices in deep weak inversion even at full-scale



## ► Thermal Noise

Equivalent Drain-current noise PSD:

$$\frac{di_{Dn}^2}{df} = 4KT \frac{g_{ms}}{2}$$


At similar biasing, dominant devices are those in weak inversion where  $(g_{ms}/I_D)_{max}$ :

$$\frac{di_{Dn}^2}{df} = 2qI_D \quad \frac{dv_{GBn}^2}{df} = 2q \frac{(nU_t)^2}{I_D}$$

Main blocks are the compressor, anti-aliasing, 1st integrator and DAC, so:

$$I_{ref} \equiv I_{tun0} \equiv I_{tunf1} \equiv I_{buffer}$$

... block contributions:

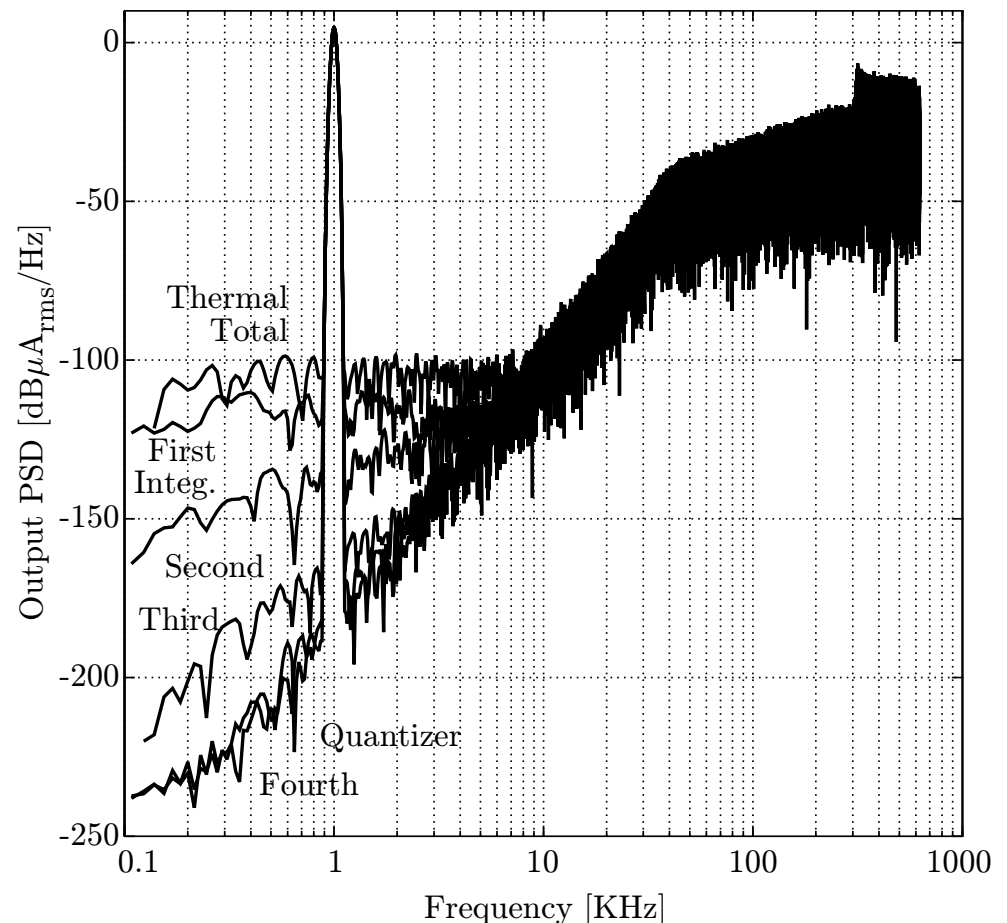

• Class-A operation results in:

$$SNR \propto +3dB/oct(I_{ref})$$



## ► NMOS Capacitors

Quasi-static Gate-to-Gate NMOS capacitance in all regions ( $V_{SB,DB}=0$ ):

$$C_i = C_{oxi} \frac{\frac{n-1}{n} + 2\sqrt{IC} (1 - e^{-\sqrt{IC}})}{1 + 2\sqrt{IC} (1 - e^{-\sqrt{IC}})}$$


$$IC = \ln^2 \left( 1 + e^{\frac{V_i - V_{TO}}{2nU_t}} \right)$$

for strong inversion ( $IC > 1$ ):

$$C_i \simeq C_{oxi} \left( 1 - \frac{U_t}{V_i - V_{TO}} \right)$$

Non-exact processing:
 
$$\frac{dQ_i}{dt} = \left( C_i + \frac{dC_i}{dV_i} V_i \right) \frac{dV_i}{dt} \quad \longrightarrow \quad \frac{dV_i}{dt} = \frac{I_{tuni}}{C_{oxi}} \frac{e^{-\frac{V_i}{nU_t}}}{1 + \frac{V_{TO}U_t}{(V_i - V_{TO})^2}} \left( e^{\frac{V_i - 1}{nU_t}} - e^{\frac{V_{dac}}{nU_t}} \right)$$



- Minimizing non-linearity through proper biasing:  $V_{ref} > V_{TO}$

► **Waveform Asymmetry**


Unbalanced DAC symbols:  $WA \doteq \frac{\int_{1/f_s} (I_{dac0 \rightarrow 1} - I_{low}) dt - \int_{1/f_s} (I_{dac1 \rightarrow 0} - I_{high}) dt}{2(I_{high} - I_{low})/f_s} \neq 0$

First-order model  $\tau_{rise}$  &  $\tau_{fall}$

Null  $WA$  conditions:

$$\begin{cases} \tau_{fall} = \tau_{rise} & I\text{-switching} \\ \tau_{fall} = \sqrt{\frac{I_{high}}{I_{low}}} \tau_{rise} & V\text{-switching} \end{cases}$$

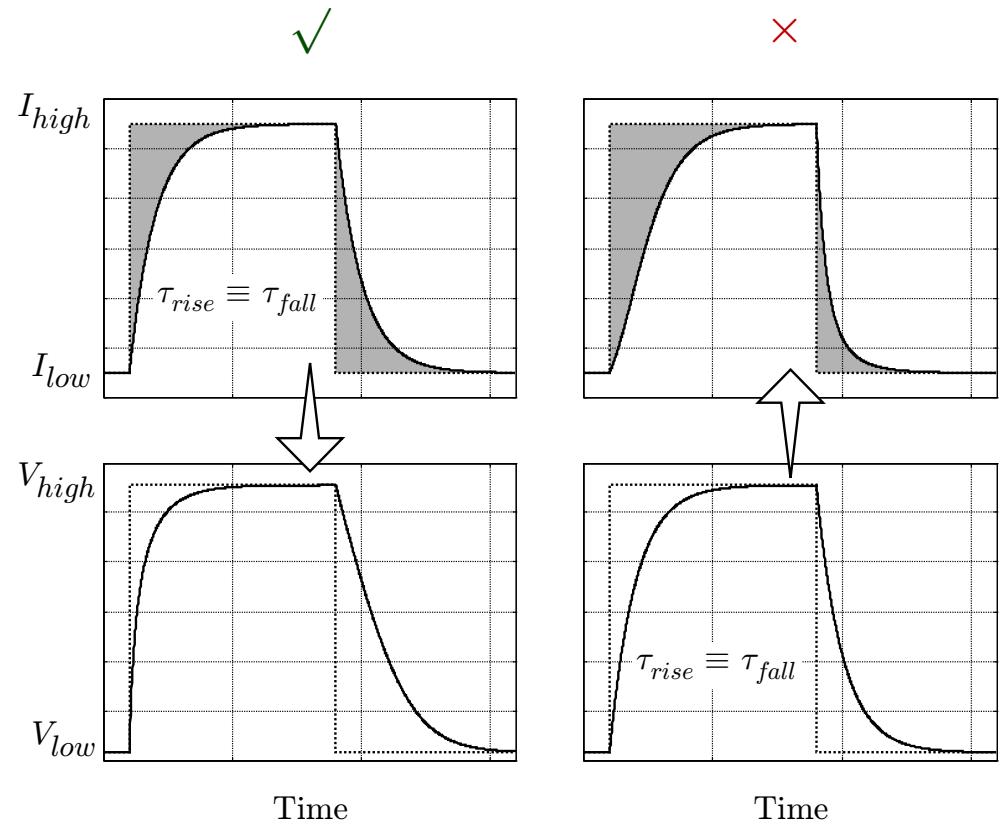When code dependent,  
 $WA$  generates white noise.




Minimizing  $WA$  effects at DAC by:

- Increasing absolute speed
- Achieving symbol symmetry
- Ensuring sequence-independence

- ▶ Introduction to  $\Sigma\Delta$  ADC
- ▶ All-MOS Log-Domain Proposal
- ▶ Low-Voltage Basic Building Blocks
- ▶ Second-Order Effects
- ▶ Design Examples
- ▶ Conclusions

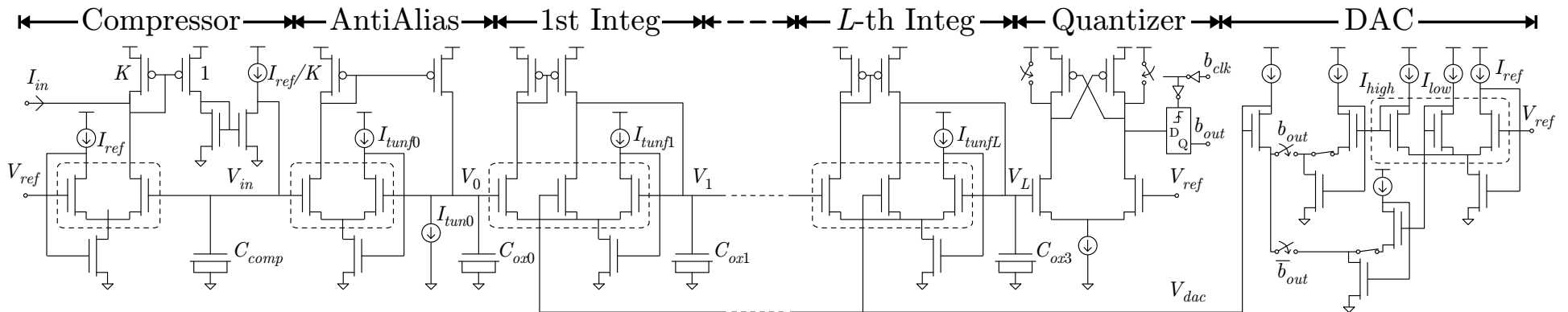
► 3rd- and 4th-order 1bit 64-oversampling  $\Sigma\Delta$  ADCs for Hearing Aids:




► Target specs in 0.35  $\mu$  digital CMOS technology:

Supply Voltage	1.0	V
Max. $V_{TON} +  V_{TOP} $	1.3	V
Input Full-Scale	10	$\mu A_{pp}$
Input Bandwidth	0.1-8	KHz
Dynamic Range	73	dB
Power Consumption	75	$\mu W$
Si Area	<0.5	$mm^2$

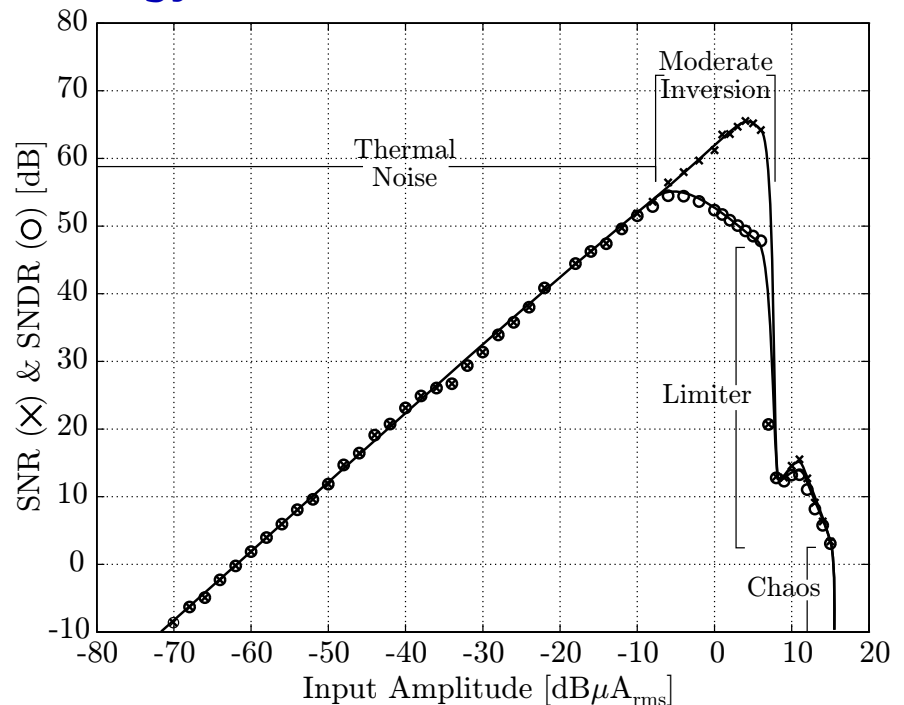$I_{ref} = 6 \mu A$ ,  $I_{tuni} \in (0.2, 6) \mu A$ ,  $C_{oxi} \in (80, 500) pF$



 - ▶ Prototypes: expected 12b  $\rightarrow$  <10b 😞  
 ... due to not modeling  $WA$  !!!



- ▶ Proposed solution:


return-to-zero ( $t_{rz}$ ) symbols +

$$\tau_{bi} = \frac{t_{rz}}{T_s} \tau_{fi} \text{ compensation}$$



code independent  $WA$

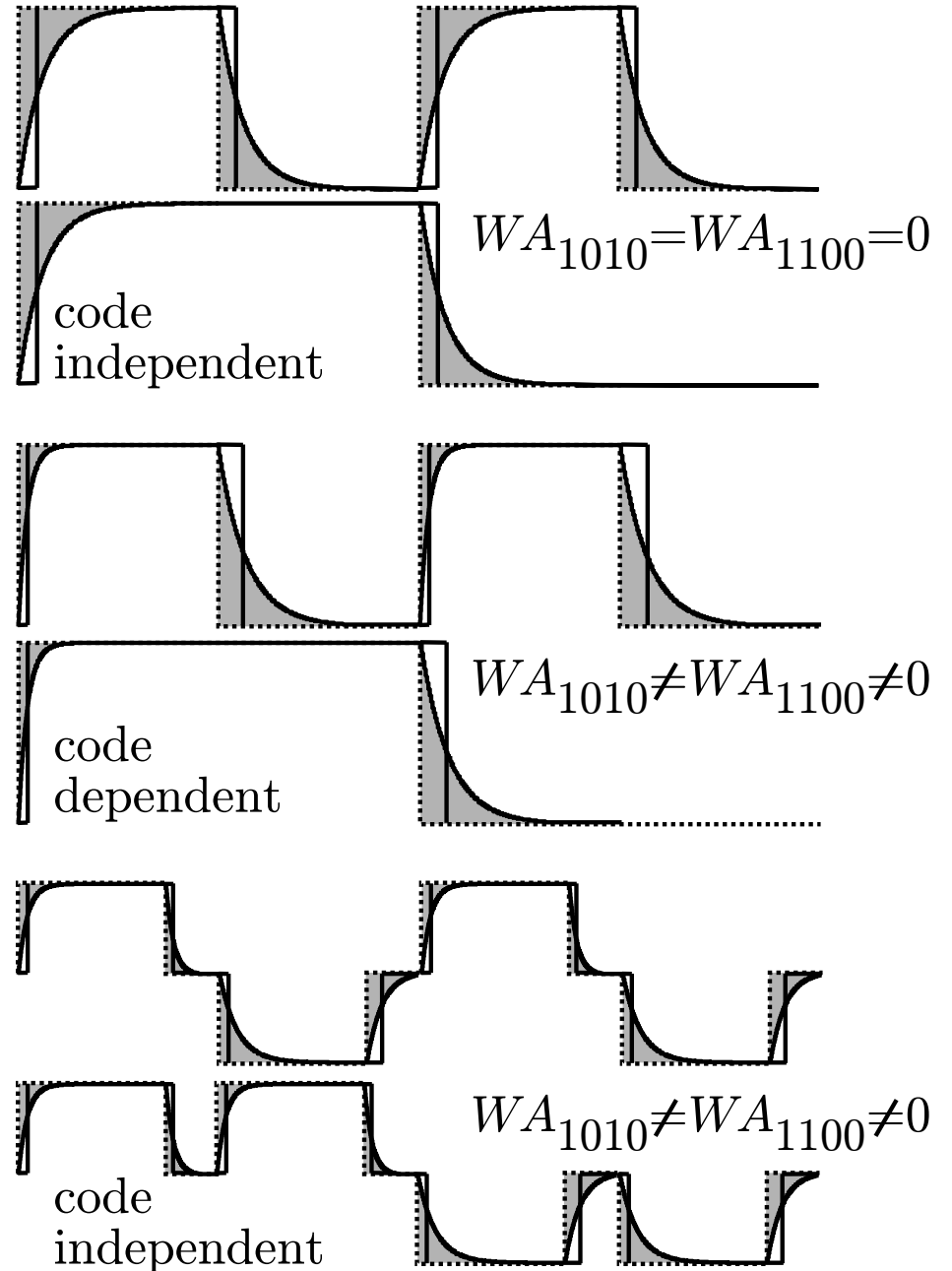- ▶ High-level models of new designs return good results... 😊



- ▶ Introduction to  $\Sigma\Delta$  ADC
- ▶ All-MOS Log-Domain Proposal
- ▶ Low-Voltage Basic Building Blocks
- ▶ Second-Order Effects
- ▶ Design Examples
- ▶ **Conclusions**

- ▶ Possibility of implementing  $\Sigma\Delta$  ADCs in the Log-domain using the MOSFET in weak inversion
- ▶ Complete set of low-voltage all-MOS basic building blocks
- ▶ Detailed modeling of main second-order effects
- ▶ Expected  $1V@100\mu A$  12b@8KHz realizations in short for audio SoCs (e.g. HAs)
- ▶ Circuit technique suitable for digital VLSI technologies

... Thank you very much for your attention!