

# How to Make Your Integrated Sensor Smarter

Francesc Serra-Graells<sup>1,2</sup>

`paco.serra@imb-cnm.csic.es`

<sup>1</sup>Integrated Circuits and Systems (ICAS)  
Instituto de Microelectrónica de Barcelona, IMB-CNM(CSIC)

<sup>2</sup>Dept. of Microelectronics and Electronic Systems  
Universitat Autònoma de Barcelona


Sep 2015

- 1 What is Missing?
- 2 Too Tiny to Be Touched
- 3 Process & Matching Nightmares
- 4 Biasing Specials
- 5 Flexibility as a Must
- 6 Massive Parallel Processing
- 7 Power-Aware Design
- 8 When Package Matters
- 9 My Nice Smart Sensor

- 1** What is Missing?
- 2** Too Tiny to Be Touched
- 3** Process & Matching Nightmares
- 4** Biasing Specials
- 5** Flexibility as a Must
- 6** Massive Parallel Processing
- 7** Power-Aware Design
- 8** When Package Matters
- 9** My Nice Smart Sensor
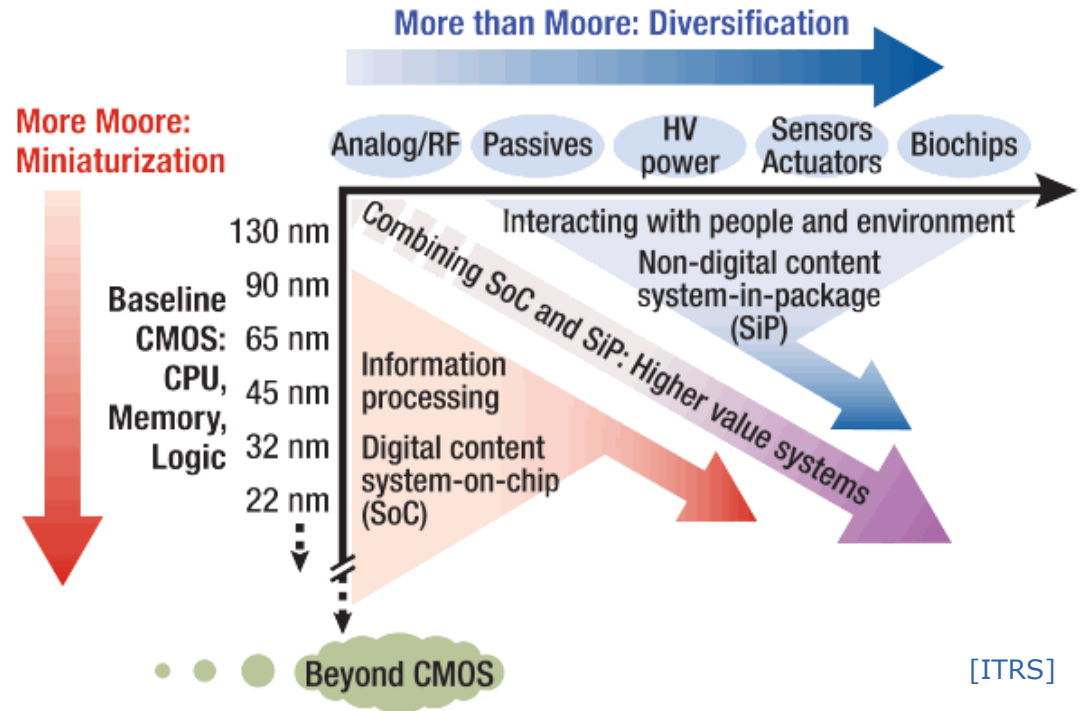
## More than Moore

- ▶ Technology **diversification** versus pure scaling
- ▶ Not only information processing applications but also **sensing**, communications, power control...
- ▲ **Ubiquitous** computing
- ▼ Interaction with the real **multi-domain** world! (physics, chemistry, biology, medicine...)






- ▲ New market demands for **custom smart sensors** as core of heterogeneous systems

# What is Missing


▼ Why some sensors are not smart enough to reach **application** stage?

**device** → **circuit** → **system**

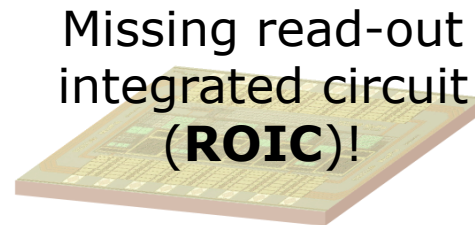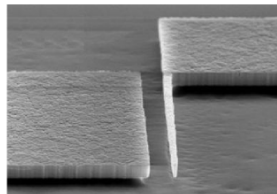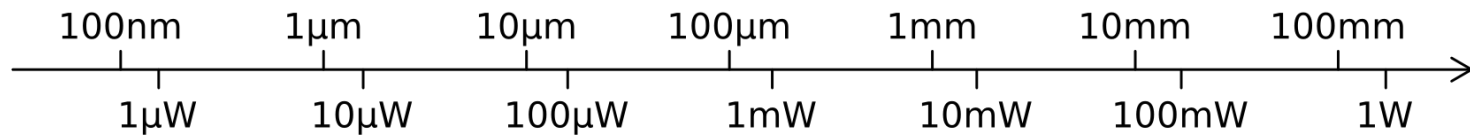

**Micro world**



**Macro world**

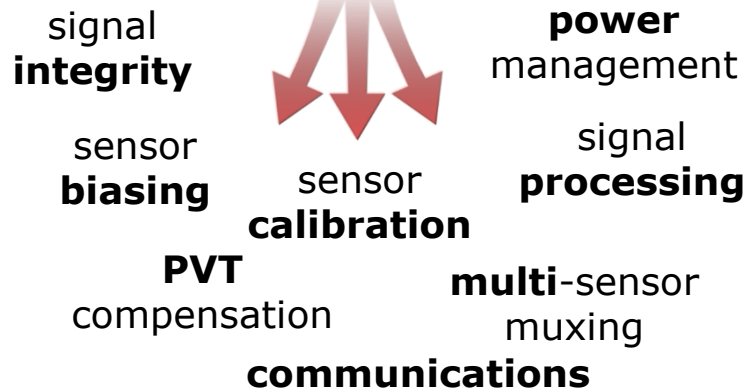


## What is Missing

- ▼ Why some sensors are not smart enough to reach **application** stage?

**device** → **circuit** → **system**

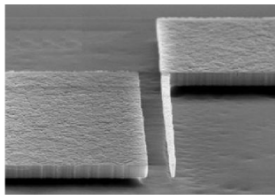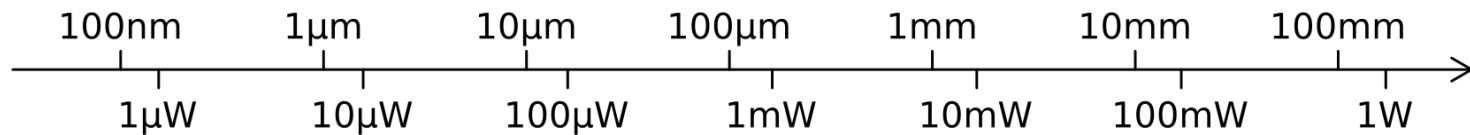

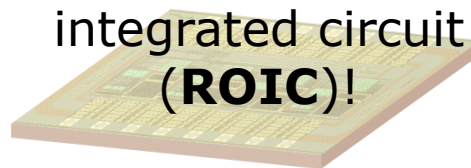Missing read-out  
integrated circuit  
(**ROIC**)!



**Micro  
world**

- Technology compatibility
- Device modeling
- Yield optimization




- Apps specs
- Controllability & observability
- Packaging strategy

**Macro  
world**

- ▼ **Multi-disciplinary** design work can be a hard task
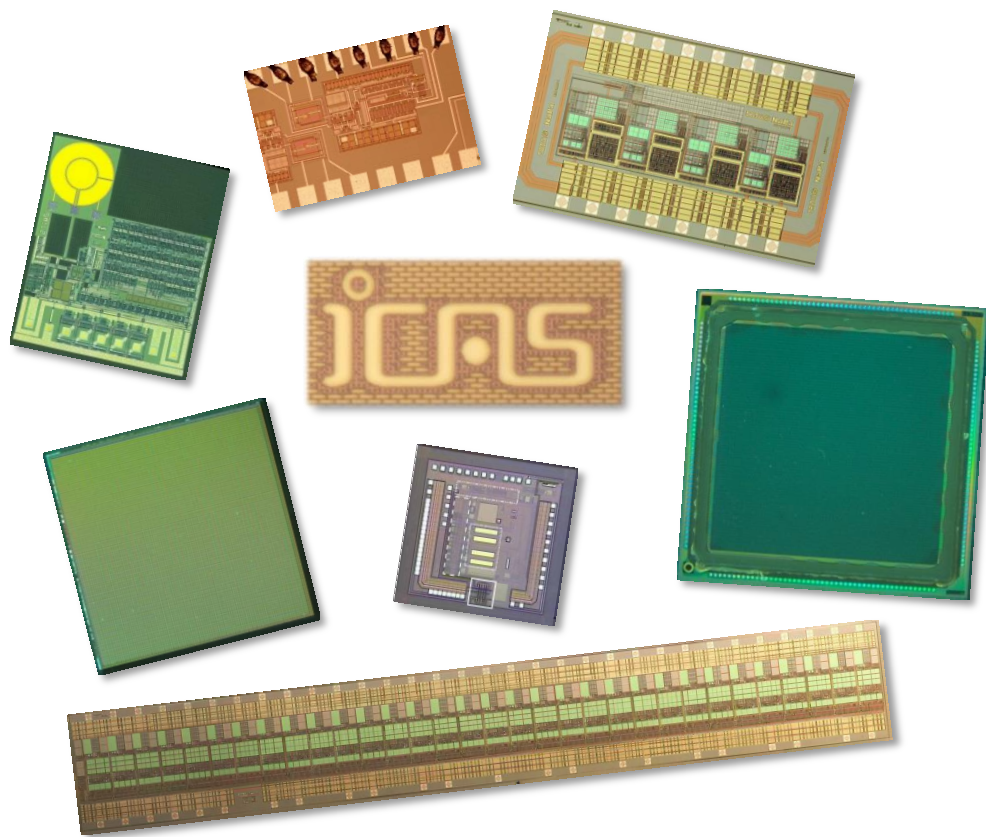
## Filling the Gap

- ▶ Each smart sensor usually requires its own **custom ROIC!**
- ▶ General ROIC figures of merit (**FOMs**):
  - **Small size** for light packaging, aggressive system scaling and ubiquity
  - **Low power** for extended operative life, minimum overheating and local energy harvesting
  - **Low cost** for mass production, disposable products and multi-sensory applications
- ▶ **Real smart sensor examples** developed by ICAS group at IMB-CNM(CSIC):








- 1 What is Missing?
- 2 Too Tiny to Be Touched
- 3 Process & Matching Nightmares
- 4 Biasing Specials
- 5 Flexibility as a Must
- 6 Massive Parallel Processing
- 7 Power-Aware Design
- 8 The Shrinking Packaging
- 9 My Nice Smart Sensor



## Too Tiny to Be Touched

- **ROIC** first challenge is to link the **micro** and **macro** worlds by supplying the needed **scaling**
- |                              |  |
|------------------------------|--|
| ■ Sensor <b>signal</b> power | ■ Signal <b>integrity</b>              |
| ■ Sensor <b>geometry</b>     | ■ <b>Connectivity</b>                  |
| ■ Sensor <b>impedance</b>    | ■ Protection against <b>parasitics</b> |

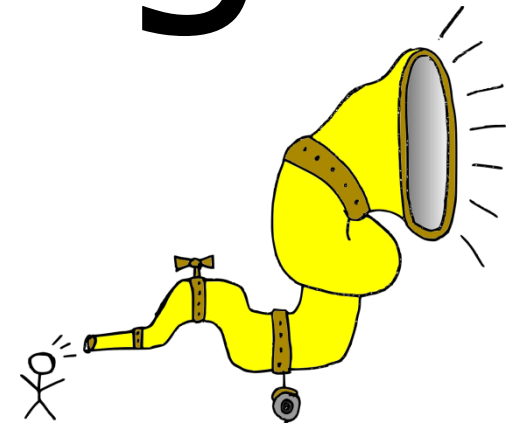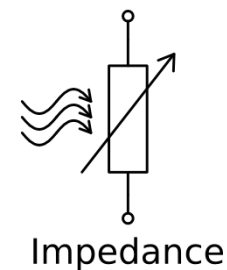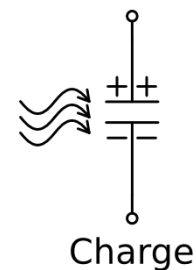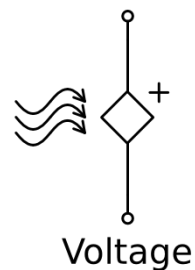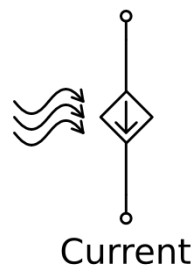- ▼ Minimum **area** and **power** overheads wanted
- ▼ Not all **integrated** sensors operate in the same signal domain, e.g.:



## NEMS Resonator Characterization

# NaPa



- ▶ Applications in quartz **crystal** monolithic replacement, accurate **mass** sensor and more...

- ▶ **Mechanical** resonator at frequencies exceeding MHz

- ▲ CMOS post-processed using nanostencil lithography (nSL) at **wafer level**

- ▲ Very high **Q factors**

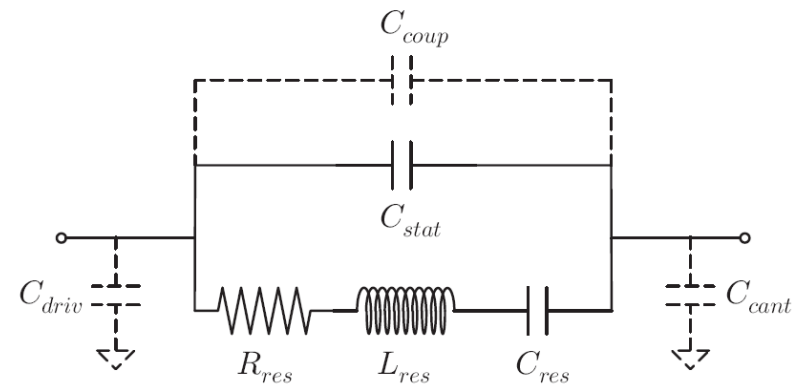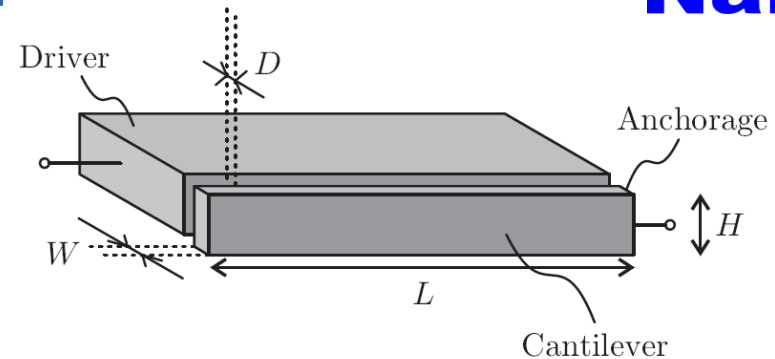- ▼ Accurate **modeling** needed in terms of **size, materials** and package air **pressure**



$$f_{res} = \frac{1.015}{2\pi} \sqrt{\frac{E}{\rho}} \frac{W}{L^2}$$


Parameter	Value	Units
$W$	265	nm
$L$	14.5	$\mu\text{m}$
$H$	580	nm
$D$	650	nm

## NEMS Resonator Characterization

- ▶ ROIC designed for the solely purpose of sensor **characterization**

- ▶ **Interface** challenge:

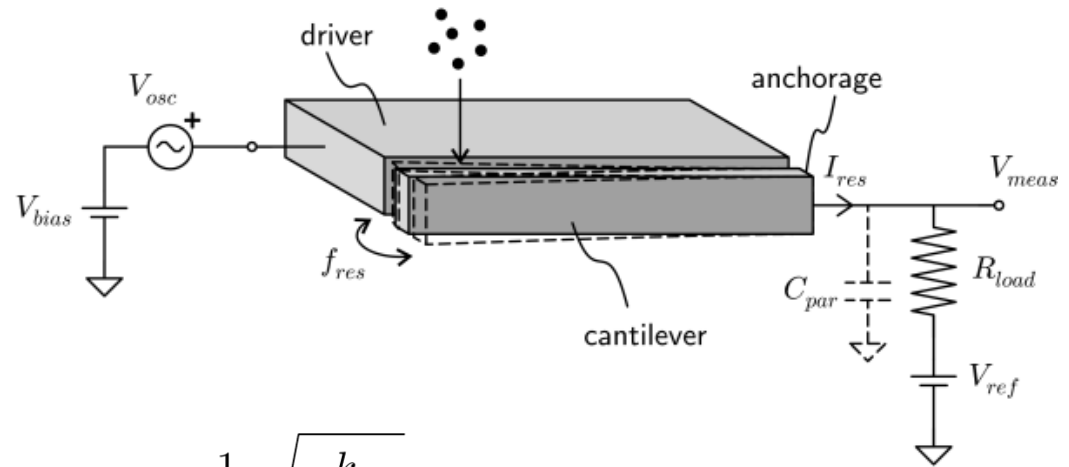- Current-mode read-out
- Weak signal (nA)
- Parasitic capacitance



$$f_i = \frac{1}{2\pi} \sqrt{\frac{k_i}{m_{eff}}}$$

$$I_{res} = \frac{dQ_{res}}{dt} \simeq C_{stat} \frac{dV_{osc}}{dt} + (V_{bias} - V_{ref}) \frac{dC_{mot}}{dt}$$

# NEMS Resonator Characterization

- ▶ ROIC designed for the solely purpose of sensor **characterization**



- ▶ **Interface** challenge:

- Current-mode read-out
- Weak signal (nA)
- Parasitic capacitance

- ▶ **Current conveyor (CII)** based ROIC:




- Low input impedance
- Output current scaler
- Built-in bias generator
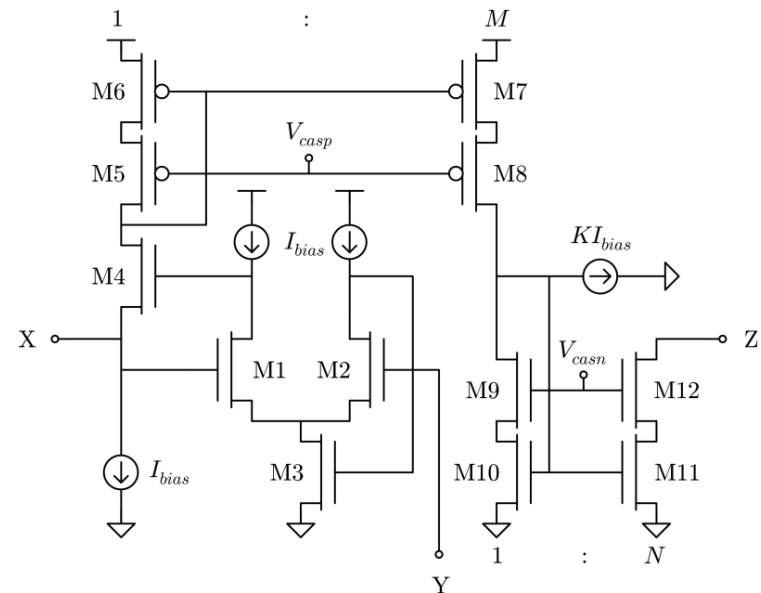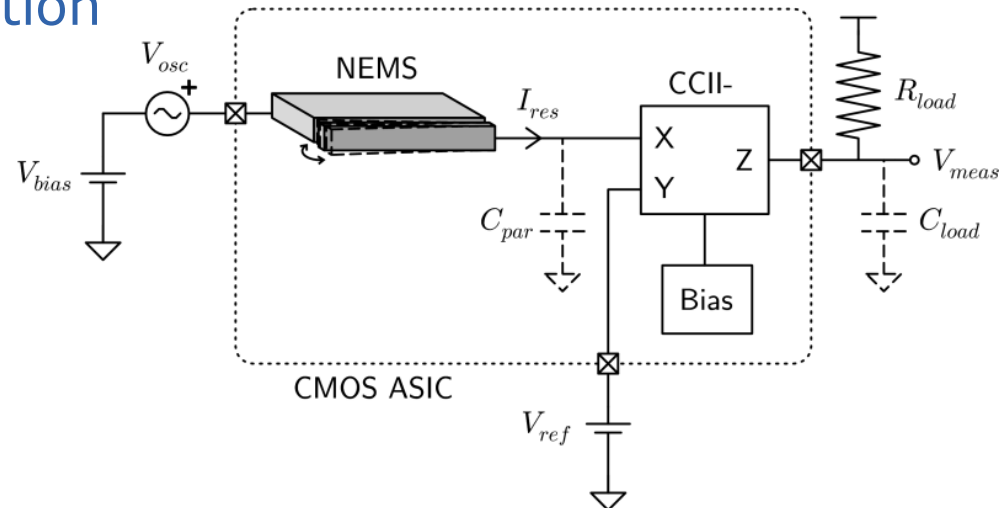
$$\begin{bmatrix} I_Y \\ V_X \\ I_Z \end{bmatrix} = \begin{bmatrix} 0 & 0 & 0 \\ 1 & 0 & 0 \\ 0 & -MN & 0 \end{bmatrix} \begin{bmatrix} V_Y \\ I_X \\ V_Z \end{bmatrix}$$



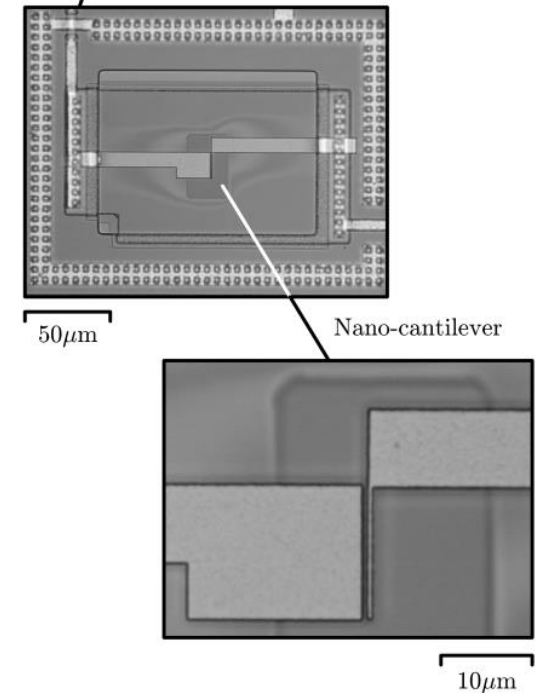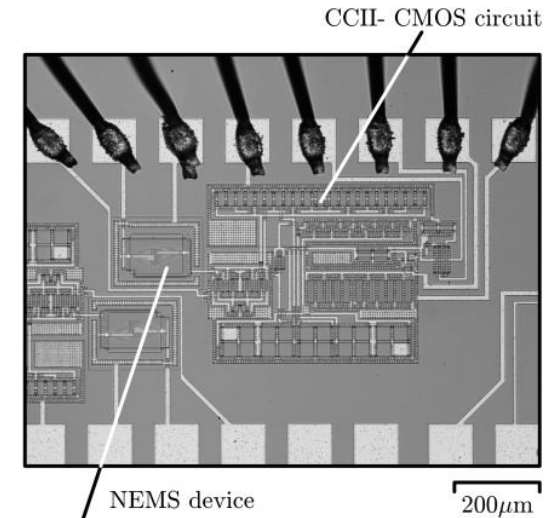
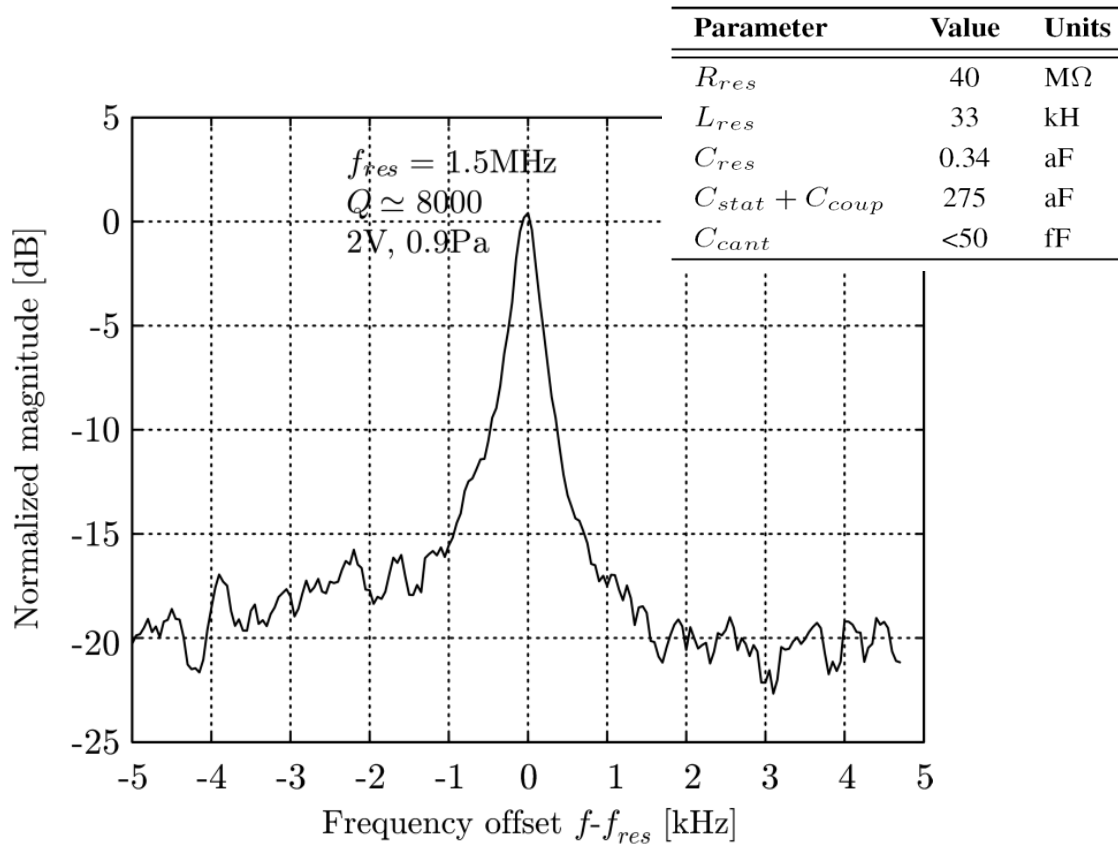
## NEMS Resonator Characterization

- ▶ Monolithic integration at IMB-CNM(CSIC) and experimental **results**:


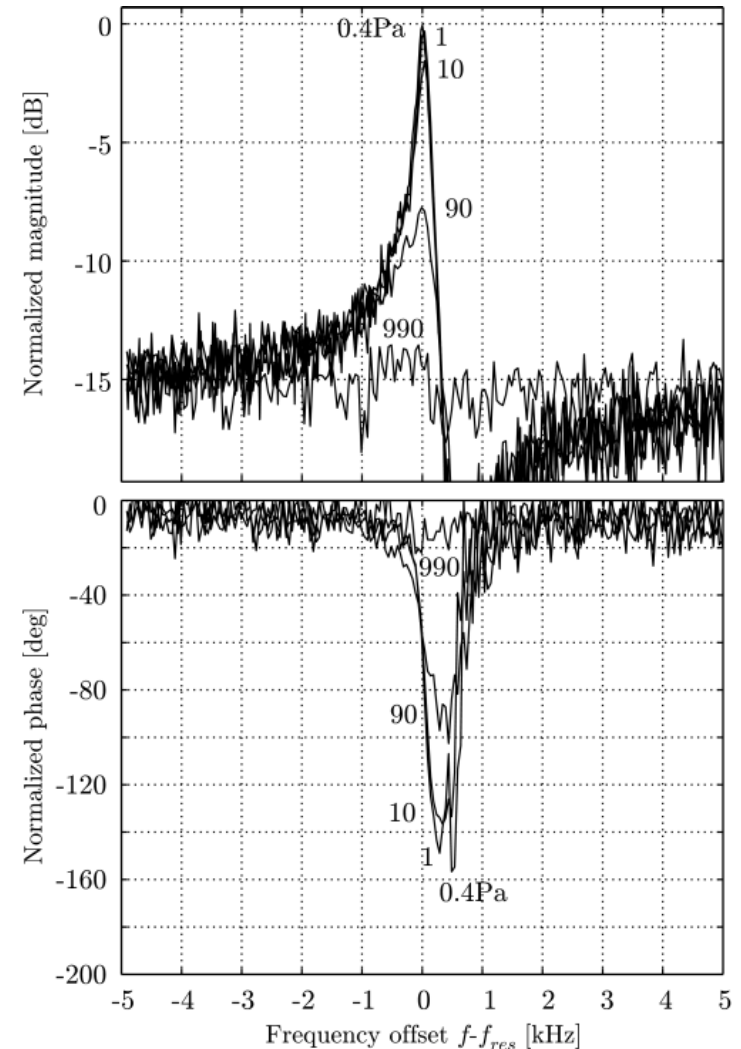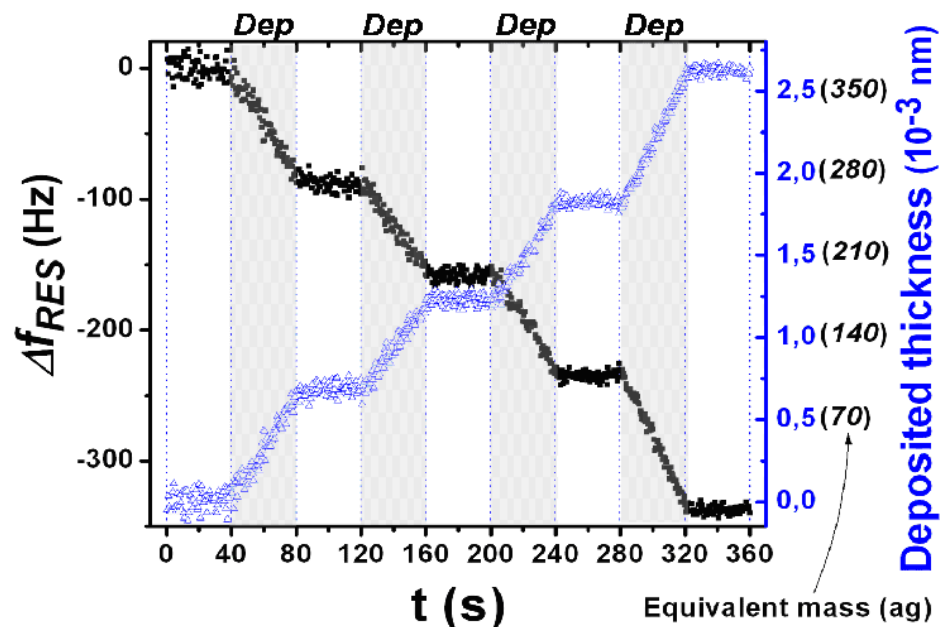
## NEMS Resonator Characterization

- ▶ Monolithic integration at IMB-CNM(CSIC) and experimental **results**:





✉ J. Arcamone et al., *A Compact and Low-Power CMOS Circuit for Fully-Integrated NEMS*

*Resonators*, IEEE Transactions on Circuits and Systems-II, Vol.54:5, pp.377-381, May 2007

- 1 What is Missing?
- 2 Too Tiny to Be Touched
- 3 Process & Matching Nightmares
- 4 Biasing Specials
- 5 Flexibility as a Must
- 6 Massive Parallel Processing
- 7 Power-Aware Design
- 8 When Package Matters
- 9 My Nice Smart Sensor
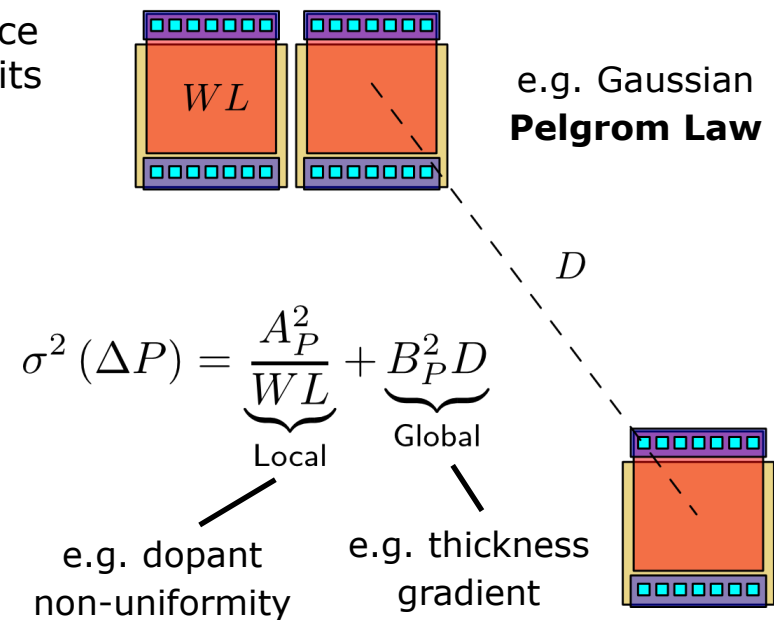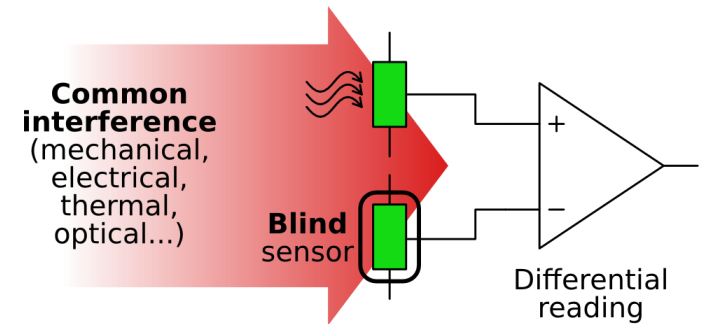
## Process & Matching Nightmares



- ▼ Sensor technologies tend to suffer from large **process** and **mismatching** deviations
- ▶ Countermeasures at ROIC level?
  - **Blind sensor** for process and interference cancellation in differential read-out, but its effectiveness can be limited by mismatching itself
  - Large **area**, minimum **distance** and **symmetrical** layout design
  - **Calibration** mechanism (automatic or with external control)
  - Digital **post-processing** may be too late to recover dynamic range!





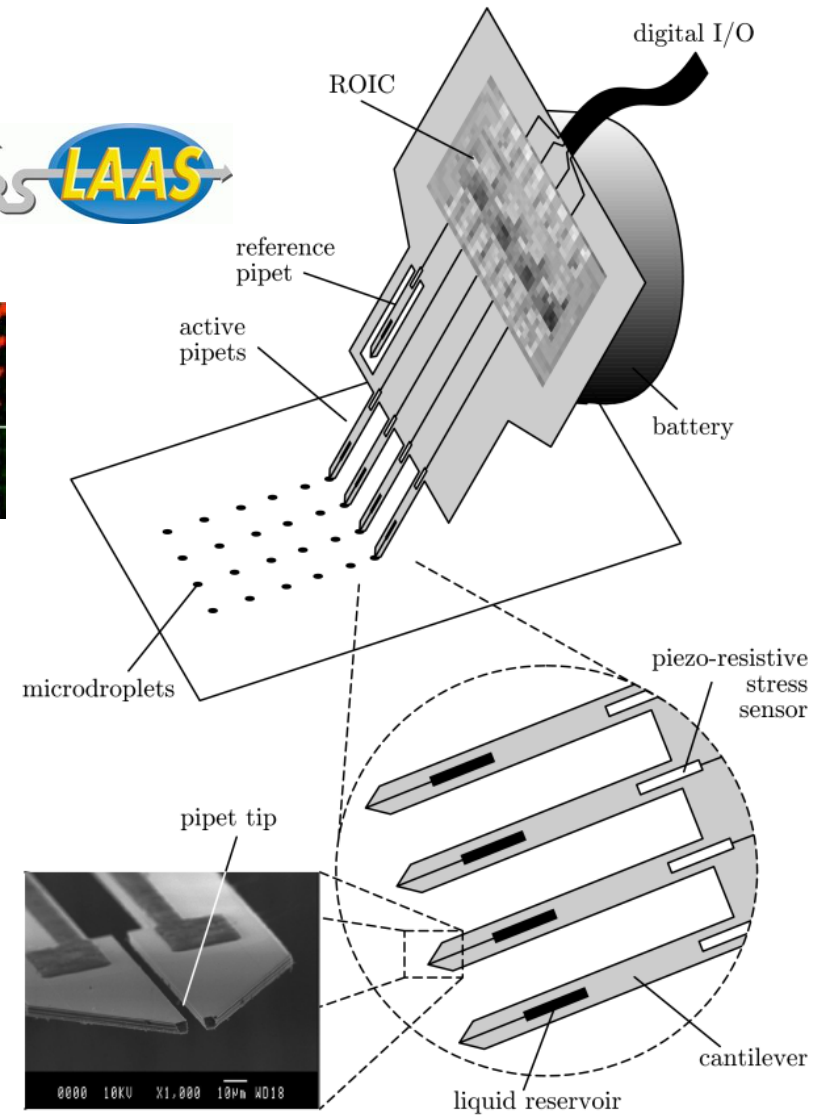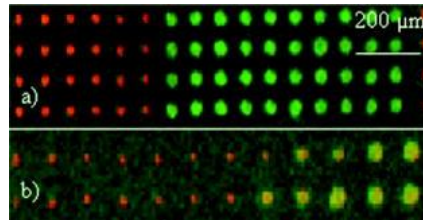
## A Microdroplet Dispensing System

- ▶ Applications in photonics, molecular electronics, biosensors...
- ▶ Fluidic NEMS operated as a **bioplume**
- ▶ Accurate **positioning** for microdroplet high uniformity
- ▶ Multi-channel digital ROIC for integrated **piezo-resistive** stress sensors:
  - **Low power** to prevent drying
  - **Low voltage** for single cell battery supply
- ▶ **Blind sensor** against interferences



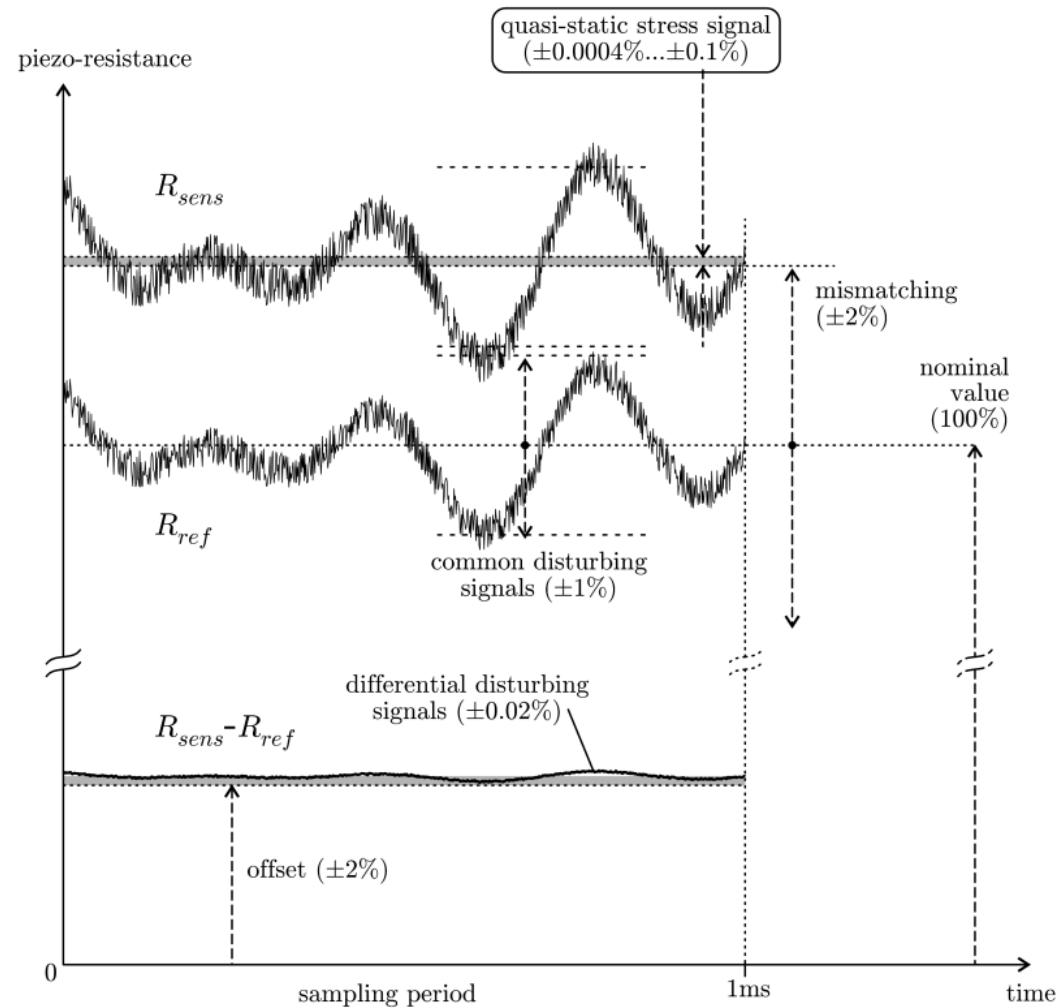
## Integrated Piezo-Resistors

- ▶ **Differential** read-out of weak stress signal  
 $\pm 0.1\% / \pm 0.0004\% = 9\text{bit}$
- ▶ **Process** corners  $\pm 20\%$
- ▼ Large **disturbing** signals in the order of  $\pm 1\%$
- ▼ Technology **mismatching** deviations  $\pm 2\%$
- ▼ **Residual** disturbing signals  $\pm 0.02\% = \pm 50\text{LSB!}$
- ▼ **Gain tuning** mechanism to be included inside ROIC  
 $\pm 2\% / 0.01\% = (8+1)\text{bit}$


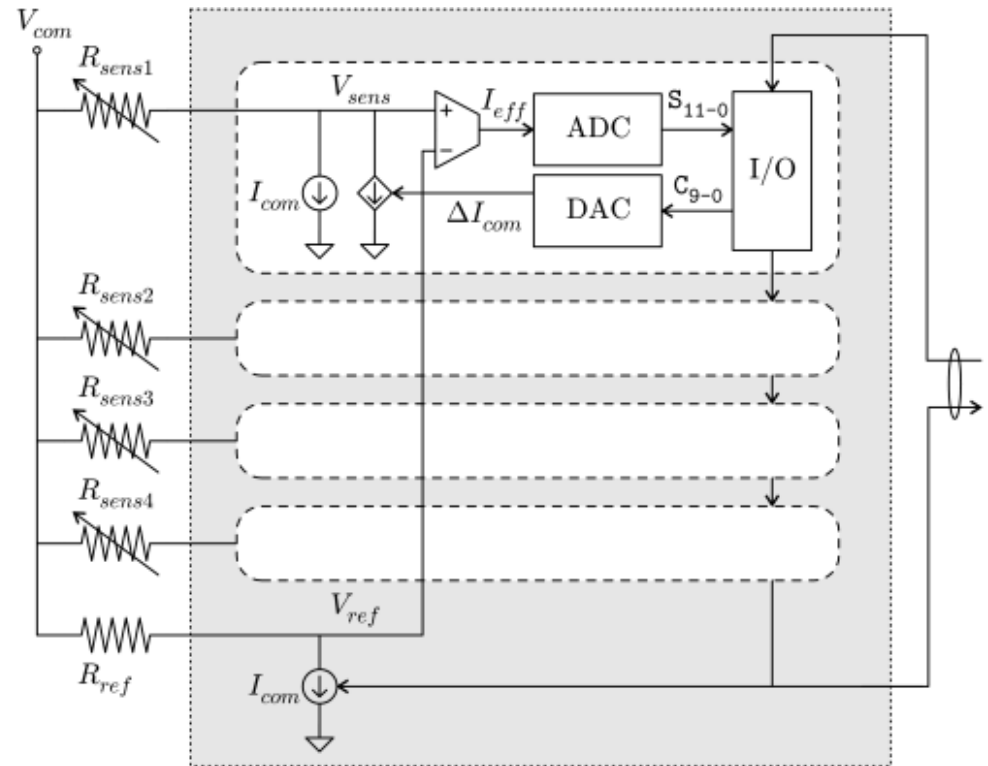
## Multichannel ROIC Architecture


- ▶ Overall programmable **sensitivity** ( $I_{com}$ )
- ▶ Differential **gain balancing** through sensor bias ( $\Delta I_{com}$ )
- ▶ Differential OTA **pre-amplification**
- ▶ Integrate & fire current-mode **A/D conversion**
- ▶ **Digital-only** read-out and program-in interface
- ▶ Channel-based **modular** ROIC design



## Low-Voltage and Low-Power CMOS Circuits

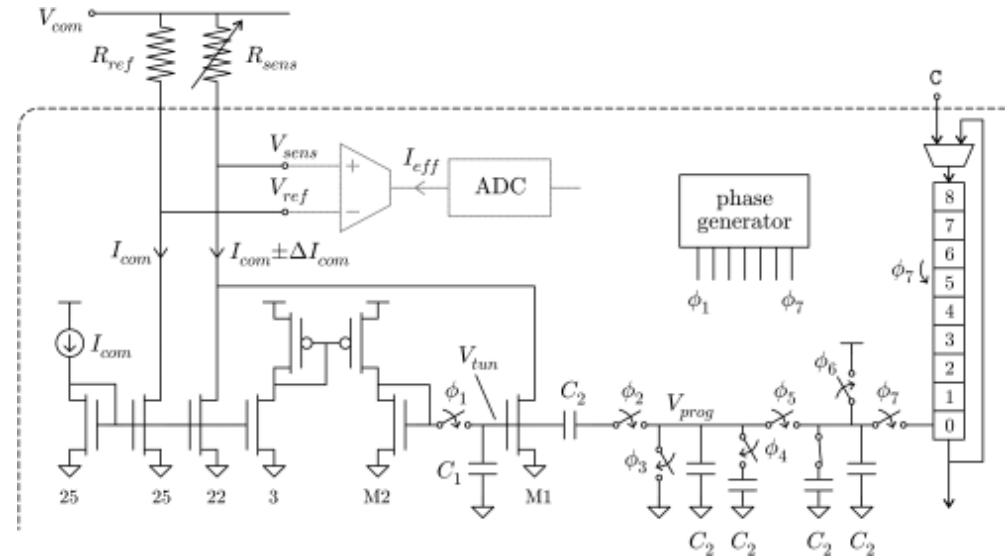
### ► Gain calibration through built-in SC DAC:

- Recalibrated at **start-up**
- Compensation of piezo-resistor **mismatch** and **OTA unbalance**


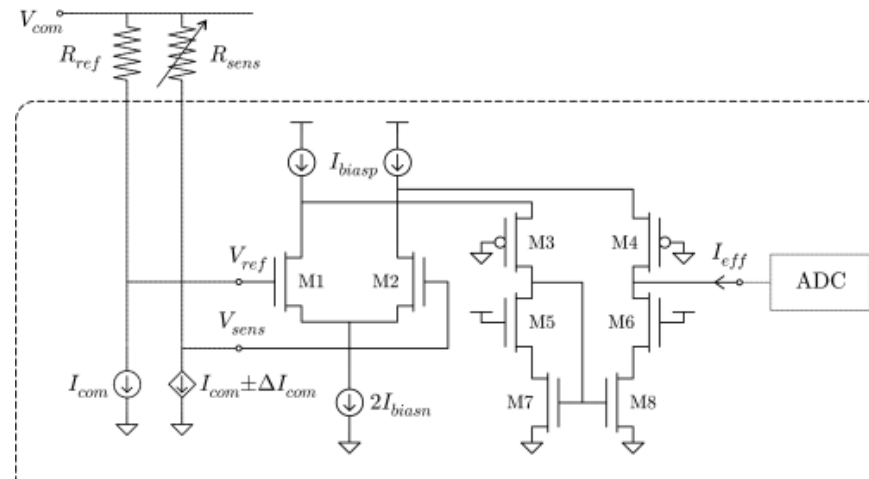
### ► Differential V to **single ended** I conversion:

- Biased in weak inversion for best  $G_m/I_D$  and lowest technology sensitivity
- Low equivalent input **noise** and high **CMRR**




## Low-Voltage and Low-Power CMOS Circuits
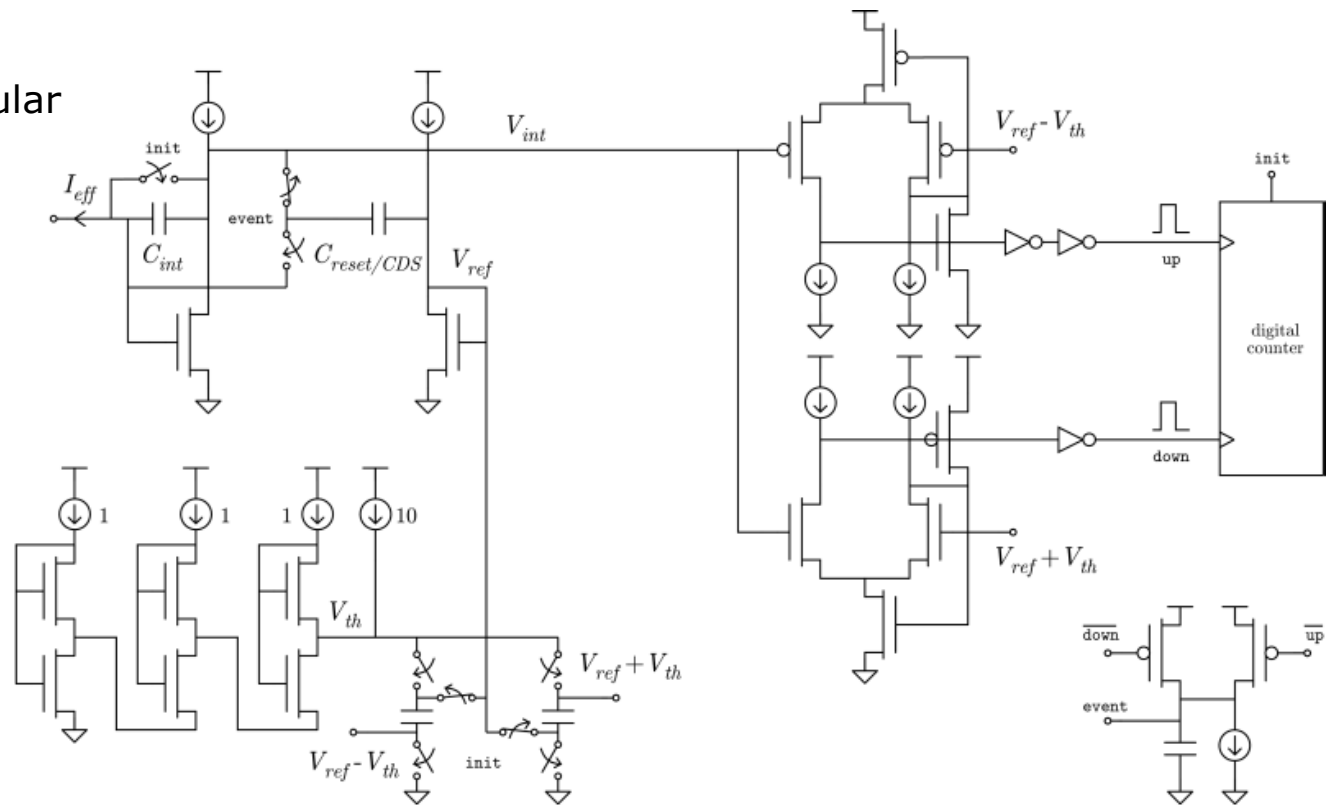
### ► Spike-counting ADC:

- **Class-AB** window comparator
- Built-in modular and **floating** threshold generator


- **Compact** CTIA with correlated double sampling (**CDS**) for low-frequency noise reduction



## Quad ROIC CMOS Integration

- ▶ 0.35 $\mu\text{m}$  2P4M CMOS technology

2.4mm x 1.3mm (3.1mm<sup>2</sup>)



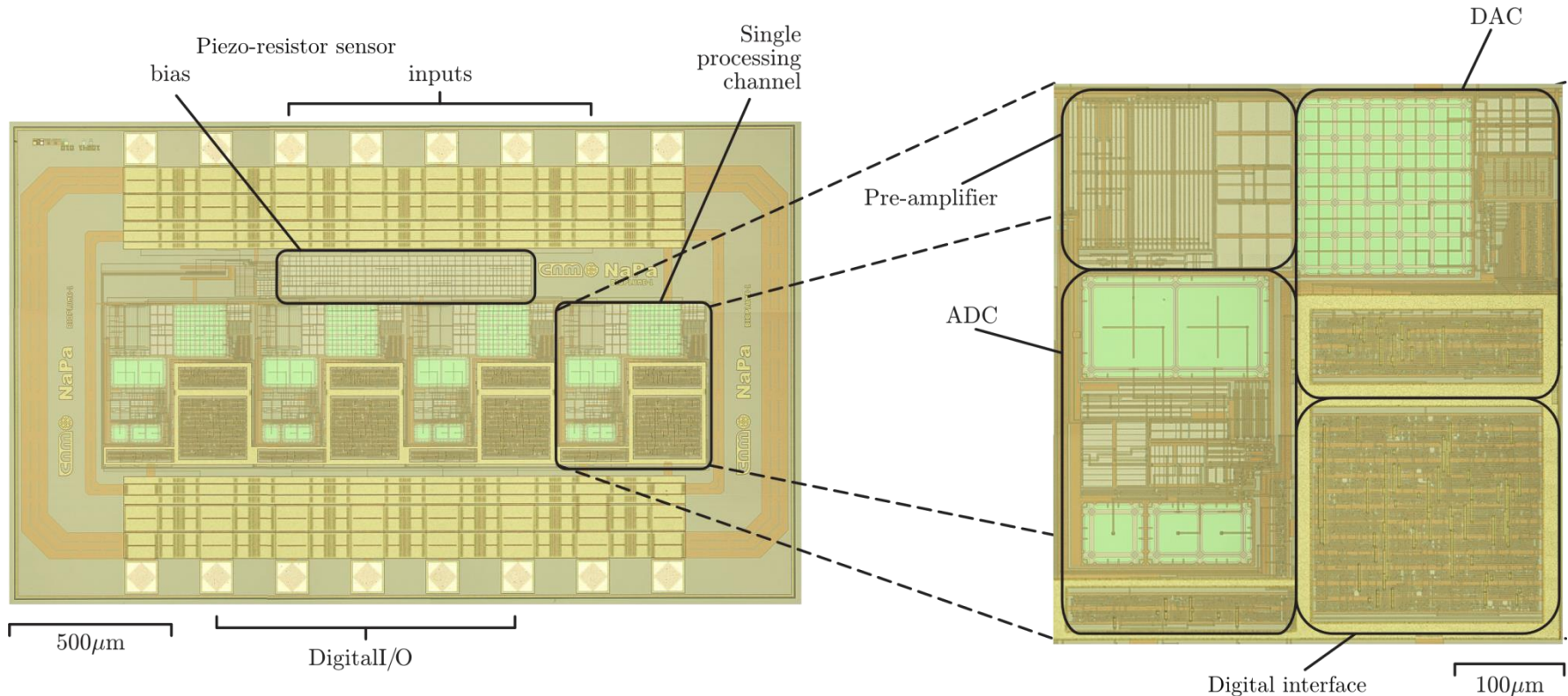


- ▶ Direct **wire-bonded** to integrated piezo-resistors substrate

## Experimental Results

$$\left| \frac{S_{11-0}}{\Delta R_{sens}/R_{sens}} \right| = \frac{G_m T_{int}}{C_{int} V_{th}} I_{com} R_{sens} \simeq 6 \text{ kLSB}/\%$$

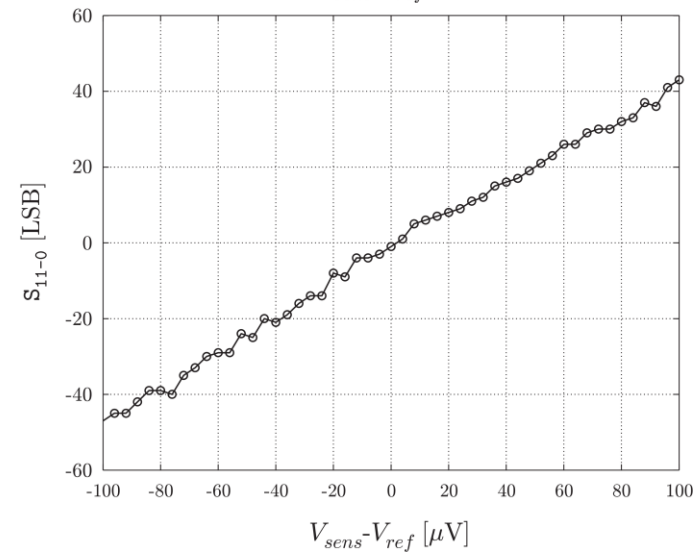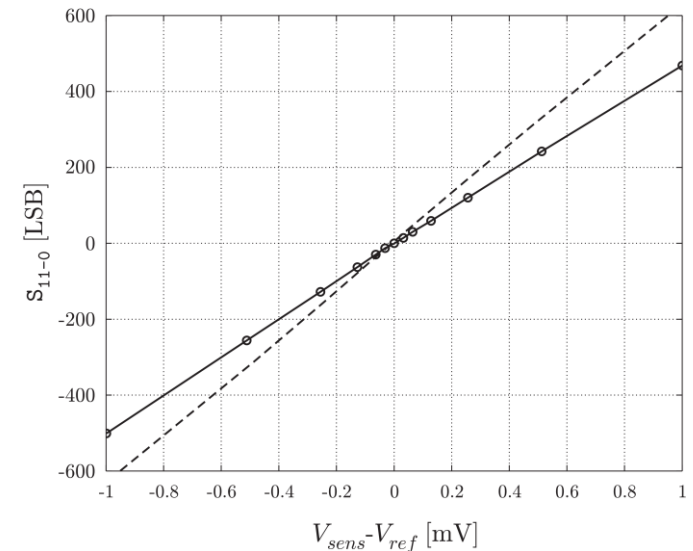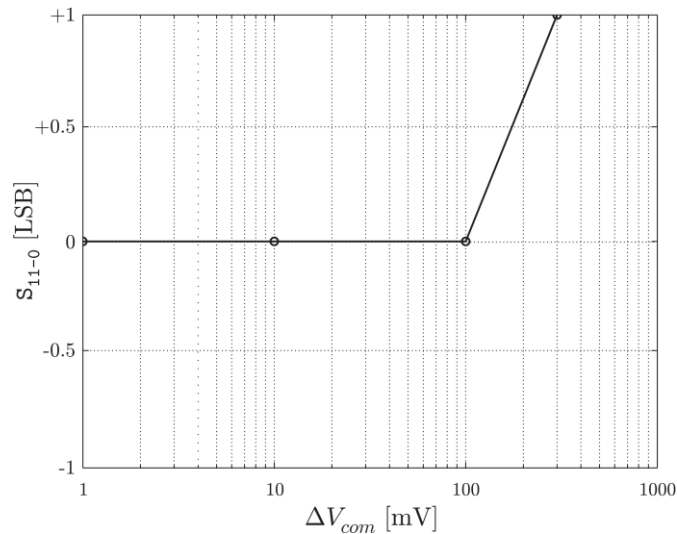- **130 $\mu$ W/ch** at **+1.25V** (+3.3V technology)
- **Thermal** compensation
- Good **linearity**
- **CMRR > 100dB**



✉ R. Durà et al., *A 0.3mW/Ch 1.25V Piezo-Resistance Digital ROIC for Liquid Dispensing MEMS*,  
IEEE Transactions on Circuits and Systems-I, 56:5(957-65), May 2009









- 1 What is Missing?
- 2 Too Tiny to Be Touched
- 3 Process & Matching Nightmares
- 4 **Biasing Specials**
- 5 Flexibility as a Must
- 6 Massive Parallel Processing
- 7 Power-Aware Design
- 8 When Package Matters
- 9 My Nice Smart Sensor


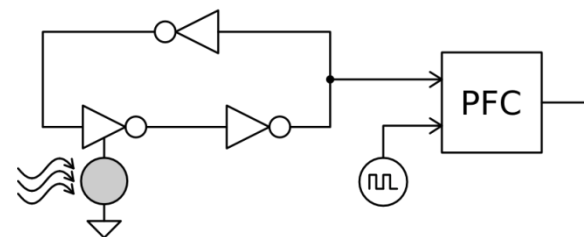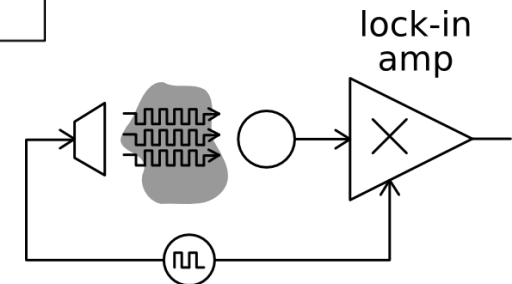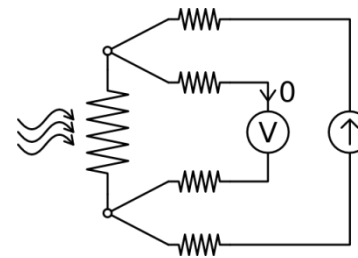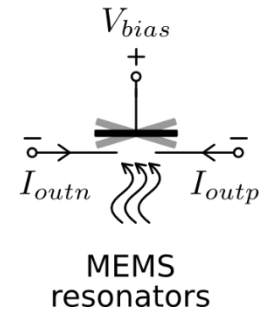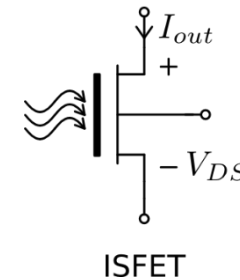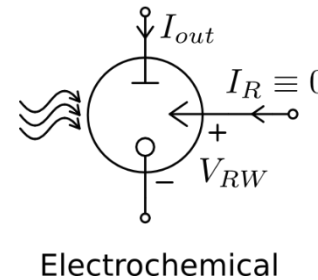
## Biasing Specials


- ▼ Some sensors require ROIC to incorporate **control loops** for their proper DC biasing
- ▼ **Multiple ports** may be needed by ROIC to compensate for unavoidable parasitics
- ▲ When possible, **lock-in** operation is advised to strongly reduce equivalent noise bandwidth
- ▲ Indirect measurement through **time-domain** processing is a promising alternative


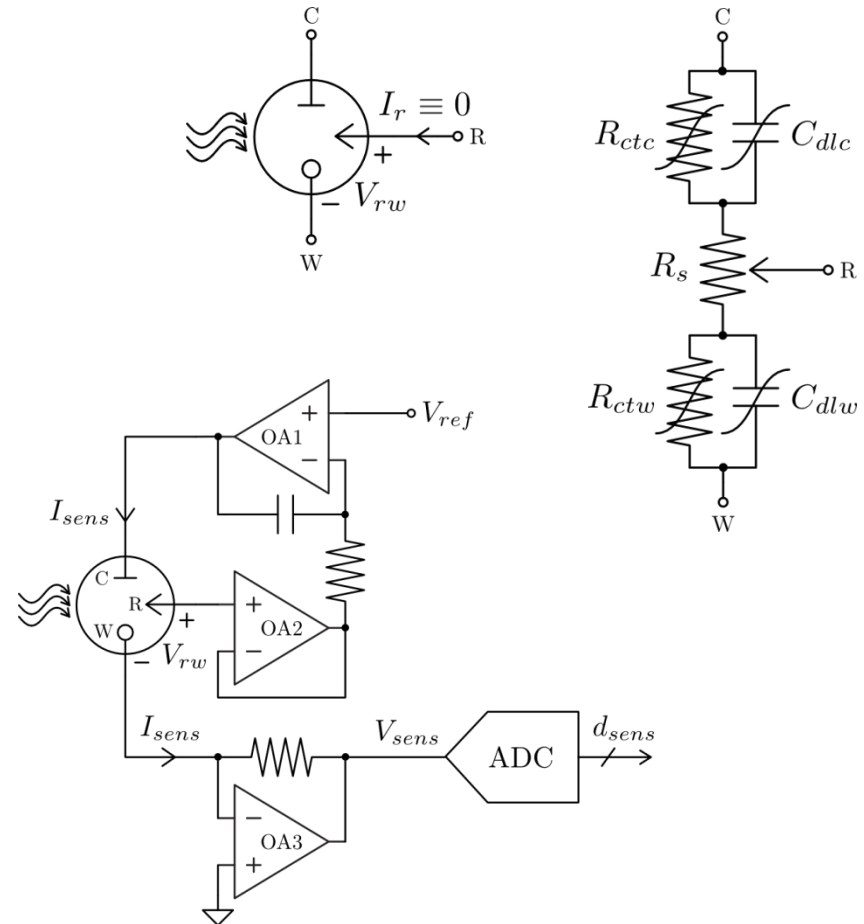
# Integrated Electrochemical Sensors






- ▶ Applications in biosensors, quality control...
- ▲ Compatible with **CMOS** monolithic integration
- ▲ **Selectivity** by functionalization of their microelectrodes surface
- ▼ Reduced **speed** ( $\sim 0.1s$ ) and **life** time
- ▼ Expensive **package**
- ▼ **Potentiostatic** operation and **amperometric** reading



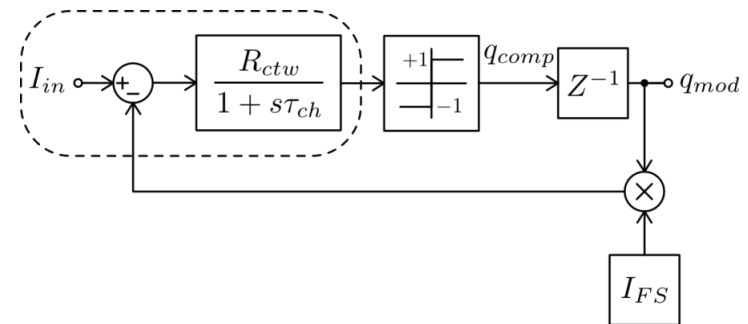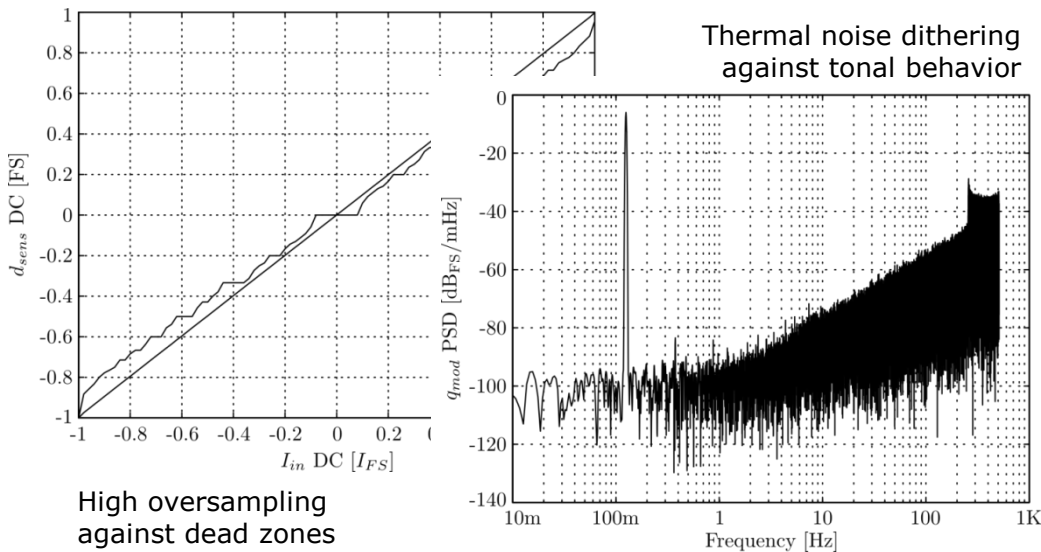
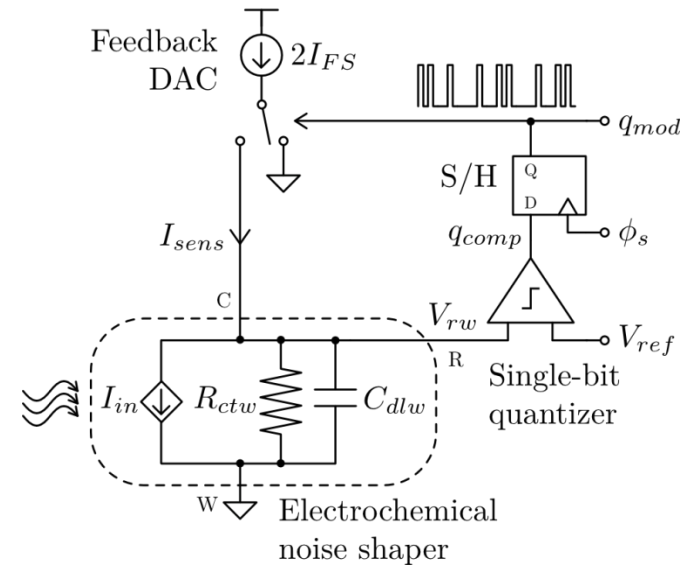
# Mixed Electrochemical ROIC Architecture

- ▶ Low-pass first-order single-bit CT  $\Delta\Sigma$  A/D **modulator** with sensor in the loop:
  - Minimalistic **analog** circuits
  - **Low power** ROIC overhead respect to sensor itself
  - Accurate sensor dynamic **modeling** needed



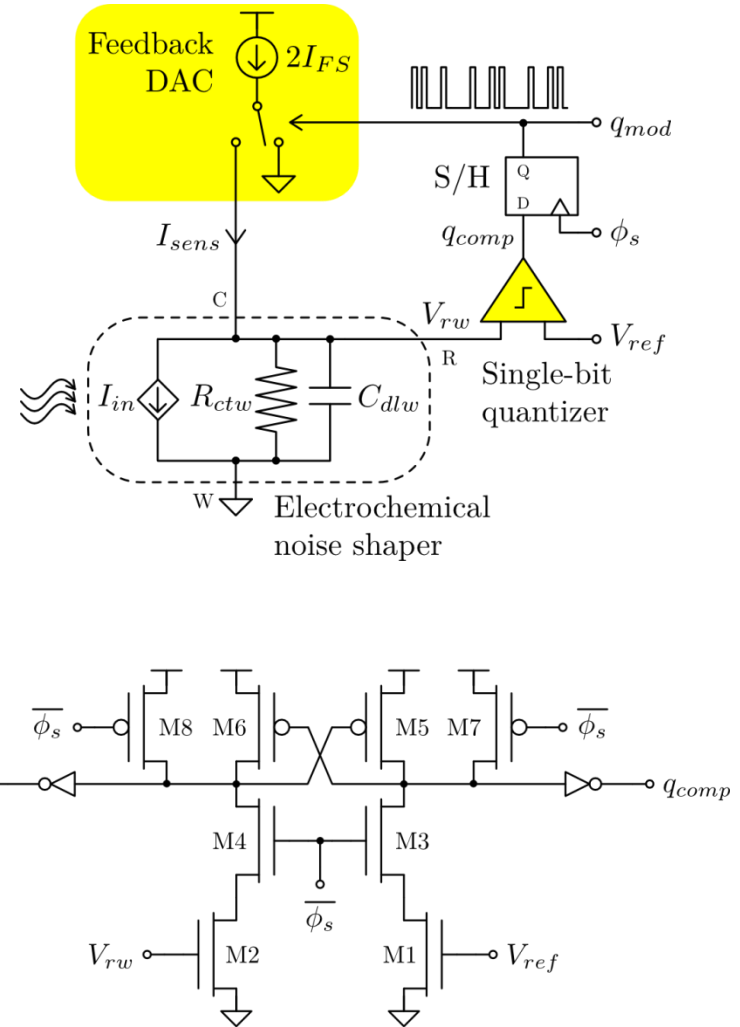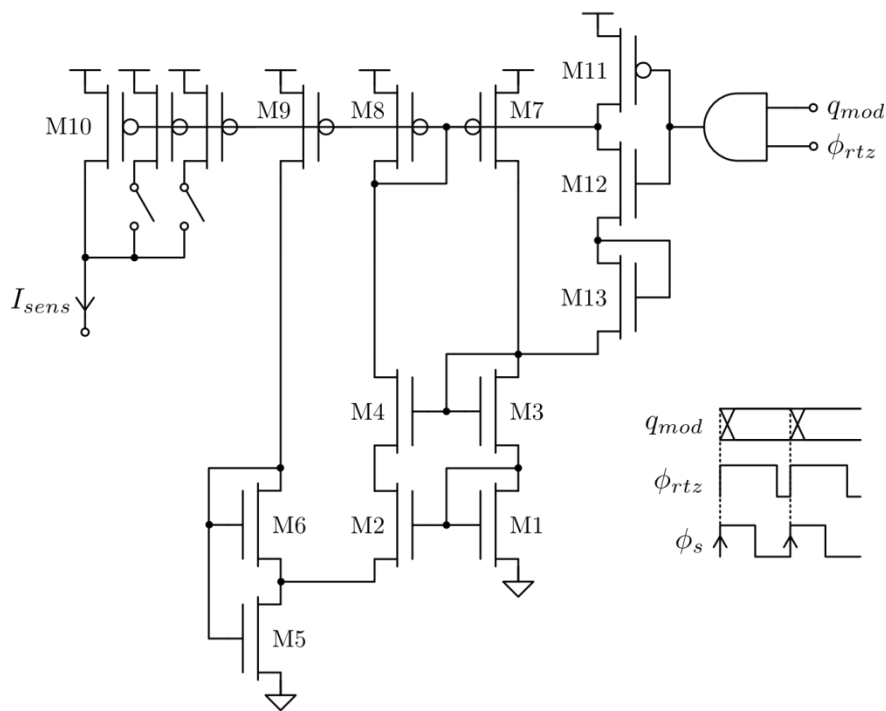
## Low-Power All-MOS Circuits

- ▲ Two **analog blocks** only
- ▶ **Latched comparator** for 1bit quantization + **current reference** for 1bit feedback DAC





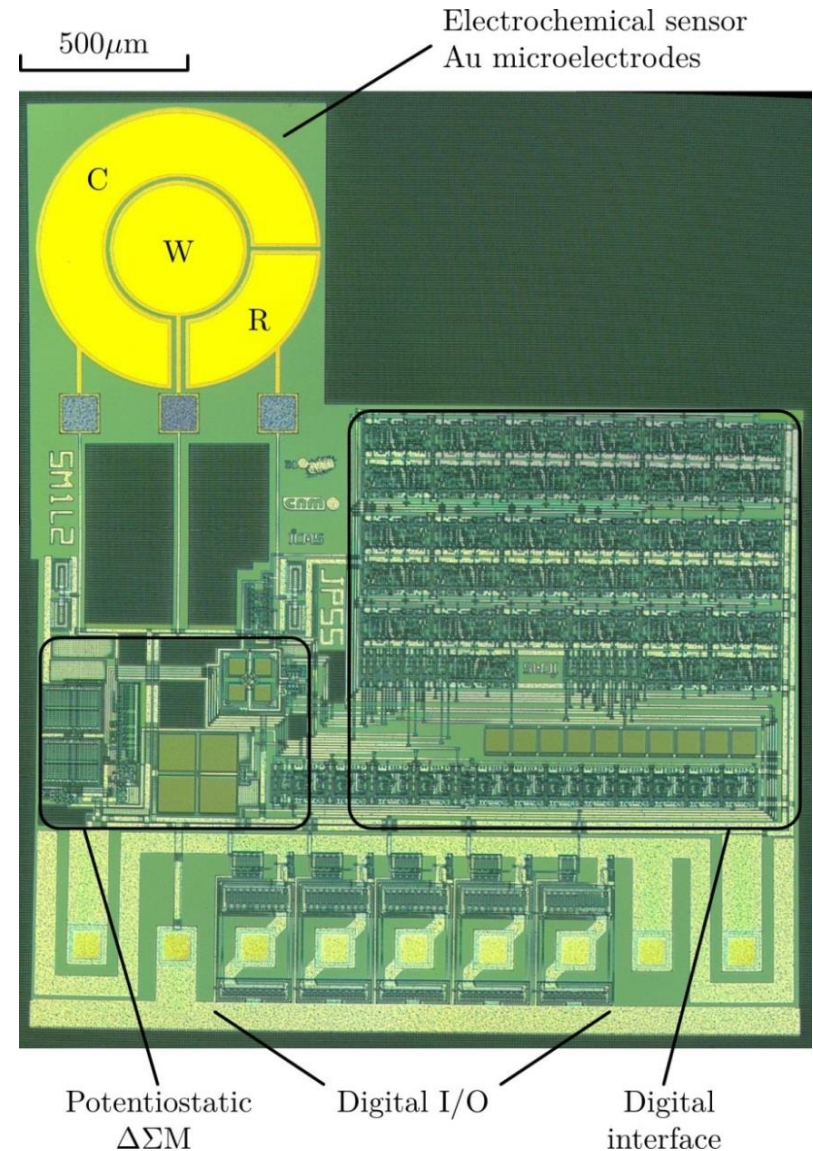
## Monolithic CMOS Integration

- ▶ IMB-CNM(CSIC) inexpensive 2.5 $\mu\text{m}$  1M CMOS technology (**CNM25**)
- ▶ In-house sensor **Au post-processing** at wafer level
- ▶ 2.3mm x 2.8mm (6.4mm<sup>2</sup>)
- ▲ **Low area** overhead of  $\Delta\Sigma$  ADC
- ▲ **Digital only interface** for low-pass filtering and programming of potentiostatic voltage and current full-scale
- ▲ Overall **25 $\mu\text{W}$**  at **+5V**


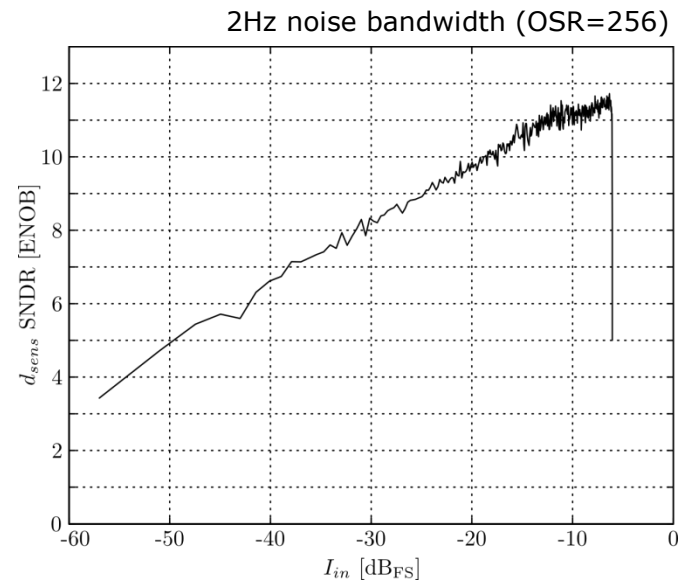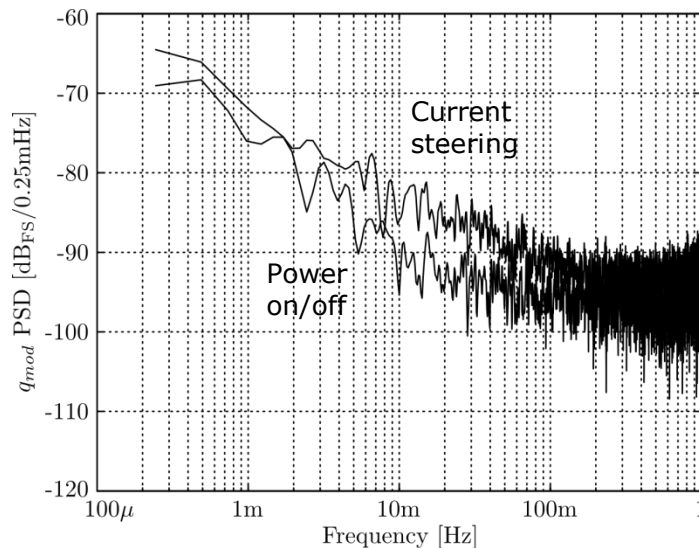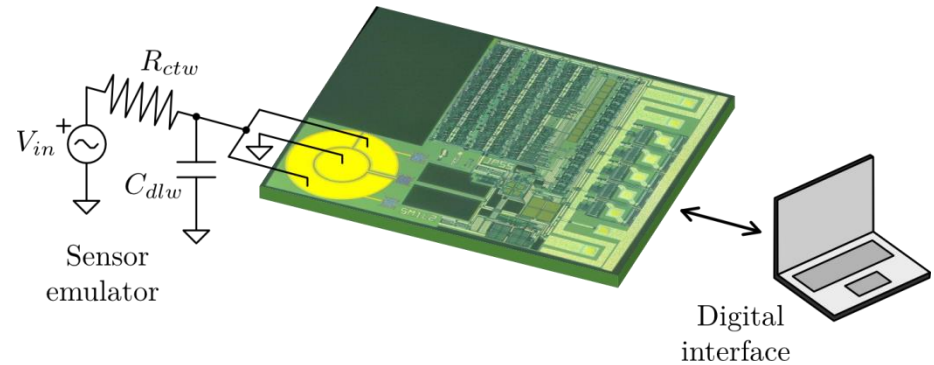
## Experimental Results




- ▲ **Electrical** tests show good enough dynamic range to not limit measurements




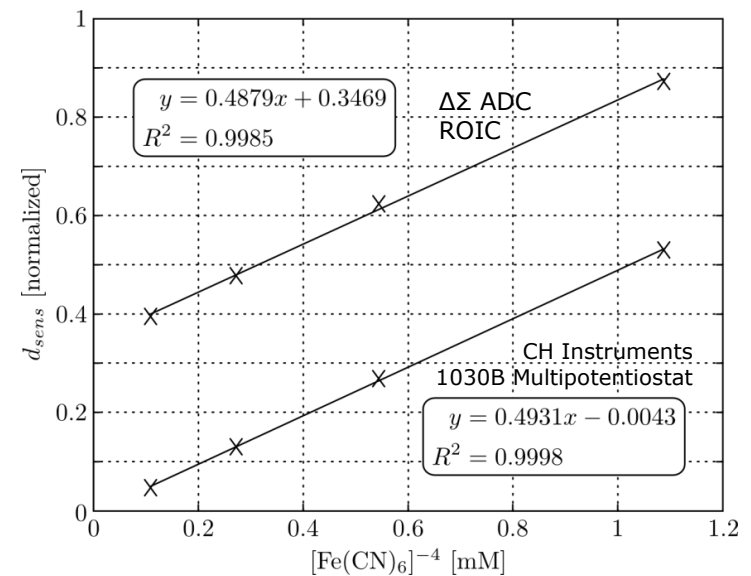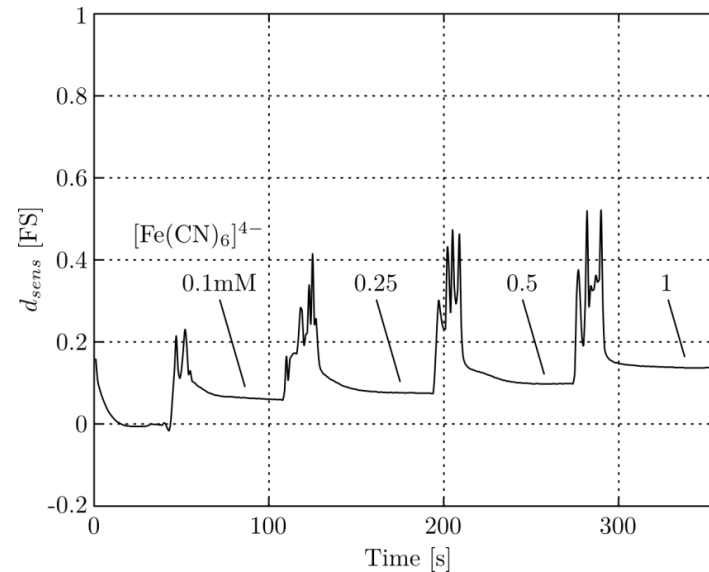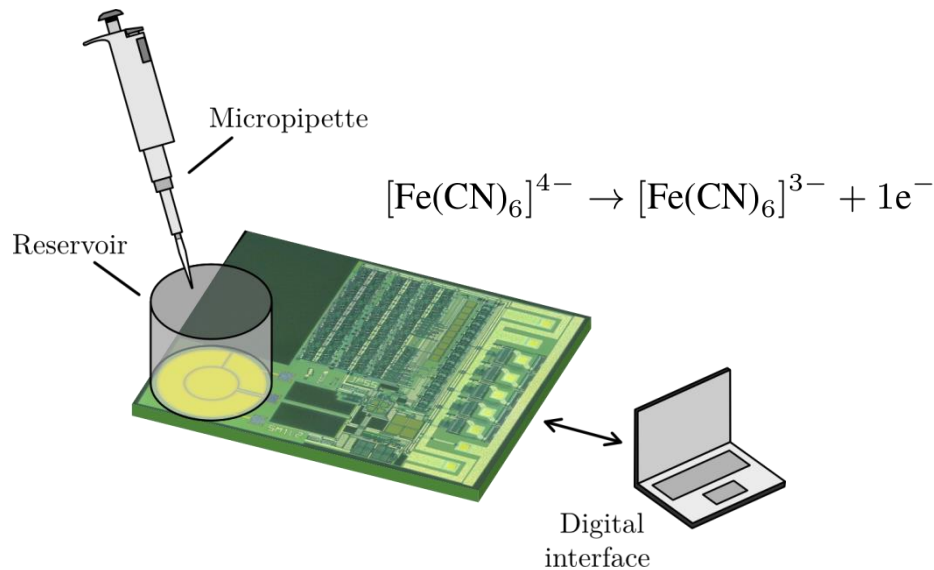
## Experimental Results

- ▲ **Electrical** tests show good enough dynamic range to not limit measurements
- ▲ **Electrochemical** tests return comparable performance to lab desktop equipment



✉ S. Sutula et al., A 25- $\mu$ W All-MOS Potentiostatic Delta-Sigma ADC for


Smart Electrochemical Sensors, IEEE Transactions on Circuits and Systems-I, 61:3(671-679), Mar 2014

- 1 What is Missing?
- 2 Too Tiny to Be Touched
- 3 Process & Matching Nightmares
- 4 Biasing Specials
- 5 Flexibility as a Must
- 6 Massive Parallel Processing
- 7 Power-Aware Design
- 8 When Package Matters
- 9 My Nice Smart Sensor


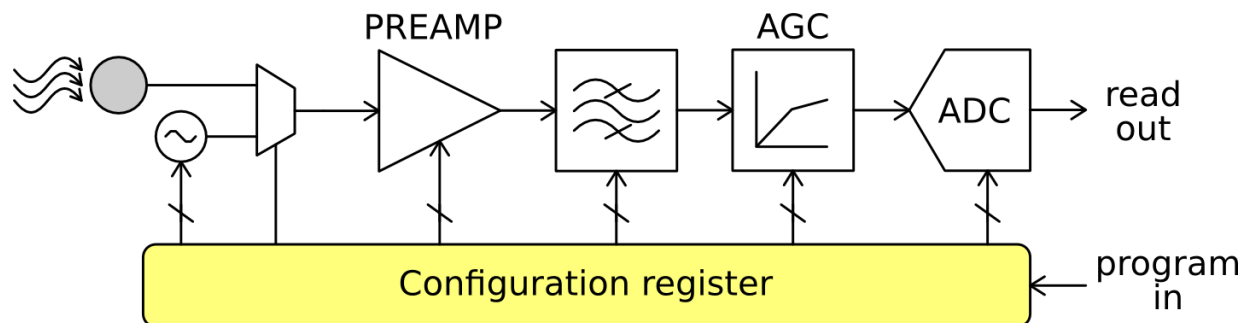
## Flexibility as a Must

- ▶ ROIC **controllability/observability** to increase overall sensor yield?




- **Single** ROIC can fit several sensor designs
- **Built-in test** mechanism to screen smart sensors before post-processing or packaging
- Compensate for **sensor aging**
- Independent optimization of **dynamic range** for each stage
- If available, **non-volatile** memory (Flash, OTP...) to store configuration
- Specially useful when sensor or application **specifications** are incomplete!
- **Extra design** work for making each stage configurable
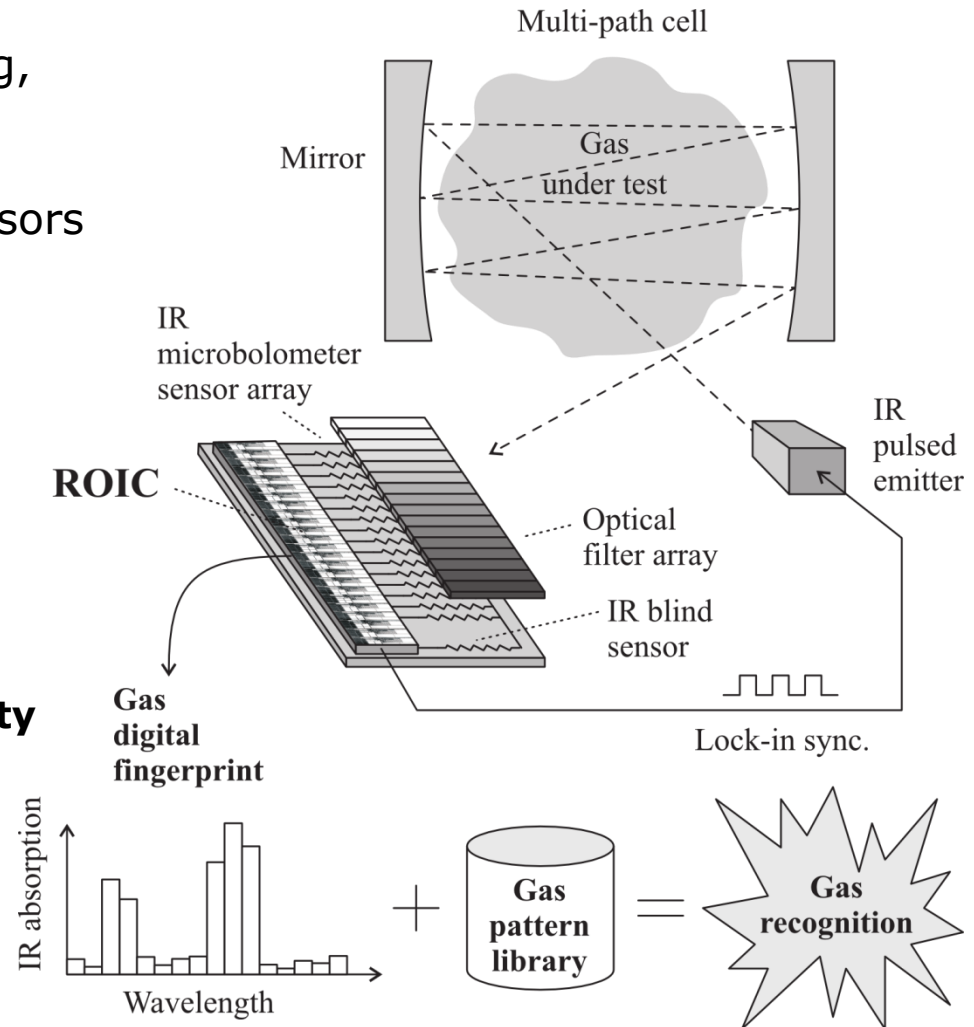
# IR Spectroscopic Gas Recognition System




- ▶ Applications in toxic gas warning, environmental monitoring...
- ▶ Thermal **μbolometer** LWIR sensors
- ▶ Multipath optical cell to amplify gas IR **absorption** effect
  - Blind reference and lock-in demodulation for **high accuracy** read-out
  - Sensor deviations and mixed IR technologies need **high flexibility** for each channel
  - **Low power** ROIC to avoid thermal drifts of IR sensors



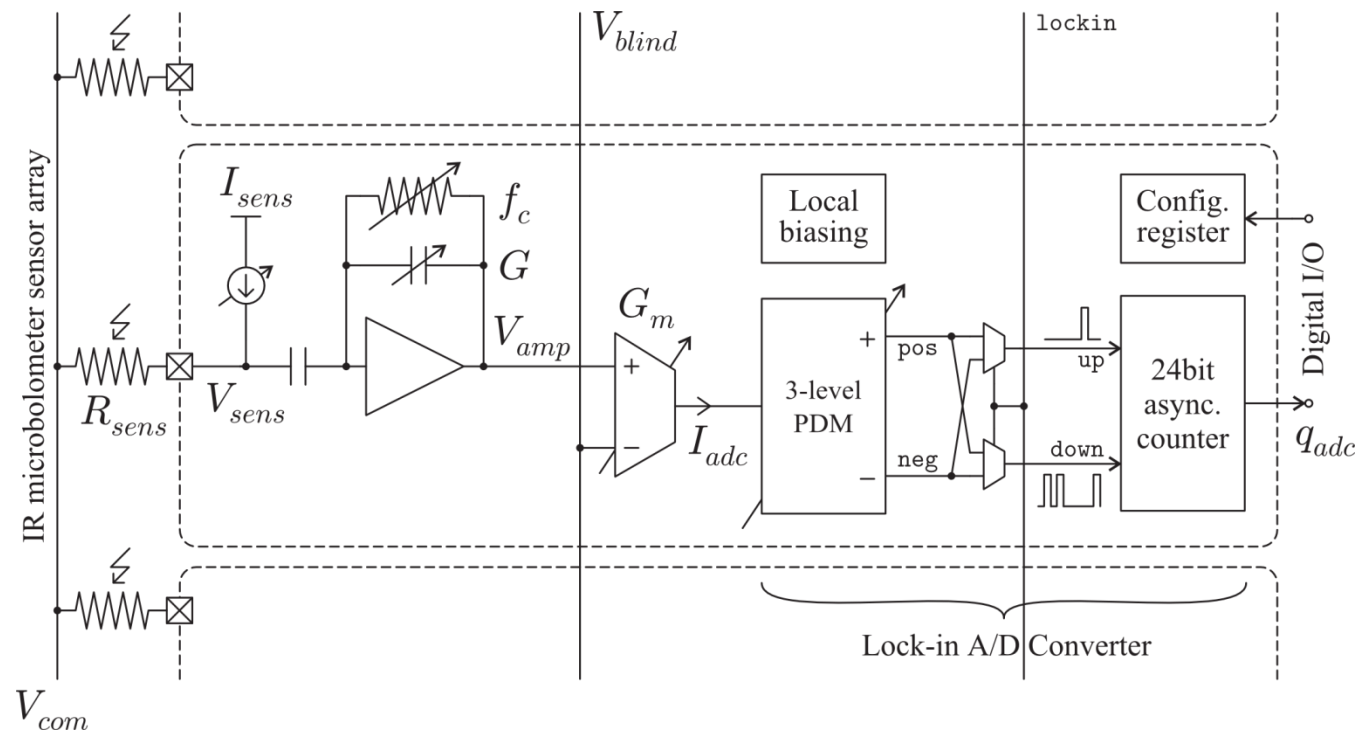
## ROIC Channel Module

- ▶ **Sub-Hz** high-pass pre-amplification
- ▶ **5-parameter** independent programmability per channel!
- ▶ Dedicated **blind channel** for cancellation of common disturbing signals
- ▶ ADC with **digital lock-in** demodulation



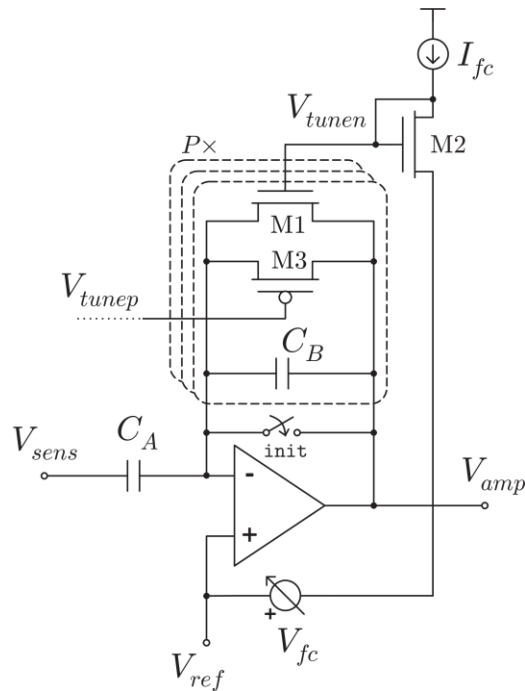
# Low-Power Channel Circuits


▲ Fully integrated sub-Hz variable **corner & gain** pre-amplifier



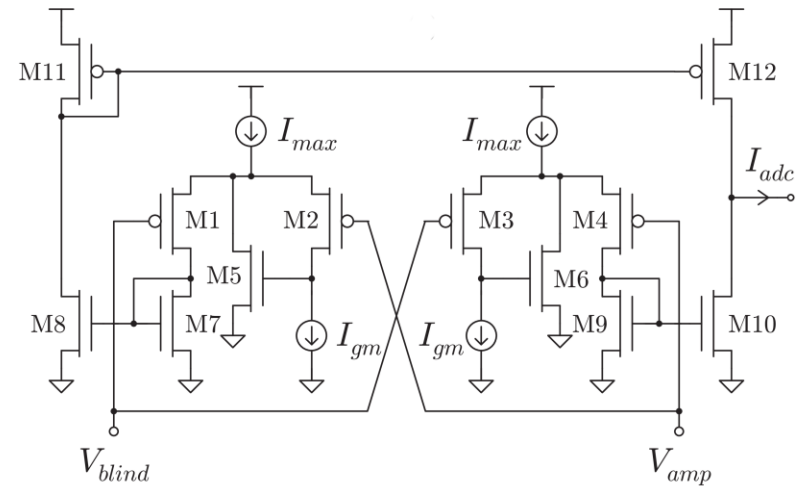▲ **Highly linear** differential transconductor with soft limiter




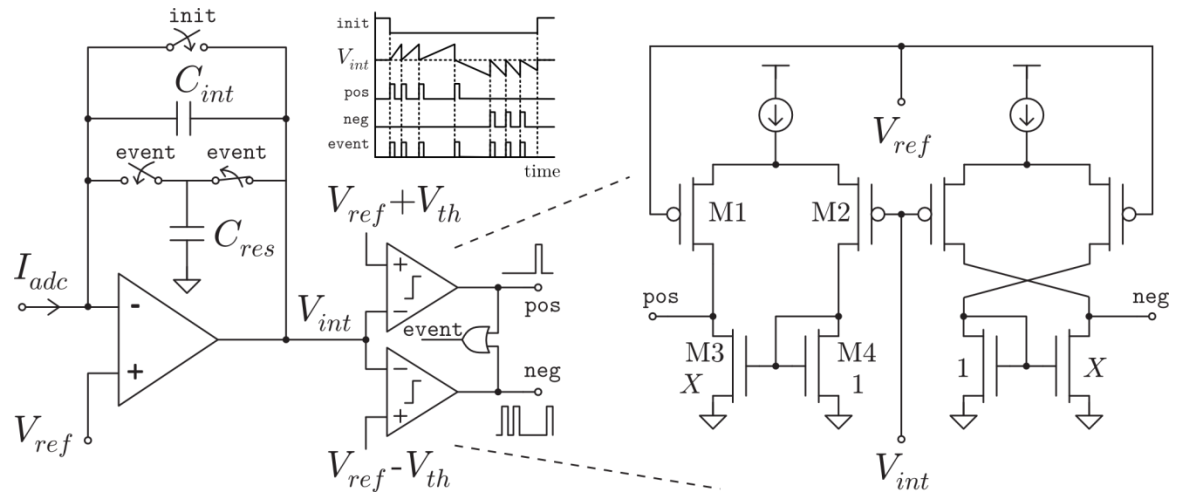
▲ Integrate & fire PDM with **3-level** quantizer


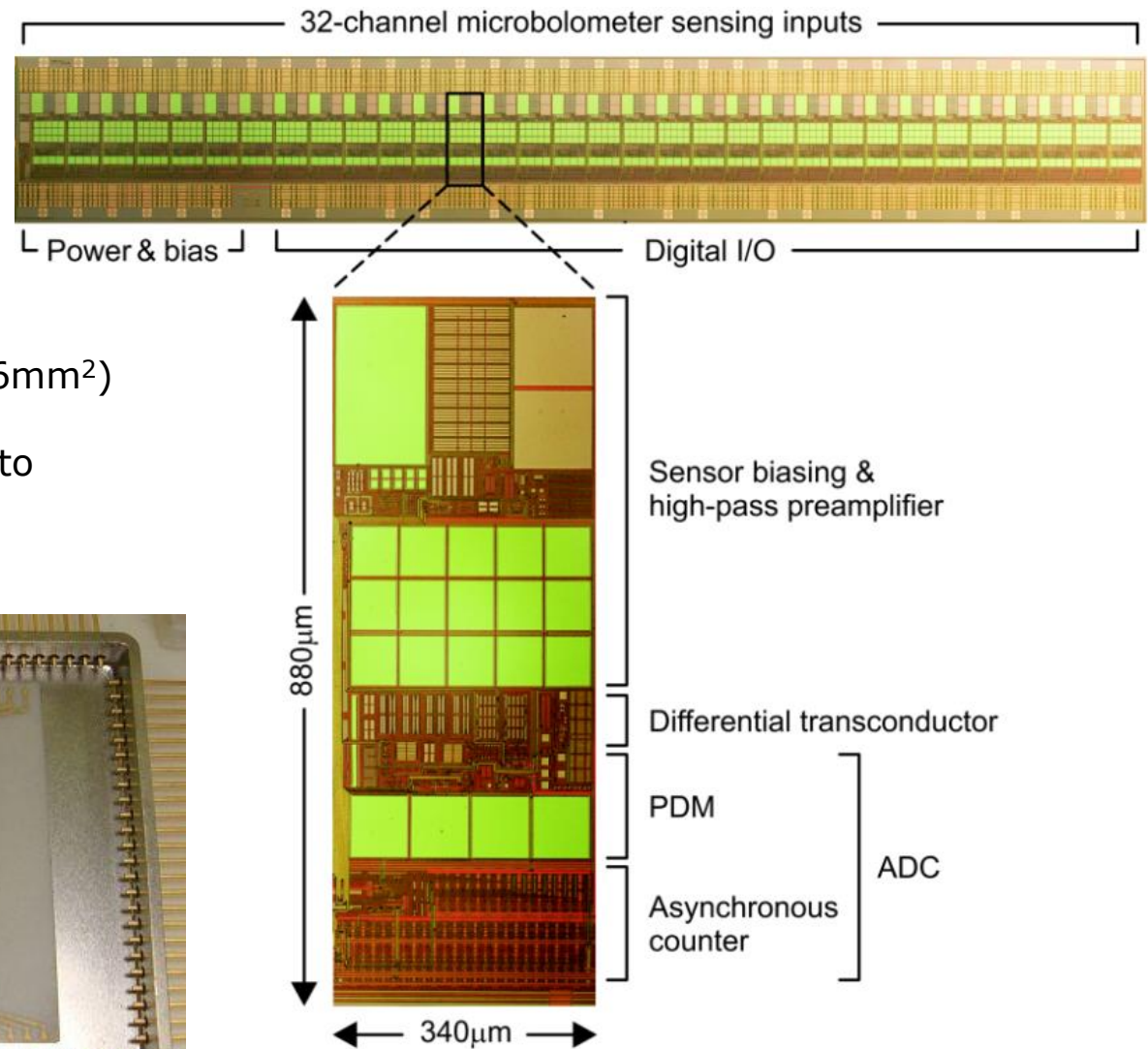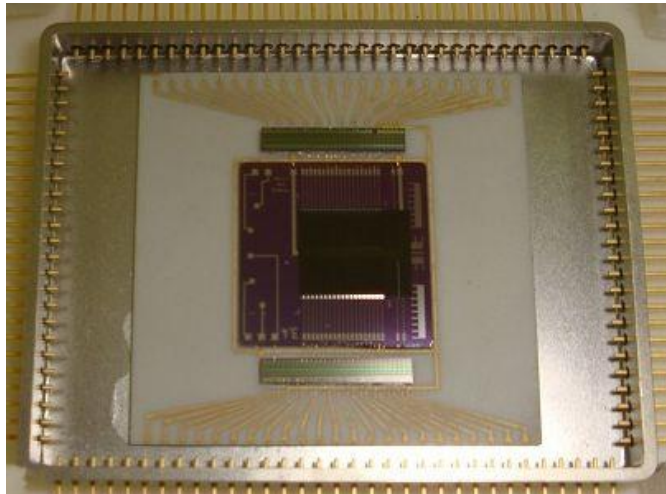
## 32-Channel ROIC

► 0.35 $\mu\text{m}$  2P4M  
CMOS technology


- 350 $\mu\text{m}$ -pitch
- 11mm x 1.6mm (17.6mm<sup>2</sup>)
- Direct **wire-bonded** to IR  $\mu$ bolometer array



## Experimental Results

- ▲ **120 $\mu$ A/ch** at +3.3V
- ▲ Full **programmability**

Parameter	Value	Units
$I_{sens}$	1 to 10	$\mu$ A
$f_c$	0.75 $\pm$ 0.10 3.6 $\pm$ 0.4 49 $\pm$ 8 389 $\pm$ 76	Hz
$G$	26 $\pm$ 0.1 34 $\pm$ 0.1 40 $\pm$ 0.1 45 $\pm$ 0.1	dB
$G_m$	18 25 36 45	$\mu$ S
$1/C_{int}V_{th}$	1.7 0.8	Hz/pA
$V_{sensneq}@10\text{Hz}$	250	nV <sub>rms</sub> / $\sqrt{\text{Hz}}$
THD $V_{amp}<300\text{mV}_{pp}$	<0.1	%
Crosstalk	<0.5	LSB

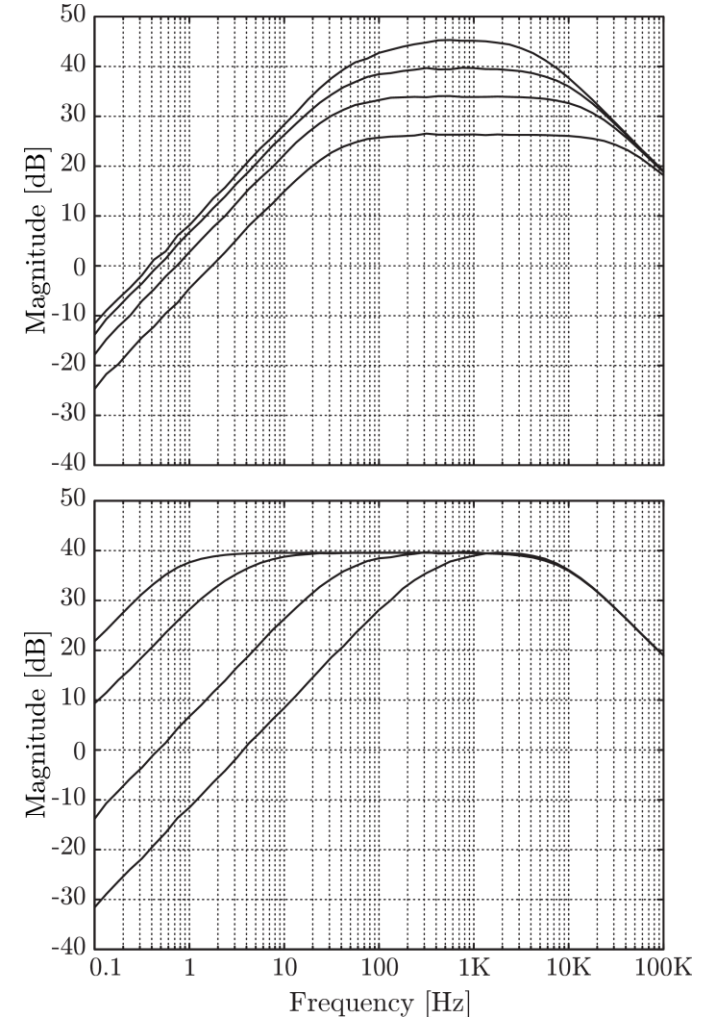


☞ S. Sutula et al., *A 400 $\mu$ W Hz-Range Lock-In A/D Frontend Channel for Infrared Spectroscopic Gas Recognition*, IEEE Transactions on Circuits and Systems-I, 58:7(1561-8), Jul 2011

- 1 What is Missing?
- 2 Too Tiny to Be Touched
- 3 Process & Matching Nightmares
- 4 Biasing Specials
- 5 Flexibility as a Must
- 6 Massive Parallel Processing
- 7 Power-Aware Design
- 8 When Package Matters
- 9 My Nice Smart Sensor


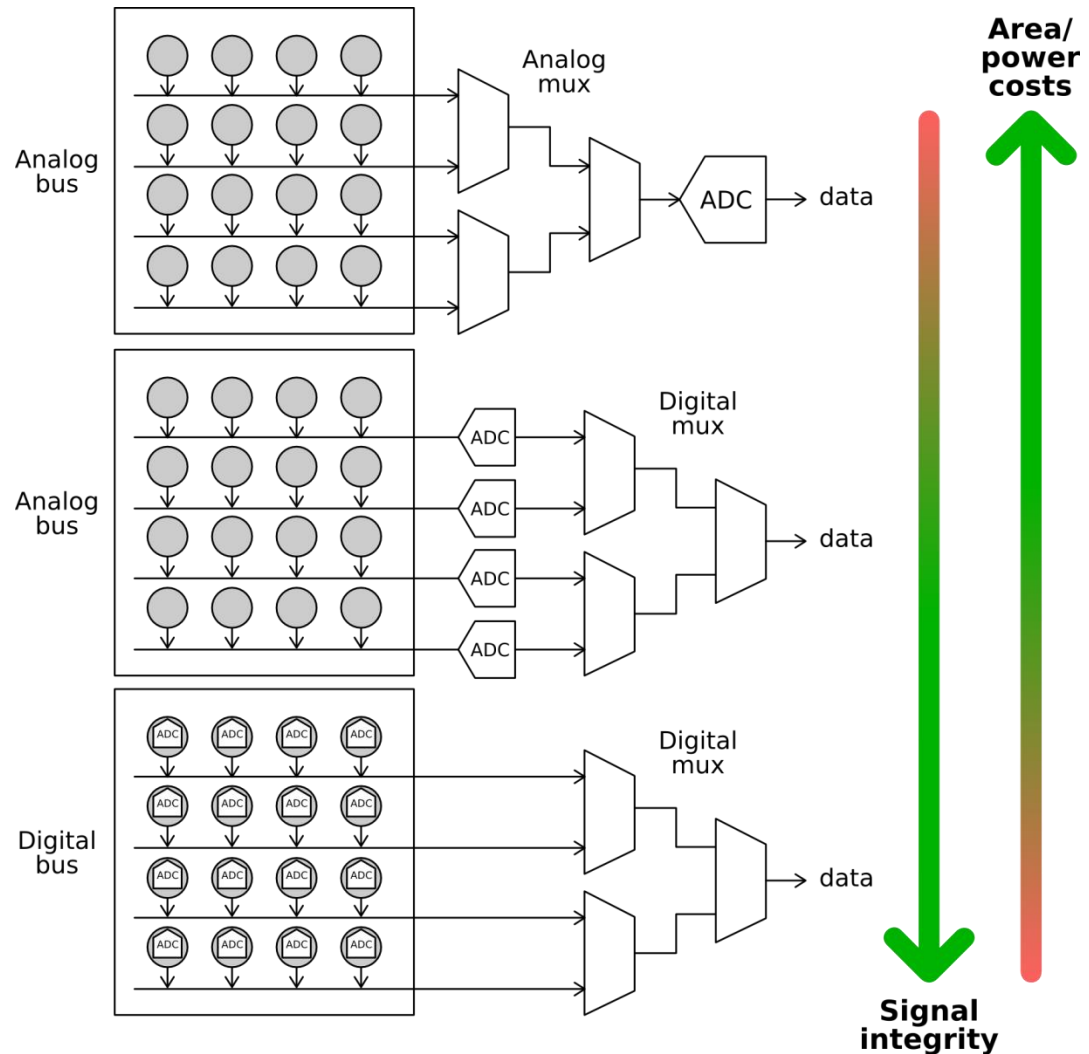
## Massive Parallel Processing


- ▼ Connectivity issues for large **sensory arrays**
- ▶ **Multi-channel** ROIC architecture?
  - Parallel A/D conversion reduces equivalent **noise bandwidth**
  - Early A/D conversion avoids **inter-symbol crosstalk**
  - Dedicated ADC per sensor increases **area** and **power** (temperature)






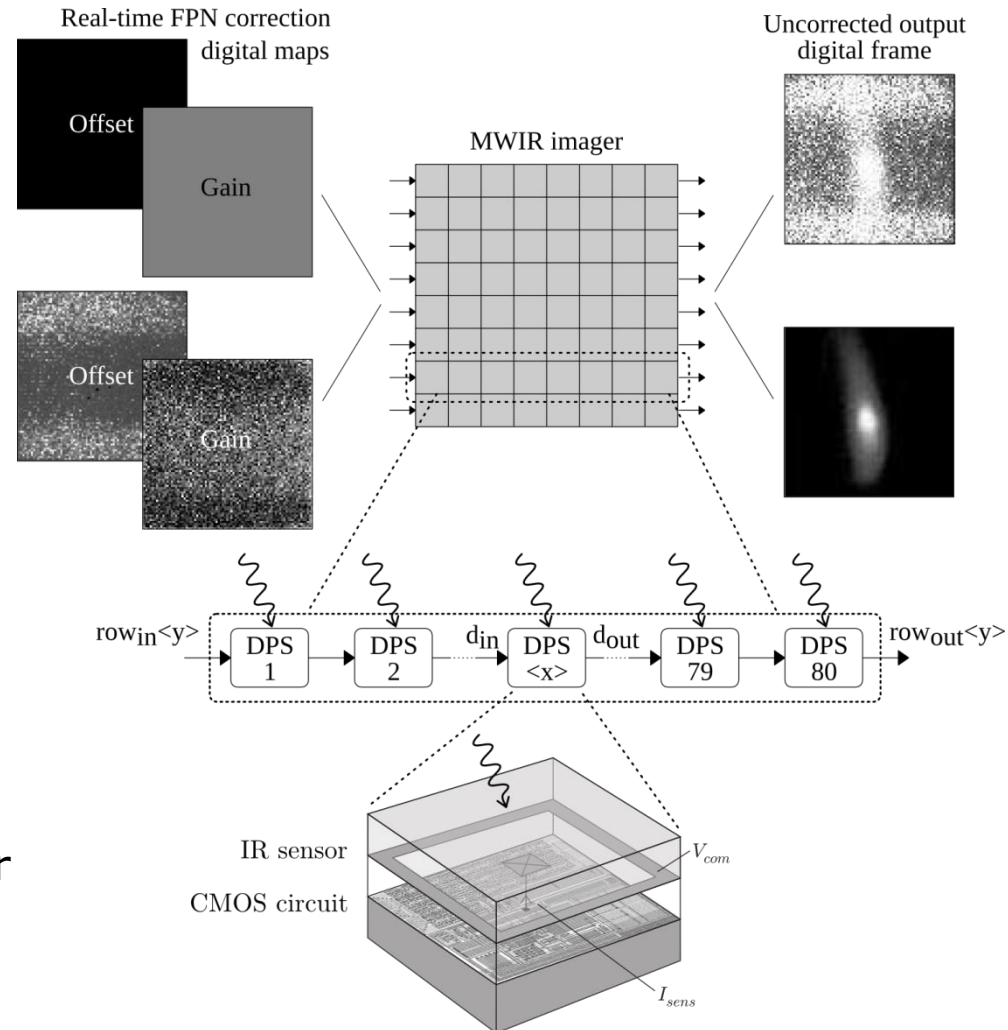
# High-Speed Uncooled IR Digital Imager

- ▶ Applications in strategic equipment, production quality control...
- ▶ Photoconductive **PbSe MWIR** sensors post-processed by VPD on top of CMOS
- High **frame rate** achievable at room temperature
- High fixed pattern noise (**FPN**)
- High speed **multiplexing** spec at focal plane array (FPA) level
- ▶ **Low power** digital pixel sensor (**DPS**) to not increase sensor temperature



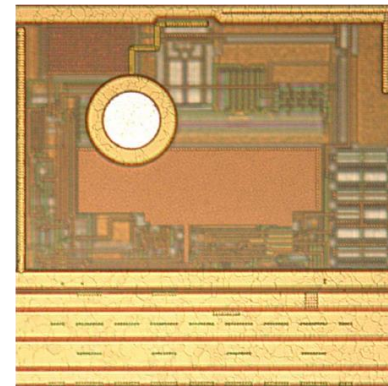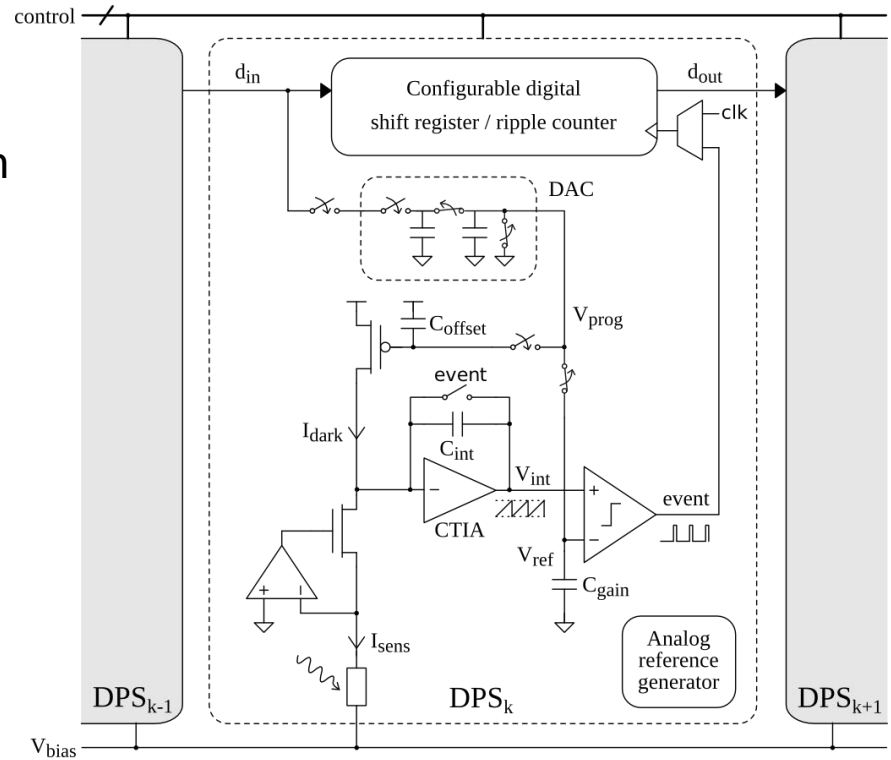
## ROIC Pixel Circuits

- ▲ Sensor **capacitance** compensation
- ▲ FPN **offset** (dark current) and **gain** (sensitivity) digital compensation
- ▲ In-pixel **A/D** conversion
- ▲ **Local bias** generator and **asynchronous** operation to minimize inter-pixel **crosstalk**
- ▲ **Daisy-chain** digital read-out and simultaneous program-in
- ▲ **Sub- $\mu\text{W}/\text{pix}$**  static power
- ▼ **135 $\mu\text{m}$ -pitch** in 0.35 $\mu\text{m}$  2P4M CMOS technology



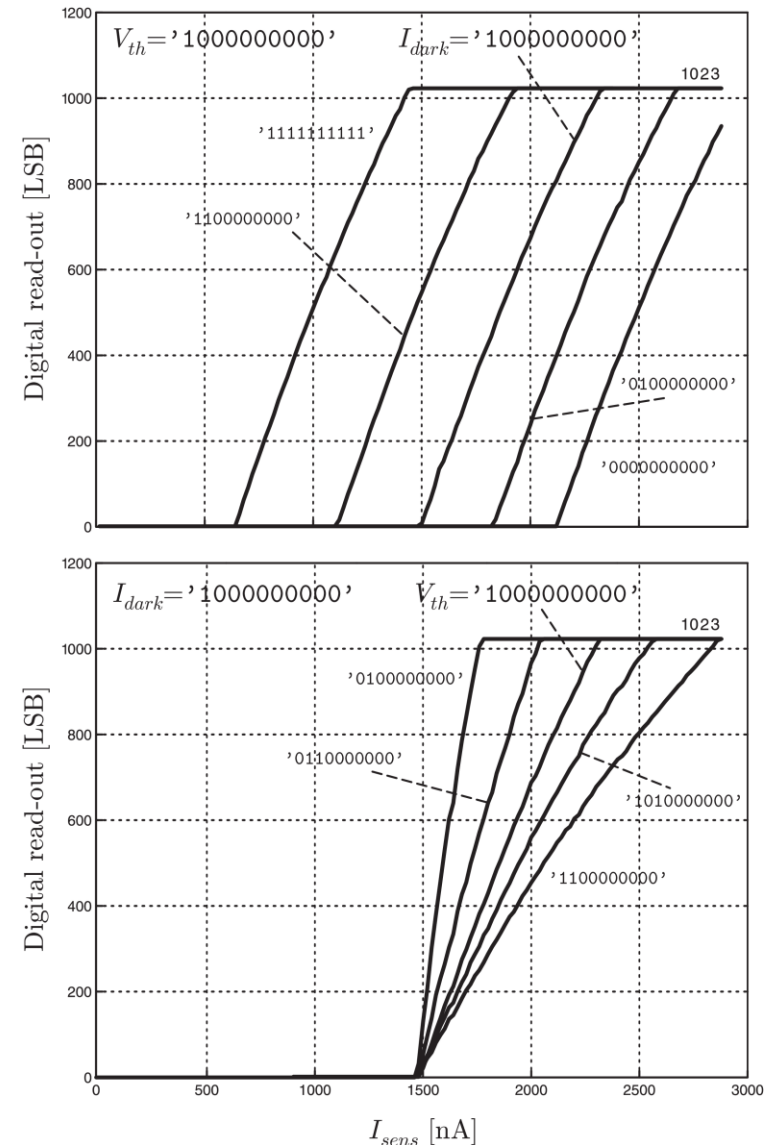
## ROIC Pixel Circuits

- ▲ Sensor **capacitance** compensation
- ▲ FPN **offset** (dark current) and **gain** (sensitivity) digital compensation
- ▲ In-pixel **A/D** conversion
- ▲ **Local bias** generator and **asynchronous** operation to minimize inter-pixel **crosstalk**
- ▲ **Daisy-chain** digital read-out and simultaneous program-in
- ▲ **Sub- $\mu\text{W}/\text{pix}$**  static power
- ▼ **135 $\mu\text{m}$ -pitch** in 0.35 $\mu\text{m}$  2P4M CMOS technology


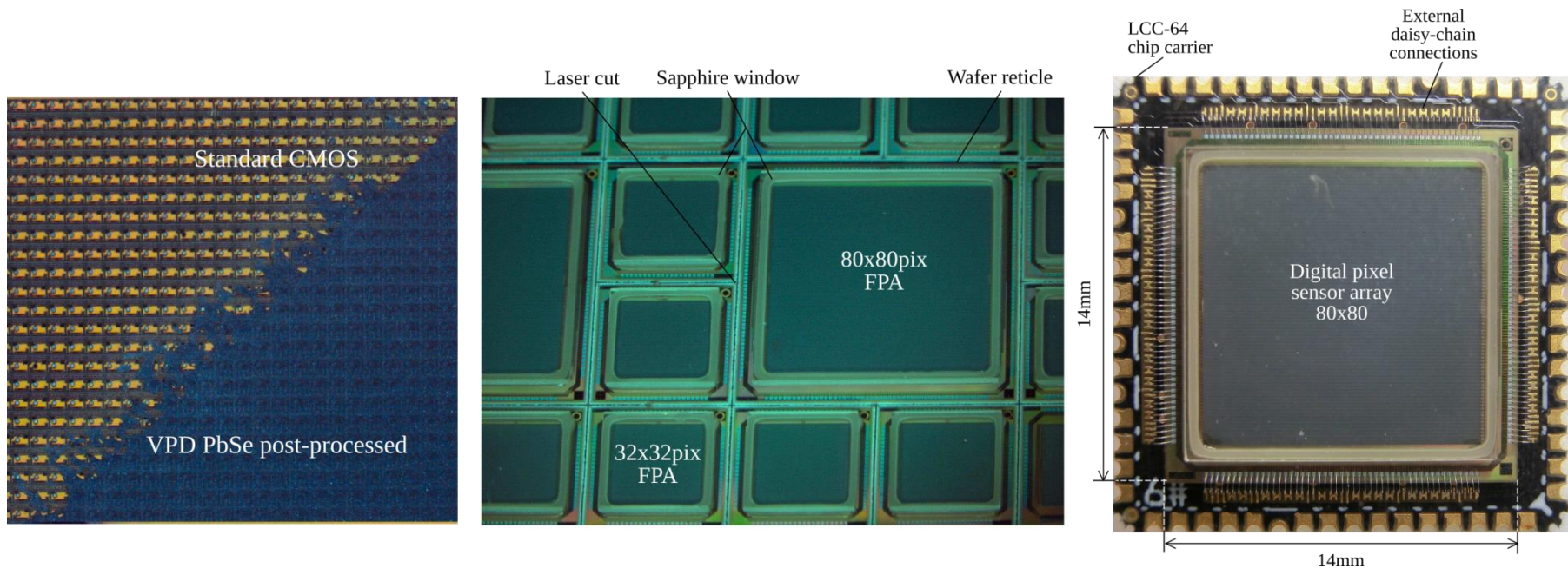
## Sensor Integration at Wafer Level


- ▶ **Au** deposition and patterning for contacts + active layer by **PbSe** VPD
- ▶ Sapphire window on top + **wire-bonding** to chip-carrier




- ▶ Access to sensor common bias terminal through ROIC pads

## IR Test Results

### ▲ In-pixel **full FPN** compensation

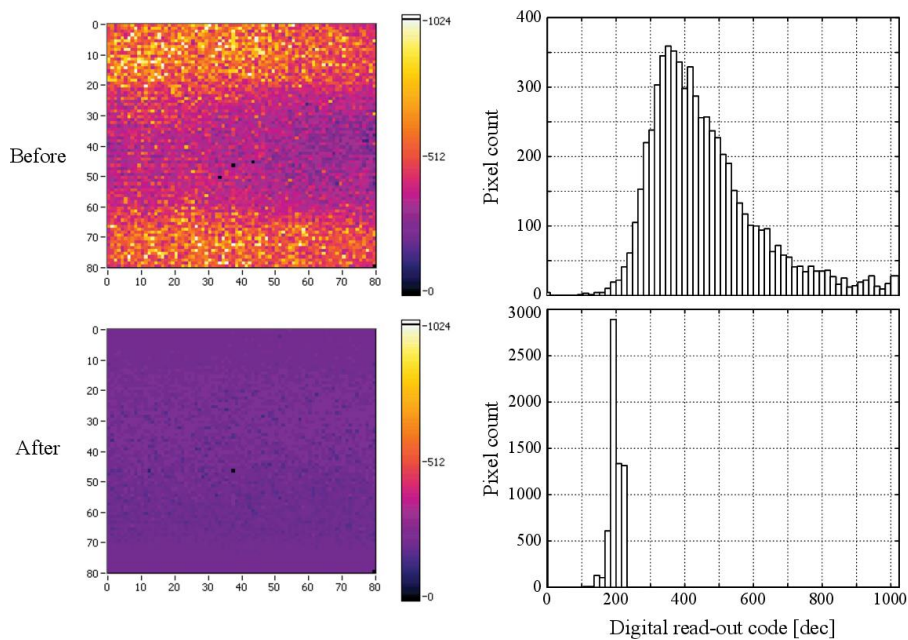
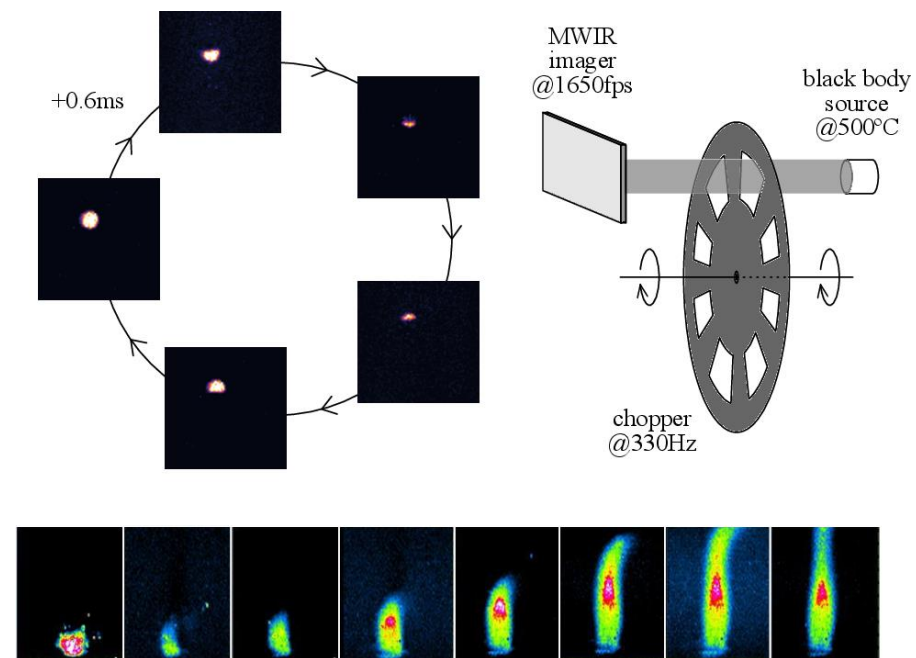
### ▲ **High speed** digital frame mux for both read-out and program-in



✉ J. Margarit et al., *A 2-kfps Sub-uW/Pix Uncooled-PbSe Digital Imager with 10-bit DR Adjustment and FPN Correction for High-Speed and Low-Cost MWIR Applications*, IEEE Journal of Solid-State Circuits, 2015, accepted




- 1 What is Missing?
- 2 Too Tiny to Be Touched
- 3 Process & Matching Nightmares
- 4 Biasing Specials
- 5 Flexibility as a Must
- 6 Massive Parallel Processing
- 7 Power-Aware Design
- 8 When Package Matters
- 9 My Nice Smart Sensor

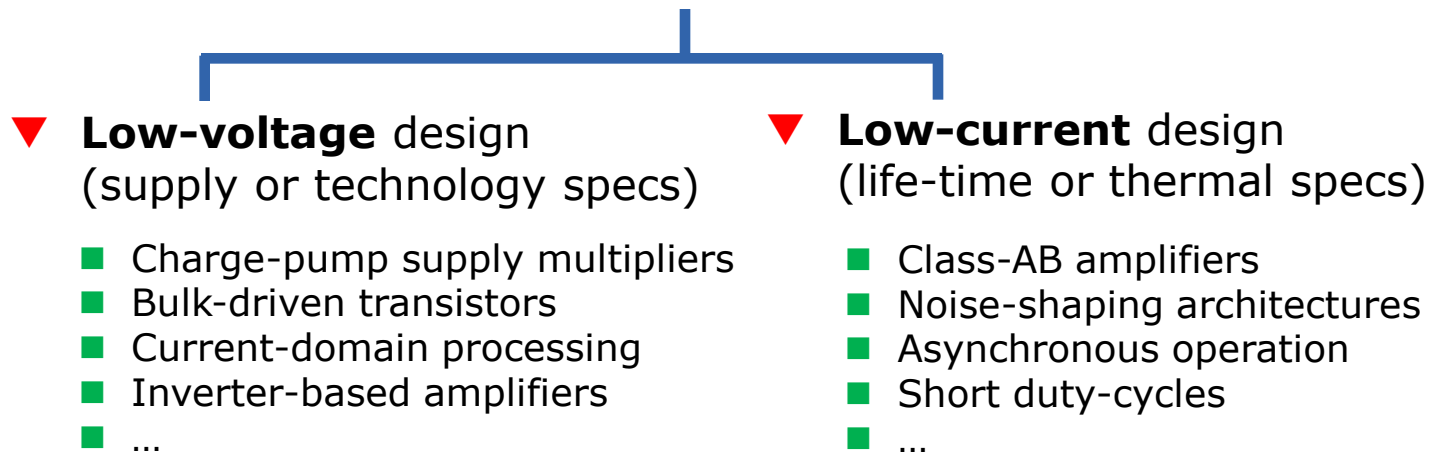
## Power-Aware Design

▼ Smart sensor **ubiquity** means limited power source!

► Analog circuit techniques for **low-power**?



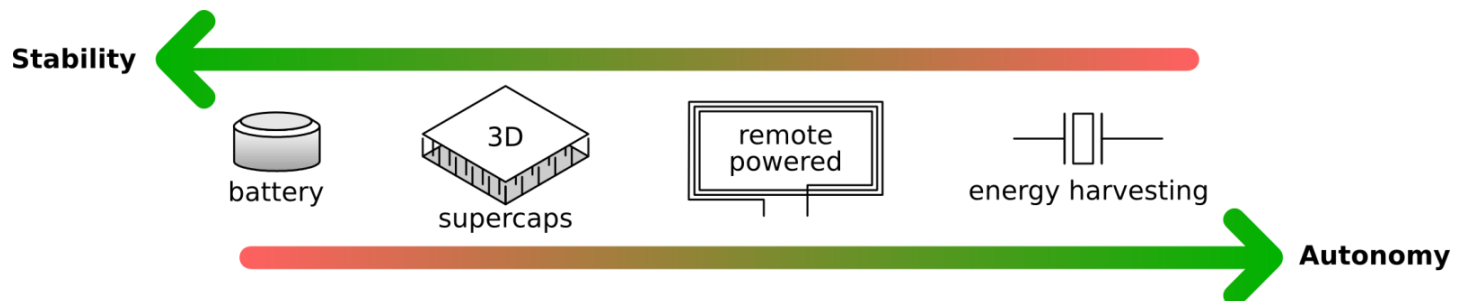► **Local energy source** solution (or combination) for each scenario?




## Remote Powered Impedimetric Sensor

- ▶ Applications in chemical industry control and biosensors...
- ▶ 13.56MHz ISM near field inductive coupling for **remote power** supply
- ▶ **Power ASK** for program-in
- ▶ **Load PWM** for read-out

- ▲ Complex I/Q impedance measurements for solution **conductivity** and **permittivity** monitoring



- ▲ Contact-less and **package-less**

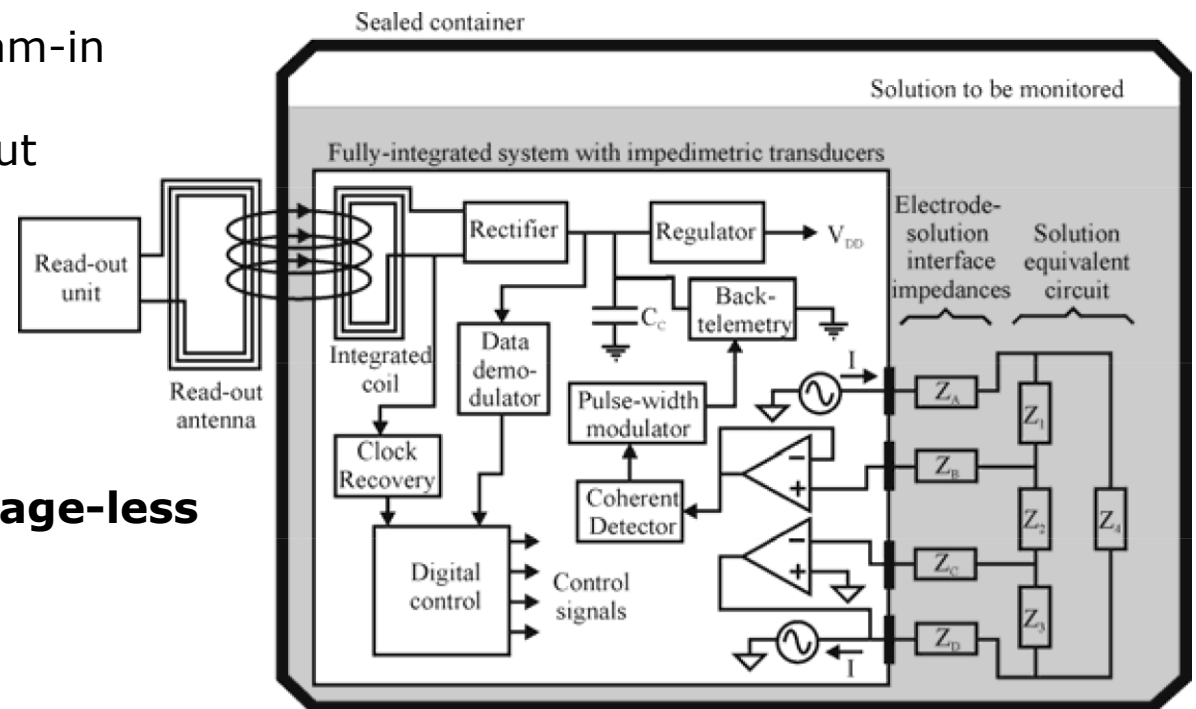



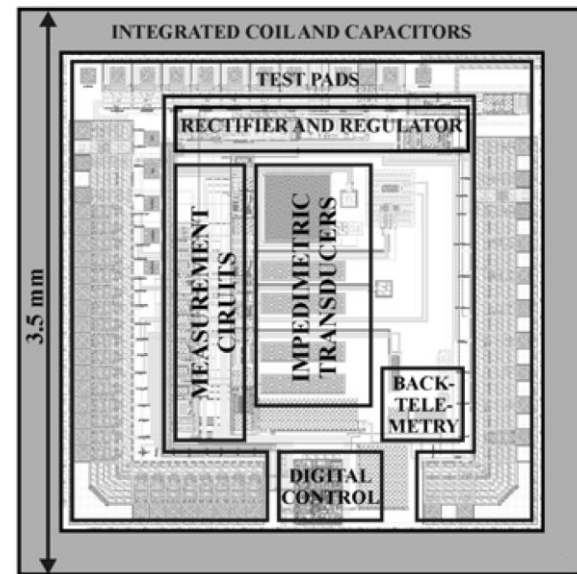
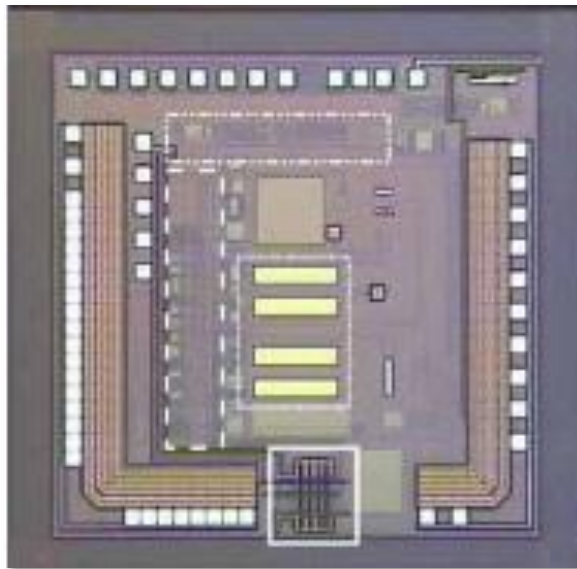
## CMOS Integration

- ▶ 0.35 $\mu\text{m}$  2P4M **high-voltage** CMOS technology
  - 3.5mm x 3.5mm (12.25mm<sup>2</sup>)
  - 3M **power coupling** coil ( $L \sim 8\mu\text{H}$ ,  $Q \sim 1$ ) and supply capacitor ( $C \sim 2\text{nF}$ ) at periphery
- ▶ Number of turns optimized for maximum **supply voltage** and out-band **self-resonant** frequency
- ▶ Pads for prototype testing purposes only



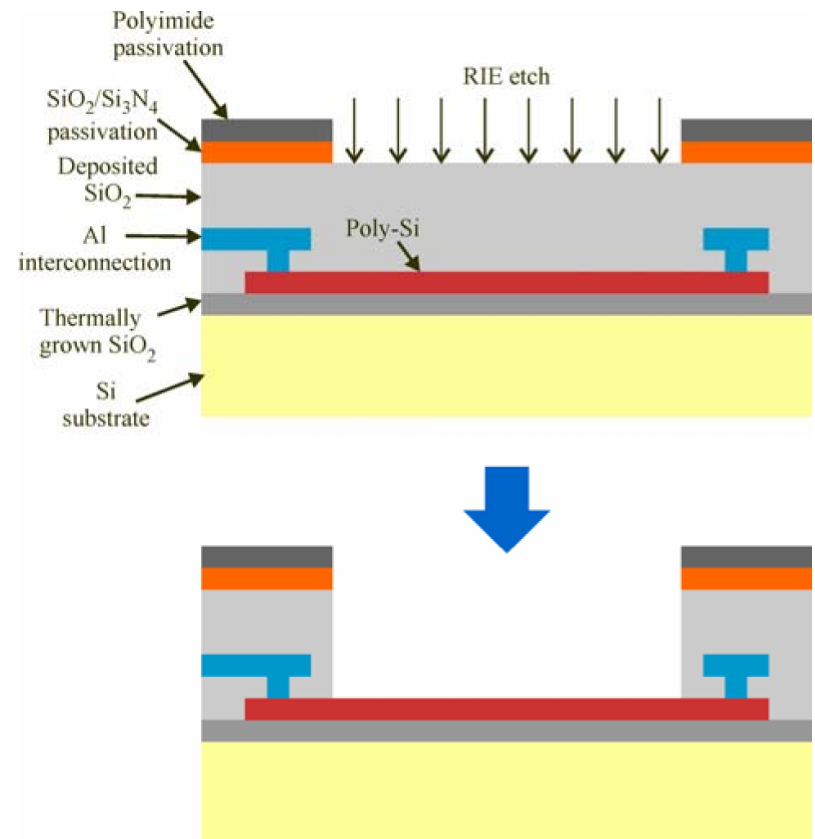
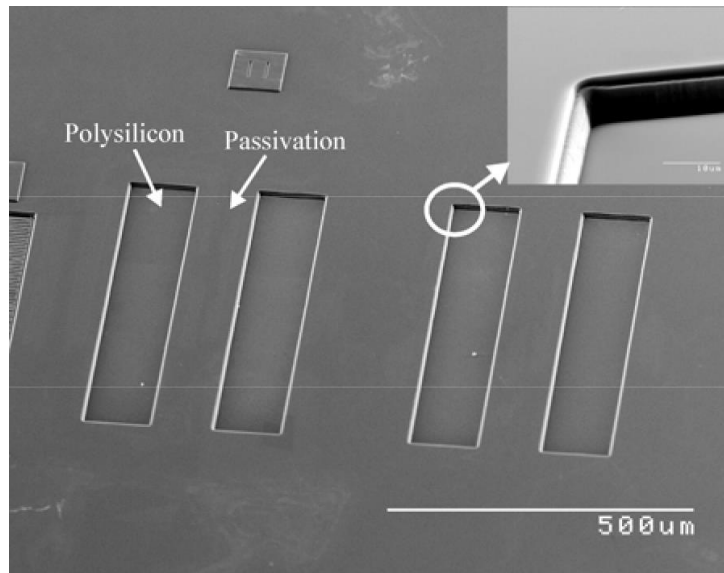
## Lithography-Less Post-Processing

- ▲ Poly-Silicon material + native oxidation (3nm) to improve microelectrode **reliability**
- ▶ **4-microelectrode** by  $\text{CHF}_3$ -based reactive ion etching (**RIE**)



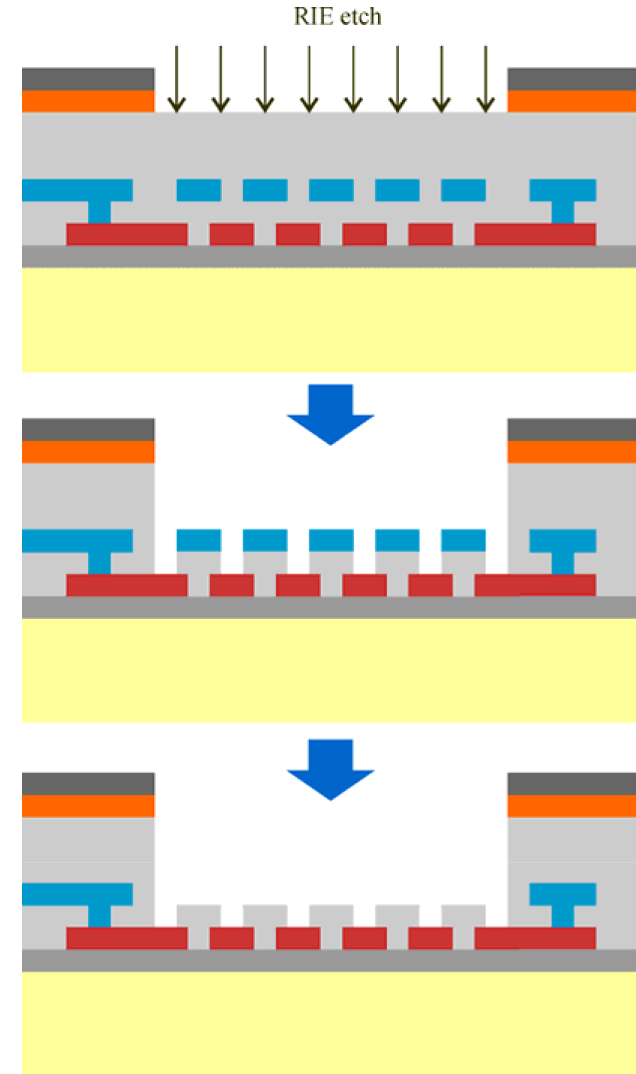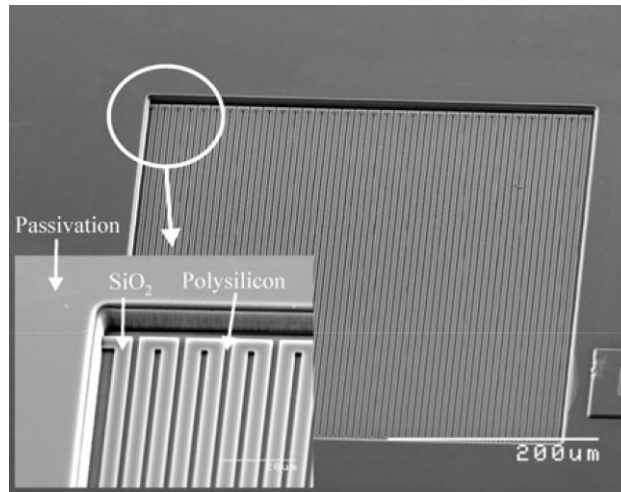
## Lithography-Less Post-Processing

- ▲ Poly-Silicon material + native oxidation (3nm) to improve microelectrode **reliability**
- ▶ **4-microelectrode** by  $\text{CHF}_3$ -based reactive ion etching (**RIE**)
- ▶ **Interdigitated 2-microelectrode** by RIE + 'piranha' ( $\text{H}_2\text{SO}_4$ ) solution



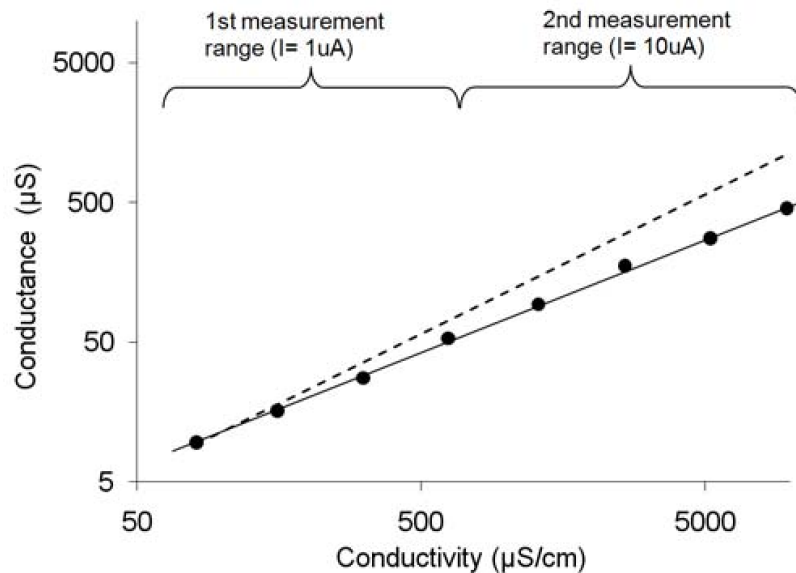
## Experimental Results

- ▲ Remote power **5mW** at **3mm** (up to >10cm with external resonator)
- ▲ Complex impedance measurement at **13kHz** (10kHz to 100kHz)



4-microelectrode

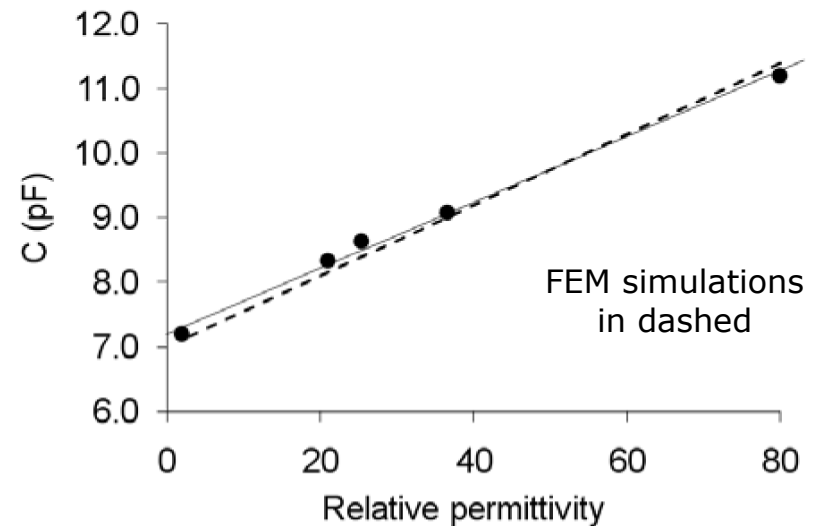

Interdigitated  
2-microelectrode

✉ F. Segura-Quijano et al., *Towards Fully Integrated Wireless Impedimetric Sensors*,  
MDPI Sensors, 10:4(4071-82), Apr 2010

- 1 What is Missing?
- 2 Too Tiny to Be Touched
- 3 Process & Matching Nightmares
- 4 Biasing Specials
- 5 Flexibility as a Must
- 6 Massive Parallel Processing
- 7 Power-Aware Design
- 8 When Package Matters
- 9 My Nice Smart Sensor

# When Package Matters

▼ Packaging costs can be dominant in **hybrid** smart sensors!



► **Sensor** needs?

- Signal integrity and parasitics
- Pitch matching
- Filling factor
- Exposure window
- ...

► **Application** requirements?

- Sensing area
- Environment compatibility
- ...

► **ROIC** optimum size


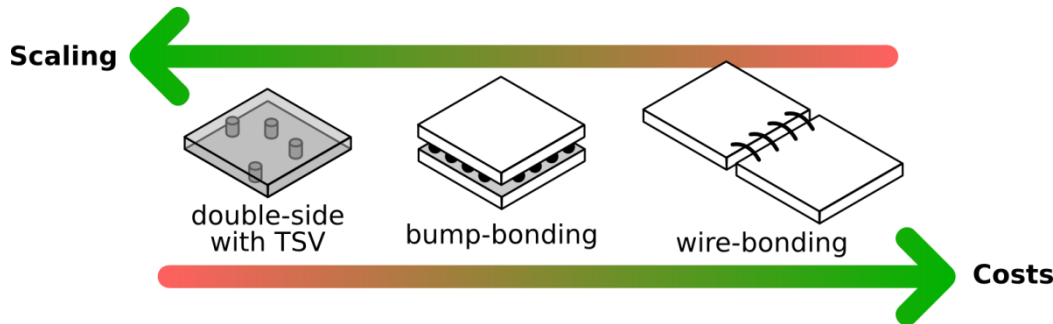
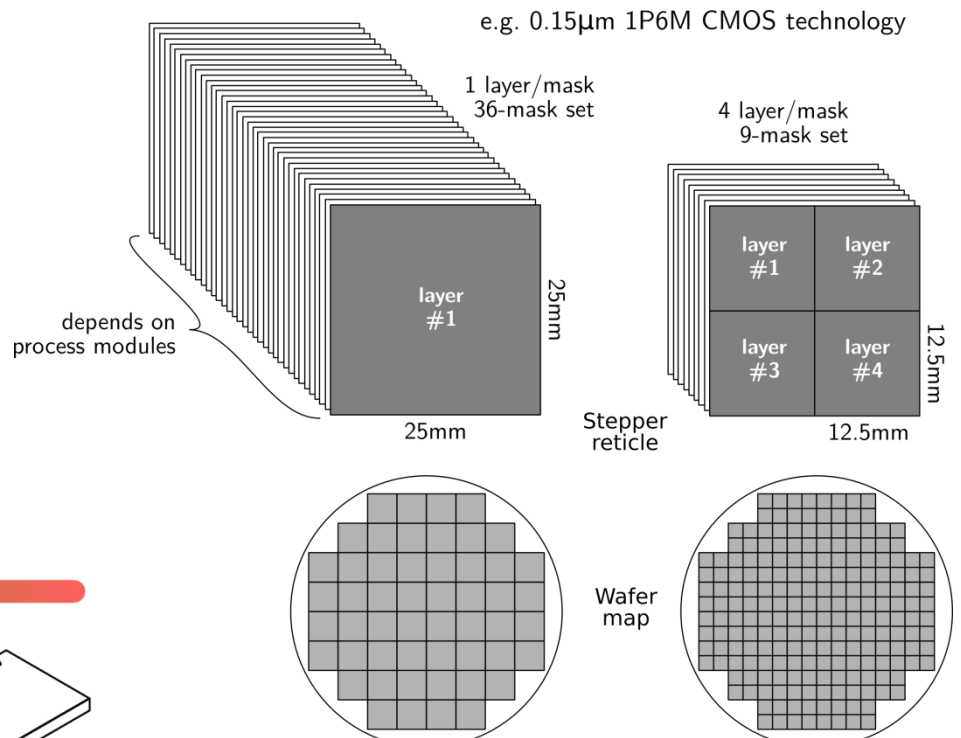


▲ **Modular** ROIC design + **MCM** packaging ?
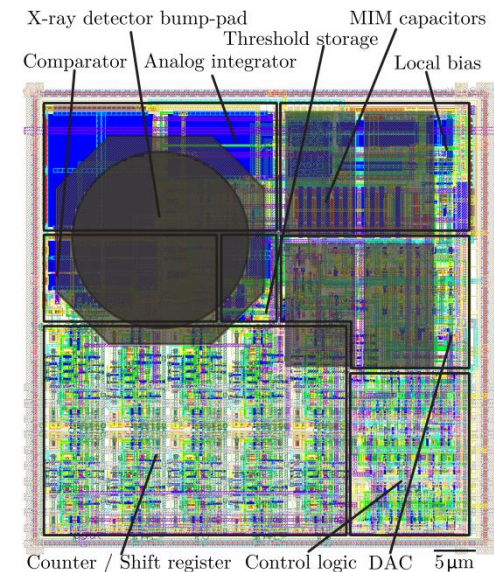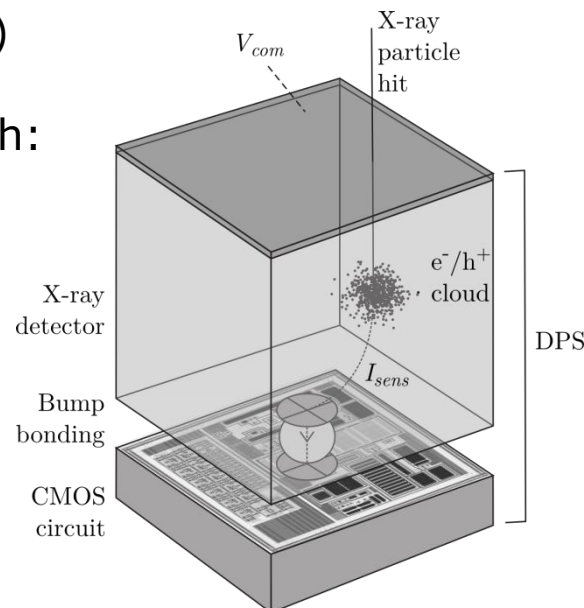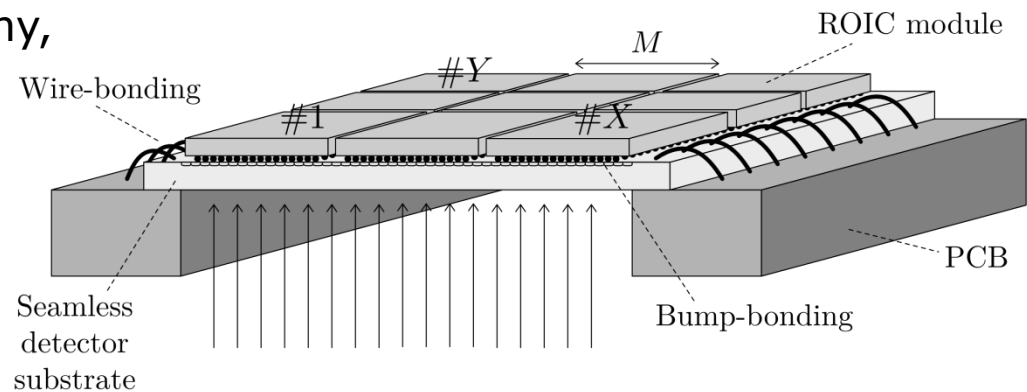
## 2D Modular Direct X-Ray Imager





- ▶ Applications in mammography, defect detection...
- ▶ CdTe or Si **direct X-ray** pixelated detectors
- ▶ Hybrid imager packaging by **bump-bonding** (bump growing + flip-chip)
- ▲ Fully autonomous **DPS** with:
  - Charge-integration ADC
  - Dark current cancellation
  - Gain FPN compensation
  - Built-in test
  - Local bias generator
- ▲ **55 $\mu\text{m}$ -pitch** detectors with high fill-factors





# Packaging for Seamless 2D Image
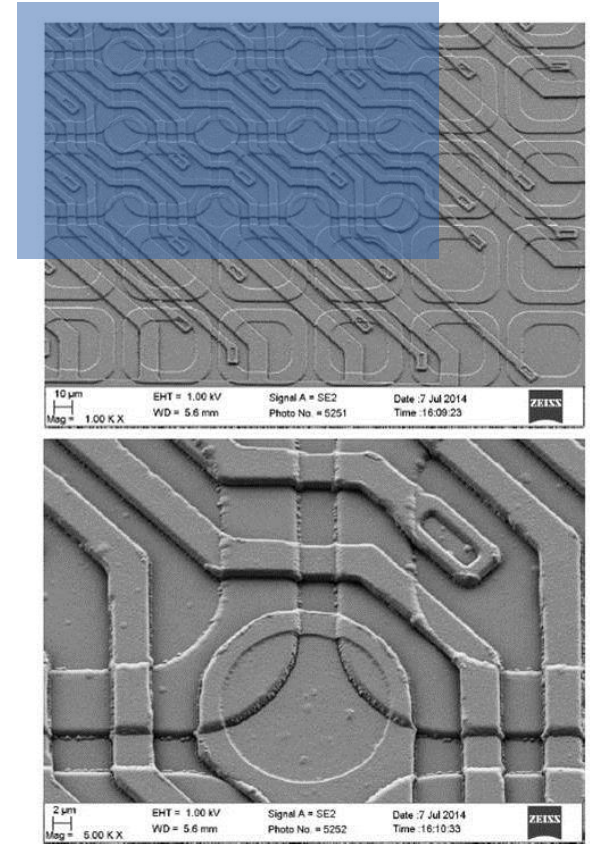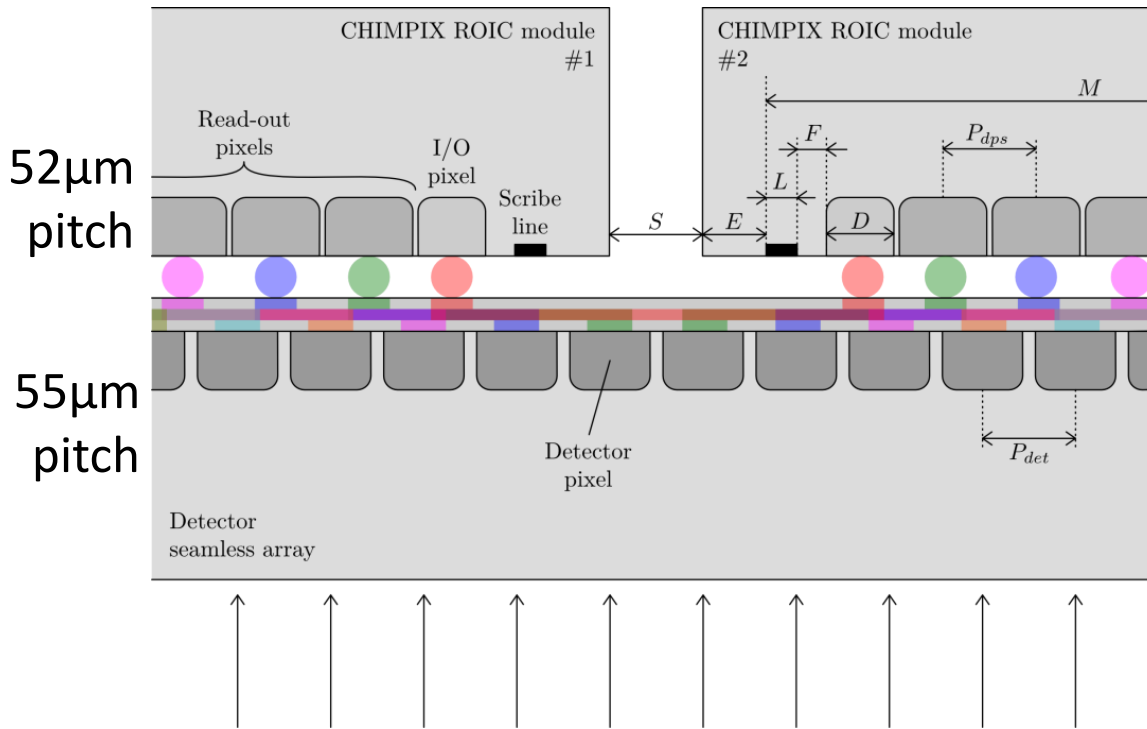
## ► Pixel detector-to-circuit rerouting...





▼ Inter-pixel crosstalk?

☞ R. Figueras et al., *A 70-um Pitch 8-uW Self-Biased Charge-Integration Active Pixel for Digital Mammography*, IEEE Transactions on Biomedical Circuits and Systems, 5:5(481-489), Oct 2011



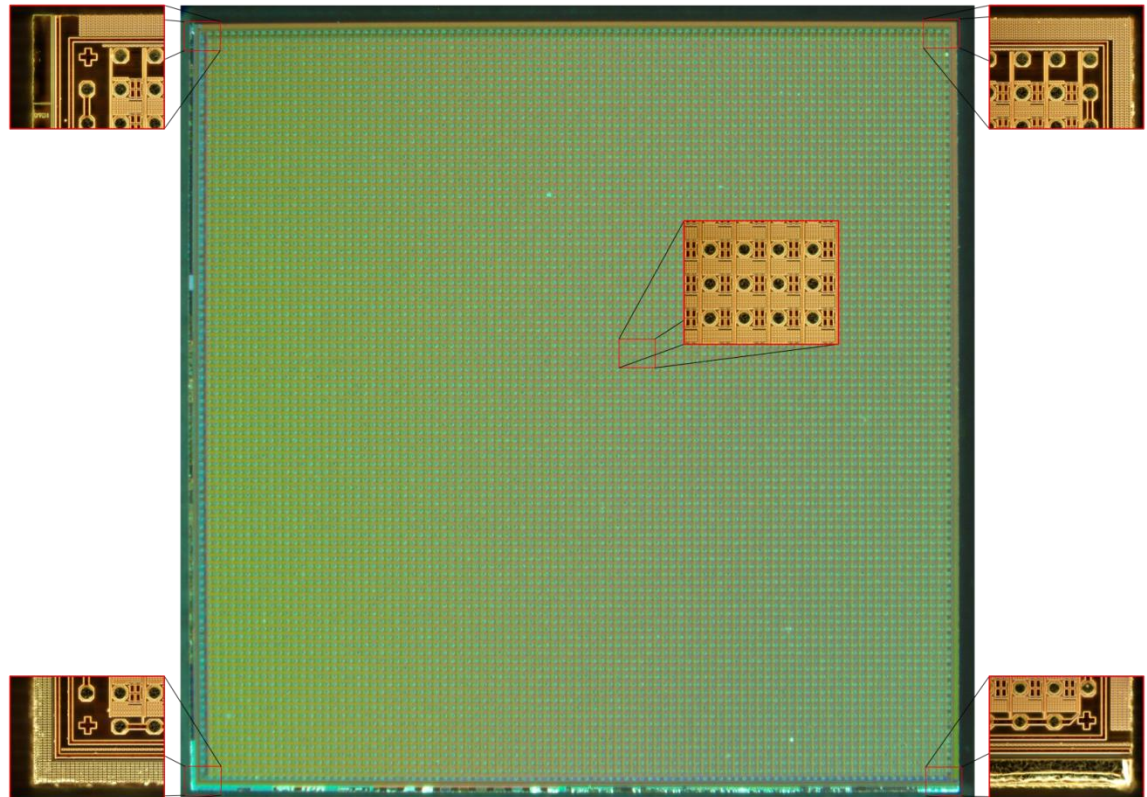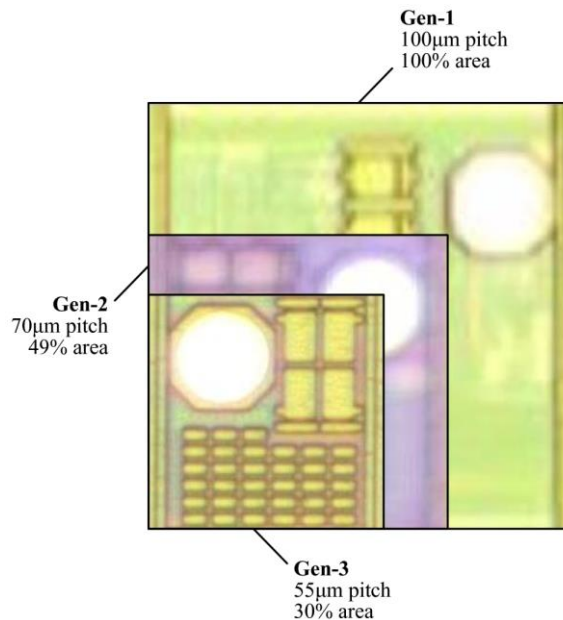
## CMOS ROIC Module

- ▶ 0.18 $\mu\text{m}$  1P6M CMOS technology
- ▶ 94 x 94 pixel (5mm x 5mm) **module**
- ▲ **52 $\mu\text{m}$ -pitch**
- ▲ **6 $\mu\text{W}$ /pix at +1.8V**


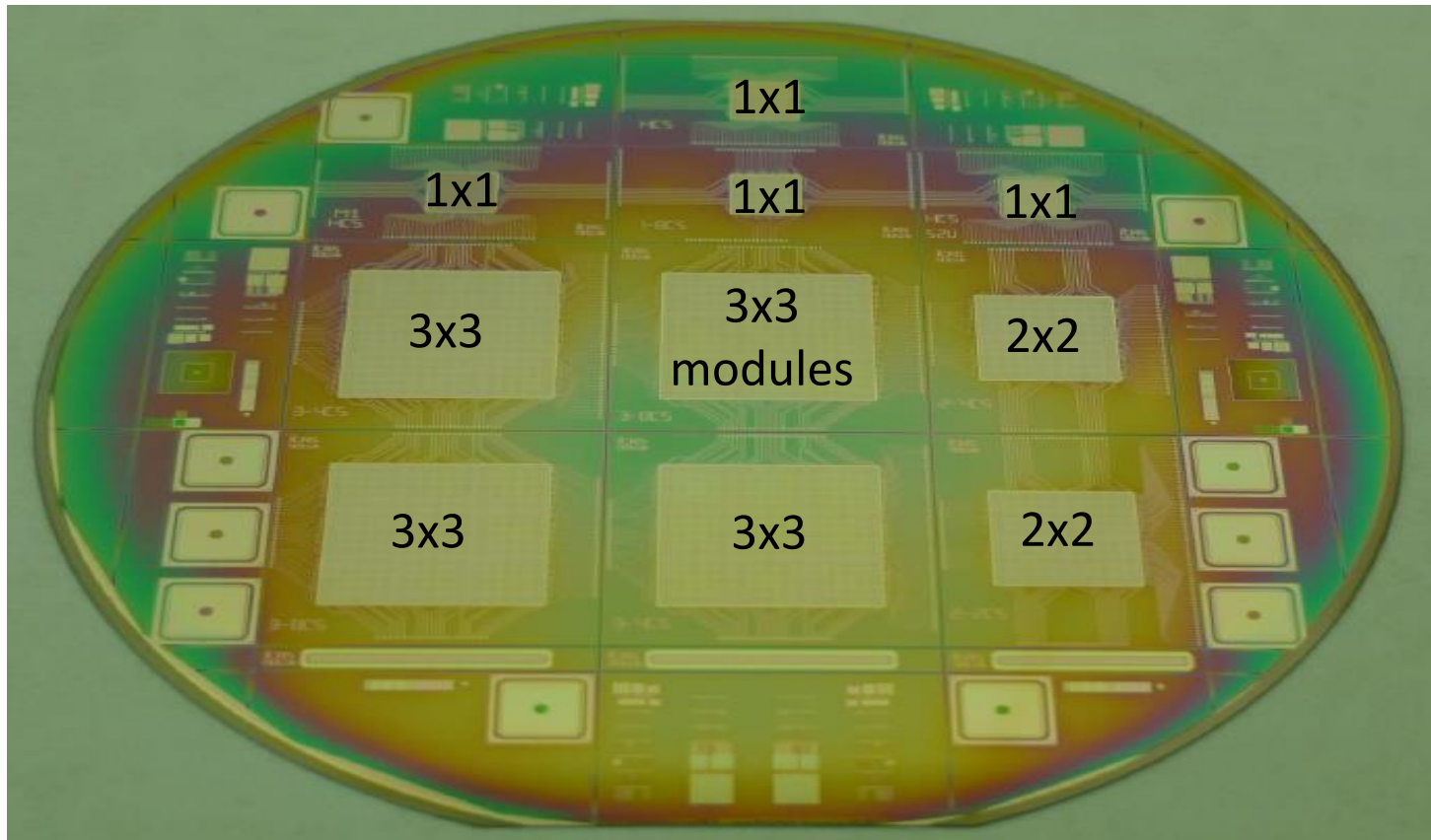
## Wafer-Level Sensor Integration

- ▶ 4"-wafer 55 $\mu$ m-pitch **Si X-ray detectors** from IMB-CNM(CSIC) to be tested...



- 1** What is Missing?
- 2** Too Tiny to Be Touched
- 3** Process & Matching Nightmares
- 4** Biasing Specials
- 5** Flexibility as a Must
- 6** Massive Parallel Processing
- 7** Power-Aware Design
- 8** When Package Matters
- 9** My Nice Smart Sensor

## My Nice Smart Sensor

- ▶ **Custom** + **standard** chip set
- ▲ Single **ROIC** design to cover a full family of sensors (e.g. chemical)
- ▲ **Local energy** harvesting + storage for ROIC + controller memory
- ▲ **Wireless** communications and remote power

