# 3. Multi-Stage OpAmps

#### Francesc Serra Graells

francesc.serra.graells@uab.cat Departament de Microelectrònica i Sistemes Electrònics Universitat Autònoma de Barcelona

> paco.serra@imb-cnm.csic.es Integrated Circuits and Systems IMB-CNM(CSIC)



### 1 Two-Stage Topologies

- 2 Frequency Compensation
- 3 Miller Effect
- 4 Design Space

#### 1 Two-Stage Topologies

- 2 Frequency Compensation
- 3 Miller Effect
- 4 Design Space

## **Splitting Functions**

**Single** stage CMOS OpAmp limitations:



## **Splitting Functions**

**V** Single stage CMOS OpAmp limitations:



## **Practical Example**

**Two-stage** fully differential folded cascode OpAmp topology:





## **Practical Example**





Frequency compensation strategy is needed under feedback (closed loop) operation...

× high-impedance nodes with dynamic

signals

- 1 Two-Stage Topologies
- 2 Frequency Compensation
- 3 Miller Effect
- 4 Design Space

#### **Basic control** theory:



$$\frac{V_{out}}{V_{in}} = \frac{G}{1 + GH} \simeq \frac{1}{H}$$

$$G \to \infty$$

# Single Stage OpAmp Case

#### ► Basic **control** theory:



 $|H| = \begin{cases} 0 & \text{open loop} \\ & & \\ 1 & \text{follower} \end{cases}$ 

$$\frac{V_{out}}{V_{in}} = \frac{G}{1 + GH} \simeq \frac{1}{H}$$

$$G \to \infty$$

#### **Single pole** amplifier:

$$G(s) = \frac{G_0}{1 + \frac{s}{w_p}}$$

$$\frac{V_{out}}{V_{in}}(s) = \frac{\frac{G_0}{1 + \frac{s}{w_p}}}{1 + \frac{G_0}{1 + \frac{s}{w_p}}H} = \frac{G_0}{1 + \frac{s}{w_p} + G_0H}$$

$$\frac{V_{out}}{V_{in}}(s) = \underbrace{\frac{G_0}{1 + G_0 H}}_{G'_0} \underbrace{\frac{1}{1 + \frac{s}{w_p(1 + G_0 H)}}}_{w'_p}$$
$$\frac{G'_0}{G_0} = \frac{1}{1 + G_0 H} \qquad \frac{w'_p}{w_p} = 1 + G_0 H$$



# Single Stage OpAmp Case



**Single pole** amplifier:





# Two-Stage OpAmp Case

**Double pole** analysis:



$$G(s) = \frac{G_0}{\left(1 + \frac{s}{w_{p1}}\right)\left(1 + \frac{s}{w_{p2}}\right)}$$

$$\frac{V_{out}}{V_{in}}(s) = \frac{G_0}{\left(1 + \frac{s}{w_{p1}}\right)\left(1 + \frac{s}{w_{p2}}\right) + G_0H}$$

$$w'_{p1,2} = -\frac{w_{p1} + w_{p2}}{2} \pm \frac{1}{2}\sqrt{(w_{p1} + w_{p2})^2 - 4(1 + G_0H)w_{p1}w_{p2}}$$



 $jw_{\bigstar}$ 

(H=0)

 $-\mathbf{x}$  $-w_{p1}$ 

 $H < \frac{1}{4G_0} \left( \frac{w_{p1}}{w_{p2}} + \frac{w_{p2}}{w_{p1}} - 2 \right) \uparrow \quad \text{in order to } \mathbf{H=1}$ 

 $H\uparrow$ 

(H=0)

 $-w_{p2}$ 

 $G_0 H < \frac{(w_{p1} + w_{p2})^2}{4w_{n1}w_{n2}} - 1$ 

root locus

 $\rightarrow \sigma$ 

# **Two-Stage OpAmp Case**

**Double pole** analysis:



$$G(s) = \frac{G_0}{\left(1 + \frac{s}{w_{p1}}\right) \left(1 + \frac{s}{w_{p2}}\right)}$$

$$\frac{V_{out}}{V_{in}}(s) = \frac{G_0}{\left(1 + \frac{s}{w_{p1}}\right)\left(1 + \frac{s}{w_{p2}}\right) + G_0H}$$

$$w'_{p1,2} = -\frac{w_{p1} + w_{p2}}{2} \pm \frac{1}{2}\sqrt{(w_{p1} + w_{p2})^2 - 4(1 + G_0 H)w_{p1}w_{p2}}$$
 dominant  
pole splitting  
is required!  $\frac{w_{p2}}{G_0 w_{p1}}$   $\uparrow$  or  $\frac{w_{p1}}{G_0 w_{p2}}$   $\uparrow$ 



ee

jw

# Two-Stage OpAmp Case

## Double pole analysis:





# 1 Two-Stage Topologies

- 2 Frequency Compensation
- 3 Miller Effect
- 4 Design Space



# **Principle of Operation**

**Transimpedance** amplifier:



$$\begin{cases} V_{out} = -GV_{in} \\ I_z = \frac{V_{in} - V_{out}}{Z} \end{cases}$$

# **Principle of Operation**





$$\begin{cases} V_{out} = -GV_{in} \\ I_z = \frac{V_{in} - V_{out}}{Z} \end{cases}$$

#### **Miller** effect:





$$Z_{in} \doteq \frac{V_{in}}{I_z} = \frac{V_{in}}{V_{in} - V_{out}}Z = \frac{Z}{1+G}$$



$$Z_{out} \doteq \frac{V_{out}}{-I_z} = \frac{V_{out}}{V_{out} - V_{in}} Z = \frac{G}{1+G} Z$$

## **Pole Adjustment**





## **Practical Example**

**Two-stage** single-ended **Miller-compensated** OpAmp topology:



## **Practical Example**



## 1 Two-Stage Topologies

- 2 Frequency Compensation
- 3 Miller Effect
- 4 Design Space



#### **Design Variables**

Single-ended Miller OpAmp example:





22/27

### **Design Variables**





- Device matching groups:
  - Current biasing

$$I_{diff} \doteq \underbrace{\frac{(W/L)_7}{(W/L)_8}}_{m_{diff}} I_{bias} \qquad I_{inv} \doteq \underbrace{\frac{(W/L)_5}{(W/L)_8}}_{m_{inv}} I_{bias}$$



## **Design Variables**



- Single-ended **Miller** OpAmp example:
- Device **matching** groups:

$$I_{diff} \doteq \underbrace{\frac{(W/L)_7}{(W/L)_8}}_{m_{diff}} I_{bias} \qquad I_{inv} \doteq \underbrace{\frac{(W/L)_5}{(W/L)_8}}_{m_{inv}} I_{bias}$$

$$\begin{pmatrix} \frac{W}{L} \\ 1 \end{pmatrix}_{1} \equiv \begin{pmatrix} \frac{W}{L} \\ 2 \end{pmatrix}_{2} \doteq \begin{pmatrix} \frac{W}{L} \\ \frac{W}{L} \end{pmatrix}_{diff}$$
$$\begin{pmatrix} \frac{W}{L} \\ 3 \end{pmatrix}_{3} \equiv \begin{pmatrix} \frac{W}{L} \\ 2 \end{pmatrix}_{4} \doteq \begin{pmatrix} \frac{W}{L} \\ \frac{W}{L} \end{pmatrix}_{sing}$$
$$\frac{I_{diff}/2}{I_{inv}} \equiv \frac{(W/L)_{3}}{(W/L)_{6}}$$
$$\begin{cases} \begin{pmatrix} \frac{W}{L} \\ 0 \end{pmatrix}_{diff} & \begin{pmatrix} \frac{W}{L} \\ 1 \end{pmatrix}_{sing} & \begin{pmatrix} \frac{W}{L} \\ 0 \end{pmatrix}_{inv} \\ I_{bias} & I_{diff} & I_{inv} & C_{comp} & L \end{cases}$$

# **Design Equations**



Single-ended **Miller** OpAmp example:



# **Design Equations**







$$SR_{+} = \frac{I_{inv} - I_{diff}}{C_{comp} + C_{load}}$$
$$SR_{-} = \frac{I_{diff}}{C_{comp}}$$
$$V_{inn} \equiv V_{out}$$
$$V_{inn} \equiv V_{inn}$$



## **Design Equations**

Single-ended **Miller** OpAmp example:

 $SR_{+} = \frac{I_{inv} - I_{diff}}{C_{comn} + C_{load}}$  $- 4 \begin{bmatrix} M7 \\ M7 \\ V \\ I_{diff} \end{bmatrix} M5$ i M8 | þ  $SR_{-} = \frac{I_{diff}}{C}$  $V_{inn} \leftarrow \left( \begin{array}{c} \mathsf{M1} \\ \mathsf{M2} \\ \mathsf{M2} \\ \mathsf{M3} \\ \mathsf{M4} \\ \mathsf{M4} \\ \mathsf{M6} \\ \mathsf{$  $I_{bias}$  $\frac{I_{diff}/2}{I_{inv}} \equiv \frac{(W/L)_{sing}}{(W/L)_{inv}}$  $GBW = \frac{g_{mg1,2}}{2\pi C_{comp}} = \frac{1}{2\pi C_{comp}} \sqrt{\frac{\beta_P}{n} \left(\frac{W}{L}\right)_{ucc}} I_{diff}$  $\sum I \sum WL$ performance  $G(DC) = \frac{g_{mg1,2}}{g_{md1,2} + g_{md3,4}} \frac{g_{mg6}}{g_{md5} + g_{md6}} = \frac{2}{n(\lambda_N + \lambda_P)^2} \sqrt{\frac{2\beta_P \beta_N \left(\frac{W}{L}\right)_{diff} \left(\frac{W}{L}\right)_{inv}}{I_{diff} I_{inv}}}$ resources



**strong** inversion forward **saturation** for all transistors