

5. Low-Power OpAmps

Francesc Serra Graells

francesc.serra.graells@uab.cat

Departament de Microelectrònica i Sistemes Electrònics
Universitat Autònoma de Barcelona

paco.serra@imb-cnm.csic.es


Integrated Circuits and Systems
IMB-CNM(CSIC)

- 1 Low-Voltage vs Low-Current
- 2 Subthreshold Operation
- 3 Class-AB Output Stages
- 4 Rail-to-Rail Topologies
- 5 Inverter-Based Pseudo-Differential Multi-Stages Architectures

- 1 Low-Voltage vs Low-Current
- 2 Subthreshold Operation
- 3 Class-AB Output Stages
- 4 Rail-to-Rail Topologies
- 5 Inverter-Based Pseudo-Differential Multi-Stages Architectures

Low-Voltage vs Low-Current


- ▶ OpAmp overall **power** consumption:

 

$$P_{DD} = I_{DD} \times V_{DD}$$

Low-Voltage vs Low-Current

- OpAmp overall **power** consumption:

 

$$P_{DD} = I_{DD} \times V_{DD}$$


- ▲ Alternative supply **sources**
(battery, solar cell, scavenging)

- ▼ **Poor** power scaling

- ▼ Limited by **technology**


- **Low-voltage** circuit techniques:

 - Rail-to-rail
- Inverter-based
- Supply multipliers
- Back gate ...



Low-Voltage vs Low-Current

- OpAmp overall **power** consumption:

 


$$P_{DD} = I_{DD} \times V_{DD}$$

- ▲ **Strong** power savings
- ▼ Limited by **noise** and **bandwidth**
- **Low-current** circuit techniques:
 - Subthreshold
 - Class-AB
 - Dynamic biasing
 - Duty cycle ...

- ▲ Alternative supply **sources**
(battery, solar cell, scavenging)
- ▼ **Poor** power scaling
- ▼ Limited by **technology**
- **Low-voltage** circuit techniques:
 - Rail-to-rail
 - Inverter-based
 - Supply multipliers
 - Back gate ...

Low-Voltage vs Low-Current

- ▶ OpAmp overall **power** consumption:

 

$$P_{DD} = I_{DD} \times V_{DD}$$

- ▲ **Strong** power savings
- ▼ Limited by **noise** and **bandwidth**

- ▶ **Low-current** circuit techniques:

- Subthreshold
- Class-AB
- Dynamic biasing
- Duty cycle ...

- ▲ Alternative supply **sources**
(battery, solar cell, scavenging)

- ▼ **Poor** power scaling

- ▼ Limited by **technology**

- ▶ **Low-voltage** circuit techniques:


- Rail-to-rail
- Inverter-based
- Supply multipliers
- Back gate ...

- ▼ **Conflicts** can arise between low-current and low-voltage design techniques!

- 1 Low-Voltage vs Low-Current
- 2 Subthreshold Operation
- 3 Class-AB Output Stages
- 4 Rail-to-Rail Topologies
- 5 Inverter-Based Pseudo-Differential Multi-Stages Architectures


Optimizing MOSFET Biasing

 - ▶ Each transistor has its own **purpose** and **requirements**!




Optimizing MOSFET Biasing

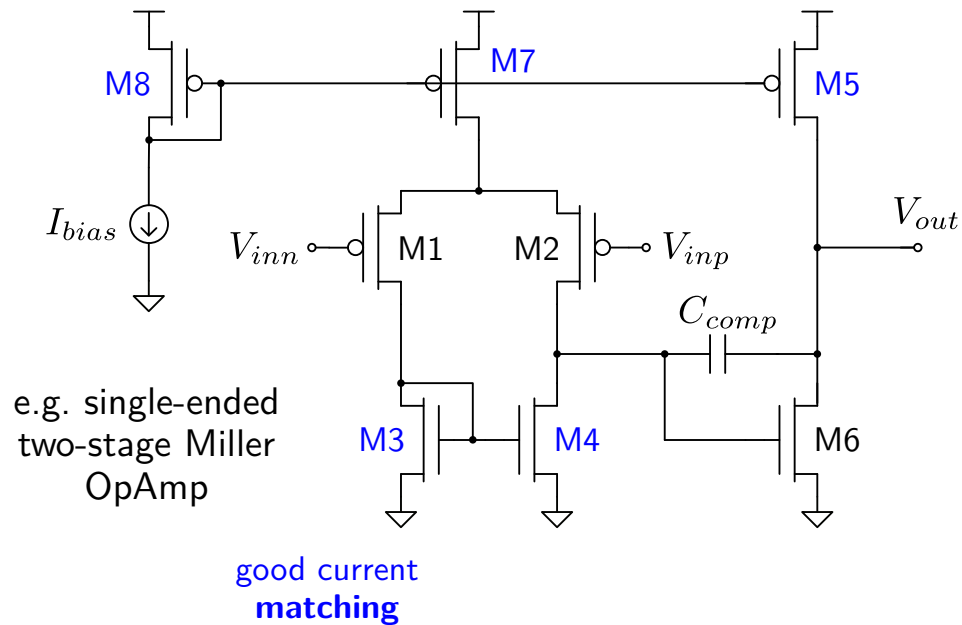- ▶ Each transistor has its own **purpose** and **requirements**!





Optimizing MOSFET Biasing

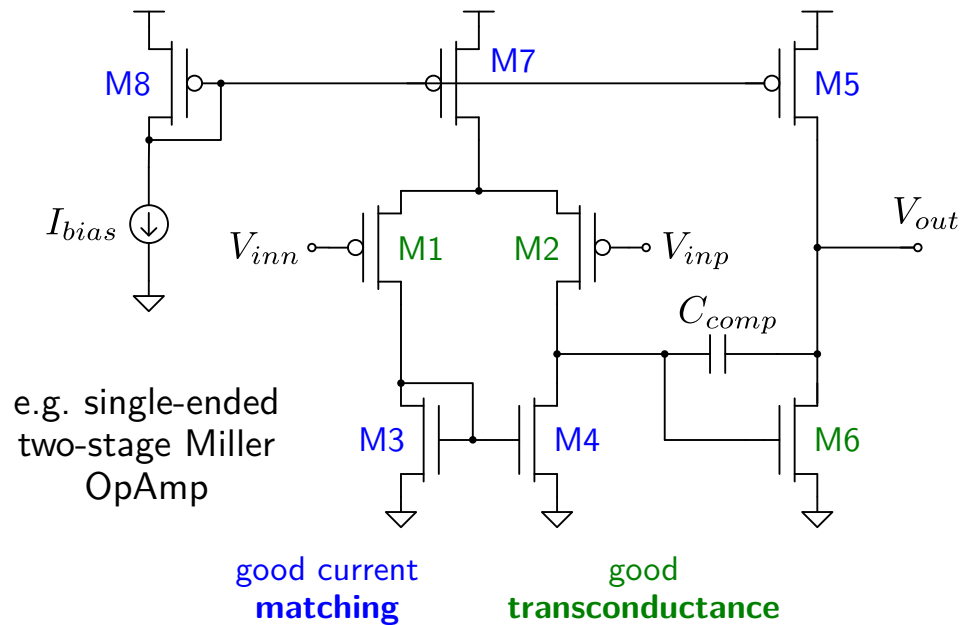- ▶ Each transistor has its own **purpose** and **requirements**!




Optimizing MOSFET Biasing

 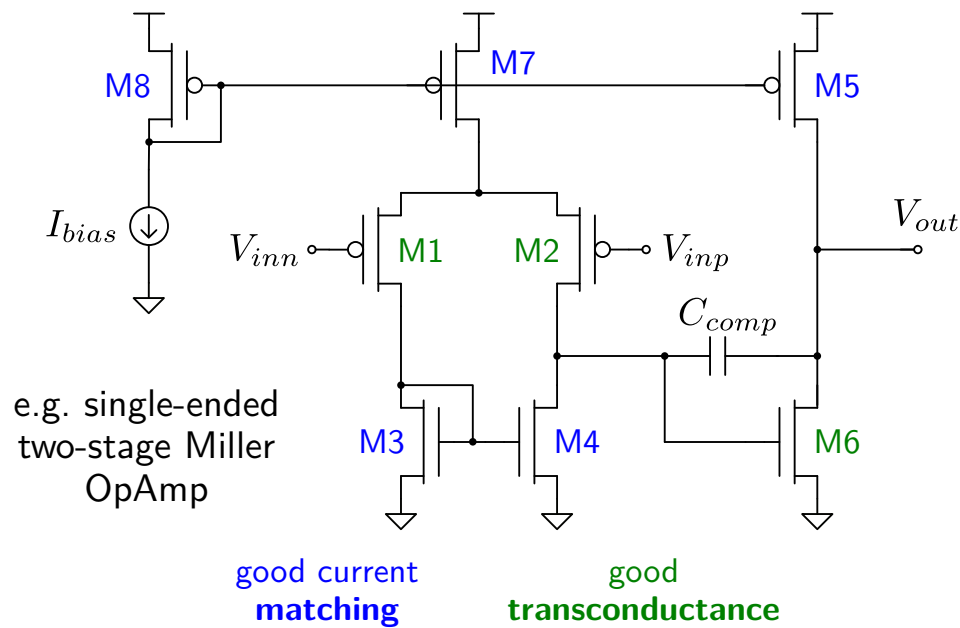- Each transistor has its own **purpose** and **requirements**!



Optimizing MOSFET Biasing

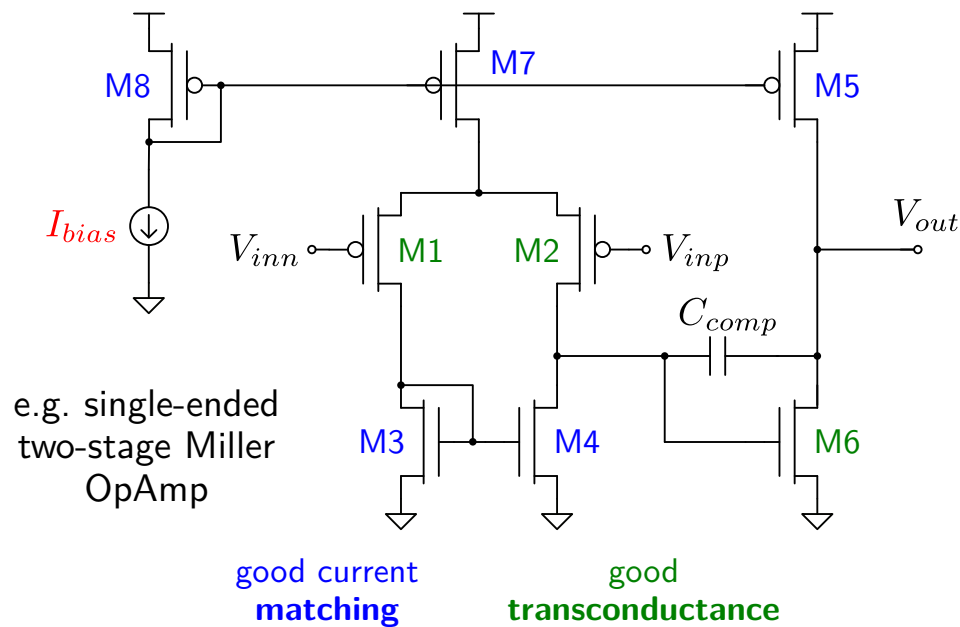
- ▶ Each transistor has its own **purpose** and **requirements**!



- ▶ **IC-based** circuit design:

- $IC \gg 1$ e.g. good current matching
- $IC \sim 1$ **optimized transconductance/power**
- $IC \ll 1$ e.g. translinear e^x functions

 - ▲ Individual operating point selection by **sizing** + **biasing**:




Specific Current Generator

► I_S -based current reference:

proportional to
absolute temperature
(PTAT)

Neglecting CLM

$$V_{ptat} = U_t \ln P$$

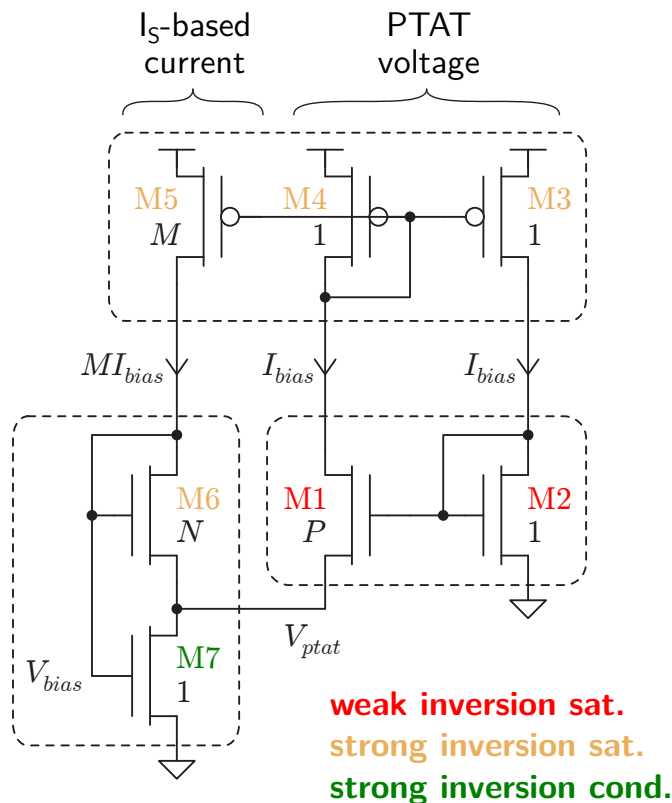

$$\begin{cases} MI_{bias} = \frac{N\beta_7}{2n} (V_{bias} - V_{TH} - nV_{ptat})^2 \\ (M+1)I_{bias} = \beta_7 \left(V_{bias} - V_{TH} - \frac{n}{2}V_{ptat} \right) V_{ptat} \end{cases}$$

$$Q = \left[\frac{\ln P}{2(M+1)} \left(\sqrt{\frac{M}{N}} + \sqrt{\frac{M}{N} + M+1} \right) \right]^2$$

$$I_{bias} \doteq Q I_{S7}$$

▲ By using I_{bias} for biasing circuits, IC selection is **independent** from technology




<http://dx.doi.org/10.1109/JSSC.2002.806258>

F. Serra-Graells et al., *Sub-1V CMOS Proportional-To-Absolute-Temperature References*, IEEE Journal of Solid-State Circuits, 38:1(84-8), Jan 2003

Specific Current Generator

- **I_S -based** current reference:

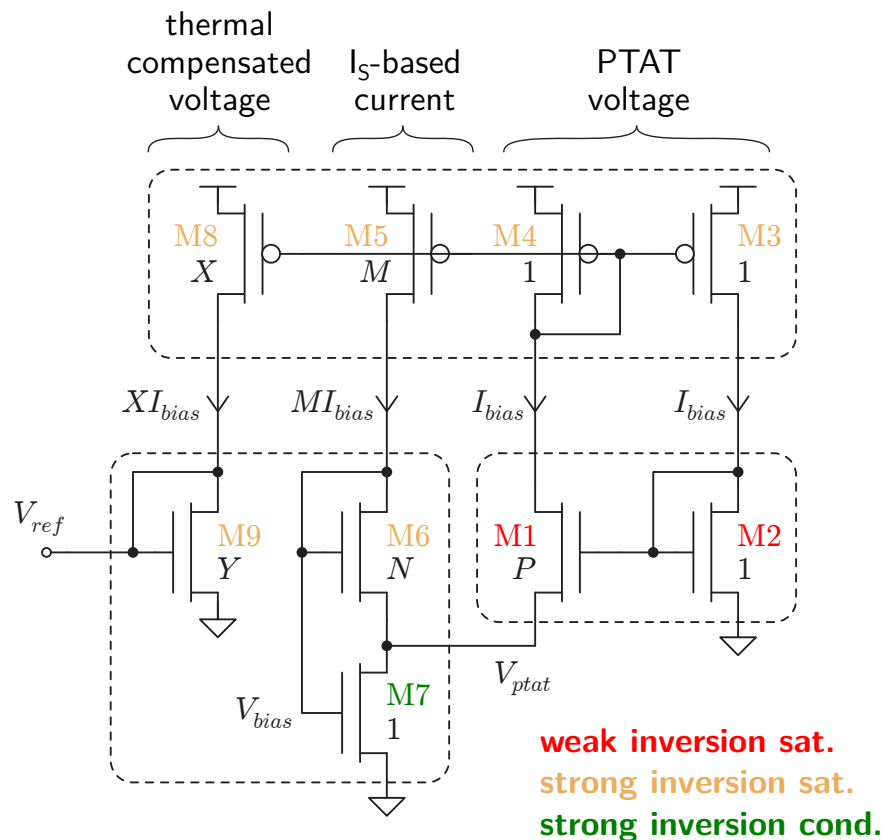

- ▲ As a side effect, **temperature compensated** voltage references can be also obtained:


$$V_{ref} = 2n\sqrt{\frac{QX}{Y}}U_t + V_{TH}$$

$$V_{TH}(T) = V_{TH}(T_O) - \alpha \left(\frac{T}{T_O} - 1 \right)$$

$$\sqrt{\frac{QX}{Y}} = \frac{1}{2n} \frac{\alpha}{U_t(T_O)}$$

$$V_{ref} \equiv \alpha + V_{TH}(T_O)$$

- ▲ By using I_{bias} for biasing circuits, IC selection is **independent** from technology


 <http://dx.doi.org/10.1109/JSSC.2002.806258>

F. Serra-Graells et al., *Sub-1V CMOS Proportional-To-Absolute-Temperature References*, IEEE Journal of Solid-State Circuits, 38:1(84-8), Jan 2003


- 1 Low-Voltage vs Low-Current
- 2 Subthreshold Operation
- 3 Class-AB Output Stages
- 4 Rail-to-Rail Topologies
- 5 Inverter-Based Pseudo-Differential Multi-Stages Architectures

Output Operation Class

- ▶ OpAmp **power** investment:

 


- ▶ **Output stage** operation modes:


 


Output Operation Class


- OpAmp **power** investment:

 


- **Output stage** operation modes:

  


Class-A

 


Class-B

 


Class-G/H

 


Class-AB

 

Class-C

 


Class-E/F

 

Class-D

Basic CMOS Topologies

► Inverter-like stage:

 


Class-AB
modulation
index

$$m = \frac{|I_{out}|_{max}}{I_{bias}}$$


MN and MP
static **bias current**

► Push-pull type stage:

 

Basic CMOS Topologies

► Inverter-like stage:

 


Class-AB
modulation
index

$$m = \frac{|I_{out}|_{max}}{I_{bias}}$$

MN and MP
static **bias current**

- High **voltage gain**
- Intrinsic high **output impedance** ($1/g_{md}$)
- Suitable for **capacitive loads only**
- Optimized **full-scale**

► Push-pull type stage:

 


- Unity **voltage gain**
- Intrinsic low **output impedance** ($1/g_{ms}$)
- Suitable for any type of **load impedance**
- Reduced **full-scale**

- **Biasing circuitry** to control I_{bias} against PVT (CMOS process, supply voltage and temperature) corners and to reach high Class-AB **m-values**?

Class-AB Stage Examples

► Translinear loops:

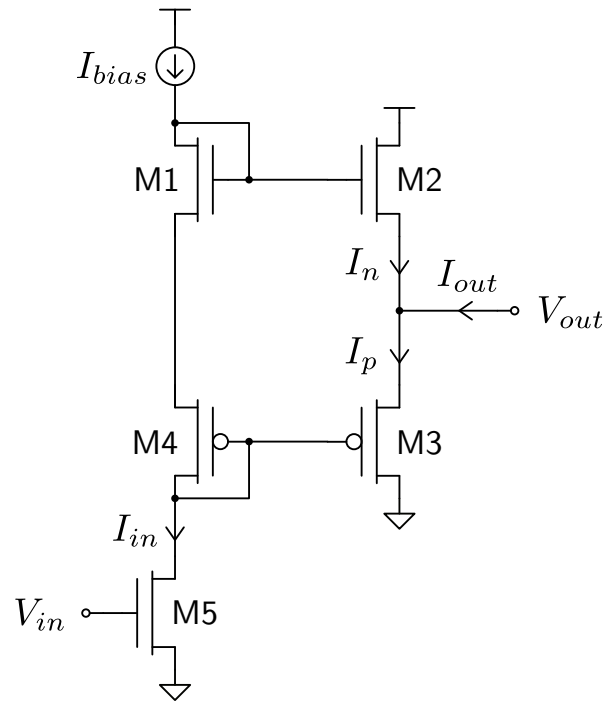


Class-AB Stage Examples

► Translinear loops:

weak inversion sat.
$$\frac{I_{bias}}{(W/L)_1} \frac{I_p}{(W/L)_3} = \frac{I_n}{(W/L)_2} \frac{I_{in}}{(W/L)_4}$$

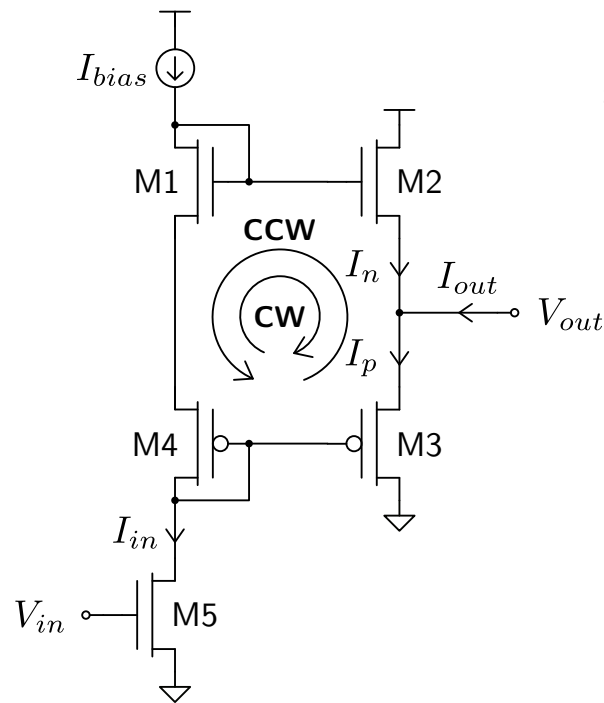strong inversion sat.
$$\sqrt{\frac{I_{bias}}{\beta_1}} + \sqrt{\frac{I_p}{\beta_3}} = \sqrt{\frac{I_n}{\beta_2}} + \sqrt{\frac{I_{in}}{\beta_4}}$$




Class-AB Stage Examples


► Translinear loops:

weak inversion sat.
$$\frac{I_{bias}}{(W/L)_1} \frac{I_p}{(W/L)_3} = \frac{I_n}{(W/L)_2} \frac{I_{in}}{(W/L)_4}$$

 strong inversion sat.
$$\sqrt{\frac{I_{bias}}{\beta_1}} + \sqrt{\frac{I_p}{\beta_3}} = \sqrt{\frac{I_n}{\beta_2}} + \sqrt{\frac{I_{in}}{\beta_4}}$$




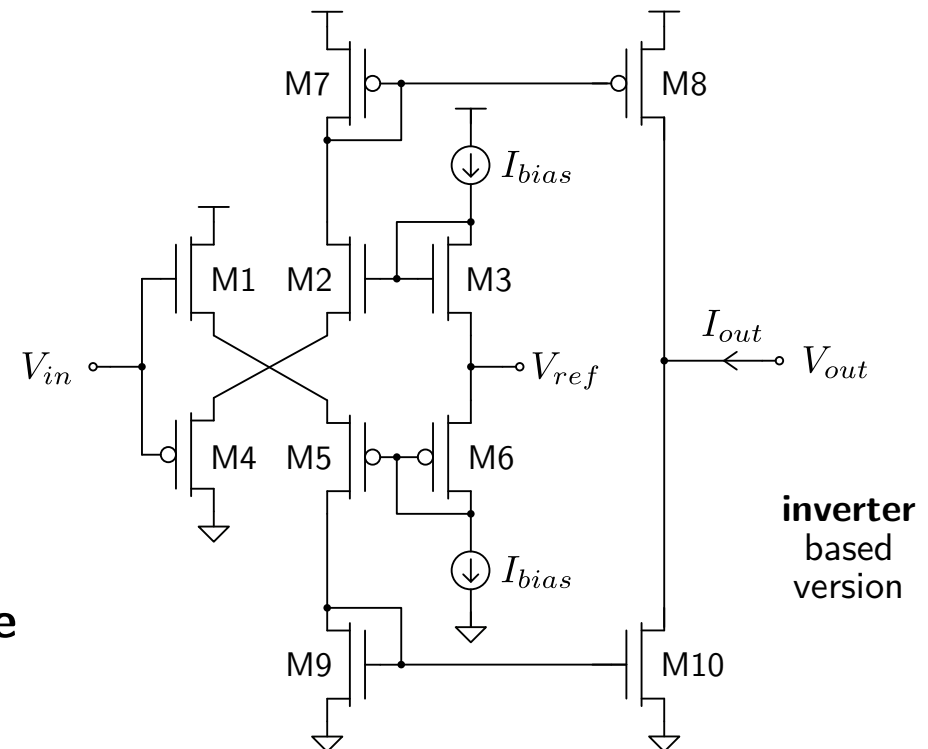▼ High supply voltage typically required...




Class-AB Stage Examples

- ▶ Class-A + **dynamic** biasing:

 


Class-AB Stage Examples

► Class-A + **dynamic** biasing:

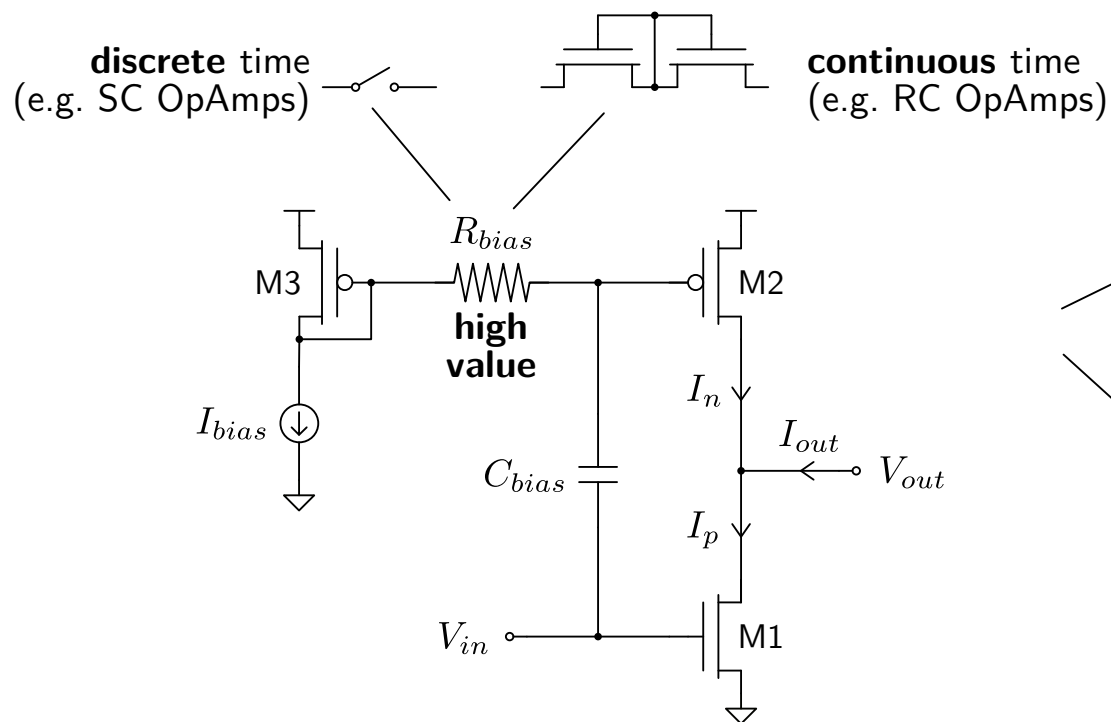


▼ **Area** overhead

▼ **Noise** excess from biasing


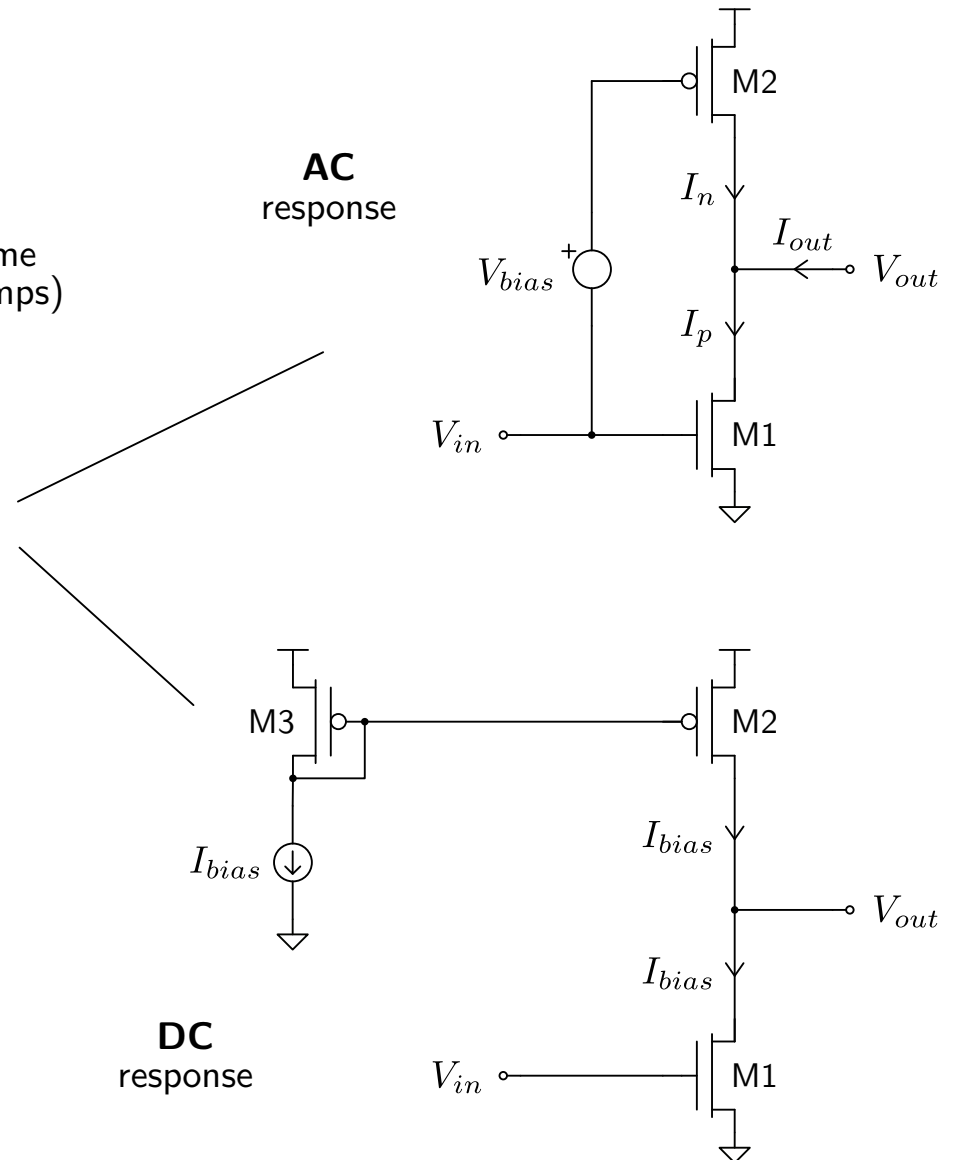


Class-AB Stage Examples

► Telescopic topologies:

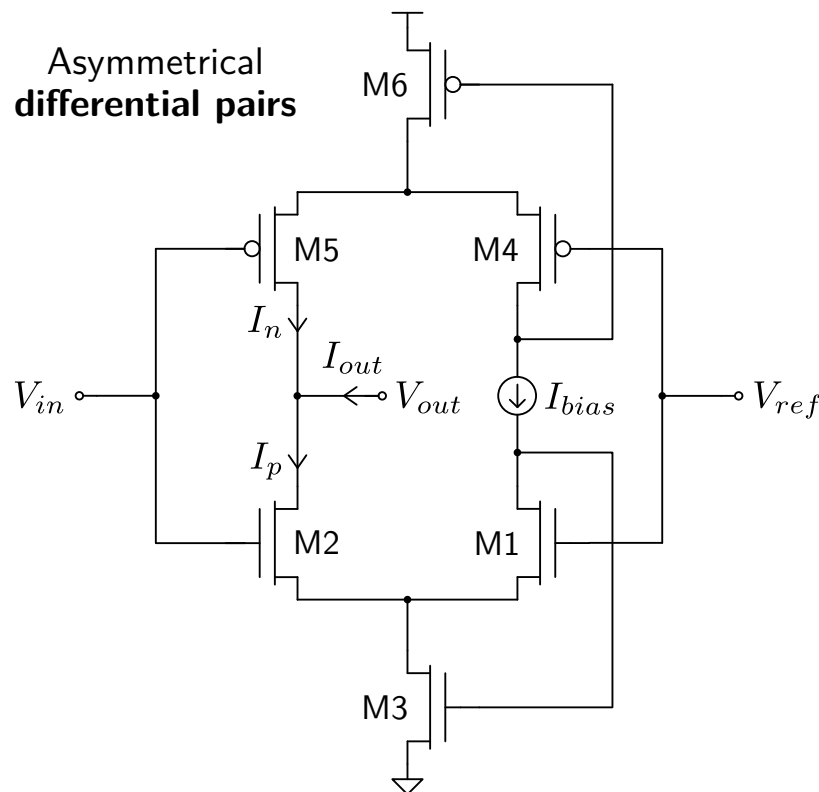


▼ Output range

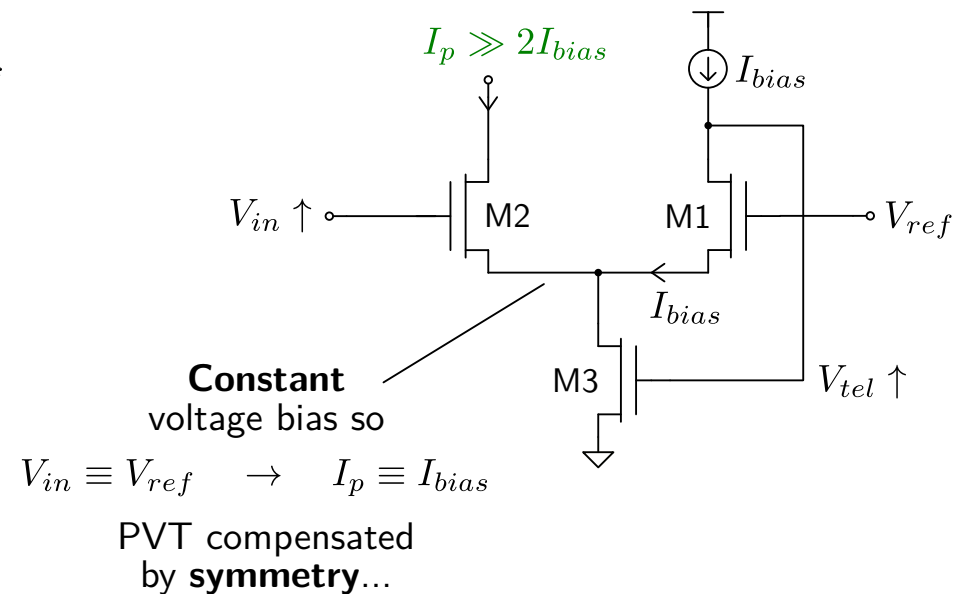 

Class-AB Stage Examples

► Telescopic topologies:

 

▼ Output range


Half-circuit analysis for strong inversion saturation

$$\begin{cases} \text{M1: } I_p = \frac{\beta_2}{2n} (V_{inp} - V_{TH} - nV_x)^2 \\ \text{M2: } I_{bias} = \frac{\beta_1}{2n} (V_{inn} - V_{TH} - nV_x)^2 \end{cases}$$

$$\sqrt{\frac{2nI_p}{\beta_2}} - \sqrt{\frac{2nI_{bias}}{\beta_1}} = V_{ind}$$

Full-circuit analysis for M1=M2
 
$$\begin{cases} \sqrt{I_p} = \sqrt{I_{bias}} + \sqrt{\frac{\beta}{2n}} V_{ind} \\ \sqrt{I_n} = \sqrt{I_{bias}} - \sqrt{\frac{\beta}{2n}} V_{ind} \end{cases}$$





- 1 Low-Voltage vs Low-Current
- 2 Subthreshold Operation
- 3 Class-AB Output Stages
- 4 Rail-to-Rail Topologies
- 5 Inverter-Based Pseudo-Differential Multi-Stages Architectures



Why Rail-to-Rail?

- ▶ Optimization of signal **full-scale** (V_{FS}) and probably dynamic range (DR)
- ▶ Compatibility with low **supply voltages** (e.g. battery-powered, energy scavenging)
- ▶ Required by **CMFB** in fully differential signal processing

  - ▲ Already available at OpAmp **output** when no cascode is used:



- ▼ Necessary at OpAmp **input**?

 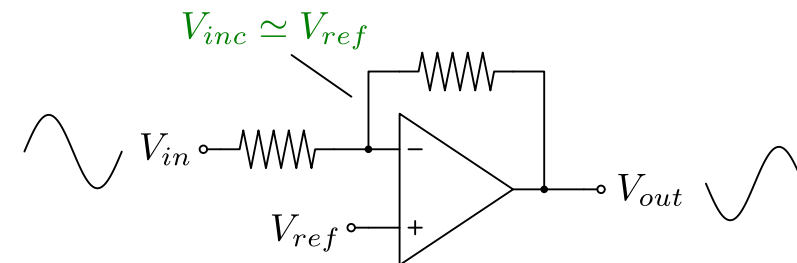

Required for certain **feedback** configurations!


OpAmp Input Transconductance

► Overall **gain** performance:

$$|G(DC)| = g_{in} r_{out}$$

input transconductance output resistance
 $v \rightarrow i$ $i \rightarrow v$

 ▼ **Input** transconductor for rail-to-rail?




OpAmp Input Transconductance

► Overall **gain** performance:


$$|G(DC)| = g_{in} r_{out}$$

input transconductance output resistance
 $v \rightarrow i$ $i \rightarrow v$

▲ **Complementary** differential pair

 

 ▼ **Input** transconductor for rail-to-rail?






OpAmp Input Transconductance

► Overall **gain** performance:


$$|G(DC)| = g_{in} r_{out}$$

input transconductance
 $v \rightarrow i$
output resistance
 $i \rightarrow v$

   ▼ **Non-constant** transconductance (gain):





▲ **Complementary** differential pair

 

► Specific OpAmp **biasing techniques** are required for rail-to-rail complementary differential pairs



3-Times Current Mirror

  - Complementary differential pair raw input **transconductance**:



3-Times Current Mirror

  - Complementary differential pair raw input **transconductance**:



- Equalization in **strong inversion**:

$$g_{mgn} + g_{mgp} \equiv \text{const}$$

$$\sqrt{2n\beta_n I_{biasn}} + \sqrt{2n\beta_p I_{biasp}} \equiv \text{const}$$



$$\text{e.g. } \frac{(W/L)_p}{(W/L)_n} \equiv \frac{\beta_{un}}{\beta_{up}} \sim 3$$

$$\sqrt{I_{biasn}} + \sqrt{I_{biasp}} \equiv \text{const}$$

$$\sqrt{I_{biasn}} + \sqrt{I_{biasp}} = \begin{cases} \sqrt{4I_{bias}} + \sqrt{0} = 2\sqrt{I_{bias}} & \text{NMOS} \\ \sqrt{I_{bias}} + \sqrt{I_{bias}} = 2\sqrt{I_{bias}} & \text{N+PMOS} \\ \sqrt{0} + \sqrt{4I_{bias}} = 2\sqrt{I_{bias}} & \text{PMOS} \end{cases}$$

3-Times Current Mirror



► Equalization in **strong inversion**:

  

$$\sqrt{I_{biasn}} + \sqrt{I_{biasp}} = \begin{cases} \sqrt{4I_{bias}} + \sqrt{0} = 2\sqrt{I_{bias}} & \text{NMOS} \\ \sqrt{I_{bias}} + \sqrt{I_{bias}} = 2\sqrt{I_{bias}} & \text{N+PMOS} \\ \sqrt{0} + \sqrt{4I_{bias}} = 2\sqrt{I_{bias}} & \text{PMOS} \end{cases}$$

3-Times Current Mirror

► Equalization in **strong inversion**:

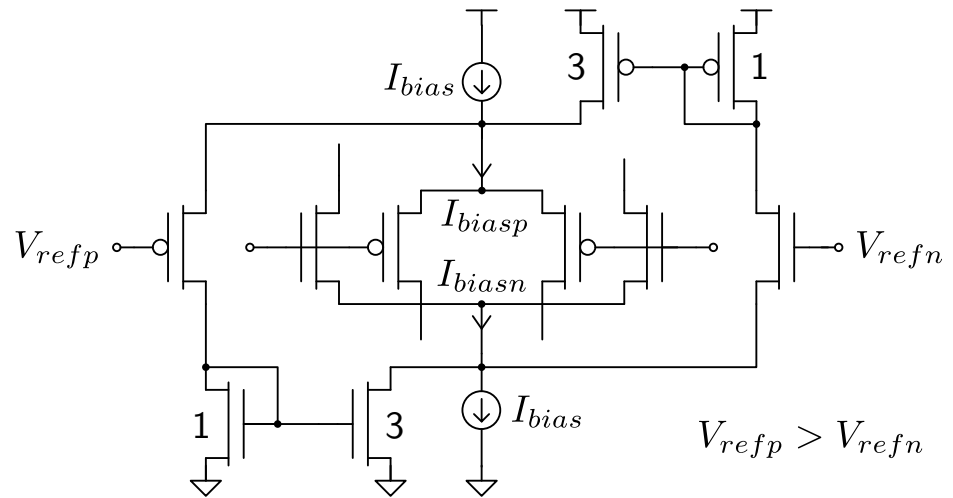 


▲ **Compact** bias control

▼ **Non-exact** solution

$$\sqrt{I_{biasn}} + \sqrt{I_{biasp}} = \begin{cases} \sqrt{4I_{bias}} + \sqrt{0} = 2\sqrt{I_{bias}} & \text{NMOS} \\ \sqrt{I_{bias}} + \sqrt{I_{bias}} = 2\sqrt{I_{bias}} & \text{N+PMOS} \\ \sqrt{0} + \sqrt{4I_{bias}} = 2\sqrt{I_{bias}} & \text{PMOS} \end{cases}$$

Current Switch


► Equalization in **weak inversion**:

 

$$g_{mgn} + g_{mgp} \equiv \text{const}$$

$$\frac{I_{biasn}}{nU_t} + \frac{I_{biasp}}{nU_t} \equiv \text{const}$$
 
$$I_{biasn} + I_{biasp} \equiv \text{const}$$




▲ **Compact** bias control

▼ Transconductance equalization **sensitivity** to reference voltage

- 1 Low-Voltage vs Low-Current
- 2 Subthreshold Operation
- 3 Class-AB Output Stages
- 4 Rail-to-Rail Topologies
- 5 Inverter-Based Pseudo-Differential Multi-Stages Architectures

Cascade vs Cascode

 - ▶ Low **supply voltage** by avoiding cascoding circuit structures




$$|G(DC)| \propto g_{mg1} \left(\frac{1}{g_{md1}} \frac{g_{mg2}}{g_{md2}} \right)$$

$$GBW = \frac{g_{mg1}}{2\pi C_{load}}$$


Cascade vs Cascode

 - ▶ Low **supply voltage** by avoiding cascoding circuit structures
- ▲ OpAmp **gain** drop may be compensated by **multistage** topologies
- ▼ Increase in **power** consumption
- ▼ Multipole frequency **compensation** can be tricky!



$$|G(DC)| \propto g_{mg1} \left(\frac{1}{g_{md1}} \frac{g_{mg2}}{g_{md2}} \right)$$

$$GBW = \frac{g_{mg1}}{2\pi C_{load}}$$

 


$$|G(DC)| \propto \left(\frac{g_{mg1}}{g_{md1}} \right) \left(\frac{g_{mg2}}{g_{md2}} \right)$$

$$GBW = \frac{g_{mg1}}{2\pi C_{comp}} < \frac{g_{mg2}}{2\pi C_{load}}$$

3-Stage Nested Miller OTA

 - Inverter as **transconductance** basic building block





$$GBW = \frac{g_{m1}}{2\pi C_{comp1}} \quad f_{p2} = \frac{g_{m2}}{2\pi C_{comp2}} \quad f_{p3} = \frac{g_{m3}}{2\pi C_{load}}$$

3-Stage Nested Miller OTA

► Inverter as **transconductance**
basic building block

▲ **Phase margin**
save design

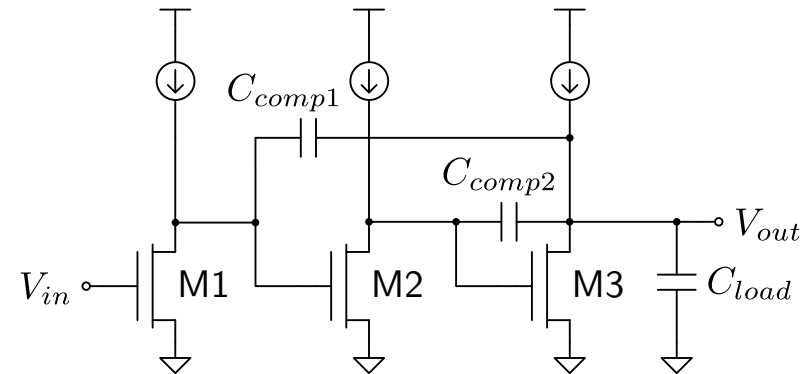 

$$GBW = \frac{g_{m1}}{2\pi C_{comp1}} \quad f_{p2} = \frac{g_{m2}}{2\pi C_{comp2}} \quad f_{p3} = \frac{g_{m3}}{2\pi C_{load}}$$

$$\phi_m = 90^\circ - \arctan\left(\frac{GBW}{f_{p2}}\right) - \arctan\left(\frac{GBW}{f_{p3}}\right)$$


▼ Increase in **power**
consumption

▼ **Bandwidth** reduction


Nested Gm-C Compensation

► Combination of nested **loops** involving:

 - **Positive/negative** transconductors
- **Miller** compensation capacitors



► **Pseudo-differential** structures:

 

e.g. **3-stage OTA**

