

6. OpAmp Application Examples

Francesc Serra Graells

francesc.serra.graells@uab.cat

Departament de Microelectrònica i Sistemes Electrònics
Universitat Autònoma de Barcelona

paco.serra@imb-cnm.csic.es


Integrated Circuits and Systems
IMB-CNM(CSIC)

- 1 Pre-Amplification
- 2 MRC-Amplifiers for AGC
- 3 Continuous-Time Gm-C Filters
- 4 Switched-Capacitor Filters

- 1 Pre-Amplification
- 2 MRC-Amplifiers for AGC
- 3 Continuous-Time Gm-C Filters
- 4 Switched-Capacitor Filters

Pre-Amplification Stages

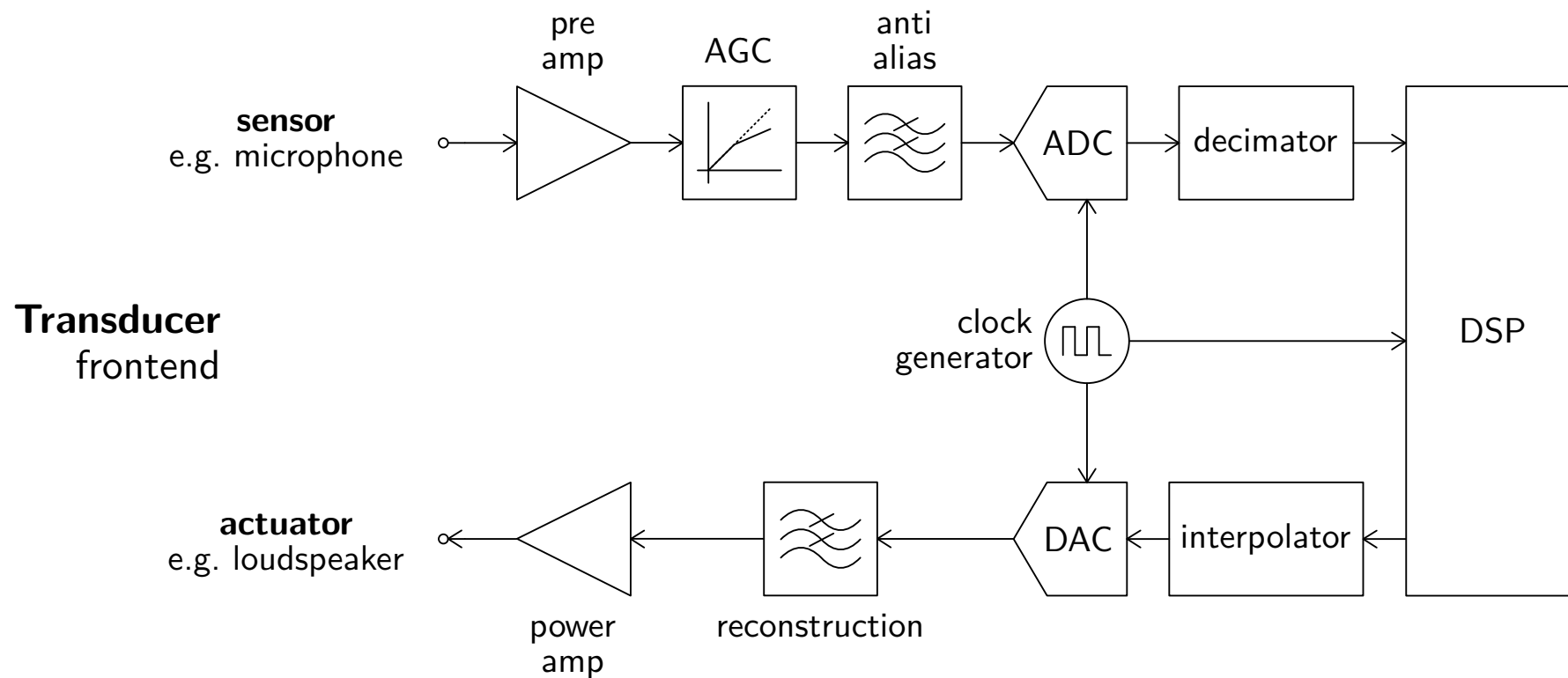
- General usage in analog **signal processing** systems:



Pre-Amplification Stages

- General usage in analog **signal processing** systems:

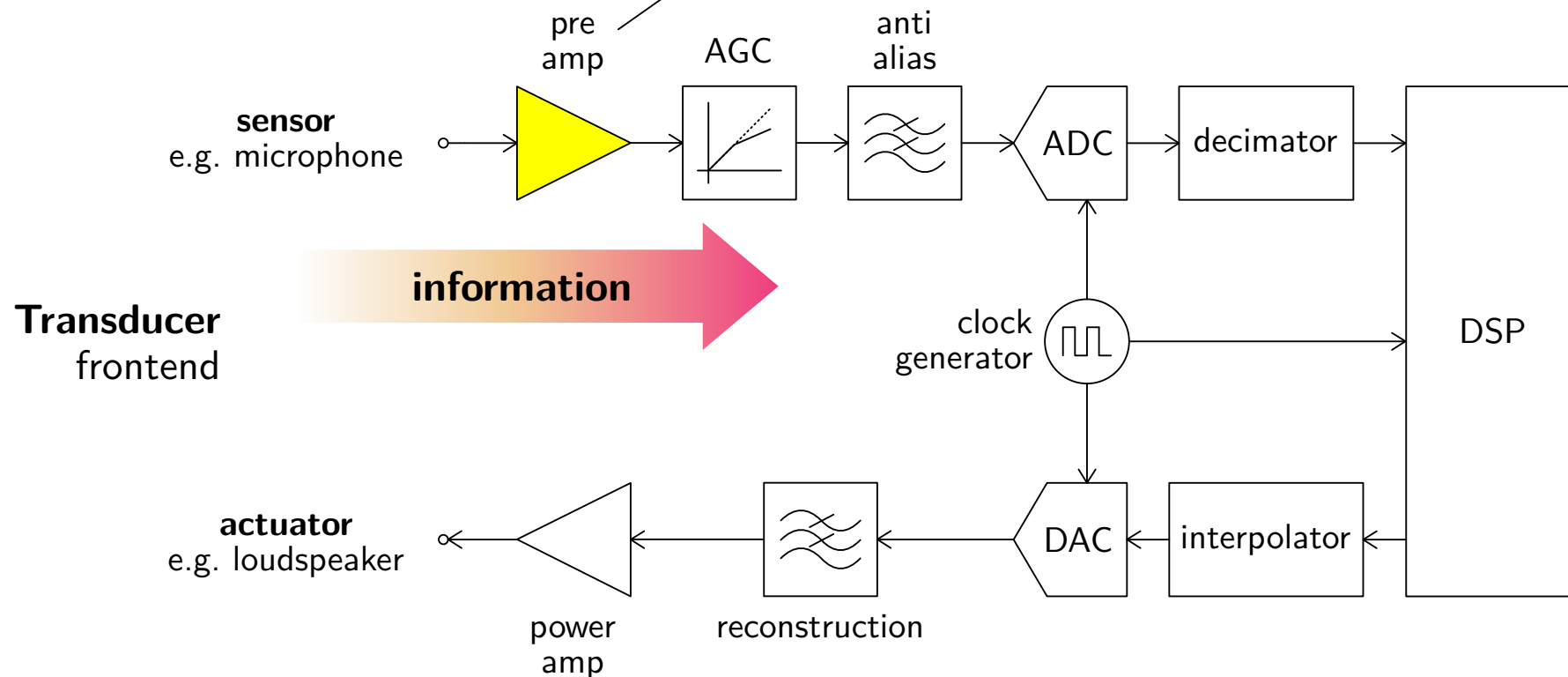to save source signal integrity (**SNDR**)
against circuit non-idealities (e.g. noise, interference)




Instrumentation Amplifiers

- ▶ OpAmp requirements for **sensor** read-out frontends:

safety rules
(e.g. no net
charge
interchange!)

**strong
common
interferer**

**weak
differential
signal**

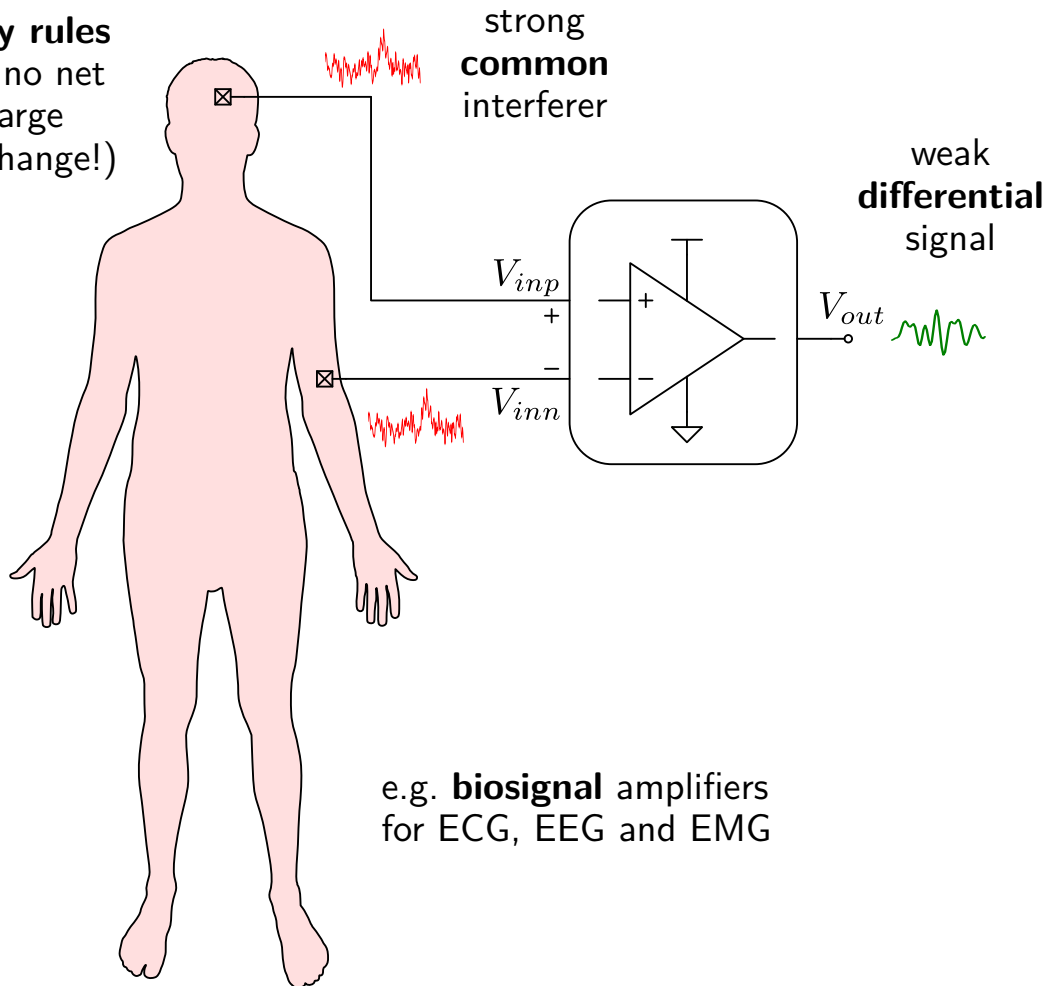


e.g. **biosignal** amplifiers
for ECG, EEG and EMG

Instrumentation Amplifiers

- OpAmp requirements for **sensor** read-out frontends:

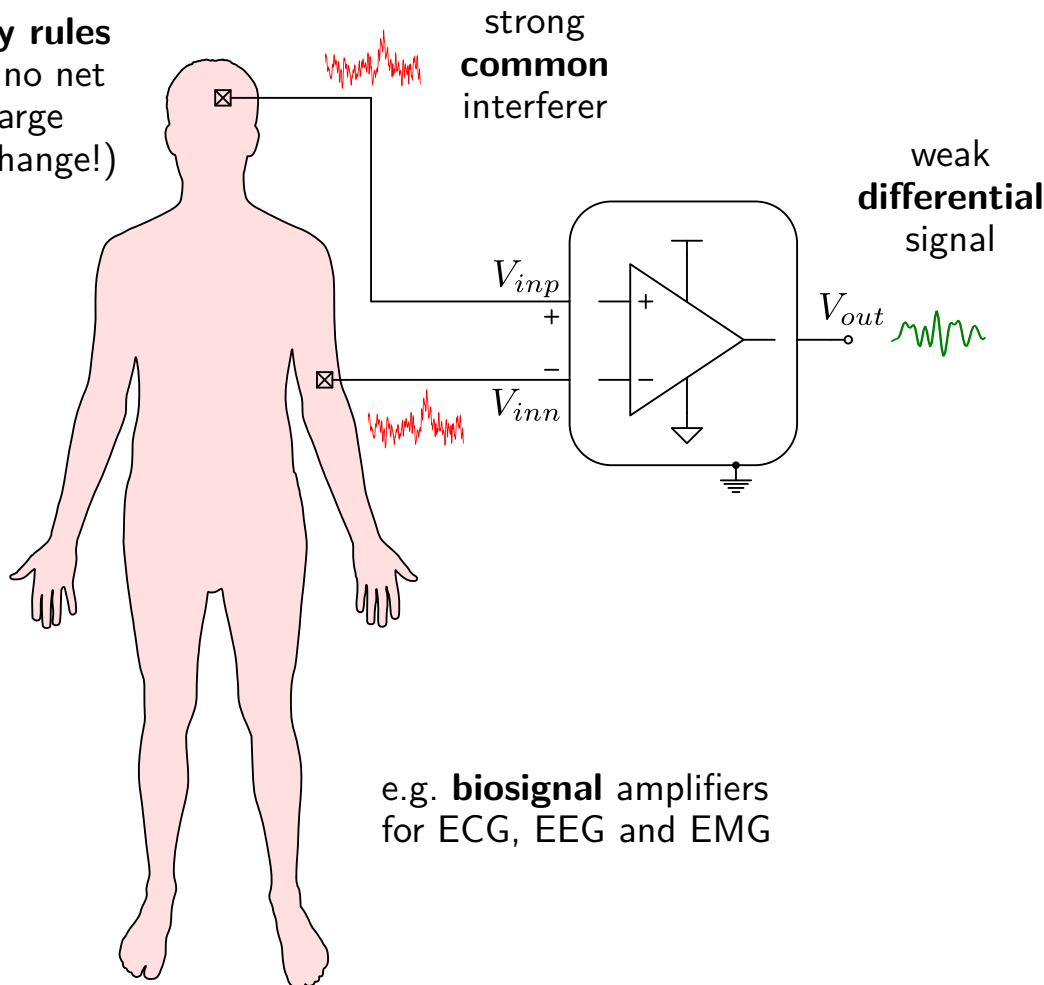safety rules
(e.g. no net charge interchange!)




- **Shielding** and **floating** supply for external interference rejection
- Infinite DC input **impedance**
- Low equivalent input **noise**
 - thermal $I_{bias} \uparrow$
 - flicker $WL \uparrow$
- Very high **CMRR**
 - $V_{ind} \sim \mu V$
 - $V_{inc} \sim V$
120dB!
- Reduced **bandwidth** (typ. kHz-range)
- Moderate output **full scale**



- ▼ **Specific** OpAmp circuits and feedback topologies

Classic Differential Preamplifiers

► 3-OpAmp topology:

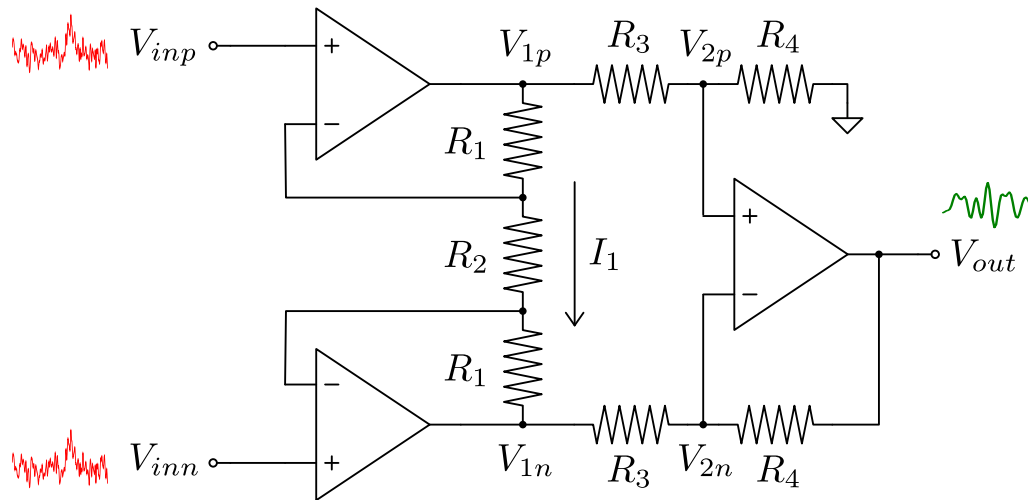

$$G_d \doteq \frac{V_{out}}{V_{inp} - V_{inn}} = \left(1 + \frac{2R_1}{R_2}\right) \frac{R_4}{R_3}$$

first stage: $I_1 = \frac{V_{inp} - V_{inn}}{R_2}$

$$\begin{cases} V_{1p} = V_{inp} + R_1 I_1 = \left(1 + \frac{R_1}{R_2}\right) V_{inp} - \frac{R_1}{R_2} V_{inn} \\ V_{1n} = V_{inn} - R_1 I_1 = \left(1 + \frac{R_1}{R_2}\right) V_{inn} - \frac{R_1}{R_2} V_{inp} \end{cases}$$

$$V_{1p} - V_{1n} \equiv \left(1 + \frac{2R_1}{R_2}\right) (V_{inp} - V_{inn})$$


second stage: $V_{2p} \simeq V_{2n}$

$$\frac{R_4}{R_3 + R_4} V_{1p} \simeq \frac{1}{R_3 + R_4} (R_4 V_{1n} + R_3 V_{out})$$

$$V_{out} \simeq \frac{R_4}{R_3} (V_{1p} - V_{1n})$$


Classic Differential Preamplifiers

► 3-OpAmp topology:

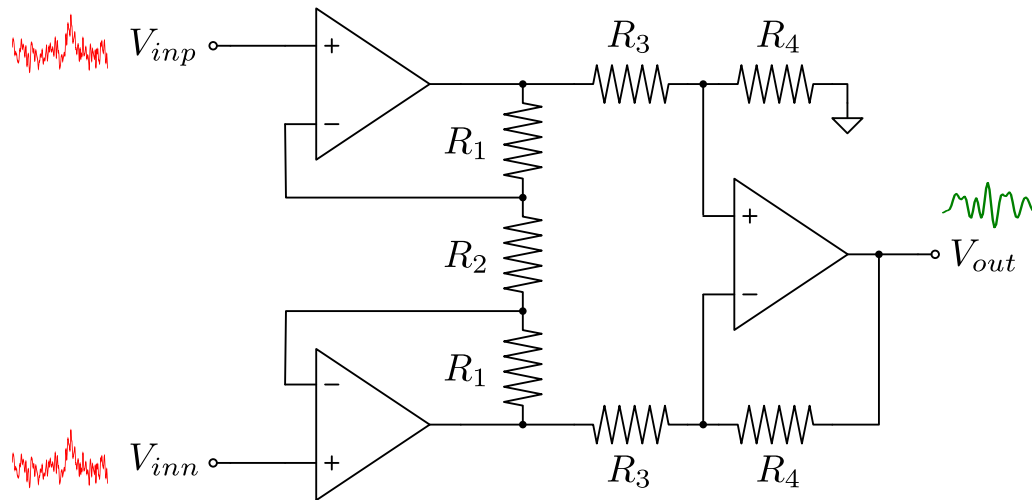

$$G_d \doteq \frac{V_{out}}{V_{inp} - V_{inn}} = \left(1 + \frac{2R_1}{R_2}\right) \frac{R_4}{R_3}$$


► 2-OpAmp circuit:

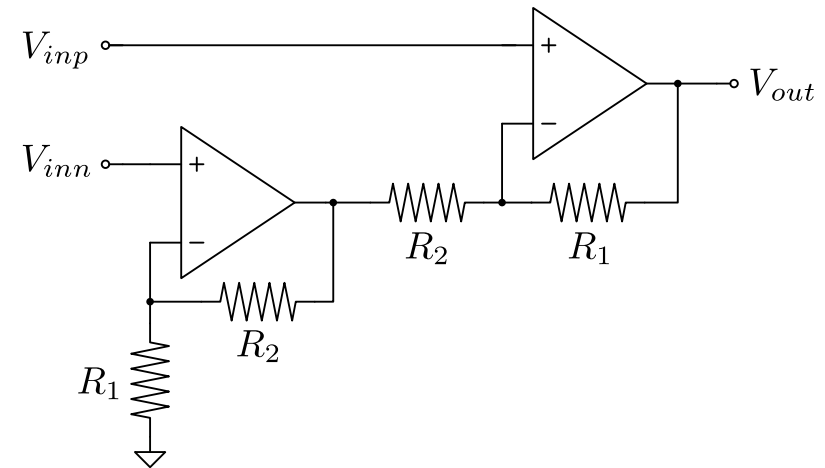

$$G_d = \left(1 + \frac{R_1}{R_2}\right)$$

Classic Differential Preamplifiers


► 3-OpAmp topology:

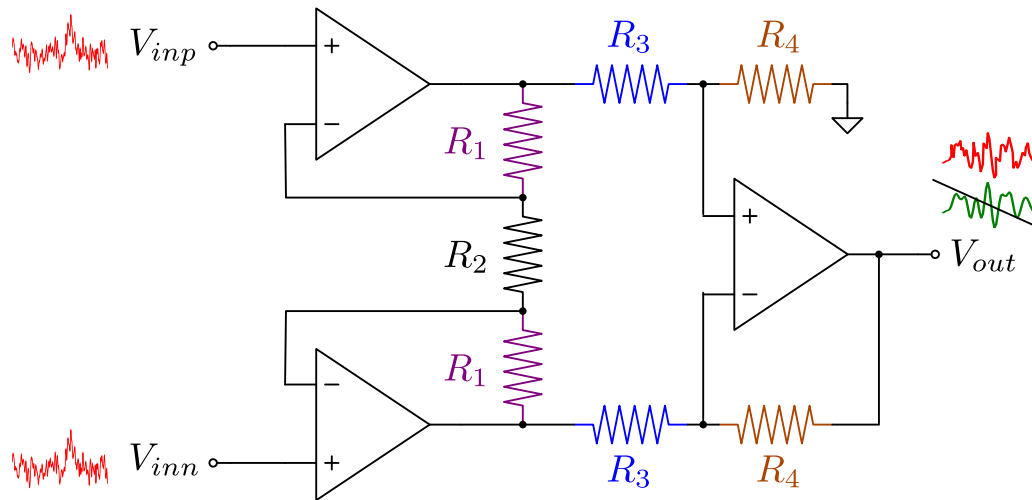

$$G_d \doteq \frac{V_{out}}{V_{inp} - V_{inn}} = \left(1 + \frac{2R_1}{R_2}\right) \frac{R_4}{R_3}$$

▼ **CMRR** losses due to technology **mismatching**!

► 2-OpAmp circuit:

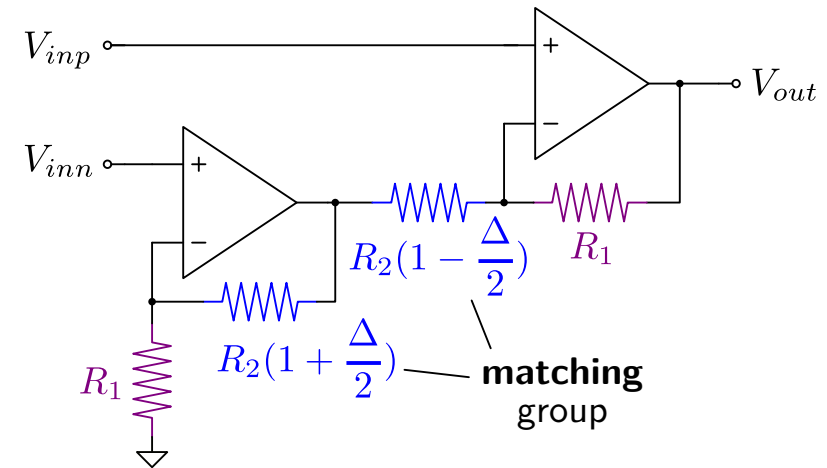

$$G_d = \left(1 + \frac{R_1}{R_2}\right)$$


$$V_{out} = \left[1 + \frac{R_1}{R_2(1 - \frac{\Delta}{2})}\right] V_{inp} - \left[1 + \frac{R_2(1 + \frac{\Delta}{2})}{R_1}\right] \frac{R_1}{R_2(1 - \frac{\Delta}{2})} V_{inn}$$

$$V_{out} = G_d V_{ind} + G_c V_{inc}$$

$$V_{ind} = \frac{V_{inp} - V_{inn}}{2} \quad V_{inc} = \frac{V_{inp} + V_{inn}}{2}$$

Specific OpAmps for Preamplifiers

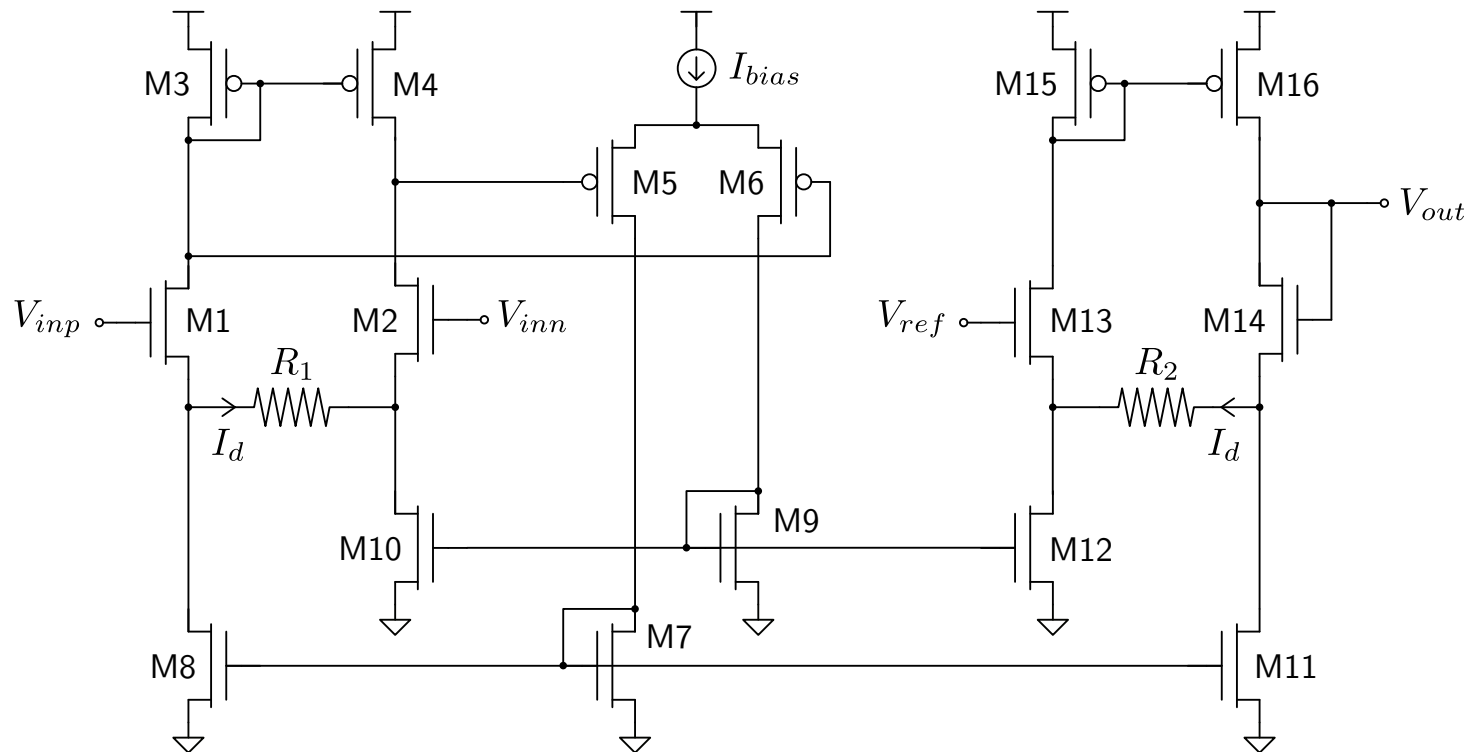
- Non-differential **floating** gain elements:



$$V_{out} = V_{ref} + G_d(V_{inp} - V_{inn}) \quad G_d = \frac{R_2}{R_1}$$

Specific OpAmps for Preamplifiers

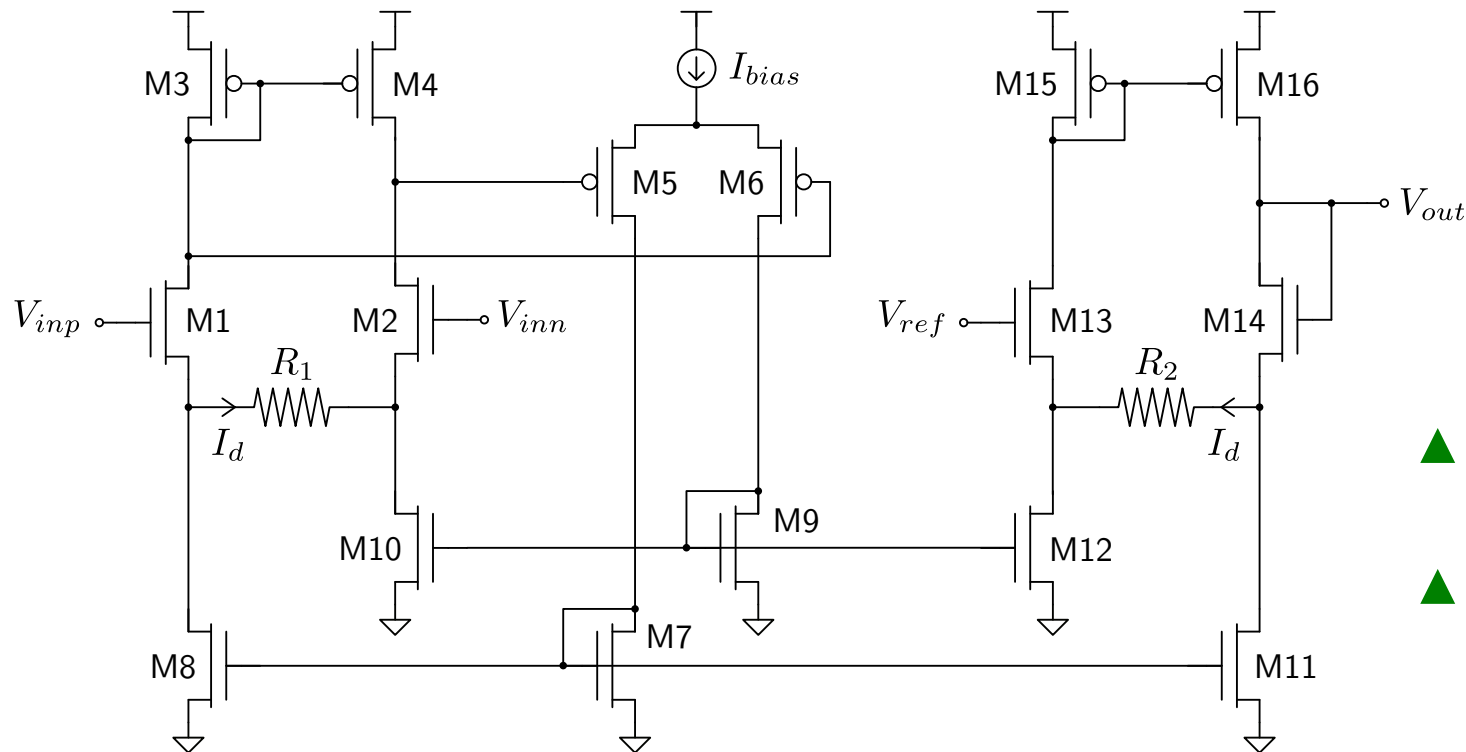- Non-differential **floating** gain elements:



$$V_{out} = V_{ref} + G_d(V_{inp} - V_{inn}) \quad G_d = \frac{R_2}{R_1}$$


- ▲ Null contributions of resistors to **CMRR**
- ▲ Input stage technology mismatching seen as static **offset**
- ▼ Input stage **noise**
- ▼ Output **full-scale**

- 1 Pre-Amplification
- 2 MRC-Amplifiers for AGC
- 3 Continuous-Time Gm-C Filters
- 4 Switched-Capacitor Filters

Automatic Gain Control

Also known as programmable/variable gain amplifier (**PGA/VGA**)

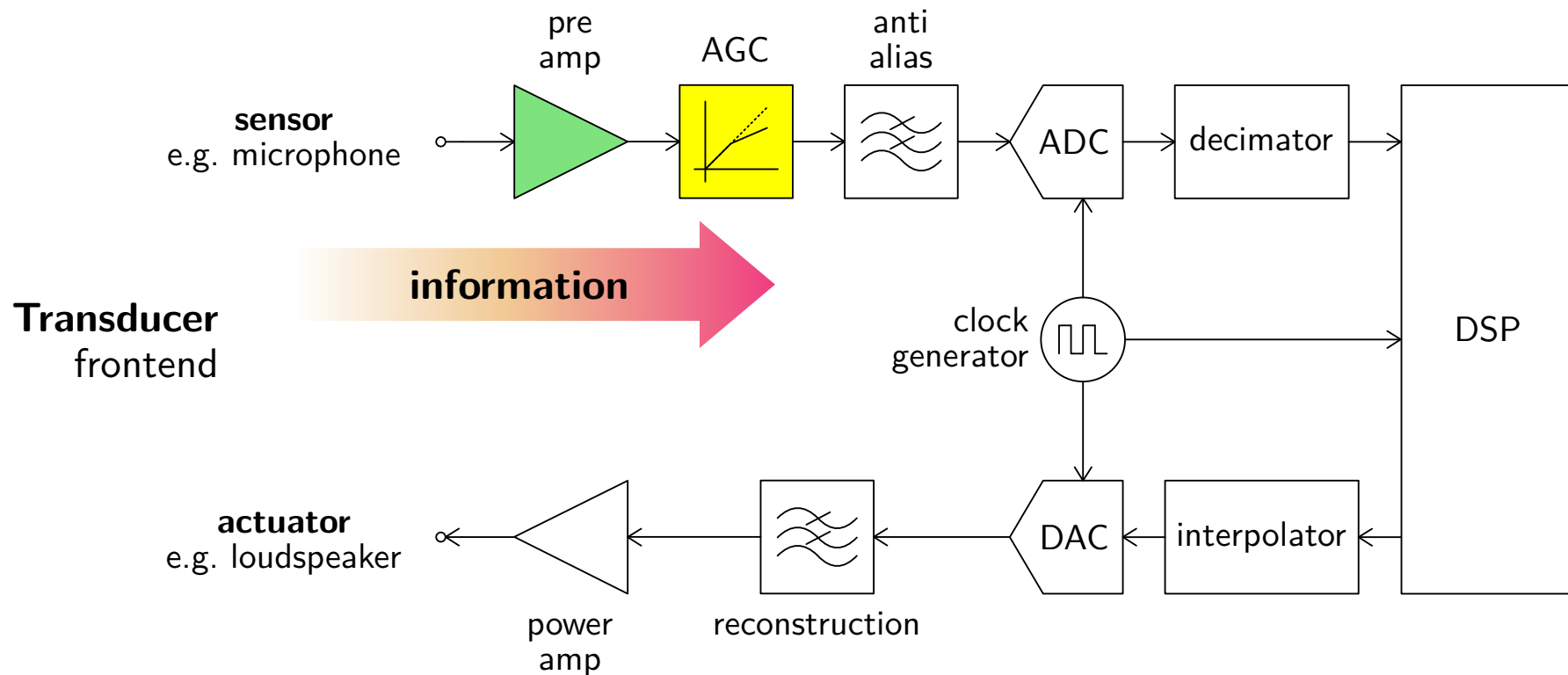
- ▶ General usage in analog **signal processing** systems:



Automatic Gain Control



Also known as programmable/variable gain amplifier (**PGA/VGA**)

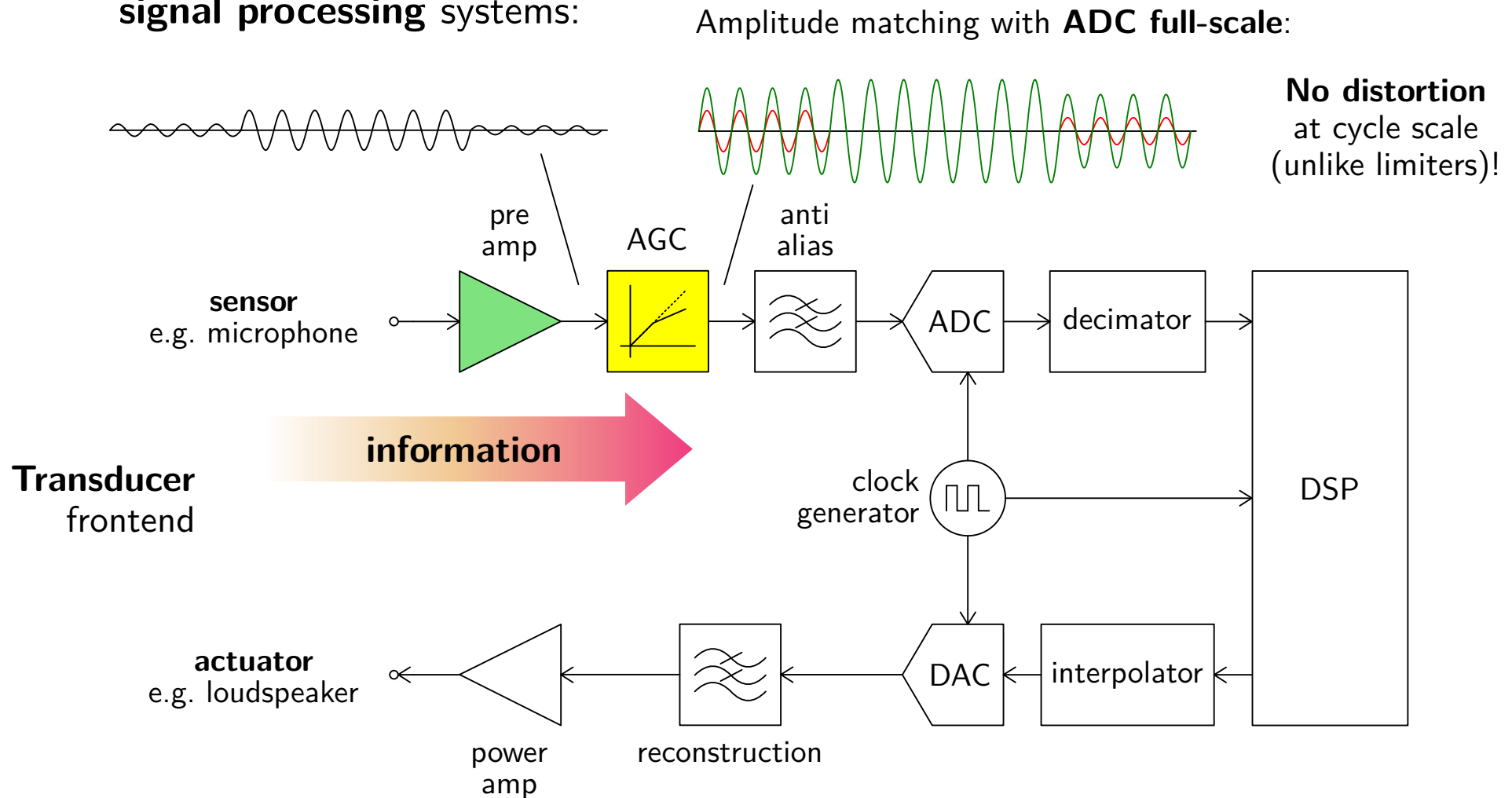- General usage in analog **signal processing** systems:





Programmable Gain

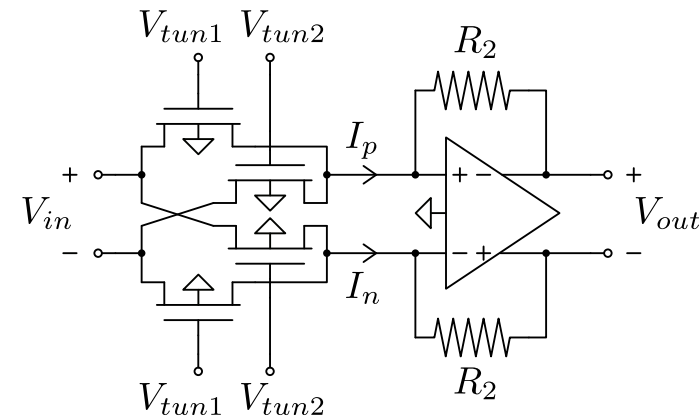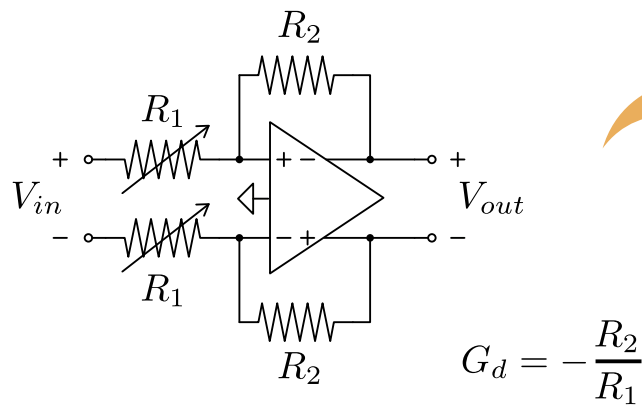- Based on MOS resistive circuits (**MRC**):



Programmable Gain

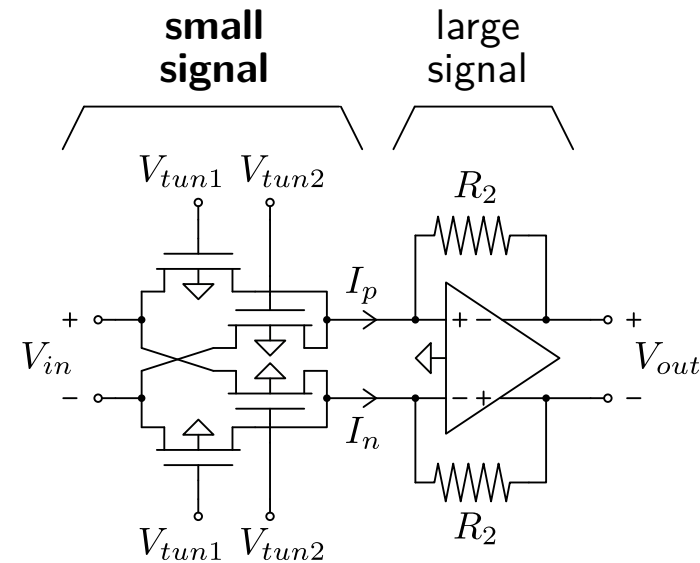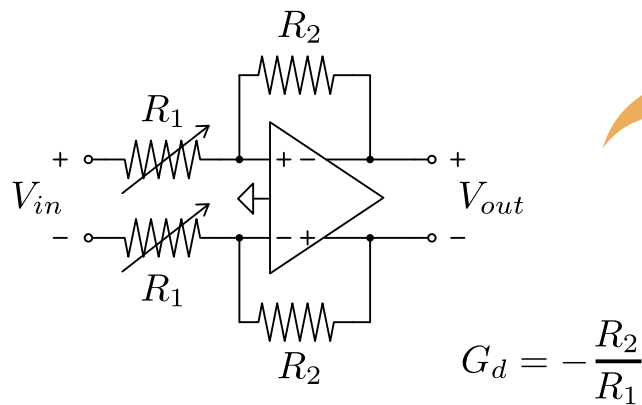- Based on MOS resistive circuits (**MRC**):





matched devices operating in strong inversion **conduction** (non-saturation):

$$I_p = \beta \left[V_{tun1} - V_{TH} - \frac{n}{2} \left(\frac{V_{in}}{2} \right) \right] \left(\frac{V_{in}}{2} \right) + \beta \left[V_{tun2} - V_{TH} - \frac{n}{2} \left(-\frac{V_{in}}{2} \right) \right] \left(-\frac{V_{in}}{2} \right)$$

$$\left. \begin{aligned} I_p &= \beta \left(V_{tun1} - V_{tun2} - n \frac{V_{in}}{2} \right) \frac{V_{in}}{2} \\ I_n &= \beta \left(V_{tun2} - V_{tun1} - n \frac{V_{in}}{2} \right) \frac{V_{in}}{2} \end{aligned} \right\} \quad I_d = I_p - I_n = \beta (V_{tun1} - V_{tun2}) V_{in} \quad R_1 \equiv \frac{1}{2\beta (V_{tun1} - V_{tun2})}$$

Programmable Gain

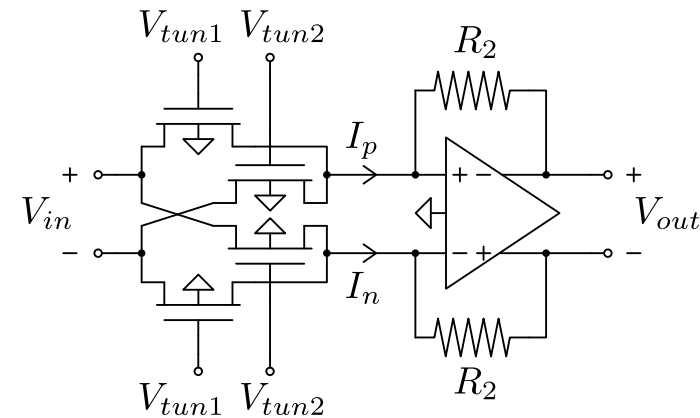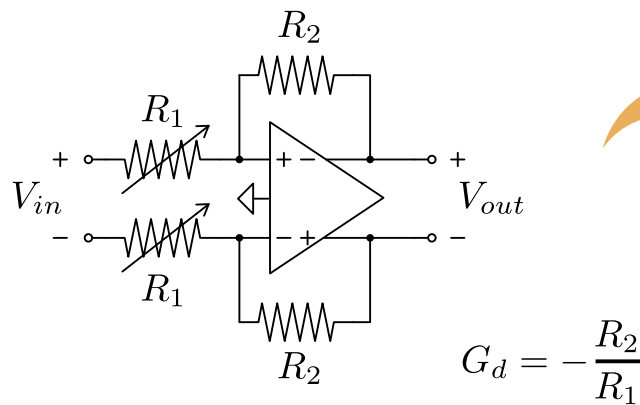- Based on MOS resistive circuits (**MRC**):



- ▲ **Compact** area
- ▲ **Electronically tunable** gain
- ▼ Technology **sensitivity**
- ▼ MOSFET flicker **noise**
- ▼ Distortion due to larger device **mismatching**


$$R_1 \equiv \frac{1}{2\beta(V_{tun1} - V_{tun2})}$$

$$G_d \propto (V_{tun1} - V_{tun2})$$

- 1 Pre-Amplification
- 2 MRC-Amplifiers for AGC
- 3 Continuous-Time Gm-C Filters
- 4 Switched-Capacitor Filters

Continuous-Time Filters

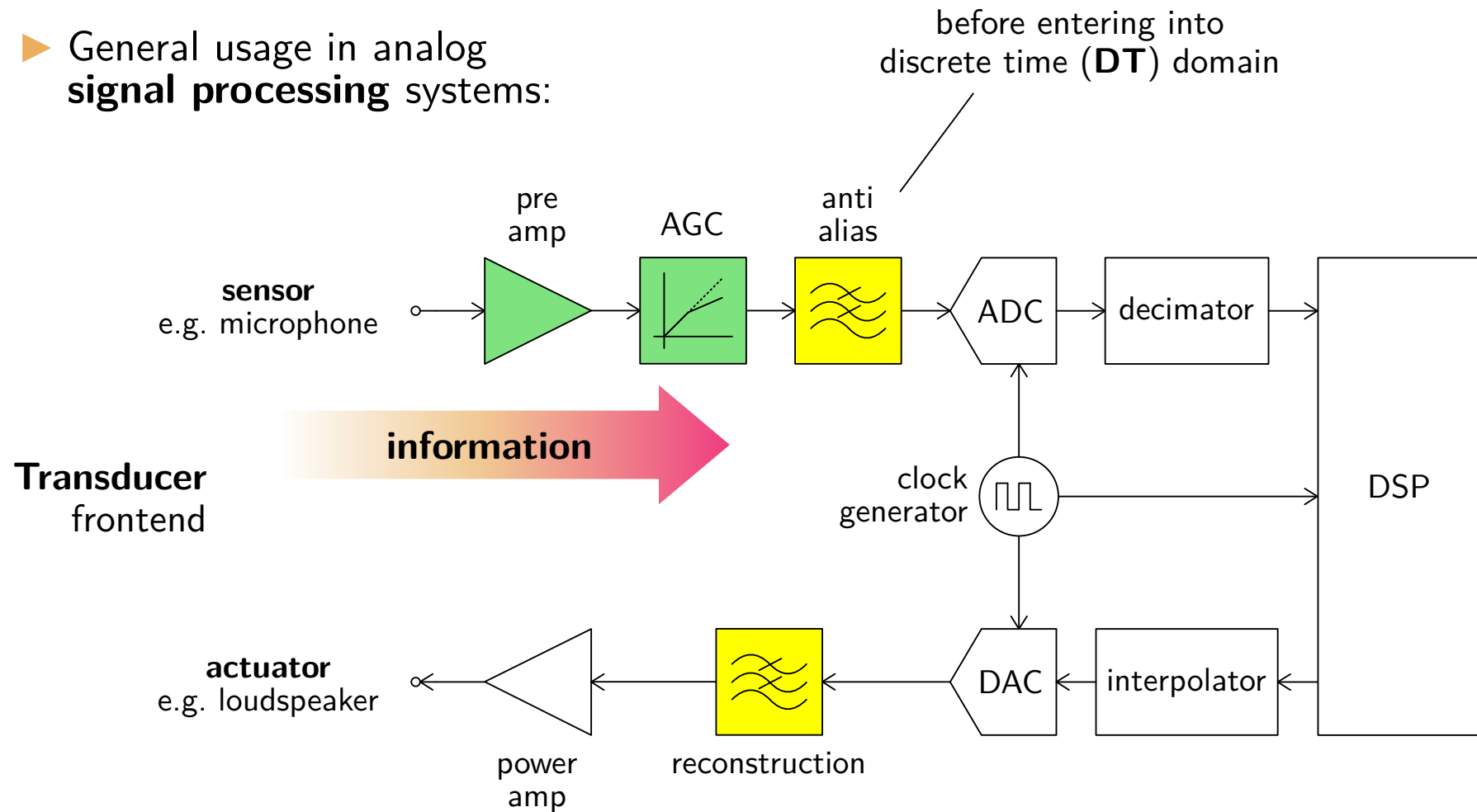
- General usage in analog **signal processing** systems:



Also common in **high-frequency** filters...


Gm-C Integrator

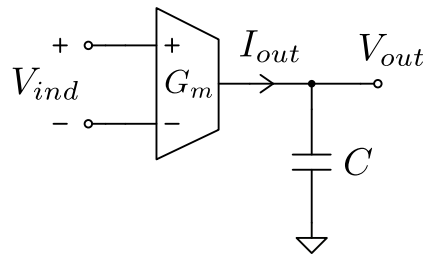- Based on **wide-range** input MOS transconductors:




$$H(s) \doteq \frac{V_{out}}{V_{ind}} = \frac{G_m}{C} \frac{1}{s}$$

not OTA!
(finite G_m)

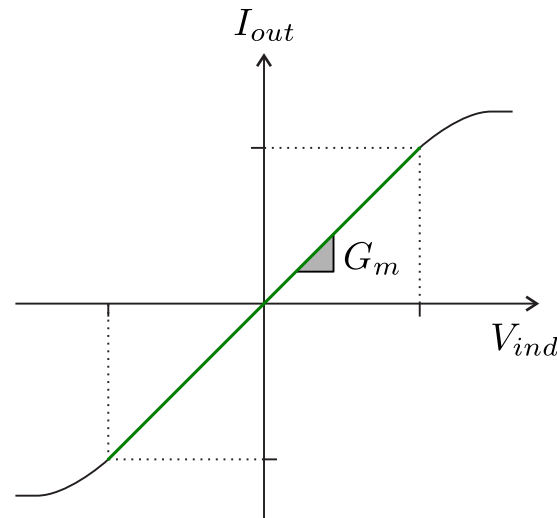


Gm-C Integrator

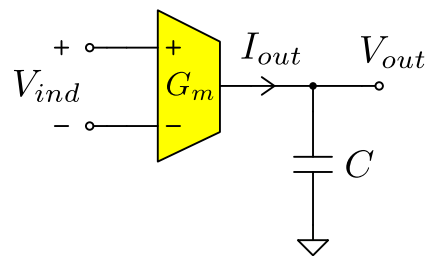- **Cross-coupled**
CMOS circuit realization:



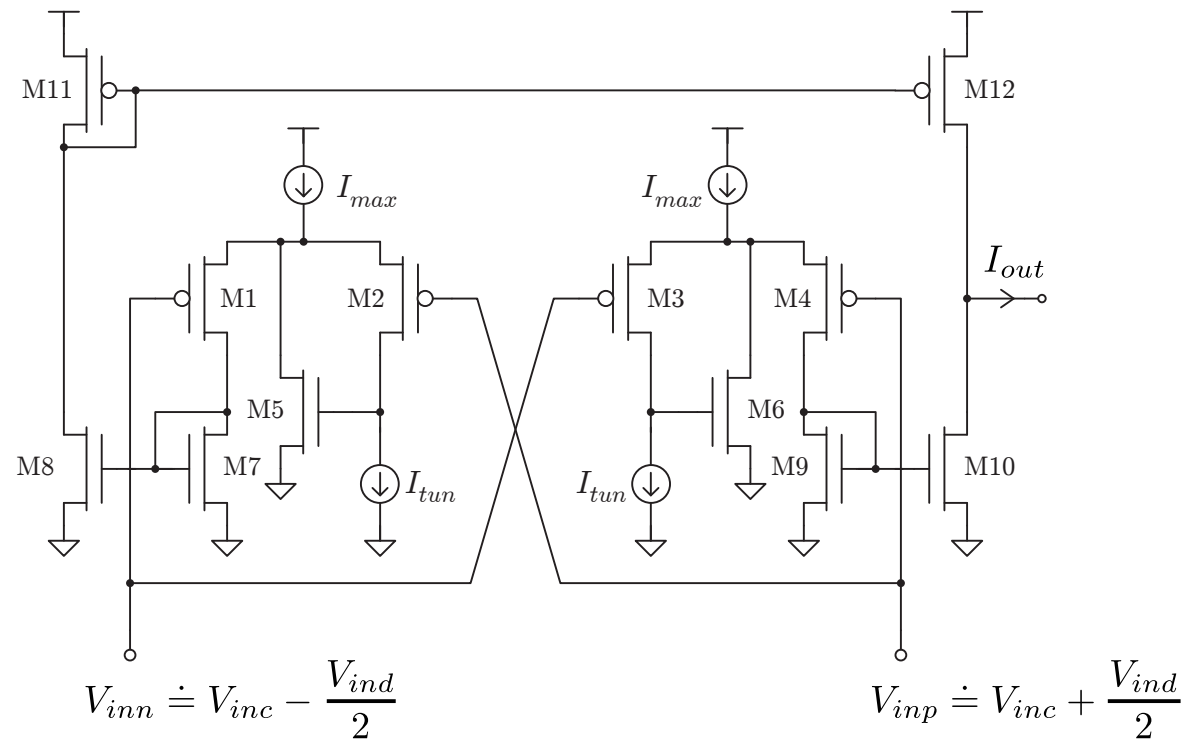matched devices operating in **strong inversion** saturation:



$$G_m \doteq \frac{I_{out}}{V_{ind}} = 2\sqrt{\frac{2\beta I_{tun}}{n}}$$


$$I_{D1} = \frac{\beta}{2n} \left[\left(V_{inc} - \frac{V_{ind}}{2} \right) - V_{TH} - \left(V_{inc} + \frac{V_{ind}}{2} - V_{TH} - \sqrt{\frac{2nI_{tun}}{\beta}} \right) \right]^2$$

$$I_{D4} = \frac{\beta}{2n} \left[\left(V_{inc} + \frac{V_{ind}}{2} \right) - V_{TH} - \left(V_{inc} - \frac{V_{ind}}{2} - V_{TH} - \sqrt{\frac{2nI_{tun}}{\beta}} \right) \right]^2$$

$$I_{out} = I_{D4} - I_{D1} = \frac{\beta}{2n} \left[\left(V_{ind} + \sqrt{\frac{2nI_{tun}}{\beta}} \right)^2 - \left(-V_{ind} + \sqrt{\frac{2nI_{tun}}{\beta}} \right)^2 \right]$$


Gm-C Integrator

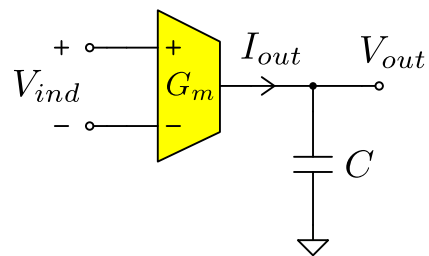- **Cross-coupled**
CMOS circuit realization:



$$G_m \doteq \frac{I_{out}}{V_{ind}} = 2\sqrt{\frac{2\beta I_{tun}}{n}}$$

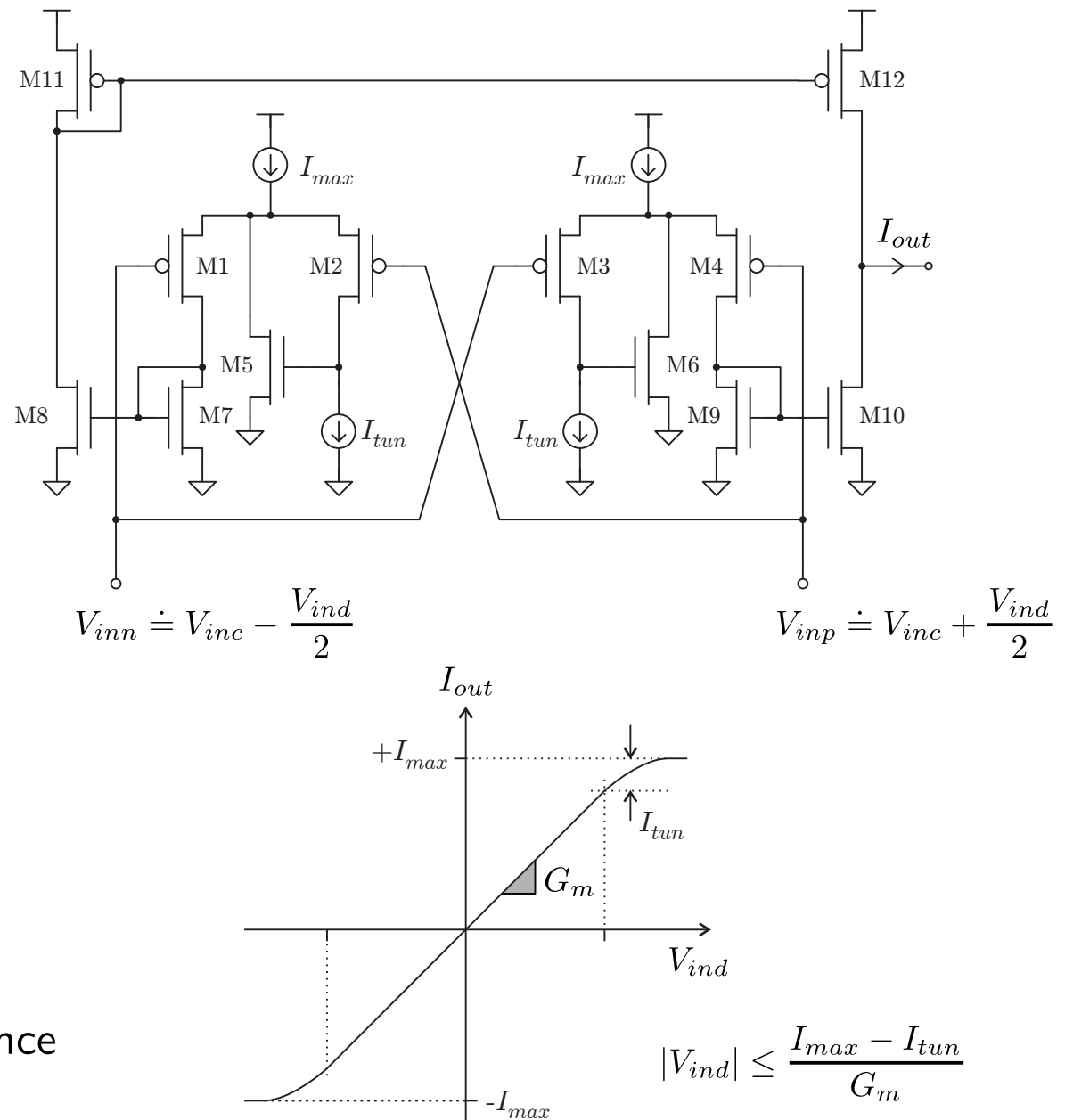- ▲ **Linear** differential transconductance
- ▲ **Built-in limiter**
- ▼ **Technology** dependence




- 1 Pre-Amplification
- 2 MRC-Amplifiers for AGC
- 3 Continuous-Time Gm-C Filters
- 4 Switched-Capacitor Filters

Switched-Capacitor Filters


- General usage in analog **signal processing** systems:

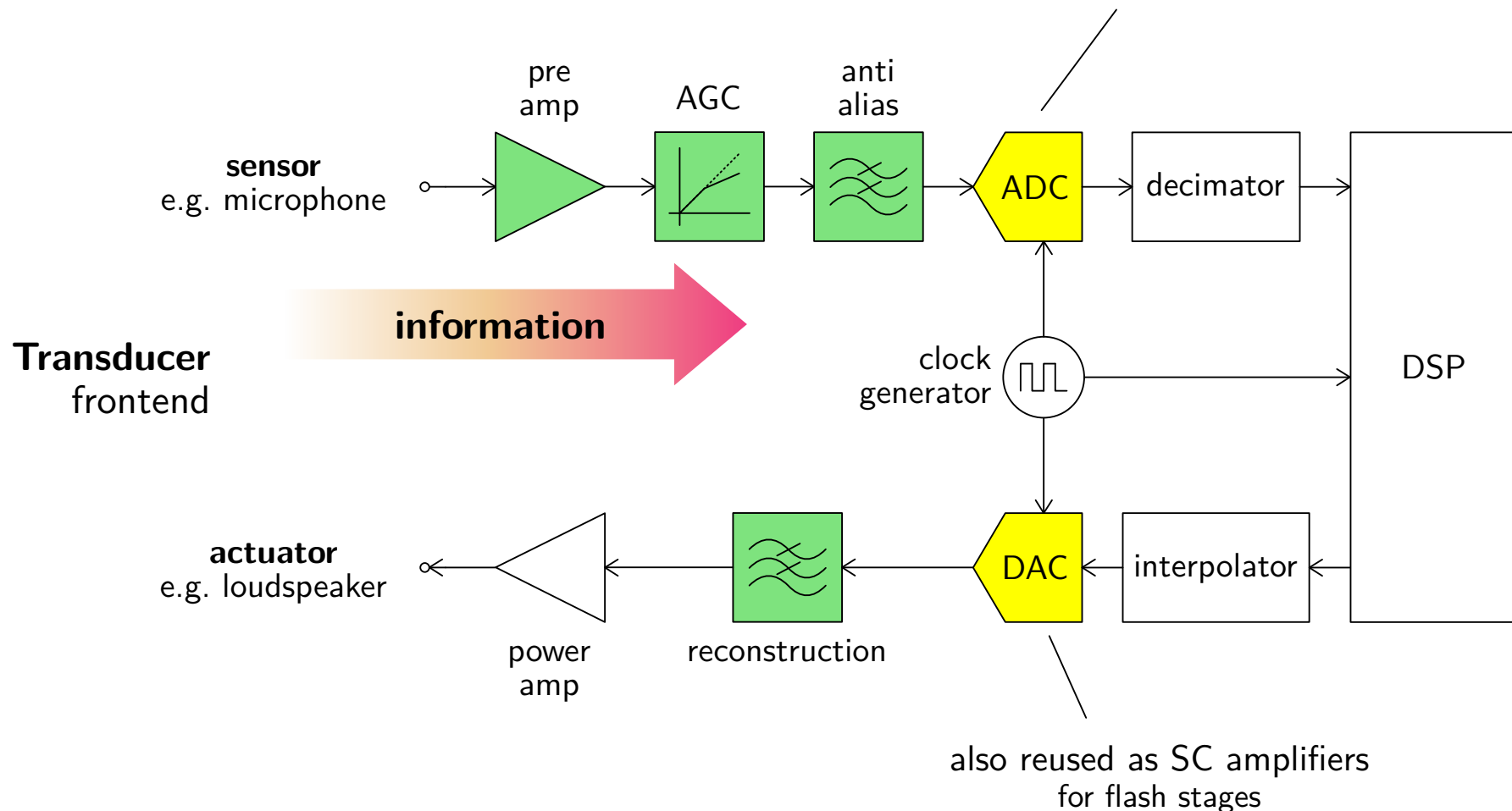discrete time (DT) but still analog domain,
e.g. **Delta-Sigma modulators**




SC Integrator

- The very basic building **block**:

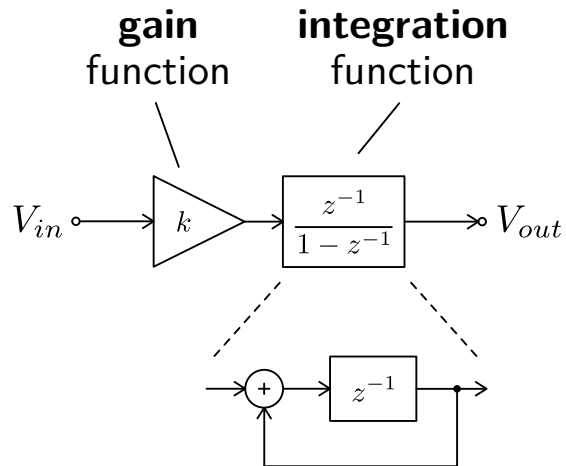


Analog circuit realization (ADC)

Digital circuit realization (DAC)


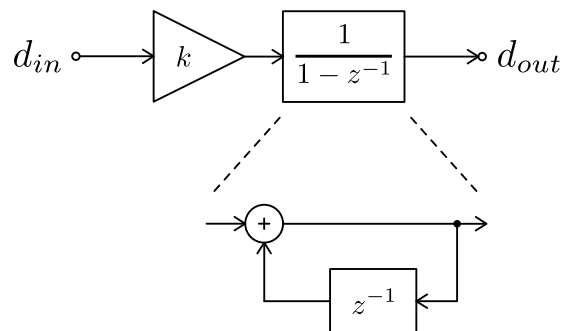


SC Integrator

- The very basic building **block**:



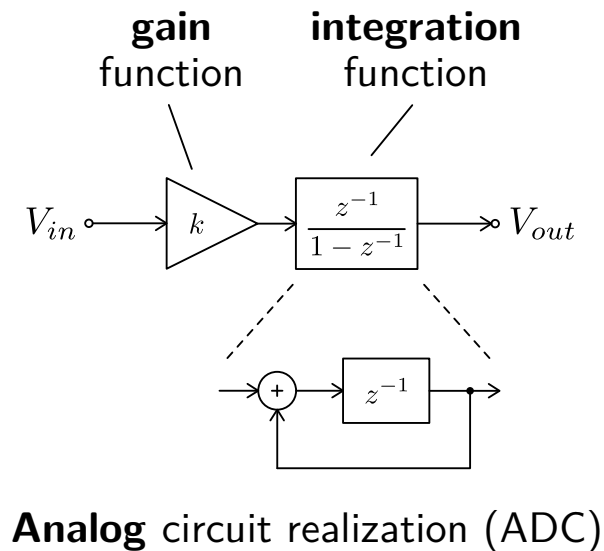


- SC-OpAmp **compact** implementation:

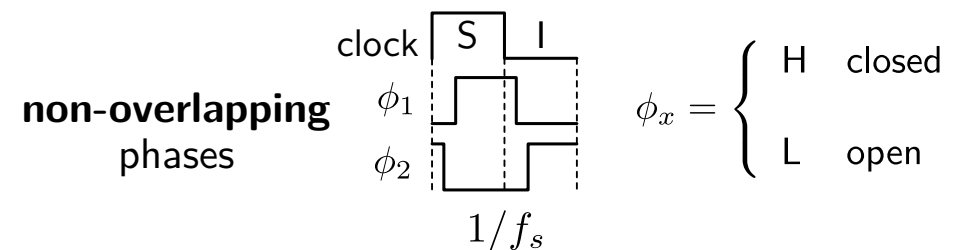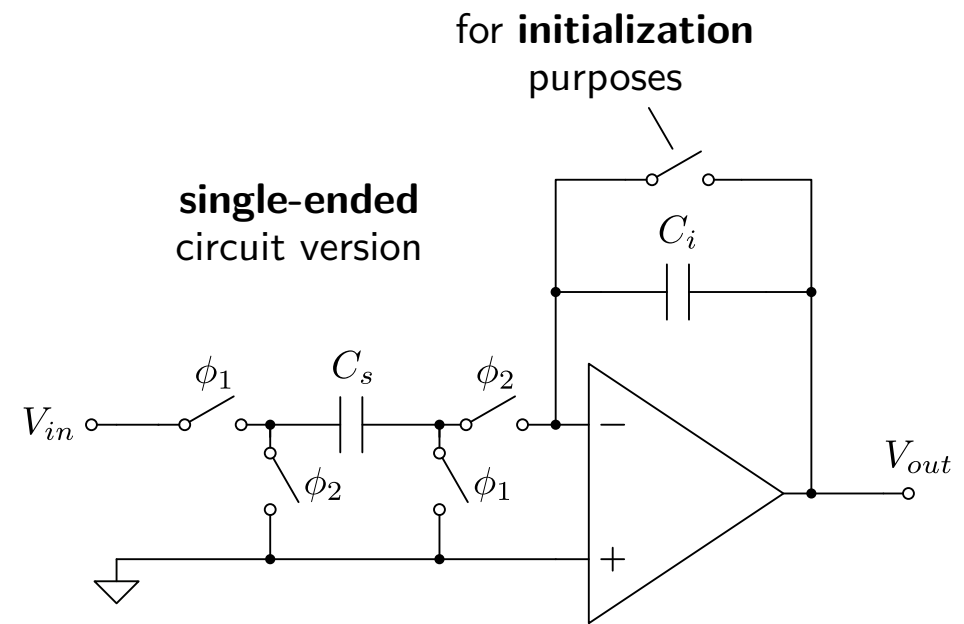



SC Integrator

► SC-OpAmp **compact** implementation:

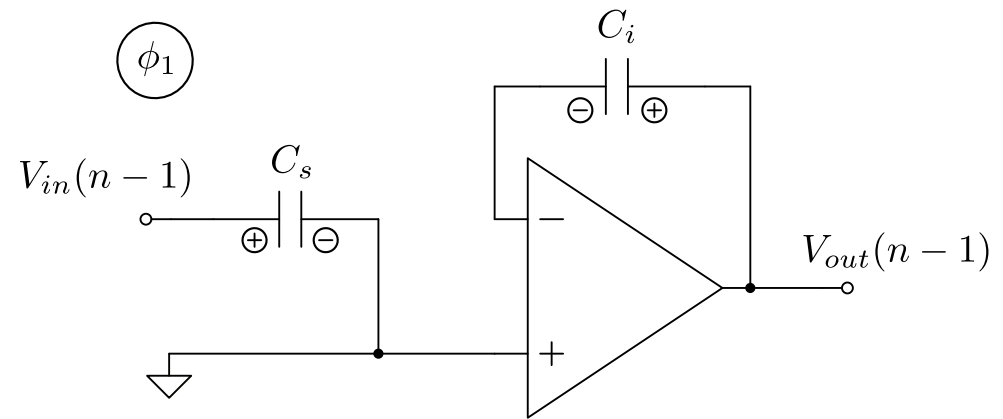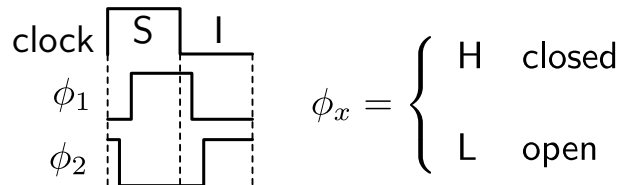
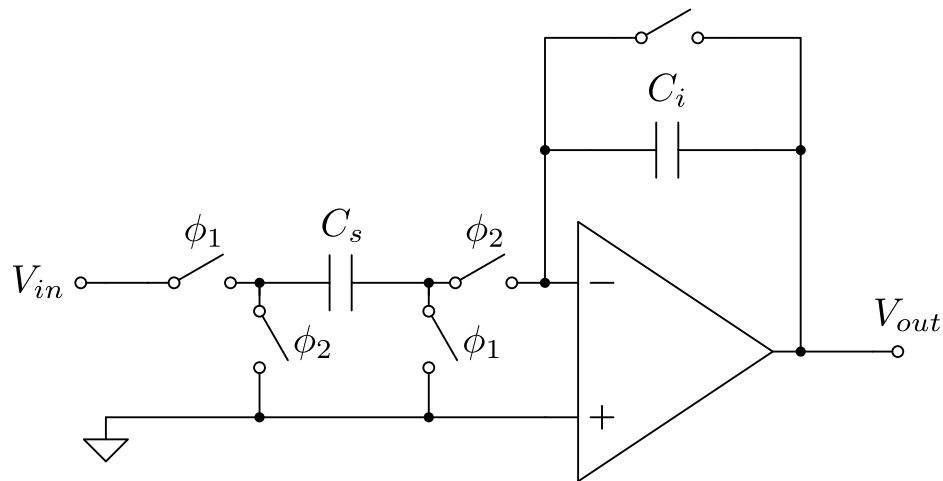


SC Integrator

► SC-OpAmp **compact** implementation:

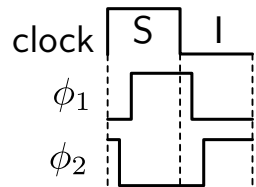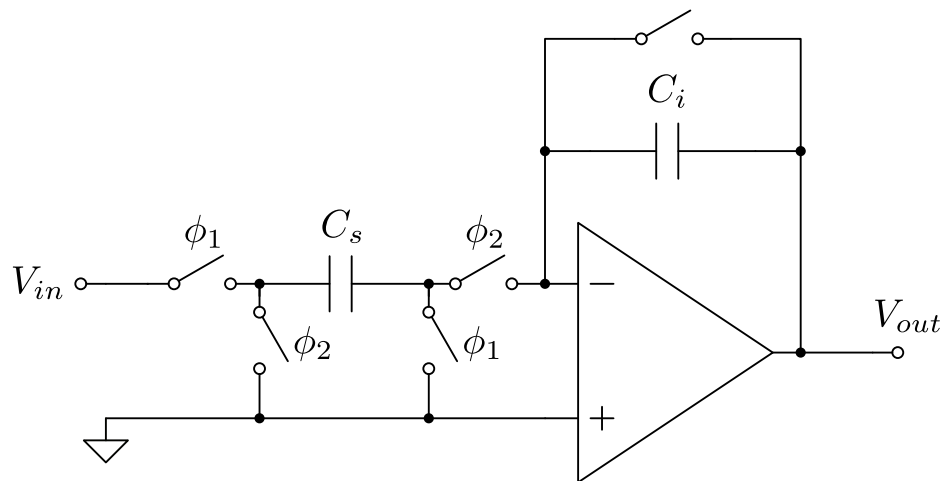
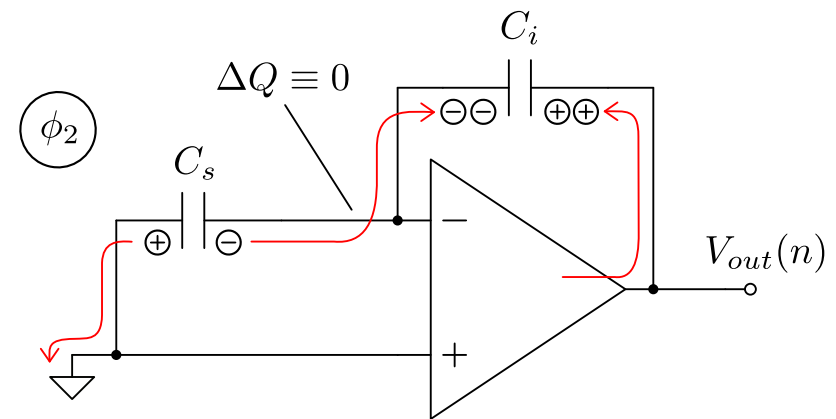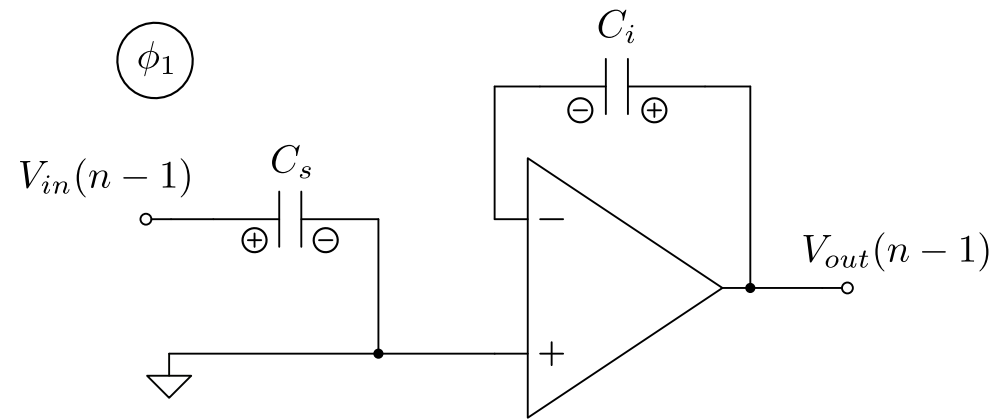
$$\phi_x = \begin{cases} \text{H} & \text{closed} \\ \text{L} & \text{open} \end{cases}$$







$$V_{out}(n) = V_{out}(n-1) + \frac{C_s}{C_i} V_{in}(n-1)$$

$$\frac{V_{out}}{V_{in}}(z) = k \frac{z^{-1}}{1 - z^{-1}} \quad k \doteq \frac{C_s}{C_i}$$


SC OpAmp Optimization

► Discrete time **dynamic** biasing:

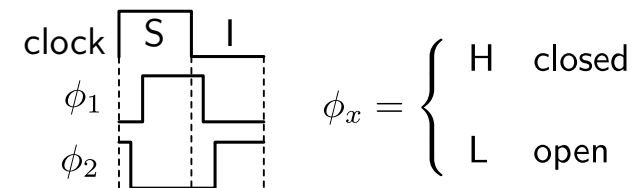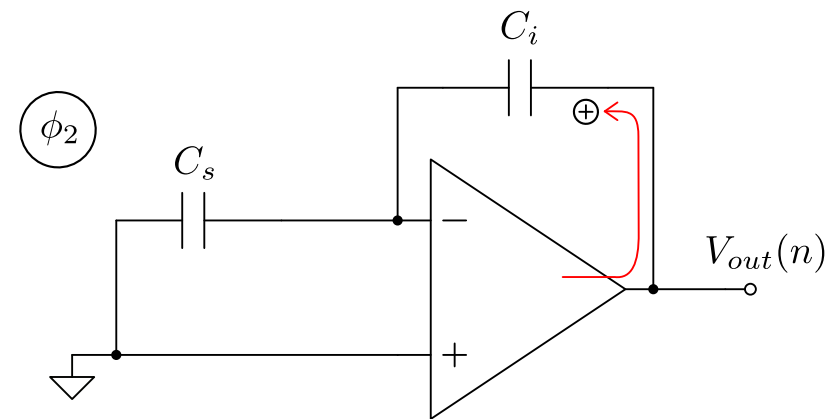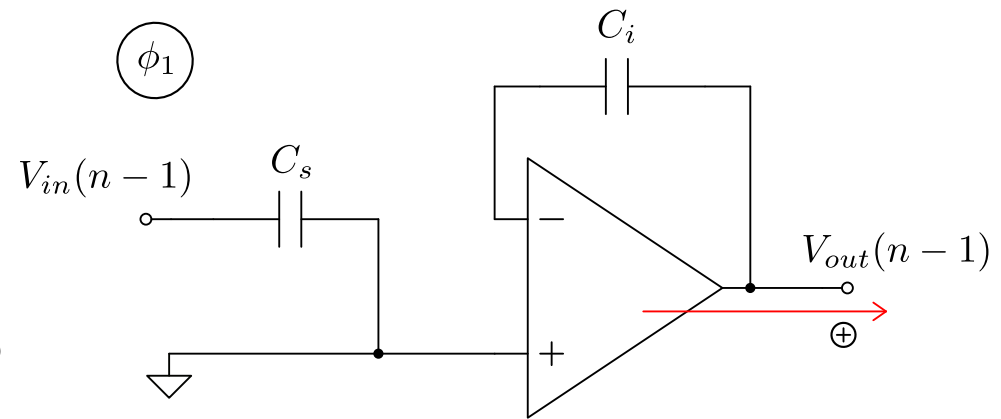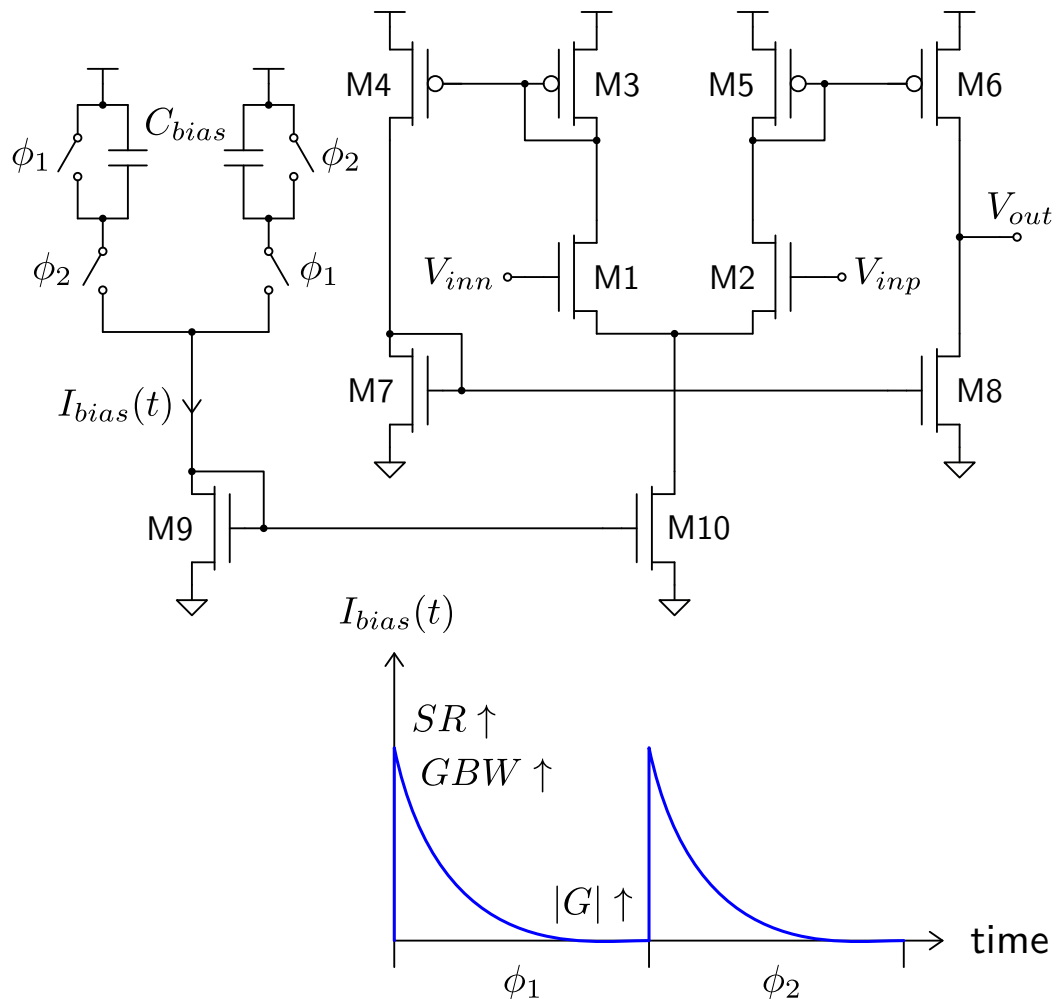

SC OpAmp Optimization

► Discrete time **dynamic** biasing:

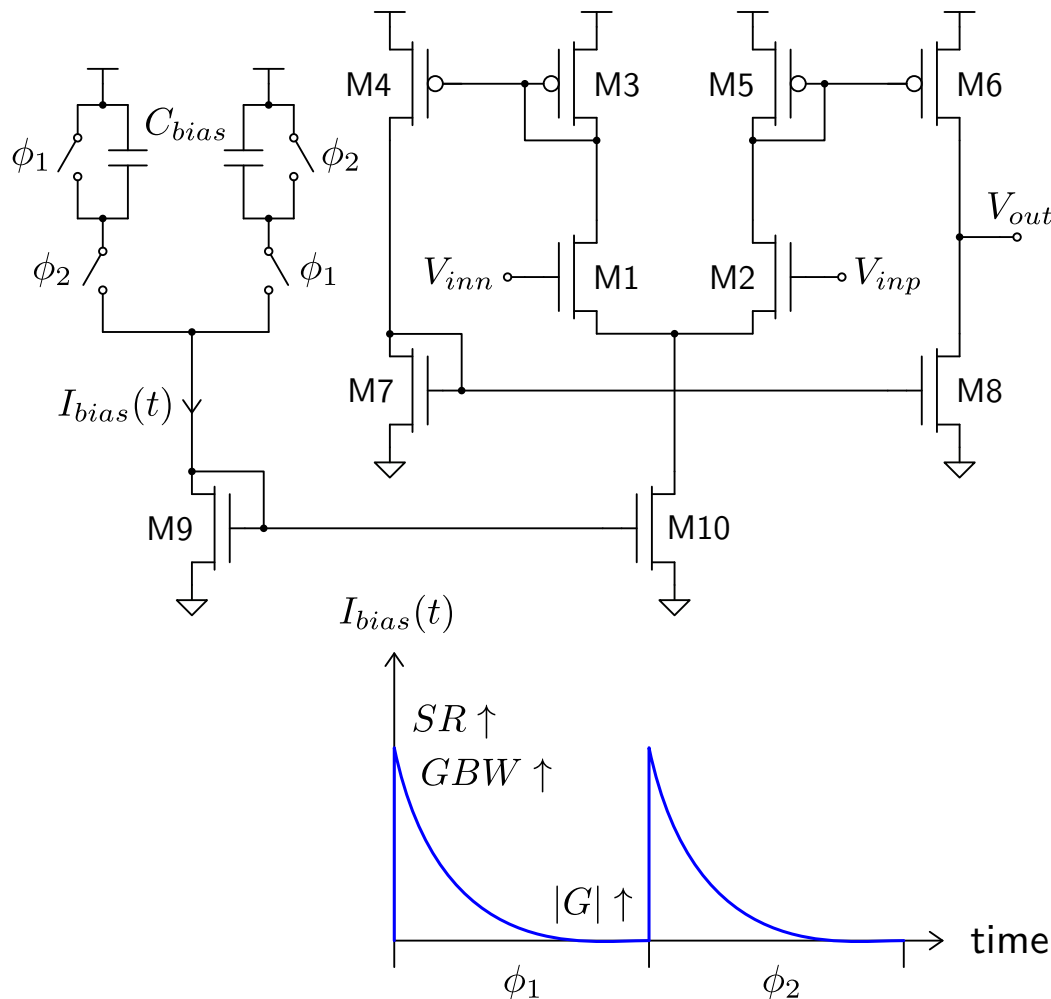

▲ Synchronous **Class-AB** operation

▲ Static **power** savings

▼ OpAmp fast on/off **recovery** time required

▼ Biasing **peak** value is technology dependent

▼ **Ripple** induced in the power rails (digital-like)