

102726

Design of Analog and Mixed Integrated Circuits and Systems Lab Manual

Francesc Serra Graells
<http://www.cnm.es/~pserra/uab/damics>
paco.serra@imb-cnm.csic.es

Contents

1 Objectives	2
2 Installation	2
3 CMOS Technology	5
3.1 Design Rules	6
3.2 Device Models	7
4 My Operational Amplifier	10
4.1 Schematic Entry	10
4.2 Electrical Simulation	14
4.3 Circuit Optimization	19
4.4 PCell-Based Netlist-Driven Layout Design	21
4.5 Design Rule Checker	34
4.6 Circuit Extraction and Electrical Rule Checker	39
4.7 Layout Versus Schematic	45
4.8 2D and 3D Parasitics Extraction	51
4.9 Post-Layout Simulation	59
4.10 Tape-Out	59
Glossary	60
References	61

1 Objectives

The aim of these lab exercises is to introduce the general electronic design automation (EDA) methodology of Fig. 1 for full-custom analog integrated circuit (IC) design. For this purpose, a practical design case based on a simple operational amplifier (OpAmp) circuit is developed step-by-step, from the metal-oxide-semiconductor (MOS) transistor schematic to the physical mask layout.



Students will deliver the following **computer files** for evaluation:

- The OpAmp **design report** in portable document format (PDF) containing the answers to questions **Q1-Q10** together with all the required supporting materials (e.g. hand calculations, simulation plots. . .).
- The OpAmp **layout** in graphic database system II (GDSII) format.

Before starting with the lab exercises of Section 4, the installation of the required EDA tools and the details of the target complementary metal-oxide-semiconductor (CMOS) technology are discussed in next two sections, respectively.

2 Installation

The EDA tools chosen for the design flow of Fig. 1 are freely available for both MS Windows and Linux operative systems. In particular:



Glade (GDS, LEF and DEF editor) by Peardrop Design Systems is an IC schematic and mask layout editor, programmable netlist and physical verification tool featuring Python language scripting. More information can be found at <http://www.peardrop.co.uk/glade>.



SpiceOpus (SPICE with integrated optimization utilities) by the CACD Group at University of Ljubljana is a port of the Berkeley SPICE3 electrical simulator featuring NUTMEG language scripting, together with a custom optimization tool and the Georgia Tech Research Institute XSpice high-level multi-domain event-driven engine. The resulting simulation suite can perform native mixed-signal circuit and system simulation and optimization. More information can be found in [1] and at <http://fides.fe.uni-lj.si/spice>.



The **physical design kit (PDK)** contains all the technological information needed by Glade and SpiceOpus according to Fig. 1, as well as the lab exercises themselves.

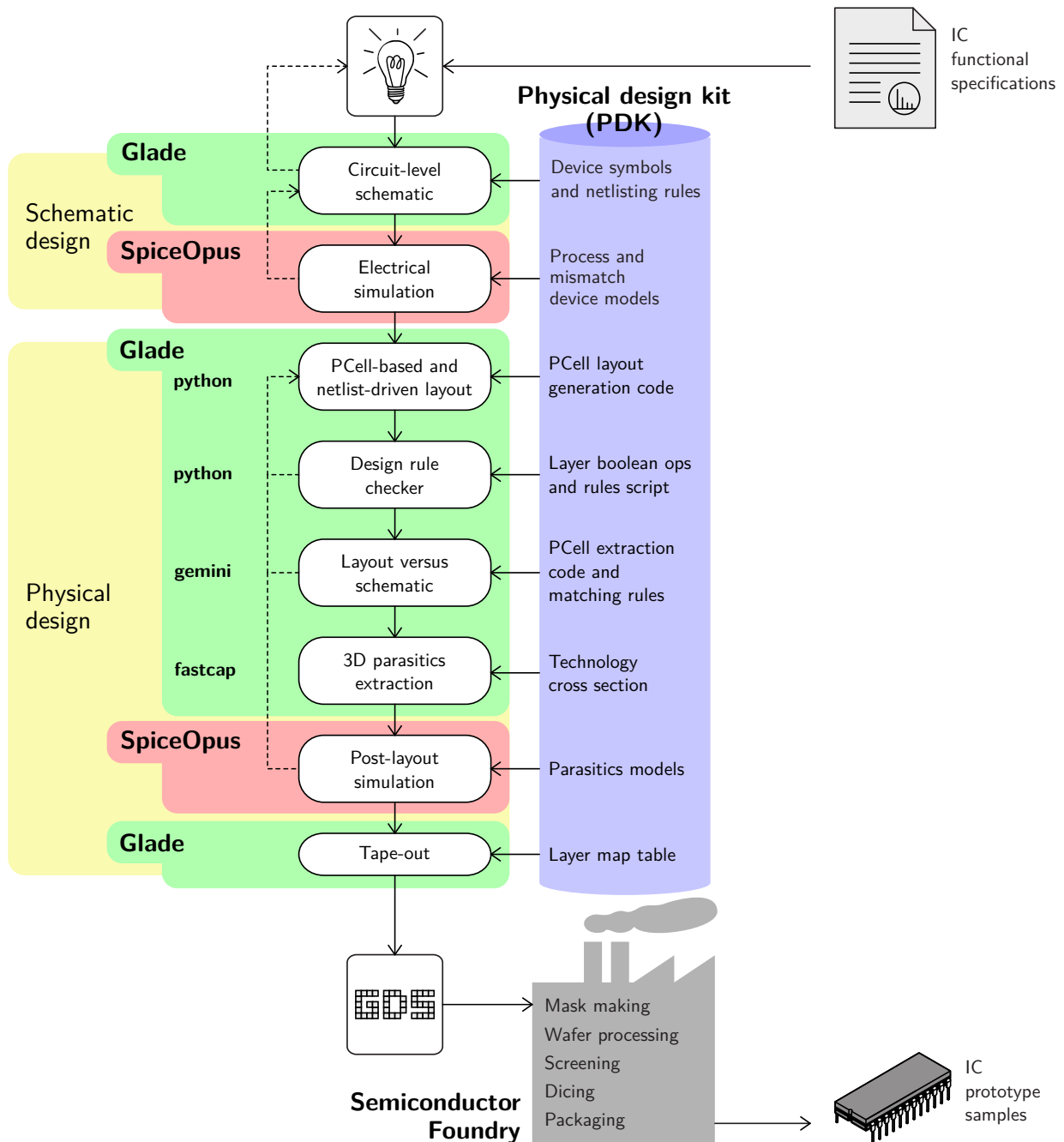




Figure 1 | General full-custom IC design methodology and proposed EDA tools.

The installation instructions to be followed before starting with the lab exercises are described below:

 Browse to <http://www.cnm.es/~pserra/uab/damics/lab.html>.

 Download and install Glade and SpiceOpus for your operative system (OS).

 Download and extract the lab PDK for your OS:


damics-kit/doc	This manual!
/glade	Schematic and layout library, technology files and verification rules
/spiceopus	Simulation models, test netlists and scripts

 For **MS Windows**, adjust **red paths** in:

```
- glade\glade.bat:
set GLADE_HOME=path_to_glade
set PATH=%GLADE_HOME%;%PATH%
set PYTHONPATH=.;\pcells;\verification
set GLADE_LOGFILE_DIR=.
set GLADE_DRC_WORK_DIR=.
set GLADE_DRC_FILE=.\verification\cnm25drc.py
set GLADE_EXT_FILE=.\verification\cnm25xtr_lvs.py
set GLADE_FASTCAP_WORK_DIR=.
del *.*.log
start /b glade.exe -script .\glade_init.py
```


If MS Visual C++ libs (i.e. MSVCP*.dll) are not already in your OS, then execute the vc_redist*.exe installer supplied with Glade.

```
- spiceopus\spiceopus.bat:
set OPUSHOME=path_to_spiceopus
set PATH=.;%OPUSHOME%\bin;%PATH%
start /b spiceopus.exe -pw .
```

 For **Linux**, adjust **red paths** in:

```
- glade/glade.sh:
#!/bin/bash
export GLADE_HOME=path_to_glade
export PATH=${GLADE_HOME}/bin:${PATH}
export LD_LIBRARY_PATH=${GLADE_HOME}/lib:
${LD_LIBRARY_PATH}
export PYTHONPATH=../pcells:/verification:
${GLADE_HOME}/bin:${PYTHONPATH}
export GLADE_LOGFILE_DIR=.
export GLADE_DRC_WORK_DIR=.
export GLADE_DRC_FILE=./verification/cnm25drc.py
export GLADE_EXT_FILE=./verification/cnm25xtr_lvs.py
export GLADE_FASTCAP_WORK_DIR=.
rm *.*.log
glade -script ./glade_init.py &
```

```
- spiceopus/spiceopus.sh:
#!/bin/bash
export OPUSHOME=path_to_spiceopus
export PATH=.:${OPUSHOME}/bin:${PATH}
export LD_LIBRARY_PATH=.:${LD_LIBRARY_PATH}
spiceopus -pw . &
```

 **Glade and SpiceOpus tools must be always launched using the above scripts!**

3 CMOS Technology

Your OpAmp will be designed for the $2.5\mu\text{m}$ 2-polySi 2-metal CMOS technology from IMB-CNM(CSIC) (CNM25). The main native devices available from this CMOS process are the bulk P-type and N-type MOS field-effect transistor (MOSFET) and the polySi-insulator-polySi (PiP) capacitor, as shown in Fig. 2. The corresponding physical layers for the full-custom layout design are listed in Table 1.

 


Figure 2 | CNM25 devices (top) and process cross section (bottom). Not to scale.

GDS num.	Name	Explanation
1	NTUB	N-well
2	GASAD	Active area
3	POLY0	PolySi for PiP capacitors only
4	POLY1	PolySi for MOS gate and routing
5	NPLUS	N ⁺ implant
6	WINDOW	Contact window
7	METAL	Metal 1
9	METAL2	Metal 2
10	VIA	Metal 1-2 via
8	CAPS	Passivation window

Table 1 | CNM25 design layer table.

3.1 Design Rules

In order to ensure the manufacturability of your CMOS circuit, its full-custom layout must be compliant with the CNM25 design rules listed in Table 2.

Ref.	Description
0.0	Design grid is 0.25um x 0.25um
1.1	N-well width $\geq 8\mu\text{m}$
1.2	N-well spacing and notch $\geq 8\mu\text{m}$
2.1	GASAD width $\geq 2\mu\text{m}$
2.2	GASAD spacing and notch $\geq 4\mu\text{m}$
2.3	N-well enclosure of P-plus active $\geq 5\mu\text{m}$
2.4	N-well spacing to N-plus active $\geq 5\mu\text{m}$
3.1	Poly0 width $\geq 2.5\mu\text{m}$
3.2	Poly0 spacing and notch $\geq 6\mu\text{m}$
3.3	Poly0 spacing to GASAD $\geq 6\mu\text{m}$
4.1.a	Poly1 width inside GASAD $\geq 3\mu\text{m}$
4.1.b	Poly1 width outside GASAD $\geq 2.5\mu\text{m}$
4.2	Poly1 spacing and notch $\geq 3\mu\text{m}$
4.3	GASAD extension of Poly1 $\geq 3\mu\text{m}$
4.4	Poly1 extension of GASAD $\geq 2.5\mu\text{m}$
4.5	Poly1 spacing to GASAD $\geq 1.25\mu\text{m}$
4.6	Poly0 enclosure of Poly1 $\geq 3\mu\text{m}$
5.1	N-plus enclosure of GASAD $\geq 2.5\mu\text{m}$
5.2	N-plus spacing to P-plus active $\geq 2.5\mu\text{m}$
5.3	N-plus spacing to Poly1 inside P-plus active $\geq 2\mu\text{m}$
5.4	N-plus extension of Poly1 inside N-plus active $\geq 1.5\mu\text{m}$
5.5	N-plus width $\geq 2.5\mu\text{m}$
5.6	N-plus spacing and notch $\geq 2.5\mu\text{m}$
6.1	Exact contact size = $2.5\mu\text{m} \times 2.5\mu\text{m}$
6.2	Contact spacing $\geq 3\mu\text{m}$
6.3	GASAD enclosure of Contact $\geq 1\mu\text{m}$
6.4	Poly1 enclosure of Contact $\geq 1.25\mu\text{m}$
6.5	Poly1 Contact spacing to GASAD $\geq 2.5\mu\text{m}$
6.6	Contact spacing to Poly1 inside GASAD $\geq 2\mu\text{m}$
6.9	Poly0 enclosure of Contact $\geq 4\mu\text{m}$
6.10	Contact spacing to Poly1 & Poly0 $\geq 4\mu\text{m}$
7.1	Metal1 width $\geq 2.5\mu\text{m}$
7.2	Metal1 spacing and notch $\geq 3\mu\text{m}$
7.3	Metal1 enclosure of Contact $\geq 1.25\mu\text{m}$
8.1	Exact via size = $3\mu\text{m} \times 3\mu\text{m}$
8.2	Via spacing $\geq 3.5\mu\text{m}$
8.3	Metal1 enclosure of Via $\geq 1.25\mu\text{m}$
8.4	Via spacing to Contact $\geq 2.5\mu\text{m}$
8.5	Via spacing to Poly1 $\geq 2.5\mu\text{m}$
9.1	Metal2 width $\geq 3.5\mu\text{m}$
9.2	Metal2 spacing and notch $\geq 3.5\mu\text{m}$
9.3	Metal2 enclosure of Via $\geq 1.25\mu\text{m}$
10.1	Exact passivation window size = $100\mu\text{m} \times 100\mu\text{m}$

 
 
 
 


Table 2 | CNM25 design rules (left) and definitions (right).

This PDK comes with tools for assisting the designer during the edition of the full-custom layout, as explained in Section 4.4. However, due to number of rules present in Table 2 and their layer interdependency, the specific physical verification step of Section 4.5 is also included in the methodology of Fig. 1.

3.2 Device Models

The methodology of Fig. 1 predicts the final performance of your IC design through the electrical simulation of its equivalent circuit extracted from the mask layout. For this purpose, the PDK includes `damics-kit/spiceopus/cnm25mod.lib`, the full set of model parameters for the CNM25 devices of Fig. 2 to be used in Simulation Program with Integrated Circuit Emphasis (SPICE). In the case of MOS transistors, the Berkeley Short-channel IGFET Model version 3.3 (BSIM3v3) is employed [2]. In general, two types of parameters are given by the foundry to cover its technology deviations:

Process parameters deal with global deviations at wafer level (e.g. drift in gate oxide thickness), with correlation distances much larger than device dimensions. Hence, process variations affect in the same way all devices in the circuit belonging to a given type (e.g. N-type MOSFETs). Usually, process parameters are defined as worse case conditions, which can be also extended to full process, supply voltage and temperature (PVT) corners. CNM25 SPICE process corners for N-type MOS (NMOS) and P-type MOS (PMOS) transistors and PiP capacitors are combined as typical (t), slow (s) and fast (f) cases of threshold voltage (V_{TO}), carrier mobility (μ_0) and capacitance density (C_j).

Matching parameters are intended for local variations at circuit level (e.g. dopant fluctuations), with correlation distances comparable to device dimensions. In this case, variations affect in a different way each component of the circuit, even belonging to the same device type. In general, the technological mismatching of P parameter (ΔP) between a pair of equally designed devices follows the simplified Pelgrom's law [3]:

$$\sigma(\Delta P) = \frac{A_P}{\sqrt{WL}} \quad (1)$$

where σ is the Gaussian standard deviation, WL stands for the device area and A_P is the mismatching coefficient of the given technology. CNM25 SPICE mismatching parameters for NMOS and PMOS transistors and PiP capacitors are also supplied as local variations of V_{TO} , μ_0 and C_j parameters for Montecarlo simulation.

```
damics-kit/spiceopus/cnm25mod.lib
1 .lib common
2 .subckt cnm25modn d g s b param: w=3u l=3u ad=0 as=0 pd=0 ps=0 m=1
3 .param vth0eff = vth0n+rndgauss(avth0/sqrt(m*w*l))
4 .param u0eff = u0n*(1+rndgauss(rau0/sqrt(m*w*l)))
5 .model nbsim nmos
6 + LEVEL = 53
7 + VERSION = 3.2.4          TNOM = 27          TOX = 3.75E-8
8 + XJ = 1.5E-7             NCH = 1.7E17         VTH0 = {vth0eff}
9 + K1 = 1.17296            K2 = -0.05           K3 = 11.2079
10 + K3B = -1.59332         WO = 1.00727E-6       NLX = -1E-9
11 + DVTOW = 0              DVT1W = 0            DVT2W = -0.032
12 + DVT0 = 4.11104         DVT1 = 0.366189       DVT2 = -0.182099
13 + U0 = {u0eff}           UA = 1.72783E-10      UB = 5E-18
14 + UC = 4.01727E-11       VSAT = 1.848E5        A0 = 1.05122
15 + AGS = 0.111468         B0 = 1.6771E-7        B1 = -5.04982E-9
16 + KETA = -0.047          A1 = 0            A2 = 1
17 + RDSW = 3.65E3          PRWG = 0.0338512      PRWB = -1E-3
18 + WR = 1                 WINT = 4.55906E-7       LINT = 9E-7
19 + XL = 0                  XW = 0              DWG = -2.5492E-8
20 + DWB = 3.22958E-8       VOFF = -0.124454     NFACTOR = 1.04789
21 + CIT = 0                 CDSC = 2.4E-4         CDSCD = 0
22 + CDSCB = 0              ETA0 = 0.0354838      ETAB = -0.07
23 + DSUB = 0.56            PCLM = 1.96809       PDIBLC1 = 0.482853
```

```

24 + PDIBLC2 = 0.01          PDIBLCB = 0          DROUT   = 0.415163
25 + PSCBE1  = 5.99202E8    PSCBE2  = 5E-5        PVAG    = 0.0141775
26 + DELTA   = 3.6636E-3    MOBMOD  = 1          PRT     = 0
27 + UTE     = -1.5         KT1     = 0          KT1L    = 0
28 + KT2     = 0            UA1     = 4.31E-9      UB1     = -7.61E-18
29 + UC1     = -5.6E-11     AT      = 3.3E4       NQSMOD  = 0
30 + WL      = 0            WLN     = 1          WW     = 0
31 + WVN     = 1            WWL     = 0          LL     = 0
32 + LLN     = 1            LW      = 0          LWN     = 1
33 + LWL     = 0            CAPMOD  = 2          CJ      = 2.940466E-4
34 + PB      = 0.6681951    MJ      = 0.438766     CJSW    = 5.450602E-10
35 + PBSW    = 0.4          MJSW    = 0.2725869    TCJ     = 0
36 + TPB     = 0            TCJSW   = 0          TPBSW   = 0
37 + NOFF    = 1            ACDE    = 1          MOIN    = 15
38 + TPBSWG  = 0            TCJSWG  = 0          PRDSW   = -3.85642E3
39 + PVSAT   = -1.8E5       CGDO    = 9.89535E-10   CGSO    = 9.89535E-10
40 + NOIMOD  = 1            AF      = 1.33        KF      = 1e-29
41 mn d g s b nbsim w={w} l={l} ad={ad} as={as} pd={pd} ps={ps} m={m}
42 .ends
43
44 .subckt cnm25modp d g s b param: w=3u l=3u ad=0 as=0 pd=0 ps=0 m=1
45 .param vth0eff = vth0+rndgauss(avth0/sqrt(m*w*l))
46 .param u0eff = u0p*(1+rndgauss(rau0/sqrt(m*w*l)))
47 .model pbsim pmos
48 + LEVEL    = 53
49 + VERSION  = 3.2.4          TNOM    = 27          TOX     = 3.75E-8
50 + XJ       = 1.5E-7         NCH    = 1.7E17      VTH0    = {vth0eff}
51 + K1       = 0.74278        K2     = -4.93305E-5  K3      = -77.5174
52 + K3B     = -3.17908        W0     = 6.70948E-6  NLX     = 1.44524E-7
53 + DVTOW   = 0              DVT1W  = 0          DVT2W   = -0.032
54 + DVTO    = 1.61621        DVT1   = 0.15752    DVT2    = -0.05
55 + UO      = {u0eff}        UA      = 2.65041E-9  UB      = 4.97595E-18
56 + UC      = -9.99573E-11   VSAT   = 5E5        A0      = 0.804733
57 + AGS     = 0.0783374     BO      = 3.55811E-7  B1      = 2.01182E-10
58 + KETA    = -0.047         A1     = 0          A2      = 1
59 + RDSW    = 5.41703E3     PRWG   = 0.013649   PRWB    = -1E-3
60 + WR      = 1              WINT   = 5E-7       LINT    = 8E-7
61 + XL      = 0              XW     = 0          DWG     = -1.44072E-8
62 + DWB     = 5.72498E-8    VOFF   = -0.196491  NFACTOR = 0.924527
63 + CIT     = 0              CDSC   = 2.4E-4     CDSCD   = 0
64 + CDSB    = 0              ETA0   = 0.3989455  ETAB    = -0.07
65 + DSUB    = 0.56          PCLM   = 4.3768578  PDIBLC1 = 0.7281865
66 + PDIBLC2 = 0.0140758     PDIBLCB = 0        DROUT   = 0.2398601
67 + PSCBE1  = 8E8           PSCBE2  = 5E-5        PVAG    = 0.0099941
68 + DELTA   = 0.0634845     MOBMOD  = 1          PRT     = 0
69 + UTE     = -1.5         KT1     = 0          KT1L    = 0
70 + KT2     = 0            UA1     = 4.31E-9      UB1     = -7.61E-18
71 + UC1     = -5.6E-11     AT      = 3.3E4       NQSMOD  = 0
72 + WL      = 0            WLN     = 1          WW     = 0
73 + WVN     = 1            WWL     = 0          LL     = 0
74 + LLN     = 1            LW      = 0          LWN     = 1
75 + LWL     = 0            CAPMOD  = 2          CJ      = 3.728047E-4
76 + PB      = 0.7982792    MJ      = 0.4562281  CJSW    = 3.946756E-10
77 + PBSW    = 0.587129    MJSW    = 0.2658605  TCJ     = 0
78 + TPB     = 0            TCJSW   = 0          TPBSW   = 0
79 + NOFF    = 1            ACDE    = 1          MOIN    = 15
80 + TPB     = 0            TPBSW   = 0          TPBSWG  = 0
81 + TCJ     = 0            TCJSW   = 0          TCJSWG  = 0
82 + CGDO    = 1.2894E-9     CGSO    = 1.2894E-9  KF      = 1e-29
83 + NOIMOD  = 1            AF      = 1.33

```



```

84 mp d g s b pbsim w={w} l={l} ad={ad} as={as} pd={pd} ps={ps} m={m}
85 .ends
86
87 .subckt cnm25cpoly t b param: w=30u l=30u m=1
88 .param cjeff = cj*(1+rndgauss(racj/sqrt(m*w*l)))
89 .model cap c CJ = {cjeff} CJSW = 0.0
90 ci t b cap w={w} l={l} m={m}
91 .ends
92 .endl
93
94 *** Process corners
95 .lib ttt
96 .param vth0n = 0.860363
97 .param vth0p = -1.52069
98 .param u0n = 0.0573986
99 .param u0p = 0.0228166
100 .param cj = 4.227E-4
101 .param avth0 = 0
102 .param rau0 = 0
103 .param racj = 0
104 .lib 'cnm25mod.lib' common
105 .endl
106
107 .lib sss
108 .param vth0n = 1.00467
109 .param vth0p = -1.73564
110 .param u0n = 0.0367598
111 .param u0p = 0.0140327
112 .param cj = 4.650E-4
113 .param avth0 = 0
114 .param rau0 = 0
115 .param racj = 0
116 .lib 'cnm25mod.lib' common
117 .endl
118
119 .lib fff
120 .param vth0n = 0.63934
121 .param vth0p = -1.20160
122 .param u0n = 0.0780374
123 .param u0p = 0.0316005
124 .param cj = 3.804E-4
125 .param avth0 = 0
126 .param rau0 = 0
127 .param racj = 0
128 .lib 'cnm25mod.lib' common
129 .endl
130
131 *** Montecarlo mismatching: AVto{n,p} = 30mVum, AUo{n,p}/Uo = 5%um and ACj/Cj = 0.5%um
132 .lib ttt_mc
133 .param vth0n = 0.860363
134 .param vth0p = -1.52069
135 .param u0n = 0.0573986
136 .param u0p = 0.0228166
137 .param cj = 4.227E-4
138 .param avth0 = 30e-9
139 .param rau0 = 5e-8
140 .param racj = 5e-9
141 .lib 'cnm25mod.lib' common
142 .endl

```

damics-kit/spiceopus/cnm25mod.lib

4 My Operational Amplifier

The CMOS circuit implementation chosen for your OpAmp is the classic two-stage Miller-compensated single-ended output topology of Fig. 3, consisting on two cascaded voltage amplification stages [4]. The first stage includes the PMOS differential pair M1-M2 with current steering M3-M4, all biased by the current mirror M8-M7. The second stage is built around the inverting amplifier M6 biased by the current mirror M8-M5. Finally, the nested capacitor C_{comp} is introduced for the frequency compensation of the multi-pole OpAmp. The initial circuit design parameters are shown in the same figure.

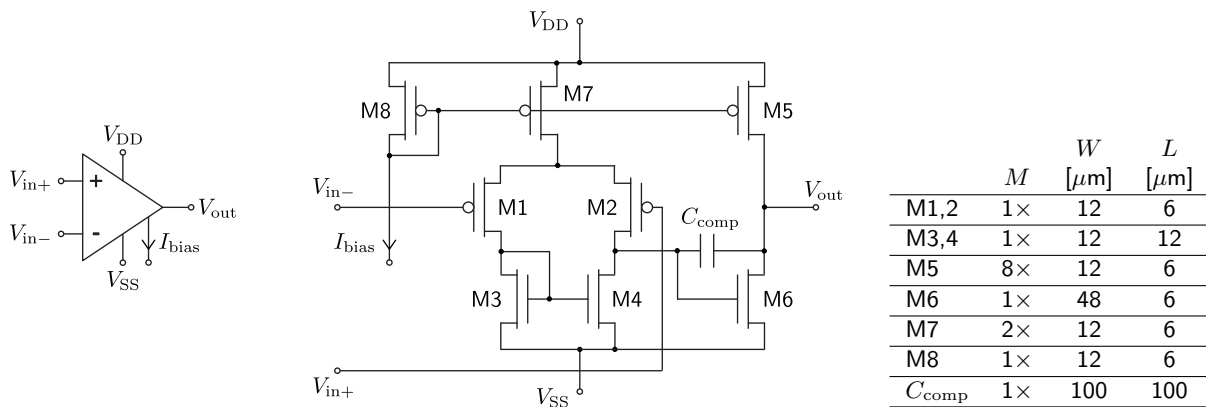


Figure 3 | OpAmp symbol, CMOS schematic and initial device sizing.

4.1 Schematic Entry

Starting with the design methodology of Fig. 1, all schematic entries at system and circuit levels are performed through the Glade editor. When in schematic mode, this tool supports symbol edition, net and pin labeling, design hierarchy and instance annotation, among other features. As an example, Fig. 4 depicts the equivalent schematic of the OpAmp presented in Fig. 3 being edited in Glade using the PDK custom library damics-kit/glade/ExampleLib. Taking advantage of Glade netlisting configurability, specific backend rules have been defined in all symbols to generate circuit description language (CDL) netlists compatible with SPICE3 simulation.

- 🔧 Launch damics-kit/glade/glade.bat (or .sh).
- 🔧 Open the OpAmp cell view ExampleLib→opamp_design→schematic with the library browser and fill the device parameter values of Fig. 3.
- 🔧 Check for schematic connectivity errors with Check→Check Cellview.
- 🔧 Save all cell view changes with File→Save Cell.

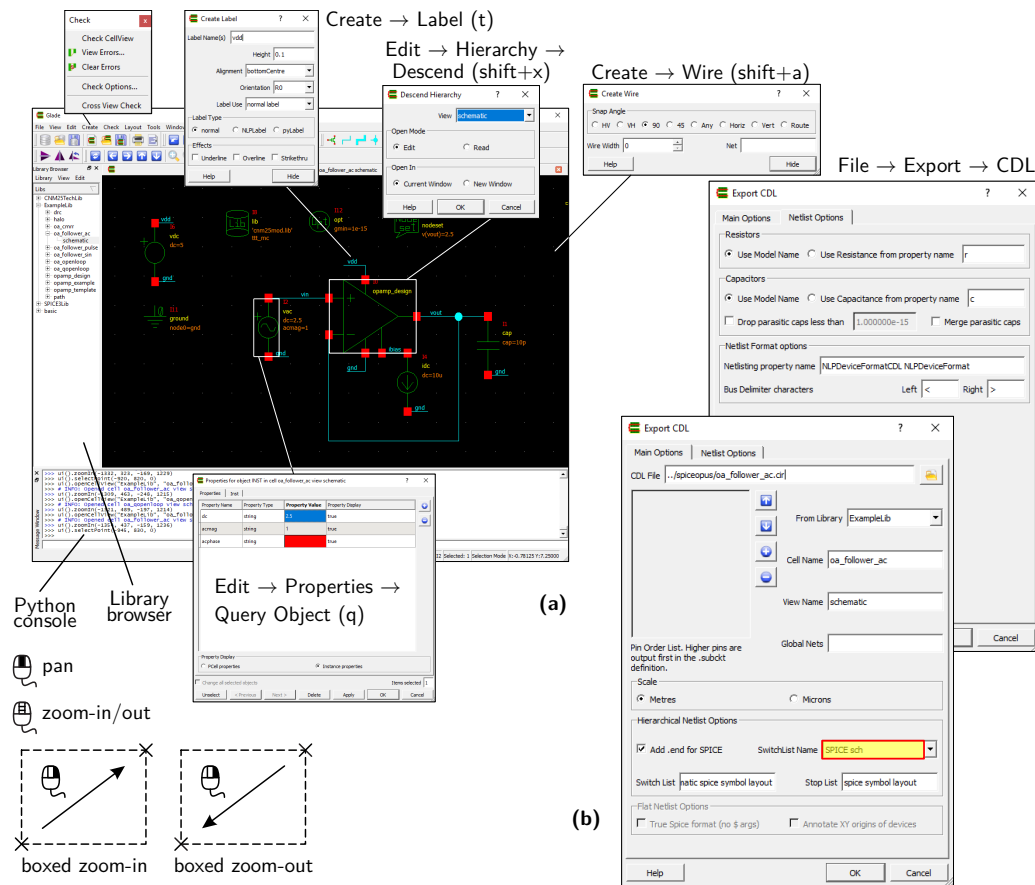


Figure 4 | Main window of the Glade schematic editor (a) and CDL export dialogue configuration (b) for SPICE schematics (pre-layout).

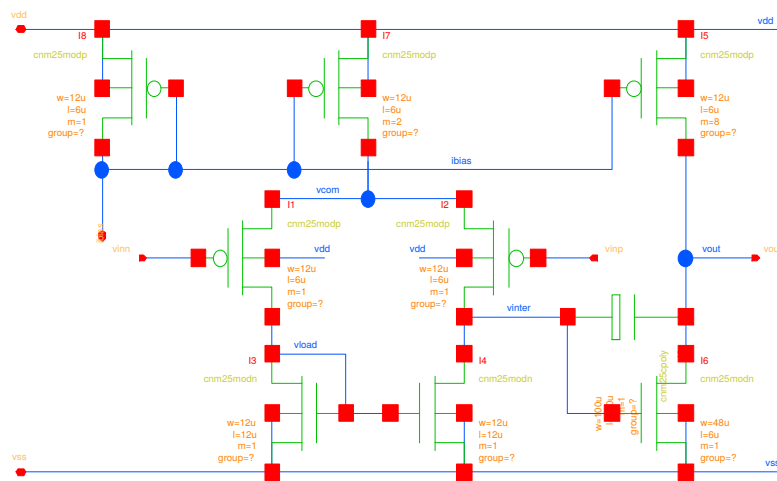


Figure 5 | Glade cell view ExampleLib→opamp_design→schematic for the OpAmp circuit of Fig. 3 after setting all device parameter values.

The first step towards the design of an IC block is to build a suitable test bench for the analysis of its performance parameters. In this sense, the PDK features a set of test-bench examples oriented to the characterization of OpAmps, as summarized in Fig. 6. This schematics collection includes: open-loop configuration (oa_openloop); quasi open-loop topology (oa_qopenloop); follower with small-signal (oa_follower_ac), pulsed (oa_follower_pulse) or sinusoidal (oa_follower_sin) input, and an specific setup for the extraction of the common-mode rejection ratio (CMRR) (oa_cmrr).

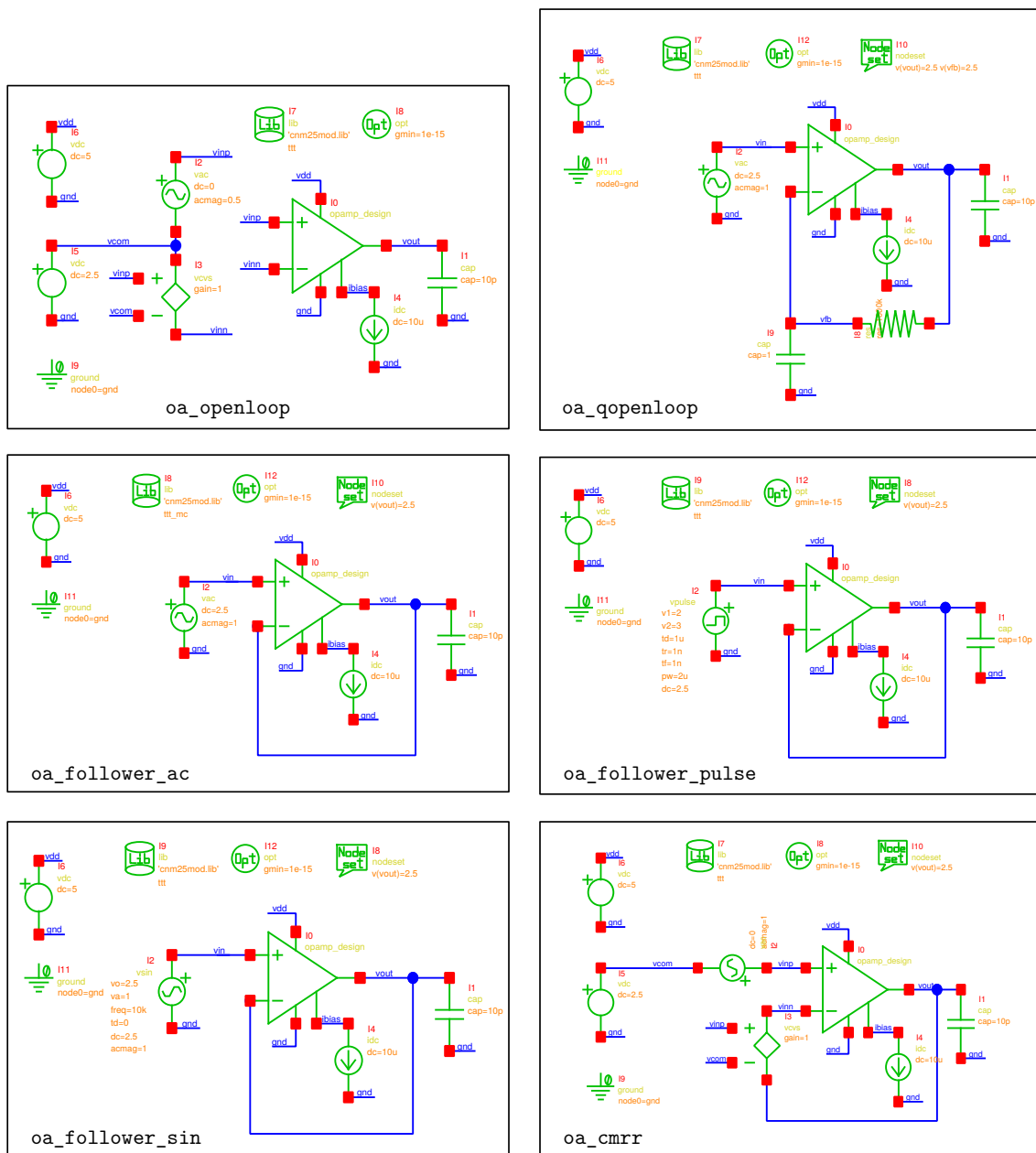


Figure 6 | Test-bench schematics available in ExampleLib for the characterization of the opamp_design circuit of Fig. 5.

When exported to CDL from Glade editor, each of these test schematics incorporates the netlist at transistor level of the CMOS OpAmp as a subcircuit thanks to the own design hierarchy, like in the example below.

```

----- oa_qopenloop.cir -----
*****
* Library : ExampleLib
* Top Cell Name: oa_qopenloop
* View Name: schematic
*****

*****
* Library Name: ExampleLib
* Cell Name:    opamp_design
* View Name:    schematic
*****
.SUBCKT opamp_design vinn vinp vout vdd vss ibias

    xI7 vdd ibias vcom vdd cnm25modp w=24u l=6u m=4
    xI3 vload vload vss vss cnm25modn w=24u l=6u m=1
    xI1 vcom vinn vload vdd cnm25modp w=32u l=6u m=6
    xI9 vout vinter cnm25cpoly w=100u l=100u m=2
    xI4 vinter vload vss vss cnm25modn w=24u l=6u m=1
    xI2 vcom vinn vinter vdd cnm25modp w=32u l=6u m=6
    xI8 vdd ibias ibias vdd cnm25modp w=24u l=6u m=1
    xI5 vdd ibias vout vdd cnm25modp w=24u l=6u m=16
    xI6 vout vinter vss vss cnm25modn w=48u l=6u m=10

.ENDS

vI6 vdd gnd dc=5
xI0 vfb vin vout vdd gnd ibias opamp_design
cI1 vout gnd c=10p
vI11 gnd 0 0
iI4 ibias gnd dc=10u
rI8 vfb vout r=1000k
vI2 vin gnd dc=2.5 acmag=1
cI9 vfb gnd c=1

.lib 'cnm25mod.lib' ttt
.options gmin=1e-15
.nodeset v(vout)=2.5 v(vfb)=2.5

.END

```

It is important to note here that each test bench is self contained in the sense that already includes all the necessary information for its simulation. Hence, apart from the circuit under test (i.e. the OpAmp itself) and its boundary conditions (e.g. load impedance, bias current and supply voltage), these test benches also incorporate: process and matching selection for CNM25 models (.lib), convergence aids (.nodeset), initial conditions (.ic) or simulation options (.options).

Regarding the CNM25 primitive devices (i.e. N/P-type MOS devices and PiP capacitors), they are netlisted as SPICE subcircuits (x-suffix) to allow the combined modeling of process and matching technology deviations following the device model structure presented in Section 3.2.

4.2 Electrical Simulation

In general, the analog behavior of your OpAmp can be accurately described by the parameters of Table 3, which includes from large to small signal performance and also from static to dynamic response.

	Static	Dynamic
Large Signal	Range: Differential input (I_R) Common mode input (CMR_{\pm}) Output (OR) Equivalent input offset (V_{off}) Quiescent power (P_D)	Slew rate (SR_{\pm}) Settling time (t_s) Maximum frequency (f_{max}) Harmonic distortion (THD)
Small Signal	Open loop differential gain (G_{DC}) Common mode rejection ($CMRR_{DC}$) Power supply rejection ($PSRR_{DC\pm}$)	Bandwidth (BW) $G_{DC} \times BW$ product (GBW) Phase margin (ϕ_m) Impedance ($Z_{in,out}$) Equivalent input noise (V_{neq})

Table 3 | OpAmp main performance parameters.

For our purposes, these figures of merit will be specified by the datasheet of Table 4. In the case of Silicon area, its final value is somehow difficult to predict before the full-custom design of its physical layout. Hence, only the sum of device areas will be taken into account based on (2), where ΔW_{cont} and ΔL_{cont} stand for the minimum depth to open a contact window according to the CNM25 design rules of Table 2.

Following the methodology of Fig. 1, the EDA tool selected for all the electrical simulations is SpiceOpus, an interactive electrical simulator based on SPICE3 [5]. Concerning netlist hierarchy, the strategy of Fig. 8 is adopted in all SpiceOpus simulations of this lab PDK. Basically, self-contained test circuits (*.cir) are generated from Glade schematics with the required CNM25 device models (cnm25*.mod). Test scripts written in NUTMEG (*.sp3) are launched simply by invoking their name from the SpiceOpus shell following Fig. 8. In practice, a single test script may manage more than one test circuit. Moreover, multiple simulation analysis can be executed on multiple circuit topologies and results can be combined all together in order to perform automated measurements and produce graphics for documentation.


Based on the test circuits of Fig. 6, a complete set of SPICE3 test scripts are also supplied for the numerical extraction of all the OpAmp parameters of Table 4:

- test_oa_vtc.sp3: differential-mode input range.
- test_oa_cmrr.sp3: CMRR transfer function.
- test_oa_cmr.sp3: common-mode input range.
- test_oa_psrr.sp3: PSRR transfer function.
- test_oa_offset.sp3: equivalent input offset.
- test_oa_sr.sp3: slew rate.
- test_oa_pd.sp3: quiescent power consumption.
- test_oa_noise.sp3: equivalent input noise.
- test_oa_bode.sp3: Bode transfer function.
- test_oa_thd.sp3: harmonic distortion.

Parameter	Comments	Min.	Typ.	Max.	Units
IR					mV _{pp}
CMR	Upper Lower				V
OR					V _{pp}
V _{off}	$\pm\sigma$				mV _{rms}
P _D	V _{in} = 2.5 V				mW
G _{DC}					dB
CMRR _{DC}					dB
PSRR _{DC}	+ −				dB
SR	+ −				V/ μ s
t _s (1%)	V _{out} = 2 V → 3 V V _{out} = 3 V → 2 V				ns
f _{max}	V _{out} = OR				kHz
THD	V _{out} = OR/2 @10kHz				%
BW	−3 dB				Hz
GBW					MHz
ϕ_m					deg
V _{nieq}	1 Hz to 10 MHz				μ V _{rms}
Area	According to (2)				mm ²

V_{DD} = +5 V, V_{SS} = 0 V, I_{bias} = 10 μ A and C_{load} = 10 pF.

Table 4 | OpAmp datasheet and test conditions.

 

$$\text{Area} \doteq \sum_j^{\text{devices}} (W_j + 2\Delta W_{cont})(L_j + 2\Delta L_{cont})M_j \quad (2)$$

Figure 7 | Rule of thumb to estimate device area for the datasheet of Table 4.

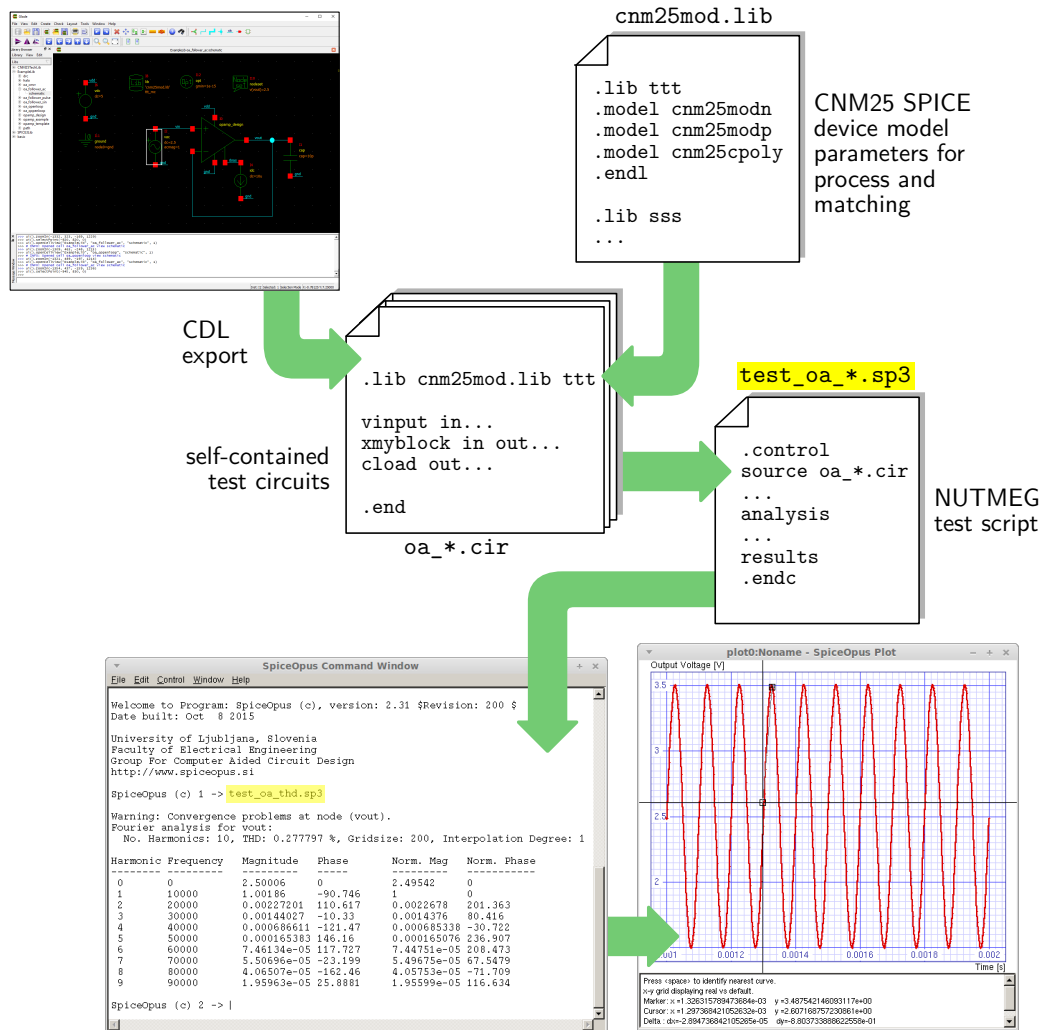


Figure 8 | SpiceOpus netlist hierarchy used in this PDK.

damics-kit/spiceopus/test_oa_vtc.sp3

```
test_oa_vtc.sp3
* Differential mode input range
.control
delcirc all
destroy all
delete all
save all
source oa_openloop.cir
dc vi2 -2.5 2.5 5m
let vdin=v(vinp)-v(vinn)
let vout=v(vout)
plot vout vs vdin xlabel 'Diff. Input Voltage...'
dc vi2 -2.5m 2.5m 5u
let vdin=v(vinp)-v(vinn)
let vout=v(vout)
plot vout vs vdin xlabel 'Diff. Input Voltage...'
.endc
.end
```

damics-kit/spiceopus/test_oa_cmr.sp3

```
test_oa_cmr.sp3
* Common mode input range
.control
delcirc all
destroy all
delete all
save all
source oa_follower_ac.cir
dc vi2 0 5 5m
let vin=v(vin)
let vout=v(vout)
plot vin vout xlabel 'Input Voltage [V]'...
.endc
.end
```



```

damics-kit/spiceopus/test_oa_offset.sp3
test_oa_offset.sp3
* Offset voltage
.control
delcirc all
destroy all
delete all
setplot new
nameplot mc
let voff=0
repeat 1000
    source oa_follower_ac.cir
    save v(vin) v(vout)
    op
    let mc.voff=(mc.voff;v(vin)-v(vout))
    echo run #{length(mc.voff)}
           {round(1e5*(v(vin)-v(vout)))/100} mV
    destroy op1
    delcirc all
end
* Gaussian fitting
let voff=voff[1,length(voff)-1]
let mn=mean(voff)*1e3
let std=sqrt(mean((voff-mean(voff))^2))*1e3
echo
echo Voffset = {round(100*mn)/100} mV
              +/- {round(100*std)/100} mV
echo
* Histogram (25-bin)
let dbin=(max(voff)-min(voff))/25
let ybin=vector(25)
let xbin=vector(25)
let counter=0
while counter le 24
    let voffleft=min(voff)+{counter}*dbin
    let voffright=voffleft+dbin
    let xbin[{counter}]=voffleft
    let ybin[{counter}]=sum((voff ge voffleft)
                           and (voff lt voffright))
    let counter=counter+1
endwhile
set plottype=comb
set linewidth=10
plot ybin vs xbin*1e3 xlabel 'Input Offset [mV]'
                        ylabel 'Samples []'
                        title 'Montecarlo mismatching'

set plottype=line
set linewidth=1
.endc
.end

```

```

damics-kit/spiceopus/test_oa_pd.sp3
test_oa_pd.sp3
* Quiescent power
.control
delcirc all
destroy all
delete all
save all
source oa_follower_ac.cir

```

```

op
let iddq=-i(vi6)
let pd=iddq*v(vdd)*1e6
echo Quiescent power consumption = {round(pd)}uW
.endc
.end

```

```

damics-kit/spiceopus/test_oa_bode.sp3
test_oa_bode.sp3
* Bode plot
.control
delcirc all
destroy all
delete all
save all
set units=degrees
source oa_qopenloop.cir
ac dec 50 1 1e7
let Gmag=20*log10(mag(v(vout)))
let Gph=phase(v(vout))
plot Gmag Gph xlog xlabel 'Frequency [Hz]'...
.endc
.end

```

```

damics-kit/spiceopus/test_oa_cmrr.sp3
test_oa_cmrr.sp3
* Common mode rejection ratio
.control
delcirc all
destroy all
delete all
save all
source oa_cmrr.cir
ac dec 50 1 1e7
let CMRR=-20*log10(mag(v(vout)))
plot CMRR xlog xlabel 'Frequency [Hz]'
                        ylabel 'CMRR [dB]'
.endc
.end

```

```

damics-kit/spiceopus/test_oa_psrr.sp3
test_oa_psrr.sp3
* Power supply rejection ratio
.control
delcirc all
destroy all
delete all
save all
source oa_follower_sin.cir
let @vi2[acmag]=0
let @vi6[acmag]=1
ac dec 50 1 1e7
let PSRRP=-20*log10(mag(v(vout)))
plot PSRRP xlog xlabel 'Frequency [Hz]'
                        ylabel 'PSRR+ [dB]'
.endc
.end

```

```
damics-kit/spiceopus/test_oa_sr.sp3
test_oa_sr.sp3
* Slew-rate +/-
.control
delcirc all
destroy all
delete all
save all
source oa_follower_pulse.cir
tran 1n 5u
let vout=v(vout)
plot vout xlabel 'Time [s]'
        ylabel 'Output Voltage [V]'
.endc
.end
```

```
damics-kit/spiceopus/test_oa_noise.sp3
test_oa_noise.sp3
* Spectral noise analysis
.control
delcirc all
destroy all
delete all
save all
source oa_follower_sin.cir
op
noise v(vout) vi2 dec 100 1 10meg
plot sqrt(noise1.onoise_spectrum)
```

```
vs noise1.frequency ylog
        xlabel 'Frequency [Hz]'
ylabel 'Equivalent Input Noise [Vrms/sqrt(Hz)]'
let vnin=sqrt(noise2.onoise_total)*1e6
echo
echo Equivalent input noise (1Hz to 10MHz) =
        {round(vnin)}uVrms
echo
.endc
.end
```

```
damics-kit/spiceopus/test_oa_thd.sp3
test_oa_thd.sp3
* Harmonic distortion analysis
.control
delcirc all
destroy all
delete all
save all
source oa_follower_sin.cir
tran 1u 2m 1m 1u
let vout=v(vout)
plot vout xlabel 'Time [s]'
        ylabel 'Output Voltage [V]'
fourier 10k vout
.endc
.end
```

Q1. For the initial OpAmp dimensions of Fig. 3, **fill the datasheet** of Table 4:

- Launch damics-kit/spiceopus/spiceopus.bat (or .sh).
- Call all test scripts by invoking their names, e.g. test_oa_vtc.sp3.
- Measure **typ.** results from graphs and shell messages.
- Repeat for process corners (sss,fff) to measure **min.** and **max.** results.

Q2. Answer the following **questions**:

- test_oa_offset.sp3: What are the meaning of the offset voltage results? Compare with test_oa_vtc.sp3.
- test_oa_bode.sp3: Why openloop.cir and qopenloop.cir show different results? Which one is correct?
- test_oa_cmrr.sp3: How is the CMRR calculated?

4.3 Circuit Optimization

The main objective of this part is to apply the OpAmp design equations seen in class sessions [4] for the optimization of a particular parameter of the datasheet, while keeping a minimum performance for the rest of them. This design process consists on changing the OpAmp initial device sizing of Fig. 3 without altering its internal circuit topology.

In particular, the optimization of your OpAmp is arranged into two steps:

Initial solution. The starting point is obtained from the results of Section 4.2. Hence, simulation results from Table 4 need to be copied into the **Initial** column of Table 5.

Optimization. A single parameter must be chosen for your OpAmp circuit optimization, while maintaining the rest of parameters within the specification range defined by the **Spec.** column. During optimization, each MOSFET and capacitor of the OpAmp is resized to enhance the selected parameter but checking for the side effects on the rest of them. After finishing this optimization process, performance results will be displayed in the **Optim.** column of Table 5.

Parameter	Comments	Spec.	Initial	Optim.	Units
IR					mV _{pp}
CMR	Upper Lower	>4 <1			V
OR		>3			V _{pp}
V _{off}	$\pm\sigma$	<10			mV _{rms}
P _D	V _{in} = 2.5 V	<1.5			mW
G _{DC}		>60			dB
CMRR _{DC}		>50			dB
PSRR _{DC}	+ –	>50 >50			dB
SR	+ –	>1.5 >1.5			V/ μ s
t _s (1%)	V _{out} = 2 V → 3 V V _{out} = 3 V → 2 V	<1500 <1500			ns
f _{max}	V _{out} = OR				kHz
THD	V _{out} = OR/2 @10kHz	<1			%
BW	–3dB				Hz
GBW		>1			MHz
ϕ_m		>50			deg
V _{nieq}	100 Hz to 10 MHz	<1			mV _{rms}
Area	According to (2)	<0.025			mm ²

$$V_{DD} = +5 \text{ V}, V_{SS} = 0 \text{ V}, I_{bias} = 10 \mu\text{A} \text{ and } C_{load} = 10 \text{ pF}.$$

Table 5 | OpAmp optimization datasheet and test conditions.

Q3. Perform your OpAmp optimization as follows:

- **Ask the professor** before choosing the optimization parameter!
Possible choices are: G_{DC} , GBW or SR_{\pm} .
- When optimizing your circuit, the size of **all devices** of Fig. 3 may be changed, including the PiP compensation capacitor.
- For each iteration of the optimization process, it is advised to carefully check the following **key parameters**: G_{DC} , GBW, SR_{\pm} , ϕ_m , Area and P_D .
- Students are encouraged to develop their **own test script** (e.g. test_oa_datasheet.sp3) in order to extract these 6 parameters automatically. For such a purpose, some useful SPICE3 NUTMEG code examples are given below. Further information can be found in [5].
- Even more important than the final value of the optimized parameter, the comprehensive explanation of the OpAmp **optimization strategy** is of major importance, as well as the analysis of the second order effects limiting the optimization process!
- **Report** must include the detailed optimization planning, device dimensions of the new OpAmp circuit, filled datasheet of Table 5 and all related plots.

————— Miscellaneous SPICE3 recipes —————

* Working with multiple circuits

```
source file1.cir
source file2.cir
setcirc ckt1
```

* Interacting with netlists

```
let w1=@mi1:xi0[w]
let @mi2:xi0[w]=w1
```

* Working with multiple analysis

```
ac dec 50 1 10meg
let GdB=20*log10(mag(v(vout)))
setcirc ckt2
ac dec 50 1 10meg
let GdB=20*log10(mag(v(vout)))
plot ac1.GdB ac2.GdB xlog xlabel 'Frequency...'
setplot ac1
```

* Automatic measurements

```
let GdBDC=G[0]
cursor c right GdB 0
let GBW=abs(frequency[%c])/1e6
```

* Reporting results

```
echo G(DC)={round(GdBDC)}dB
echo GBW={round(GBW*10)/10}MHz
```

* Cleaning memory

```
destroy ac2
delcirc ckt2
```

* Parametric analysis

```
foreach wpar 10u 20u 30u
  let @mi6:xi0[w]={wpar}
  ac dec 50 1 10meg
  let GdBDC=20*log10(mag(v(vout)[0]))
  let ac1.GdBDC=(ac1.GdBDC;GdBDC)
end
let mydata=ac1.GdBDC
```

* Exporting results

```
set nobreak
set noprinthead
set noprint index
set width=132
print mydata > fileout.txt
```

————— Miscellaneous SPICE3 recipes —————

4.4 PCell-Based Netlist-Driven Layout Design

Once the optimal device sizing of your OpAmp schematic has been obtained, the physical CMOS design of the IC can start according to the methodology of Fig. 1. Unlike in full-custom digital circuits, where compactness and speed are the major design targets, the main goals in analog IC design are both signal integrity and device matching. For the former, signal decoupling is improved by introducing ground guards, avoiding cross-coupling and using differential signaling when routing. As for device matching, the symmetry rules of Table 6 are strongly recommended.

Layout Rule	Bad	Good
Unitary Elements		
Large Area		
Same Orientation		
Minimum Distance		
Same Surround		
Same Symmetry		

Table 6 | Analog layout style guide for best device matching [6].

Glade is the EDA tool selected in the design methodology of Fig. 1 for the full-custom edition and physical verification of IC mask layouts. This layout editor includes advanced geometrical operations (e.g. stretching, chopping, merging), full and partial object selection, multi hierarchical design browsing, lots of display options, as well as the effective management of technological layers following Fig. 9. Due to the intensive mouse usage when in interactive mode, most commands can be invoked through the corresponding bindkeys predefined in Edit→Edit Bindkeys.

One particularly useful tool of Glade is the design rule driven (DRD) edition. As illustrated in the canvas of Fig. 9, this operation mode displays the design rules on the fly, during object edition. To prevent from a negative impact on the editor speed performance, the DRD mode can be configured to check rules between the object being edited and the rest of elements belonging to the same layer only.

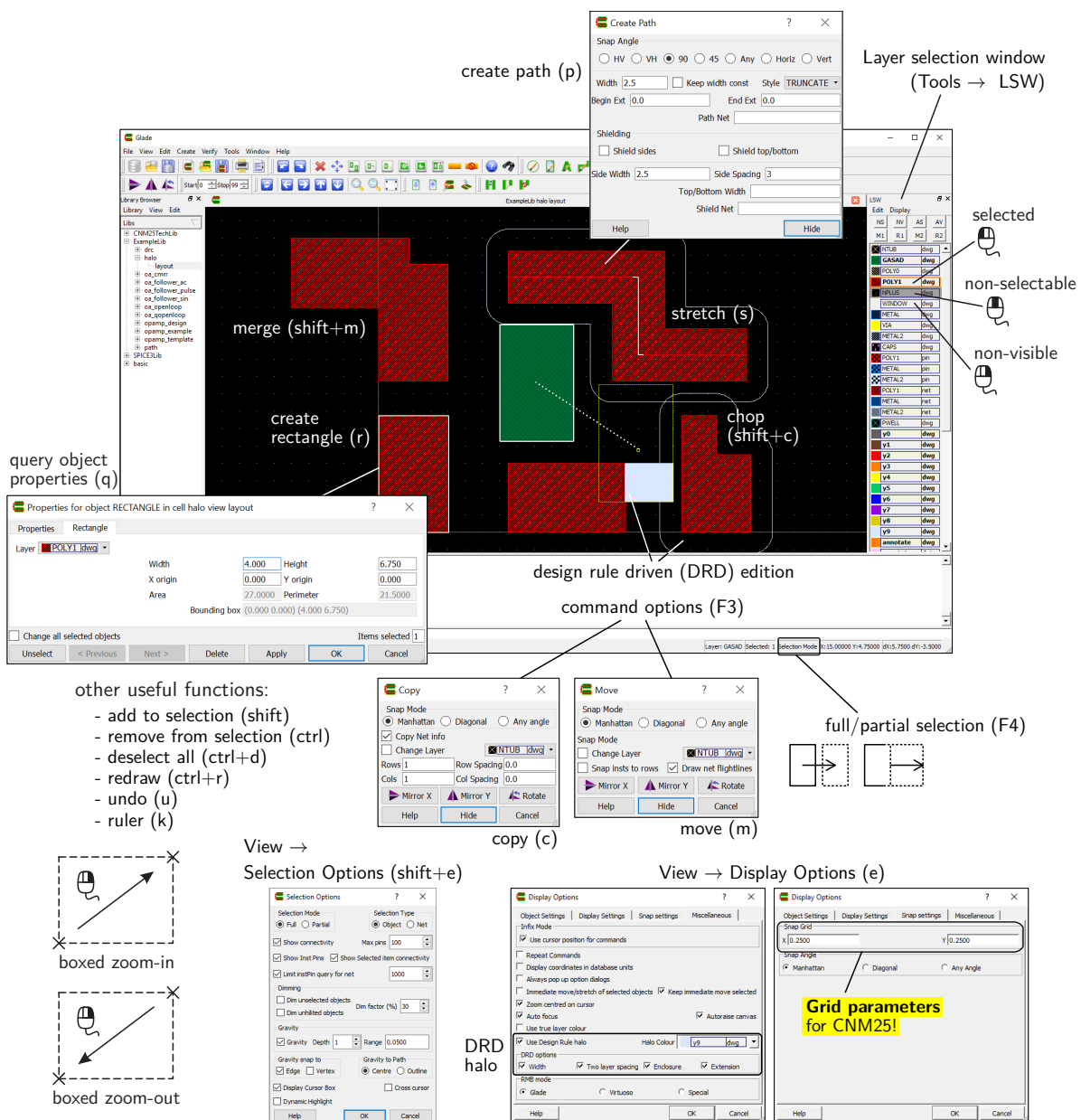


Figure 9 | Glade layout editor main window and associated tools.

Glade takes most of the CMOS process information from the technology file, like: layer table, layer connectivity, basic design rules, contact rules, periodic structures, among others. For this purpose, the CNM25 PDK comes with the technology file `damics-kit/glade/cnm25.tch`, which is already compiled inside the lab design library `damics-kit/glade/ExampleLib`.

```

1 //
2 //
3 //      Name      Purpose gds_num gds_dtyp RGBA      sel? vis? fillstyle linestyle
4 LAYER  NTUB      drawing  1      0      (255,230,191,255) t    t    cross    plain ;
5 LAYER  GASAD     drawing  2      0      (0,204,102,255)  t    t    dots1    plain ;
6 LAYER  POLY0     drawing  3      0      (255,230,191,255) t    t    zagr     plain ;
7 LAYER  POLY1     drawing  4      0      (255,0,0,255)    t    t    right_bars plain ;
8 LAYER  NPLUS     drawing  5      0      (255,230,191,255) t    t    points_1 plain ;
9 LAYER  WINDOW    drawing  6      0      (0,255,255,255)  t    t    full     plain ;
10 LAYER  METAL     drawing  7      0      (0,128,255,255)  t    t    zagr     plain ;
11 LAYER  VIA       drawing 10      0      (255,255,0,255)  t    t    solid    plain ;
12 LAYER  METAL2    drawing  9      0      (204,230,255,255) t    t    zagl     plain ;
13 LAYER  CAPS      drawing  8      0      (255,170,255,255) t    t    crosses  plain ;
14 LAYER  POLY1     pin      20      0      (255,0,0,255)    t    t    squares_1 plain ;
15 LAYER  METAL     pin      21      0      (0,128,255,255)  t    t    squares_2 plain ;
16 LAYER  METAL2    pin      22      0      (204,230,255,255) t    t    squares_2 plain ;
17 LAYER  POLY1     net      23      0      (255,0,0,255)    t    t    dots1    plain ;
18 LAYER  METAL     net      24      0      (0,128,255,255)  t    t    dots1    plain ;
19 LAYER  METAL2    net      25      0      (204,230,255,255) t    t    dots1    plain ;
20 LAYER  PWELL     drawing  26      0      (73,214,186,255) t    t    cross    plain ;
21 //
22 // Layer function
23 //
24 FUNCTION POLY0 drawing ROUTING ;
25 FUNCTION POLY1 drawing ROUTING ;
26 FUNCTION WINDOW drawing CUT ;
27 FUNCTION METAL drawing ROUTING ;
28 FUNCTION VIA drawing CUT ;
29 FUNCTION METAL2 drawing ROUTING ;
30 FUNCTION POLY1 pin PIN ;
31 FUNCTION METAL pin PIN ;
32 FUNCTION METAL2 pin PIN ;
33 FUNCTION POLY1 net PIN ;
34 FUNCTION METAL net PIN ;
35 FUNCTION METAL2 net PIN ;
36 //
37 // Layer Connections
38 //
39 CONNECT POLY0 drawing BY WINDOW drawing TO METAL drawing ;
40 CONNECT POLY1 drawing BY WINDOW drawing TO METAL drawing ;
41 CONNECT METAL drawing BY VIA drawing TO METAL2 drawing ;
42 //
43 // Layout rules
44 //
45 MINWIDTH NTUB drawing 8.000 ;
46 MINSPACE NTUB drawing 8.000 ;
47 MINWIDTH GASAD drawing 2.000 ;
48 MINSPACE GASAD drawing 4.000 ;
49 MINENC NTUB drawing GASAD drawing 5.000 ;
50 MINSPACE NTUB drawing GASAD drawing 5.000 ;
51 MINWIDTH POLY0 drawing 2.500 ;
52 MINSPACE POLY0 drawing 6.000 ;
53 MINSPACE POLY0 drawing GASAD drawing 6.000 ;
54 MINWIDTH POLY1 drawing 2.500 ;

```

```

54 | MINSIZE POLY1 drawing 3.000 ;
55 | MINEXT POLY1 drawing GASAD drawing 2.500 ;
56 | MINEXT GASAD drawing POLY1 drawing 3.000 ;
57 | MINSIZE POLY1 drawing GASAD drawing 1.250 ;
58 | MINENC POLY0 drawing POLY1 drawing 3.000 ;
59 | MINENC NPLUS drawing GASAD drawing 2.500 ;
60 | MINWIDTH NPLUS drawing 2.500 ;
61 | MINSIZE NPLUS drawing 2.500 ;
62 | MINWIDTH WINDOW drawing 2.500 ;
63 | MINSIZE WINDOW drawing 3.000 ;
64 | MINENC GASAD drawing WINDOW drawing 1.000 ;
65 | MINENC POLY1 drawing WINDOW drawing 1.250 ;
66 | MINENC POLY0 drawing WINDOW drawing 4.000 ;
67 | MINSIZE WINDOW drawing POLY1 drawing 4.000 ;
68 | MINSIZE WINDOW drawing POLY0 drawing 4.000 ;
69 | MINWIDTH METAL drawing 2.500 ;
70 | MINSIZE METAL drawing 3.000 ;
71 | MINENC METAL drawing WINDOW drawing 1.250 ;
72 | MINWIDTH VIA drawing 3.000 ;
73 | MINSIZE VIA drawing 3.500 ;
74 | MINENC METAL drawing VIA drawing 1.250 ;
75 | MINSIZE VIA drawing WINDOW drawing 2.500 ;
76 | MINSIZE VIA drawing POLY1 drawing 2.500 ;
77 | MINWIDTH METAL2 drawing 3.500 ;
78 | MINSIZE METAL2 drawing 3.500 ;
79 | MINENC METAL2 drawing VIA drawing 1.250 ;
80 | //
81 | // Via rules
82 | //
83 | VIA dff_m1
84 |     GASAD drawing -2.250 -2.250 2.250 2.250
85 |     WINDOW drawing -1.250 -1.250 1.250 1.250
86 |     METAL drawing -2.500 -2.500 2.500 2.500
87 | ;
88 | VIA p0_m1
89 |     POLY0 drawing -5.250 -5.250 5.250 5.250
90 |     WINDOW drawing -1.250 -1.250 1.250 1.250
91 |     METAL drawing -2.500 -2.500 2.500 2.500
92 | ;
93 | VIA p1_m1
94 |     POLY1 drawing -2.500 -2.500 2.500 2.500
95 |     WINDOW drawing -1.250 -1.250 1.250 1.250
96 |     METAL drawing -2.500 -2.500 2.500 2.500
97 | ;
98 | VIA m1_m2
99 |     METAL drawing -2.750 -2.750 2.750 2.750
100 |     VIA drawing -1.500 -1.500 1.500 1.500
101 |     METAL2 drawing -2.750 -2.750 2.750 2.750
102 | ;
103 | //
104 | // MultiPartPath rules
105 | //
106 | MPP nguard LAYER NTUB drawing WIDTH 14.5 BEGEXT 7.25 ENDEXT 7.25 ;
107 | MPP nguard LAYER GASAD drawing WIDTH 4.5 BEGEXT 2.25 ENDEXT 2.25 ;
108 | MPP nguard LAYER NPLUS drawing WIDTH 9.5 BEGEXT 4.75 ENDEXT 4.75 ;
109 | MPP nguard LAYER WINDOW drawing WIDTH 2.5 BEGEXT -1.25 ENDEXT 1.25 SPACE 3 LENGTH 2.5 ;
110 | MPP nguard LAYER METAL drawing WIDTH 5.0 BEGEXT 2.5 ENDEXT 2.5 ;
111 |
112 | MPP pguard LAYER GASAD drawing WIDTH 4.5 BEGEXT 2.25 ENDEXT 2.25 ;
113 | MPP pguard LAYER WINDOW drawing WIDTH 2.5 BEGEXT -1.25 ENDEXT 1.25 SPACE 3 LENGTH 2.5 ;

```



```

114 MPP pguard LAYER METAL drawing WIDTH 5.0 BEGEXT 2.5 ENDEXT 2.5 ;
115
116 MPP p0m1 LAYER POLY0 drawing WIDTH 10.5 BEGEXT 5.25 ENDEXT 5.25 ;
117 MPP p0m1 LAYER WINDOW drawing WIDTH 2.5 BEGEXT -1.25 ENDEXT 1.25 SPACE 3 LENGTH 2.5 ;
118 MPP p0m1 LAYER METAL drawing WIDTH 5.0 BEGEXT 2.5 ENDEXT 2.5 ;
119
120 MPP p1m1 LAYER POLY1 drawing WIDTH 5 BEGEXT 2.50 ENDEXT 2.50 ;
121 MPP p1m1 LAYER WINDOW drawing WIDTH 2.5 BEGEXT -1.25 ENDEXT 1.25 SPACE 3 LENGTH 2.5 ;
122 MPP p1m1 LAYER METAL drawing WIDTH 5.0 BEGEXT 2.5 ENDEXT 2.5 ;
123
124 MPP m1m2 LAYER METAL drawing WIDTH 5.5 BEGEXT 2.75 ENDEXT 2.75 ;
125 MPP m1m2 LAYER VIA drawing WIDTH 3 BEGEXT -1.5 ENDEXT 1.5 SPACE 3.5 LENGTH 3 ;
126 MPP m1m2 LAYER METAL2 drawing WIDTH 5.5 BEGEXT 2.75 ENDEXT 2.75 ;
127 //
128 // Fastcap conductor data in um
129 //
130 METLYR METAL drawing HEIGHT 1.000 THICKNESS 1.000 ;
131 VIALYR VIA drawing HEIGHT 2.000 THICKNESS 0.800 ;
132 METLYR METAL2 drawing HEIGHT 2.800 THICKNESS 1.100 ;
133 //
134 // Layout generation tool
135 //
136 MAP cnm25modn T0 cnm25modn_m layout ;
137 MAP cnm25modp T0 cnm25modp_m layout ;
138 MAP cnm25cpoly T0 cnm25cpoly_m layout ;
139 //
140 // Line Styles...
141 // Stipple Patterns
142 STIPPLE rightBars STIPPLE
143 1 1 0 0 1 1 0 0 1 1 0 0 1 1 0 0
144 1 0 0 1 1 0 0 1 1 0 0 1 1 0 0 1
145 0 0 1 1 0 0 1 1 0 0 1 1 0 0 1 1
146 0 1 1 0 0 1 1 0 0 1 1 0 0 1 1 0
147 1 1 0 0 1 1 0 0 1 1 0 0 1 1 0 0
148 1 0 0 1 1 0 0 1 1 0 0 1 1 0 0 1
149 0 0 1 1 0 0 1 1 0 0 1 1 0 0 1 1
150 0 1 1 0 0 1 1 0 0 1 1 0 0 1 1 0
151 1 1 0 0 1 1 0 0 1 1 0 0 1 1 0 0
152 1 0 0 1 1 0 0 1 1 0 0 1 1 0 0 1
153 0 0 1 1 0 0 1 1 0 0 1 1 0 0 1 1
154 0 1 1 0 0 1 1 0 0 1 1 0 0 1 1 0
155 1 1 0 0 1 1 0 0 1 1 0 0 1 1 0 0
156 1 0 0 1 1 0 0 1 1 0 0 1 1 0 0 1
157 0 0 1 1 0 0 1 1 0 0 1 1 0 0 1 1
158 0 1 1 0 0 1 1 0 0 1 1 0 0 1 1 0
159 ;
160 STIPPLE squares_2 STIPPLE
161 1 1 1 1 0 0 0 0 1 1 1 1 0 0 0 0
162 1 1 1 1 0 0 0 0 1 1 1 1 0 0 0 0
163 1 1 1 1 0 0 0 0 1 1 1 1 0 0 0 0
164 1 1 1 1 0 0 0 0 1 1 1 1 0 0 0 0
165 0 0 0 0 1 1 1 1 0 0 0 0 1 1 1 1
166 0 0 0 0 1 1 1 1 0 0 0 0 1 1 1 1
167 0 0 0 0 1 1 1 1 0 0 0 0 1 1 1 1
168 0 0 0 0 1 1 1 1 0 0 0 0 1 1 1 1
169 1 1 1 1 0 0 0 0 1 1 1 1 0 0 0 0
170 1 1 1 1 0 0 0 0 1 1 1 1 0 0 0 0
171 1 1 1 1 0 0 0 0 1 1 1 1 0 0 0 0
172 ...

```

damics-kit/glade/cnm25.tch

In order to speed up the full-custom edition of the IC layout, this PDK supports the use of a parameterized cell (PCell) for each native CNM25 device. A PCell is a geometrical element, in between plain full-custom primitives (e.g. rectangle, irregular polygon, path) and semi-custom cells (e.g. logic gates), which is automatically generated according to variable sizing parameters. In the case of CNM25, layout PCells are available in CNM25TechLib for NMOS transistors (`cnm25modn_m`), PMOS transistors (`cnm25modp_m`) and PiP capacitors (`cnm25cpoly_m`), as shown in Fig. 10. In Glade, PCells can be programmed for each CMOS technology using Python language, like the code example shown below.

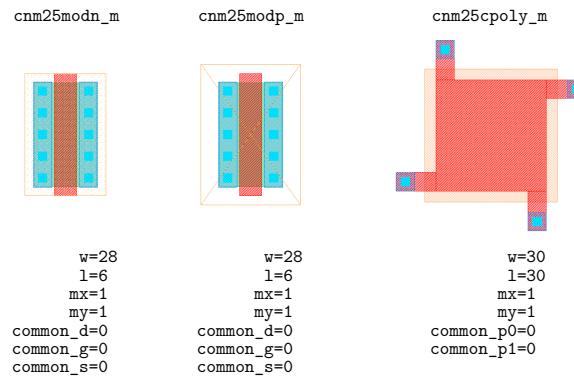


Figure 10 | Glade layout PCells available in the CNM25 PDK and sizing parameters. PCell devices can be called through Create→Instance (i).

```

1  from ui import *
2  def cnm25modn_m(cv, w=4.5e-6, l=3.0e-6, mx=1, my=1, common_d=0, common_g=0, common_s=0) :
3      lib = cv.lib()
4      tech = lib.tech()
5      dbu = lib.dbuPerUU()
6      width = abs(int(w * 1.0e6 * dbu))
7      length = abs(int(l * 1.0e6 * dbu))
8      xelem = abs(int(mx))
9      yelem = abs(int(my))
10     commd = bool(common_d)
11     commg = bool(common_g)
12     comms = bool(common_s)
13     # Layer rules
14     xygrid = int(0.25 * dbu)
15     gasad_width = int(2.00 * dbu)
16     gasad_space = int(4.00 * dbu)
17     ntub_ov_gasad = int(5.00 * dbu)
18     nplus_ov_gasad = int(2.50 * dbu)
19     poly_width = int(3.0 * dbu)
20     poly_space = int(3.0 * dbu)
21     poly_space_gasad = int(1.25 * dbu)
22     poly_ext_gasad = int(2.5 * dbu)
23     cont_size = int(2.50 * dbu)
24     cont_space = int(3.00 * dbu)
25     cont_space_poly = int(2.00 * dbu)
26     gasad_ov_cont = int(1.00 * dbu)
27     poly_ov_cont = int(1.25 * dbu)
28     metal_width = int(2.50 * dbu)
29     metal_space = int(3.00 * dbu)
30     metal_ov_cont = int(1.25 * dbu)
31     # Device rules
32     min_length = poly_width
33     min_width = max(gasad_width, cont_size + 2*gasad_ov_cont)

```

```

34 min_xelem = 1
35 min_yelem = 1
36 # Checking parameters
37 if length%xygrid!=0 :
38     length = int(xygrid * int(length / xygrid))
39     cv.dbReplaceProp("l", 1e-6 * (length / dbu))
40     print "** cnm25modn WARNING: l is off-grid. Adjusting element length. **"
41     cv.update()
42 if width%xygrid!=0 :
43     width = int(xygrid * int(width / xygrid))
44     cv.dbReplaceProp("w", 1e-6 * (width / dbu))
45     print "** cnm25modn WARNING: w is off-grid. Adjusting element width. **"
46     cv.update()
47 if length < min_length :
48     length = min_length
49     cv.dbReplaceProp("l", 1e-6 * (length / dbu))
50     print "** cnm25modn WARNING: l < minimum length. Resetting element length. **"
51     cv.update()
52 if width < min_width :
53     width = min_width
54     cv.dbReplaceProp("w", 1e-6 * (width / dbu))
55     print "** cnm25modn WARNING: w < minimum width. Resetting element width. **"
56     cv.update()
57 if xelem < min_xelem :
58     xelem = min_xelem
59     cv.dbReplaceProp("mx", xelem)
60     print "** cnm25modn WARNING: mx == 0. Resetting number of horizontal elements to ",
61                                     xelem, ". **"
62     cv.update()
63 if yelem < min_yelem :
64     yelem = min_yelem
65     cv.dbReplaceProp("my", yelem)
66     print "** cnm25modn WARNING: my == 0. Resetting number of vertical elements to ",
67                                     yelem, ". **"
68 # Calculate XY incremental offsets
69 dxoffset_min = length + 2*cont_space_poly + cont_size
70 dxoffset_extra = cont_size + 2*gasad_ov_cont + max(gasad_space,
71             (metal_ov_cont-gasad_ov_cont) + metal_space)
72 dxoffset_alt = [ dxoffset_min + (not commd) * dxoffset_extra, dxoffset_min +
73             (not comms) * dxoffset_extra]
74 dyoffset = width + max(gasad_space, (not commg) * (2*poly_ext_gasad + poly_space),
75             ((not commd) or (not comms)) * (2*(metal_ov_cont-gasad_ov_cont) + metal_space))
76 # 2D element array iteration
77 xoffset = 0
78 for x in range(xelem) :
79     yoffset = 0
80     for y in range(yelem) :
81         # Create active
82         layer = tech.getLayerNum("GASAD", "drawing")
83         r = Rect(-(cont_space_poly + cont_size + gasad_ov_cont), 0, length +
84             cont_space_poly + cont_size + gasad_ov_cont, width)
85         r.offset(xoffset, yoffset)
86         active = cv.dbCreateRect(r, layer)
87         # Create gate
88         layer = tech.getLayerNum("POLY1", "drawing")
89         poly_ext_one_side = max(poly_ext_gasad, commg * max(gasad_space/2, ((not commd) or
90             (not comms)) * ((metal_ov_cont-gasad_ov_cont) + metal_space/2)))
91         r = Rect(0, -poly_ext_one_side, length, width + poly_ext_one_side)
92         r.offset(xoffset, yoffset)
93         poly = cv.dbCreateRect(r, layer)

```

```

94     gate_net = cv.dbCreateNet("G")
95     pin = cv.dbCreatePin("G", gate_net, DB_PIN_INPUT)
96     cv.dbCreatePort(pin, poly)
97     # Create drain and source contacts
98     layer = tech.getLayerNum("WINDOW", "drawing")
99     n_cont = int((width - 2*gasad_ov_cont + cont_space) / (cont_size + cont_space))
100    s_cont = 0
101    if (n_cont > 1) :
102        s_cont = cont_space
103    for n in range(n_cont) :
104        r = Rect(-cont_space_poly - cont_size, gasad_ov_cont + n *
105                (cont_size + s_cont), -cont_space_poly, gasad_ov_cont +
106                cont_size + n * (cont_size + s_cont))
107        r.offset(xoffset, yoffset)
108        contact = cv.dbCreateRect(r, layer)
109        r = Rect(length + cont_space_poly, gasad_ov_cont + n * (cont_size +
110                s_cont), length + cont_space_poly + cont_size, gasad_ov_cont +
111                cont_size + n * (cont_size + s_cont))
112        r.offset(xoffset, yoffset)
113        contact = cv.dbCreateRect(r, layer)
114    # Create drain and source metal
115    layer = tech.getLayerNum("METAL", "drawing")
116    metal_ext_one_side = max(metal_ov_cont - gasad_ov_cont, (((x%2!=0) and commd)
117                            or ((x%2==0) and (comms)))) * (dyoffset - width)/2)
118    r = Rect(-(cont_space_poly + cont_size + metal_ov_cont), -metal_ext_one_side,
119            -cont_space_poly + metal_ov_cont, width + metal_ext_one_side)
120    r.offset(xoffset, yoffset)
121    metal = cv.dbCreateRect(r, layer)
122    source_net = cv.dbCreateNet("S")
123    pin = cv.dbCreatePin("S", source_net, DB_PIN_INOUT)
124    cv.dbCreatePort(pin, metal)
125    metal_ext_one_side = max(metal_ov_cont - gasad_ov_cont, (((x%2==0) and
126                            (commd)) or ((x%2!=0) and (comms)))) * (dyoffset - width)/2)
127    r = Rect(length + cont_space_poly - metal_ov_cont, -metal_ext_one_side, length
128            + cont_space_poly + cont_size + metal_ov_cont, width + metal_ext_one_side)
129    r.offset(xoffset, yoffset)
130    metal = cv.dbCreateRect(r, layer)
131    drain_net = cv.dbCreateNet("D")
132    pin = cv.dbCreatePin("D", drain_net, DB_PIN_INOUT)
133    cv.dbCreatePort(pin, metal)
134    yoffset = yoffset + dyoffset
135    xoffset = xoffset + dxoffset_alt[x%2!=0]
136    # Create n-plus
137    layer = tech.getLayerNum("NPLUS", "drawing")
138    nplus_x_ext = cont_space_poly + cont_size + gasad_ov_cont + nplus_ov_gasad
139    r = Rect(-nplus_x_ext, -nplus_ov_gasad, length + nplus_x_ext + xoffset - dxoffset_alt[x%2!=0],
140            width + nplus_ov_gasad + yoffset - dyoffset)
141    nplus = cv.dbCreateRect(r, layer)
142    # Create p-well
143    layer = tech.getLayerNum("backgnd", "drawing")
144    ntub_x_ext = cont_space_poly + cont_size + gasad_ov_cont + ntub_ov_gasad
145    r = Rect(-ntub_x_ext, -ntub_ov_gasad, length + ntub_x_ext + xoffset - dxoffset_alt[x%2!=0],
146            width + ntub_ov_gasad + yoffset - dyoffset)
147    ptub = cv.dbCreateRect(r, layer)
148    bulk_net = cv.dbCreateNet("B")
149    pin = cv.dbCreatePin("B", bulk_net, DB_PIN_INOUT)
150    cv.dbCreatePort(pin, ptub)
151    # Save results
152    cv.update()

```

damics-kit/glade/pcells/cnm25modn_m.py

Examples of usage for CNM25 PCells can be found in Figs. 11 and 12. As a positive side effect, PCell-based layouts are less prone to introduce violations since they have been already programmed taking into account the process design rules of Table 2.

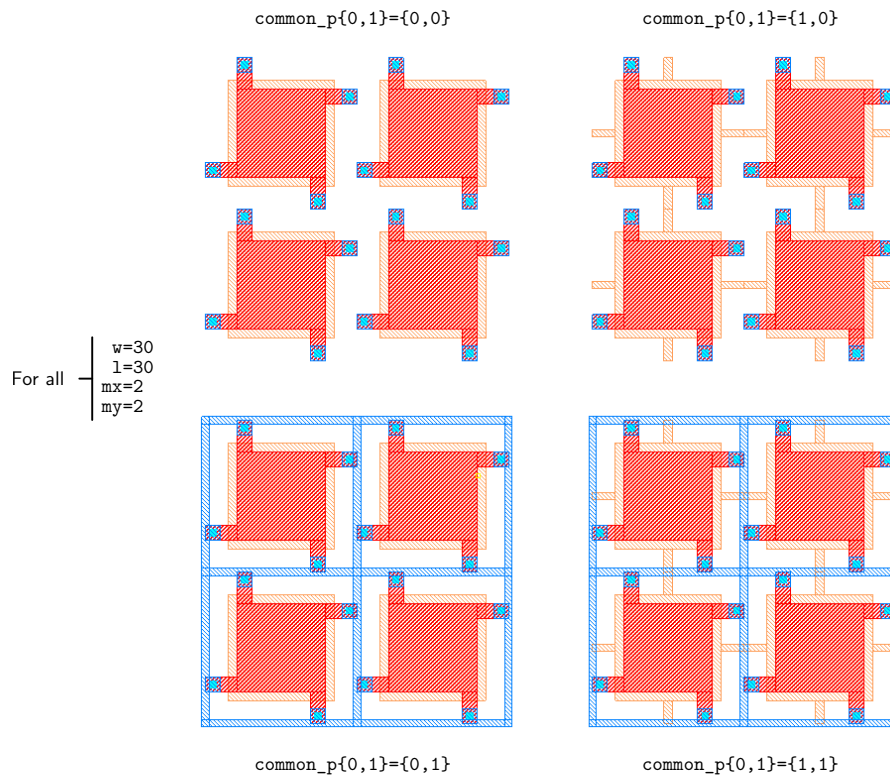


Figure 11 | Example of automatic PiP capacitor generation using CNM25 PCell `cnm25cpoly_m`. Parameters for this PCell are: element width (w) and length (l), number of vertical (mx) and horizontal (my) elements, and conditional options for common bottom (`common_p0`) and/or top (`common_p1`) plates.

Concerning the connection of the above PCell devices inside your layout, Manhattan-style paths are of major help. Glade uses the physical layer connectivity defined in the technology file to switch from the current to the upper or downer routing layer through automatic contact or via generation. The CNM25 available layers for routing are POLY1, METAL and METAL2, as illustrated in Fig. 13.

Finally, the Glade MultiPartPath (MPP) command allows the automated generation of periodic linear structures, which are extremely useful to adapt guard rings and contact linear arrays around devices. Examples of the CNM25 MPPs are shown in Fig. 14, where `nguard` and `pguard` stand for N-type and P-type guard rings, while `p0m1`, `p1m1` and `m1m2` are intended for contact linear arrays between METAL and POLY0, POLY1 and METAL2, respectively. All these layout elements are fully tunable after creation, as their periodic structure is automatically regenerated when stretched.

For further assistance with the design of the full-custom layout of your IC, Glade also features the schematic-driven layout generation tool of Fig. 15. First, this tool allows to manage matching groups at schematic level through device property group. Such management includes the definition of device array dimensions and distribution of unitary elements for better matching (e.g. common centroid). Second, the same tool automatically places all the required PCells in the layout and highlights their terminal connectivity according to the schematic information. However, it is designer responsibility to arrange such arrays and to route their interconnections for best device matching and signal decoupling, respectively.

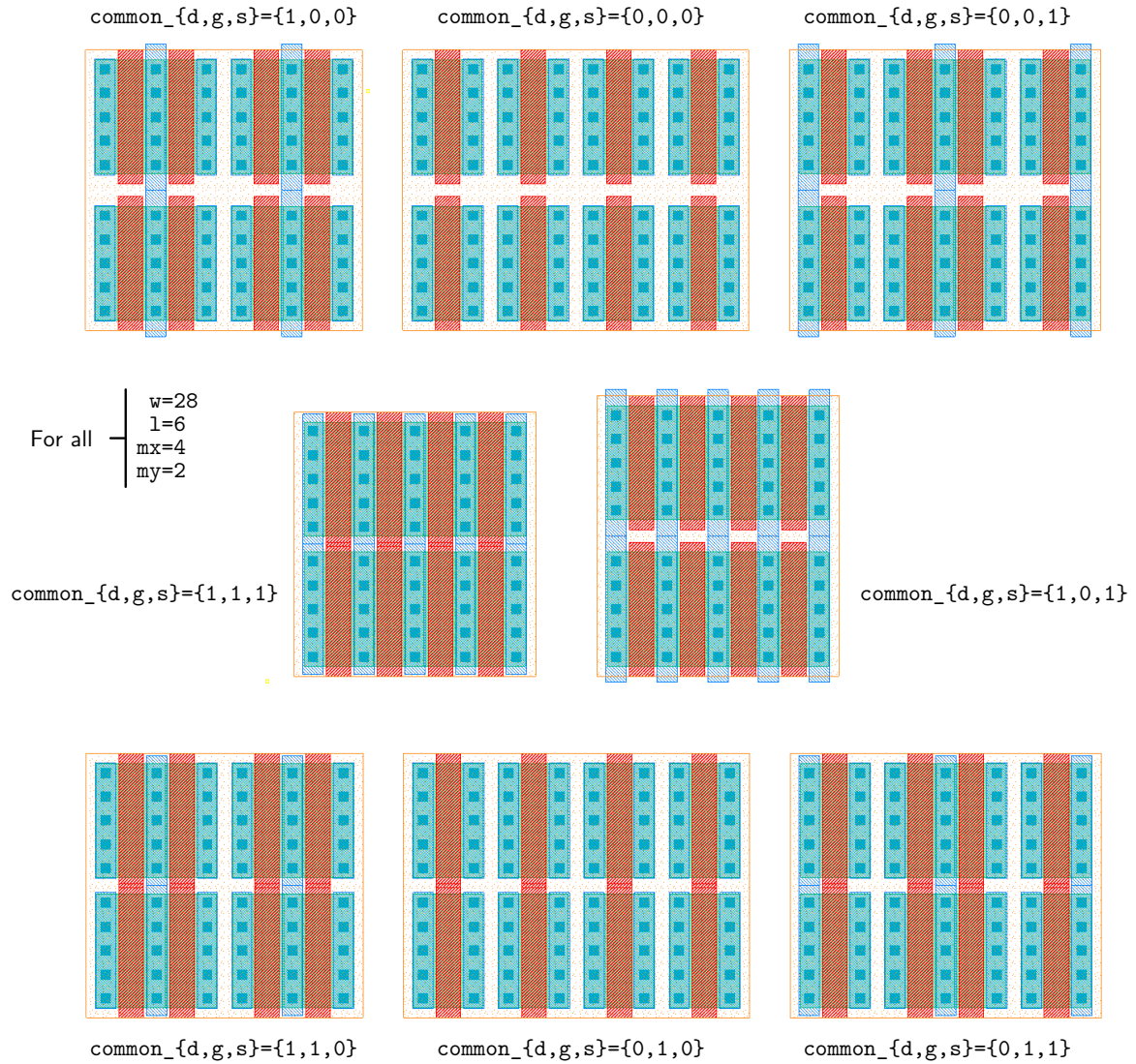


Figure 12 | Example of automatic NMOS device generation using CNM25 PCell `cnm25modn_m`. Parameters for this PCell are: element width (w) and length (l), vertical (mx) and horizontal (my) multiplicity, and conditional options for common drain (`common_d`), gate (`common_g`), and/or source (`common_s`).


 


Figure 13 | Example of Glade Create→Path (p) command usage for CNM25 routing.

 

p0m1 = POLY0-WINDOW-METAL
m1m2 = METAL-VIA-METAL2
pguard = GASAD-WINDOW-METAL (P-bulk guard ring)
p1m1 = POLY1-WINDOW-METAL
nguard = NTUB-GASAD-NPLUS-WINDOW-METAL (N-bulk guard ring)

 


Figure 14 | CNM25 automatic and stretchable MPP structures available through the Glade Create→MultiPartPath command.

 


Figure 15 | Usage of Glade layout generation tool for managing matching groups (a) and for automated PCell placement (b).

- ✎ Update device dimensions of Glade ExampleLib→opamp_design→schematic according to the **optimized** device sizes obtained in Section 4.3!
- ✎ Use the Glade layout generation tool of Fig. 15 to generate all PCell devices of your OpAmp in ExampleLib→opamp_design→layout.
- ✎ Check grid and snap parameters are set to **X=0.25** and **Y=0.25**, as in Fig. 9.

Q4. Complete the **full-custom layout** of your optimized OpAmp:

- Exploit the advantage of **paths** and **MPPs** as in Figs. 13 and 14.
- Follow the matching design **guidelines** of Table 6.
- Ensure layout compatibility with the cell **template** of Fig. 16.

 


Figure 16 | Glade cell view ExampleLib→opamp_template→layout to be used for the design boundaries of your OpAmp layout. Standard-cell height is $200\mu\text{m}$.

 


Figure 17 | Glade cell view ExampleLib→opamp_example→layout to illustrate the use of the cell template of Fig. 16 and the matching guidelines of Table 6. Overall cell width is $226\mu\text{m}$.

4.5 Design Rule Checker

Once the geometrical edition of your full-custom IC layout is completed, the first physical verification step in the methodology of Fig. 1 is the design rule checker (DRC). The main purpose of this stage is to verify the fabrication feasibility of your CMOS circuit in CNM25 from the geometrical viewpoint only (e.g. adequate spacing, width, overlap, extension, enclosure and area of the mask patterning).

In this sense, this PDK is already shipped with `damics-kit/glade/verification/cnm25drc.py`, a Python script which includes the main design rules of Table 2. Also, a sample layout with typical CNM25 structures is supplied in `ExampleLib→drc→layout` for DRC training, as shown in Fig. 18.

```

damics-kit/glade/verification/cnm25drc.py
1  # CNM25 2M DRC deck
2  def printErrors(msg) :
3      n = geomGetCount()
4      if n > 0 :
5          print n, msg
6
7  # Initialise DRC package
8  from ui import *
9  cv = ui().getEditCellView()
10 drcInit(cv)
11
12 # Get raw layers
13 nwell      = geomGetShapes("NTUB", "drawing")
14 active     = geomGetShapes("GASAD", "drawing")
15 polygate   = geomGetShapes("POLY1", "drawing")
16 polycap    = geomGetShapes("POLY0", "drawing")
17 nimp       = geomGetShapes("NPLUS", "drawing")
18 cont       = geomGetShapes("WINDOW", "drawing")
19 metal1     = geomGetShapes("METAL", "drawing")
20 via12      = geomGetShapes("VIA", "drawing")
21 metal2     = geomGetShapes("METAL2", "drawing")
22 pad        = geomGetShapes("CAPS", "drawing")
23
24 # Form derived layers
25 gate       = geomAnd(polygate, active)
26 ngate      = geomAnd(gate, nimp)
27 pgate      = geomAndNot(gate, ngate)
28 cpoly      = geomAnd(polygate, polycap)
29 polygatecont = geomAnd(polygate, cont)
30 polycapcont = geomAnd(polycap, cont)
31 activecont = geomAnd(active, cont)
32 allcon     = geomOr(geomOr(polygatecont, polycapcont), activecont)
33 badcon     = geomAndNot(allcon, metal1)
34 metal1via  = geomAnd(metal1, via12)
35 badvia     = geomAndNot(metal1via, metal2)
36 diff       = geomAndNot(active, gate)
37 ndiff      = geomAnd(diff, nimp)
38 pdiff      = geomAndNot(diff, nimp)
39 ntap       = geomAnd(ndiff, nwell)
40 ptap       = geomAndNot(pdiff, nwell)
41
42 # Form connectivity
43 geomConnect( [
44     [ntap, nwell, ndiff],
45     [cont, ndiff, metal1],
46     [cont, pdiff, metal1],

```

```

47         [cont, polygate, metal1],
48         [cont, polycap, metal1],
49         [via12, metal1, metal2]
50     ] )
51
52 # Start design rule checking
53
54 print "0.0. Checking off-grid..."
55 geomOffGrid(nwell, 0.25, 1, "0.0. Design grid is 0.25um x 0.25um")
56 geomOffGrid(active, 0.25, 1, "0.0. Design grid is 0.25um x 0.25um")
57 geomOffGrid(polygate, 0.25, 1, "0.0. Design grid is 0.25um x 0.25um")
58 geomOffGrid(polycap, 0.25, 1, "0.0. Design grid is 0.25um x 0.25um")
59 geomOffGrid(nimp, 0.25, 1, "0.0. Design grid is 0.25um x 0.25um")
60 geomOffGrid(cont, 0.25, 1, "0.0. Design grid is 0.25um x 0.25um")
61 geomOffGrid(metal1, 0.25, 1, "0.0. Design grid is 0.25um x 0.25um")
62 geomOffGrid(via12, 0.25, 1, "0.0. Design grid is 0.25um x 0.25um")
63 geomOffGrid(metal2, 0.25, 1, "0.0. Design grid is 0.25um x 0.25um")
64 geomOffGrid(pad, 0.25, 1, "0.0. Design grid is 0.25um x 0.25um")
65
66 print "1.X. Checking N-well..."
67 geomWidth(nwell, 8, "1.1. N-well width >= 8um")
68 geomSpacing(nwell, 8, samenet, "1.2. N-well spacing (same net) >= 8um")
69 geomSpacing(nwell, 8, diffnet, "1.2. N-well spacing (different net) >= 8um")
70 geomNotch(nwell, 8, "1.2. N-well notch >= 8um")
71
72 print "2.X. Checking GASAD..."
73 geomWidth(active, 2, "2.1. GASAD width >= 2um")
74 geomSpacing(active, 4, samenet, "2.2. GASAD spacing (same net) >= 4um")
75 geomSpacing(active, 4, diffnet, "2.2. GASAD spacing (different net) >= 4um")
76 geomNotch(active, 4, "2.2. GASAD notch >= 4um")
77 geomEnclose(nwell, pdiff, 5, "2.3. N-well enclosure of P-plus active >= 5um")
78 geomSpacing(nwell, ndiff, 5, samenet, "2.4. N-well spacing to N-plus active (same net) >= 5um")
79 geomSpacing(nwell, ndiff, 5, diffnet, "2.4. N-well spacing to N-plus active (different net) >= 5um")
80
81 print "3.X. Checking Poly0..."
82 geomWidth(polycap, 2.5, "3.1. Poly0 width >= 2.5um")
83 geomSpacing(polycap, 6, samenet, "3.2. Poly0 spacing (same net) >= 6um")
84 geomSpacing(polycap, 6, diffnet, "3.2. Poly0 spacing (different net) >= 6um")
85 geomNotch(polycap, 6, "3.2. Poly0 notch >= 6um")
86 geomSpacing(polycap, active, 6, samenet, "3.3. Poly0 spacing to GASAD (same net) >= 6um")
87 geomSpacing(polycap, active, 6, diffnet, "3.3. Poly0 spacing to GASAD (different net) >= 6um")
88
89 print "4.X. Checking Poly1..."
90 geomWidth(gate, 3, "4.1.a. Poly1 width inside GASAD >= 3um")
91 geomWidth(geomAndNot(polygate, gate), 2.5, "4.1.b. Poly1 width outside GASAD >= 2.5um")
92 geomSpacing(polygate, 3, samenet, "4.2. Poly1 spacing (same net) >= 3um")
93 geomSpacing(polygate, 3, diffnet, "4.2. Poly1 spacing (different net) >= 3um")
94 geomNotch(polygate, 3, "4.2. Poly1 notch >= 3um")
95 geomExtension(active, polygate, 3, "4.3. GASAD extension of Poly1 >= 3um")
96 geomExtension(polygate, active, 2.5, "4.4. Poly1 extension of GASAD >= 2.5um")
97 geomSpacing(polygate, active, 1.25, samenet, "4.5. Poly1 spacing to GASAD (same net) >= 1.25um")
98 geomSpacing(polygate, active, 1.25, diffnet, "4.5. Poly1 spacing to GASAD (different net) >= 1.25um")
99 geomEnclose(polycap, cpoly, 3, "4.6. Poly0 enclosure of Poly1 >= 3um")
100
101 print "5.X. Checking N-plus..."
102 geomEnclose(nimp, active, 2.5, "5.1. N-plus enclosure of GASAD >= 2.5um")
103 geomSpacing(nimp, pdiff, 2.5, samenet, "5.2. N-plus spacing to P-plus active (same net) >= 2.5um")
104 geomSpacing(nimp, pdiff, 2.5, diffnet, "5.2. N-plus spacing to P-plus active (different net) >= ...")
105 geomSpacing(nimp, pgate, 2, samenet, "5.3. N-plus spacing to Poly1 inside P-plus active (same ...")
106 geomSpacing(nimp, pgate, 2, diffnet, "5.3. N-plus spacing to Poly1 inside P-plus active (different ...")

```

```

107 geomExtension(nimp, ngate, 1.5, "5.4. N-plus extension of Poly1 inside N-plus active >= 1.5um")
108 geomWidth(nimp, 2.5, "5.5. N-plus width >= 2.5um")
109 geomSpace(nimp, 2.5, samenet, "5.6. N-plus spacing (same net) >= 2.5um")
110 geomSpace(nimp, 2.5, diffnet, "5.6. N-plus spacing (different net) >= 2.5um")
111 geomNotch(nimp, 2.5, "5.6. N-plus notch >= 2.5um")
112
113 print "6.X. Checking contact..."
114 saveDerived(badcon, "6.0. Contact requires Metal1")
115 geomArea(cont, 6.25, 6.25, "6.1. Exact contact size = 2.5um x 2.5um")
116 geomWidth(cont, 2.5, "6.1. Exact contact size = 2.5um x 2.5um")
117 geomSpace(cont, 3, samenet, "6.2. Contact spacing (same net) >= 3um")
118 geomSpace(cont, 3, diffnet, "6.2. Contact spacing (different net) >= 3um")
119 geomNotch(cont, 3, "6.2. Contact notch >= 3um")
120 geomEnclose(active, cont, 1, "6.3. GASAD enclosure of Contact >= 1um")
121 geomEnclose(polygate, cont, 1.25, "6.4. Poly1 enclosure of Contact >= 1.25um")
122 geomSpace(polygatecont, 2.5, samenet, "6.5. Poly1 Contact spacing to GASAD (same net) >= 2.5um")
123 geomSpace(polygatecont, 2.5, diffnet, "6.5. Poly1 Contact spacing to GASAD (different net) >= ..."
124 geomSpace(cont, gate, 2, samenet, "6.6. Contact spacing to Poly1 inside GASAD (same net) >= 2um")
125 geomSpace(cont, gate, 2, diffnet, "6.6. Contact spacing to Poly1 inside GASAD (different net) >= ..."
126 # 6.7 and 6.8 not implemented!
127 geomEnclose(polycap, cont, 4, "6.9. Poly0 enclosure of Contact >= 4um")
128 geomSpace(cont, cpoly, 4, diffnet, "6.10. Contact spacing to Poly1 & Poly0 (different net) >= 4um")
129
130 print "7.X. Checking Metal1..."
131 geomWidth(metal1, 2.5, "7.1. Metal1 width >= 2.5um")
132 geomSpace(metal1, 3, samenet, "7.2. Metal1 spacing (same net) >= 3um")
133 geomSpace(metal1, 3, diffnet, "7.2. Metal1 spacing (different net) >= 3um")
134 geomNotch(metal1, 3, "7.2. Metal1 notch >= 3um")
135 geomEnclose(metal1, cont, 1.25, "7.3. Metal1 enclosure of Contact >= 1.25um")
136
137 print "8.X. Checking Via..."
138 saveDerived(badvia, "8.0. Via requires Metal2")
139 geomArea(via12, 9, 9, "8.1. Exact via size = 3um x 3um")
140 geomWidth(via12, 3, "8.1. Exact via size = 3um x 3um")
141 geomSpace(via12, 3.5, samenet, "8.2. Via spacing (same net) >= 3.5um")
142 geomSpace(via12, 3.5, diffnet, "8.2. Via spacing (different net) >= 3.5um")
143 geomNotch(via12, 3.5, "8.2. Via notch >= 3.5um")
144 geomEnclose(metal1, via12, 1.25, "8.3. Metal1 enclosure of Via >= 1.25um")
145 geomSpace(via12, cont, 2.5, samenet, "8.4. Via spacing to contact (same net) >= 2.5um")
146 geomSpace(via12, cont, 2.5, diffnet, "8.4. Via spacing to contact (different net) >= 2.5um")
147 geomSpace(via12, polygate, 2.5, samenet, "8.5. Via spacing to Poly1 (same net) >= 2.5um")
148 geomSpace(via12, polygate, 2.5, diffnet, "8.5. Via spacing to Poly1 (different net) >= 2.5um")
149
150 print "9.X. Checking Metal2..."
151 geomWidth(metal2, 3.5, "9.1. Metal2 width >= 3.5um")
152 geomSpace(metal2, 3.5, samenet, "9.2. Metal2 spacing (same net) >= 3.5um")
153 geomSpace(metal2, 3.5, diffnet, "9.2. Metal2 spacing (different net) >= 3.5um")
154 geomNotch(metal2, 3.5, "9.2. Metal2 notch >= 3.5um")
155 geomEnclose(metal2, via12, 1.25, "9.3. Metal2 enclosure of Via >= 1.25um")
156
157 print "10.X. Checking Pad..."
158 geomArea(pad, 10000, 10000, "10.1. Exact passivation size = 100um x 100um")
159 geomWidth(pad, 100, "10.1. Exact passivation size = 100um x 100um")
160
161 num_err = geomGetTotalCount()
162 print "** Total error count = ", num_err
163
164 # Exit DRC package, freeing memory
165 drcUnInit()

```

damics-kit/glade/verification/cnm25drc.py


 


Figure 18 | Glade cell view ExampleLib→drc→layout includes examples of CNM25 layout structures with (top) and without (bottom) DRC errors.

Performing the full DRC verification of your OpAmp layout in Glade is as simple as following the procedure described below:

1. Open your ExampleLib→opamp_design→layout.
2. Execute Verify→DRC→Run (shift+I).
3. Select the rules file damics-kit/glade/verification/cnm25drc.py and launch the DRC process.
4. Open the DRC results browser through Verify→DRC→View Errors, or select a particular error marker and query for its properties (q), as shown in Fig. 19.
5. Correct all the reported errors according to the design rules of Table 2 and iterate above until the console window shows the following message: **** Total error count = 0.**

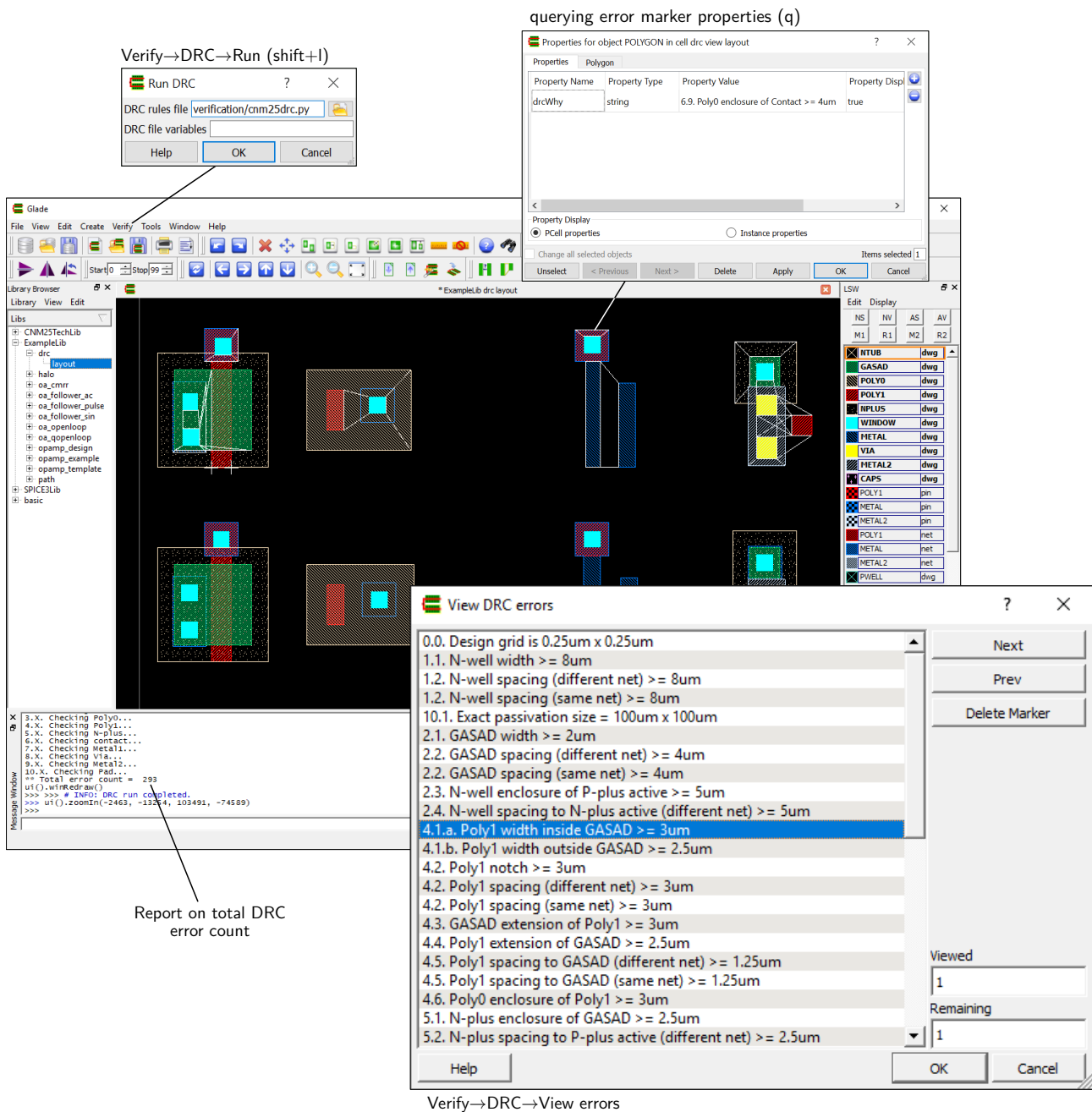Q5. Execute the above verification procedure in your optimized OpAmp, and correct any rule violation in order to obtain a **DRC error-free layout**. Which are the most common DRC errors of your design?



4.6 Circuit Extraction and Electrical Rule Checker

According to the full-custom design methodology of Fig. 1, the next physical verification step is the extraction of the equivalent electrical circuit from your DRC-compliant IC layout geometry. Previously, the following information about the circuit connectivity needs to be declared:

Pin annotation. In this step, the input/output (I/O) pins of the circuit cell are located in the layout. After executing the procedure listed below, the placed pins should look like in the OpAmp example of Fig. 20:

1. Select METAL2-pin layer from the layer selection window (LSW).
2. Create a text label with origin within the I/O pin location through Create→Create Label (t).
3. Enter the same pin name as in the OpAmp schematic of Fig. 5.
4. Iterate above for each I/O pin of the OpAmp (i.e. vinn, vinp, vout and ibias).
5. Repeat steps 1 to 4 for the supply pins (i.e. vdd and vss) but using METAL-pin layer.

Net annotation. This step is optional, since the internal nodes of the circuit are automatically named during the extraction process if no labels are present. Anyway, it is a good practice to specify the net names for all the internal circuit nodes in order to simplify the debugging of any connectivity error in Section 4.7. Again, Fig. 20 illustrates the following process:

1. Select the appropriate {POLY1,METAL,METAL2}-net layer from the LSW.
2. Create a text label with origin in the internal net area through Create→Create Label (t).
3. Enter the same net name as in the OpAmp schematic of Fig. 5.
4. Iterate above for each internal net of the OpAmp (i.e. vcomm, vinter and vload).

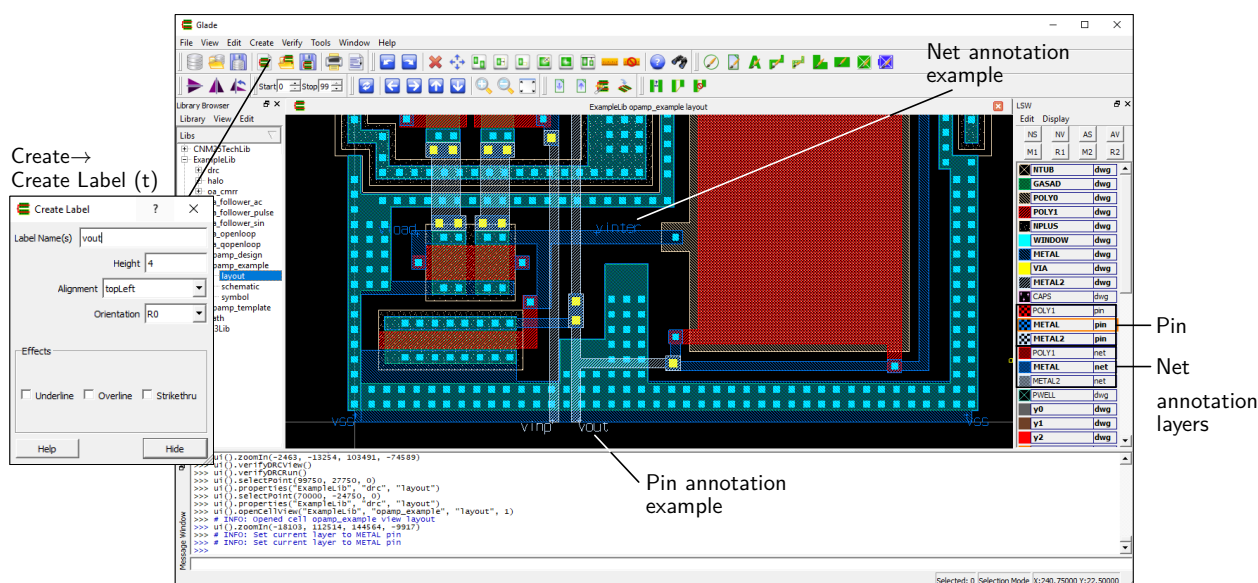


Figure 20 | Glade cell view `ExampleLib→opamp_example→layout` with pin and net annotation examples.

Once the electrical I/O connectivity information is annotated into the layout by the designer, the automated circuit extraction itself can start. In general, this process involves the following tasks:

- Identify the location of all instances of the technology native devices present in the layout.
- Extract the connectivity between these devices (and also between them and the I/O pins).
- For each identified device, call the corresponding extraction PCells to compute its sizing parameters.

As expected, the PDK comes with an specific Python code to cover such functionalities, which is called `damics-kit/glade/verification/cnm25xtr_lvs.py` and is shown below.

```

damics-kit/glade/verification/cnm25xtr_lvs.py
1
2  # CNM25 2M extraction deck
3  # Initialise boolean package
4  from ui import *
5  ui = cvar.uiiptr
6  cv = ui.getEditCellView()
7  geomBegin(cv)
8  libxtrlvs = cv.lib()
9
10 # Get raw layers
11 nwell      = geomGetShapes("NTUB", "drawing")
12 active     = geomGetShapes("GASAD", "drawing")
13 polygate   = geomGetShapes("POLY1", "drawing")
14 polycap    = geomGetShapes("POLY0", "drawing")
15 nimp       = geomGetShapes("NPLUS", "drawing")
16 cont       = geomGetShapes("WINDOW", "drawing")
17 metal1     = geomGetShapes("METAL", "drawing")
18 via12      = geomGetShapes("VIA", "drawing")
19 metal2     = geomGetShapes("METAL2", "drawing")
20
21 # Form derived layers
22 bkgnd      = geomBkgnd()
23 pwell      = geomAndNot(bkgnd, nwell)
24 gate       = geomAnd(polygate, active)
25 ngate      = geomAnd(gate, nimp)
26 pgate      = geomAndNot(gate, ngate)
27 cpoly      = geomAnd(polygate, polycap)
28 diff       = geomAndNot(active, gate)
29 ndiff      = geomAnd(diff, nimp)
30 pdiff      = geomAndNot(diff, nimp)
31 ntap       = geomAnd(ndiff, nwell)
32 ptap       = geomAnd(pdiff, pwell)
33
34 # Extract pin and net names before geomConnect
35 geomLabel(polygate, "POLY1", "pin", 1)
36 geomLabel(metal1, "METAL", "pin", 1)
37 geomLabel(metal2, "METAL2", "pin", 1)
38 geomLabel(polygate, "POLY1", "net", 0)
39 geomLabel(metal1, "METAL", "net", 0)
40 geomLabel(metal2, "METAL2", "net", 0)
41
42 # Form connectivity
43 geomConnect( [

```



```

44     [pwell, bkgnd, pwell],
45     [ptap, pwell, pdiff],
46     [ntap, nwell, ndiff],
47     [cont, ndiff, pdiff, polygate, polycap, metal1],
48     [via12, metal1, metal2]
49 ] )
50
51 # Save interconnect
52 saveInterconnect( [
53     [pwell, "PWELL"],
54     nwell,
55     [ptap, "GASAD"],
56     [ntap, "GASAD"],
57     [ndiff, "GASAD"],
58     [pdiff, "GASAD"],
59     polycap,
60     polygate,
61     cont,
62     metal1,
63     via12,
64     metal2,
65 ] )
66
67 # Extracting devices
68 if geomNumShapes(ngate) > 0 :
69     print "# Extract NMOS transistors"
70     extractMOS("cnm25modn", ngate, polygate, ndiff, pwell)
71
72 if geomNumShapes(pgate) > 0 :
73     print "# Extract PMOS transistors"
74     extractMOS("cnm25modp", pgate, polygate, pdiff, nwell)
75
76 if geomNumShapes(cpoly) > 0 :
77     print "# Extract PiP capacitors"
78     extractDevice("cnm25cpoly", cpoly, [[polygate, "T"], [polycap, "B"]])
79
80 print "# Ending circuit extraction"
81 geomEnd()
82
83 # Opening extracted view and reporting results
84 ui.openCellView(libxtrlvs.libName(), cv.cellName(), "extracted")
85 cv_ex = libxtrlvs.dbFindCellViewByName(cv.cellName(), "extracted")
86 box = cv_ex.bBox()
87 objs = cv_ex.dbGetOverlaps(box,0,1)
88 obj = objs.first()
89 num_dev=0
90 while obj :
91     if obj.isInst() :
92         num_dev=num_dev+1
93     obj = objs.next()
94 print "** Total device count = ", num_dev
95
damics-kit/glade/verification/cnm25xtr_lvs.py

```

During the execution of the above script (see code lines 68-78), the corresponding CNM25 extraction PCells are called for each identified device of Fig. 2. These Python PCells are in charge of extracting device sizing properties and annotating device terminal locations, like in the case of CNM25 PiP capacitors:

```

damics-kit/glade/pcells/cnm25cpoly.py
1  from ui import *
2  def cnm25cpoly(cv, ptlist=[[0,0],[30000,0],[30000,30000],[0,30000]]) :
3      lib = cv.lib()
4      dbu = float(lib.dbuPerUU())
5      npts = len(ptlist)
6
7      # Calculate total area an perimeter for arbitrary Manhattan shapes
8      asum = 0.0
9      perimeter = 0.0
10     i = npts-1
11     j = 0
12     while (j < npts) :
13         dx = float(ptlist[i][0]) / dbu
14         dy = float(ptlist[i][1]) / dbu
15         dx1 = float(ptlist[j][0]) / dbu
16         dy1 = float(ptlist[j][1]) / dbu
17         # compute perimeter
18         perimeter = perimeter + ((dx1 - dx) * (dx1 - dx) + (dy1 - dy) * (dy1 - dy))**0.5
19         # compute area
20         asum = asum + (dx + dx1) * (dy1 - dy)
21
22         # increment vertex
23         i = j
24         j = j + 1
25     area = asum / 2.0
26
27     # Derive rectangular w and l properties:
28     # area = w*l
29     # perimeter = 2*(w+l)
30     a = 1.0
31     b = -perimeter / 2.0
32     c = area
33     l = float((-b+(b**2-4*a*c)**0.5)/(2*a))
34     w = float(area/l)
35
36     # Update the master pcell property
37     cv.dbAddProp("w", w*1e-6)
38     cv.dbAddProp("l", l*1e-6)
39
40     # Create the recognition region shape
41     xpts = intarray(npts)
42     ypts = intarray(npts)
43     for i in range (npts) :
44         xpts[i] = ptlist[i][0]
45         ypts[i] = ptlist[i][1]
46     cv.dbCreatePolygon(xpts, ypts, npts, TECH_YO_LAYER);
47
48     # Create pins
49     top_net = cv.dbCreateNet("T")
50     cv.dbCreatePin("T", top_net, DB_PIN_INPUT)
51     bot_net = cv.dbCreateNet("B")
52     cv.dbCreatePin("B", bot_net, DB_PIN_INPUT)
53
54     # Setting device type to capacitor

```

```

55 cv.dbAddProp("type", "cap")
56
57 # Set the device modelName property for netlisting
58 cv.dbAddProp("modelName", "cnm25cpoly")
59
60 # Set the NLP property for netlisting
61 cv.dbAddProp("NLPDeviceFormat", "c[@instName] [|T:%] [|B:%] [@modelName] [@w:w=:%:w=30u]
62                                     [|l:l=:%:l=30u] [@m:m=:%:m=1] ")
63 cv.dbAddProp("NLPDeviceFormatCDL", "x[@instName] [|T:%] [|B:%] [@modelName] [@w:w=:%:w=30u]
64                                     [|l:l=:%:l=30u] [@m:m=:%:m=1] ")
65
66 # Update the bounding box
67 cv.update()

```

damics-kit/glade/pcells/cnm25cpoly.py

As a result of the extraction process, Glade creates the extracted view of your cell layout and reports any short-circuit between labeled nets in the message window. However, the above extraction script does not identify other types of electrical errors (e.g. open circuits). For such a purpose, the net browser of Fig. 21 can be used as an interactive electrical rule checker (ERC), since it highlights the physical location of a given net, including multi-layer nets. Also, the list of device terminals attached to a particular circuit net can be easily explored through the query function. In consequence, the ERC steps are as follows:

1. Open your ExampleLib→opamp_design→layout.
2. Execute Verify→Extract→Run (shift+y).
3. Select the script damics-kit/glade/verification/cnm25xtr_lvs.py and launch the extraction process.
4. Inspect for any noticeable ERC error, as depicted in Fig. 21.
5. If present, correct ERC errors in the layout and iterate Section 4.5 and 4.6.

Q6. Execute the above verification procedure in your optimized OpAmp layout to obtain an **ERC error-free extracted view**. Did you find any connectivity error?

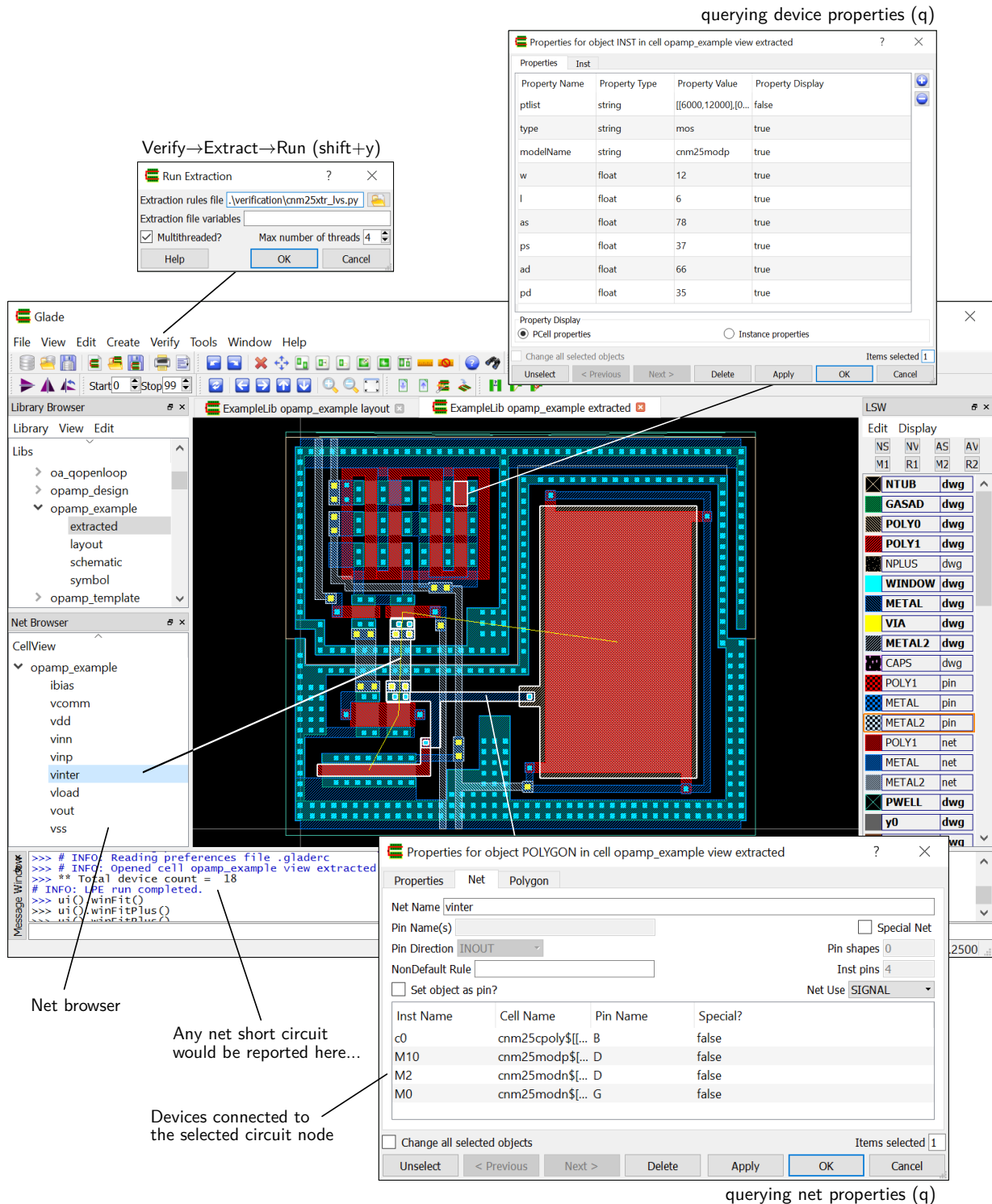


Figure 21 | Glade ERC inspection for ExampleLib→opamp_example→extracted.

4.7 Layout Versus Schematic

Passing the DRC and ERC validation steps ensures your circuit layout is both compliant with the geometrical rules of the CMOS technology and it is free of basic interconnection errors. However, these properties are useless if the resulting layout is not exactly equivalent to your optimized circuit schematic. For this reason, the design methodology of Fig. 1 also incorporates the layout versus schematic (LVS) verification step.

The basic idea behind the LVS checking is to take two circuit netlists, one obtained from the layout circuit extraction of Section 4.6 and the other one from the simulated schematic, and compare their topologies to identify element-by-element correspondences at pin, net and device levels. As a result of this comparison, open and short circuits, missing devices, device properties mismatching and pin mismatching errors can be identified in the layout. In general, LVS involves the solution of graph isomorphism problems, but taking benefit of the reduction and permutation properties of the specific devices, like in the example of Fig. 22.

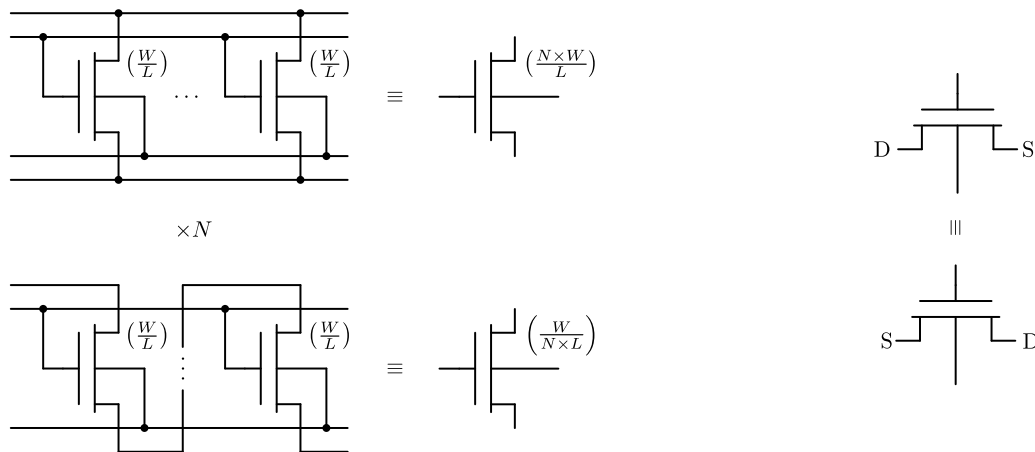


Figure 22 | Typical reduction (left) and permutation (right) LVS rules for the case of MOS transistors.

In our context, Glade relies on the venerable tool Gemini¹ [7] for the LVS verification. First, Glade generates the SPICE netlist of both the target schematic and the extracted layout, and then it calls Gemini to perform the comparison process between both netlists. The LVS verification results returned by Gemini are finally reported in the Glade message window, while both net and device errors are directly highlighted through geometrical markers in the extracted view.

In practice, the implementation of the analog layout guidelines proposed in Table 6 involve the introduction of some dummy elements inside the device matching arrays of your circuit layout to improve geometrical symmetry. These extra devices will be extracted by Glade, thus they need to be added in the schematic view as well.

¹More information can be found at <https://www.cs.washington.edu/node/2177>.

Based on the above explanation, the complete steps to perform the LVS verification process are as follows:

1. Add the equivalent **dummy devices** of your layout to ExampleLib→opamp_design→schematic!
2. Open your ExampleLib→opamp_design→extracted view.
3. Execute Verify→LVS→Run (shift+I).
4. Configure Gemini according to Fig. 23 and run the LVS process.
5. Once completed, review the results in the message window and in the extracted view.

 


Figure 23 Gemini configuration for the LVS verification of your ExampleLib→opamp_design→extracted view.

For illustration purposes, the PDK comes with the schematic of Fig. 24, which is the equivalent circuit of the OpAmp layout example used in the previous section and presented in Fig. 17. In this case, one PMOS dummy device needs to be added to match the physical transistor array of current mirrors.

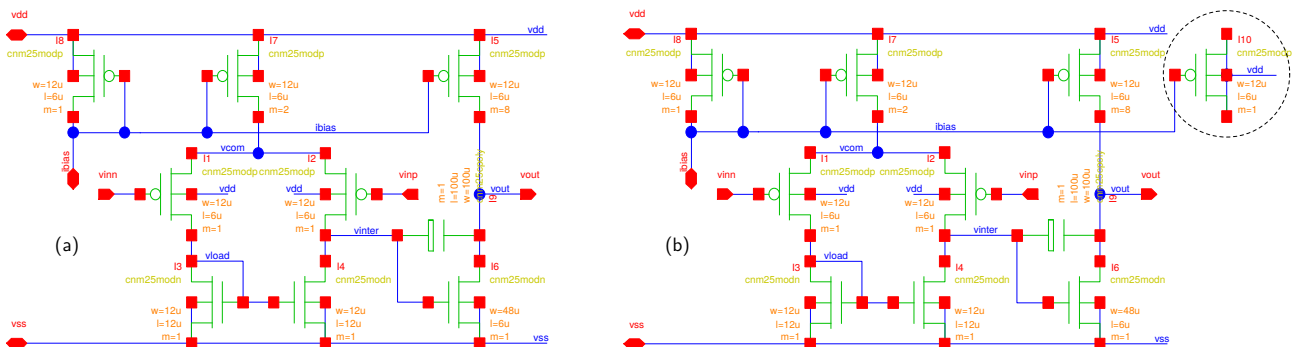


Figure 24 Glade ExampleLib→opamp_example→schematic view of the OpAmp layout example used in Fig. 21 before (a) and after (b) including the correspond-ing layout dummy devices.

The resulting SPICE schematic netlists **before** (left) and **after** (right) dummy-element correction are:

damics-kit/glade/opamp_example.cdl	damics-kit/glade/opamp_example.cdl
<pre>***** * Library Name: ExampleLib * Cell Name: opamp_example * View Name: schematic ***** .SUBCKT opamp_example vinn vinp vout vdd vss ibias *.PININFO vss:B vinp:I vdd:B vout:O vinn:I ibias:B MI7 vdd ibias vcom vdd cnm25modp w=12u l=6u m=2 MI3 vload vload vss vss cnm25modn w=12u l=12u m=1 MI1 vcom vinn vload vdd cnm25modp w=12u l=6u m=1 CI9 vout vinter cnm25cpoly w=100u l=100u m=1 MI4 vinter vload vss vss cnm25modn w=12u l=12u m=1 MI2 vcom vinp vinter vdd cnm25modp w=12u l=6u m=1 MI5 vdd ibias vout vdd cnm25modp w=12u l=6u m=8 MI8 vdd ibias ibias vdd cnm25modp w=12u l=6u m=1 MI6 vout vinter vss vss cnm25modn w=48u l=6u m=1 .ENDS</pre>	<pre>***** * Library Name: ExampleLib * Cell Name: opamp_example * View Name: schematic ***** .SUBCKT opamp_example vinn vinp vout vdd vss ibias *.PININFO vss:B vinp:I vdd:B vout:O vinn:I ibias:B MI7 vdd ibias vcom vdd cnm25modp w=12u l=6u m=2 MI10 vdd ibias vdd vdd cnm25modp w=12u l=6u m=1 MI3 vload vload vss vss cnm25modn w=12u l=12u m=1 MI1 vcom vinn vload vdd cnm25modp w=12u l=6u m=1 CI9 vout vinter cnm25cpoly w=100u l=100u m=1 MI4 vinter vload vss vss cnm25modn w=12u l=12u m=1 MI2 vcom vinp vinter vdd cnm25modp w=12u l=6u m=1 MI5 vdd ibias vout vdd cnm25modp w=12u l=6u m=8 MI8 vdd ibias ibias vdd cnm25modp w=12u l=6u m=1 MI6 vout vinter vss vss cnm25modn w=48u l=6u m=1 .ENDS</pre>

During the LVS verification, Gemini compares the above circuits to the following extracted netlist:

damics-kit/glade/opamp_example_extracted.cdl
<pre>***** * Library Name: ExampleLib * Cell Name: opamp_example * View Name: extracted ***** .SUBCKT opamp_example *.PININFO vss:B vinp:B vcomm:B vdd:B vout:B ibias:B vinn:B vinter:B vload:B MM6 vdd ibias vcomm vdd cnm25modp w=1.2e-05 l=6e-06 as=7.8e-11 ps=3.7e-05 ad=6.6e-11 pd=3.5e-05 \$X=3.325e-05 ... MM9 vcomm ibias vdd vdd cnm25modp w=1.2e-05 l=6e-06 as=7.8e-11 ps=3.7e-05 ad=6.6e-11 pd=3.5e-05 \$X=4.575e-05 ... MM4 vdd ibias ibias vdd cnm25modp w=1.2e-05 l=6e-06 as=7.8e-11 ps=3.7e-05 ad=6.6e-11 pd=3.5e-05 \$X=3.325e-05 ... MM7 vdd ibias vdd vdd cnm25modp w=1.2e-05 l=6e-06 as=7.8e-11 ps=3.7e-05 ad=6.6e-11 pd=3.5e-05 \$X=4.575e-05 ... MM13 vdd ibias vout vdd cnm25modp w=1.2e-05 l=6e-06 as=7.8e-11 ps=3.7e-05 ad=6.6e-11 pd=3.5e-05 \$X=6.675e-05 ... MM5 vdd ibias vout vdd cnm25modp w=1.2e-05 l=6e-06 as=7.8e-11 ps=3.7e-05 ad=6.6e-11 pd=3.5e-05 \$X=3.325e-05 ... MM2 vinter vload vss vss cnm25modn w=1.2e-05 l=1.2e-05 as=6.6e-11 ps=3.5e-05 ad=6.6e-11 pd=3.5e-05 \$X=4.45 ... MM15 vout ibias vdd vdd cnm25modp w=1.2e-05 l=6e-06 as=7.8e-11 ps=3.7e-05 ad=6.6e-11 pd=3.5e-05 \$X=7.925e-05 ... MM14 vout ibias vdd vdd cnm25modp w=1.2e-05 l=6e-06 as=7.8e-11 ps=3.7e-05 ad=6.6e-11 pd=3.5e-05 \$X=7.925e-05 ... MM8 vout ibias vdd vdd cnm25modp w=1.2e-05 l=6e-06 as=7.8e-11 ps=3.7e-05 ad=6.6e-11 pd=3.5e-05 \$X=4.575e-05 ... MM3 vload vinn vcomm vdd cnm25modp w=1.2e-05 l=6e-06 as=6.6e-11 ps=3.5e-05 ad=6.6e-11 pd=3.5e-05 \$X=2.65e-05 ... Cc0 vinter vout w=6.42928e-05 l=0.000156207 \$X=0.000122999 \$Y=2.5749e-05 MM16 vout ibias vdd vdd cnm25modp w=1.2e-05 l=6e-06 as=7.8e-11 ps=3.7e-05 ad=6.6e-11 pd=3.5e-05 \$X=7.925e-05 ... MM12 vdd ibias vout vdd cnm25modp w=1.2e-05 l=6e-06 as=7.8e-11 ps=3.7e-05 ad=6.6e-11 pd=3.5e-05 \$X=6.675e-05 ... MM11 vdd ibias vout vdd cnm25modp w=1.2e-05 l=6e-06 as=7.8e-11 ps=3.7e-05 ad=6.6e-11 pd=3.5e-05 \$X=6.675e-05 ... MM0 vout vinter vss vss cnm25modn w=4.8e-05 l=6e-06 as=2.64e-10 ps=0.000107 ad=2.64e-10 pd=0.000107 \$X=1.125 ... MM1 vload vload vss vss cnm25modn w=1.2e-05 l=1.2e-05 as=6.6e-11 ps=3.5e-05 ad=6.6e-11 pd=3.5e-05 \$X=2.85 ... MM10 vinter vinp vcomm vdd cnm25modp w=1.2e-05 l=6e-06 as=6.6e-11 ps=3.5e-05 ad=6.6e-11 pd=3.5e-05 \$X=4.65ENDS</pre>

Before updating the schematic with the layout dummy devices as in Fig. 24(a), the LVS process clearly returns a negative match between the schematic and extracted circuits due to the absence of these elements in the former. Not only this result is reported in the Glade message window, but the physical location of the specific LVS errors is highlighted in the extracted view itself, as shown in Fig. 25.

----- Glade log file BEFORE schematic dummy correction -----

Netlist summary : opamp_example_extracted.cdl

Number of devices before reduction: 18
Number of nets before reduction: 9

Number of devices after reduction: 10
Number of nets after reduction: 9

Netlist summary : opamp_example_lvs_err.sub

Number of devices before reduction: 9
Number of nets before reduction: 9

Number of devices after reduction: 9
Number of nets after reduction: 9

The circuits are different.

The following netlist mismatches occurred:

Netlist errors : opamp_example_extracted.cdl

2 NETS do not match:

NET "vdd" 11 connections

NET "ibias" 5 connections

N: (inst MM11) [g] ibias :: [s,d,sub] vdd, vout, vdd
N: (inst MM7) [g] ibias :: [s,d,sub] vdd, vdd, vdd
N: (inst MM9) [g] ibias :: [s,d,sub] vcomm, vdd, vdd
N: (inst MM4) [g] ibias :: [s,d,sub] vdd, ibias, vdd
N: (inst MM4) [g] ibias :: [s,d,sub] vdd, ibias, vdd

2 DEVICES could not be matched, possibly because of other unmatched devices:

DEVICE N: (inst MM4) [g] ibias :: [s,d,sub] vdd, ibias, vdd
DEVICE N: (inst MM7) [g] ibias :: [s,d,sub] vdd, vdd, vdd

Netlist errors : opamp_example_lvs_err.sub

2 NETS do not match:

NET "vdd" 8 connections

N: (inst MI8) [g] ibias :: [s,d,sub] vdd, ibias, vdd
N: (inst MI5) [g] ibias :: [s,d,sub] vdd, vout, vdd
N: (inst MI7) [g] ibias :: [s,d,sub] vdd, vcom, vdd
N: (inst MI2) [g] vinp :: [s,d,sub] vcom, vint, vdd
N: (inst MI1) [g] vinn :: [s,d,sub] vcom, vload, vdd
N: (inst MI7) [g] ibias :: [s,d,sub] vdd, vcom, vdd
N: (inst MI5) [g] ibias :: [s,d,sub] vdd, vout, vdd
N: (inst MI8) [g] ibias :: [s,d,sub] vdd, ibias, vdd

NET "ibias" 4 connections

N: (inst MI8) [g] ibias :: [s,d,sub] vdd, ibias, vdd
N: (inst MI5) [g] ibias :: [s,d,sub] vdd, vout, vdd
N: (inst MI7) [g] ibias :: [s,d,sub] vdd, vcom, vdd
N: (inst MI8) [g] ibias :: [s,d,sub] vdd, ibias, vdd

1 DEVICES do not match:

DEVICE N: (inst MI8) [g] ibias :: [s,d,sub] vdd, ibias, vdd

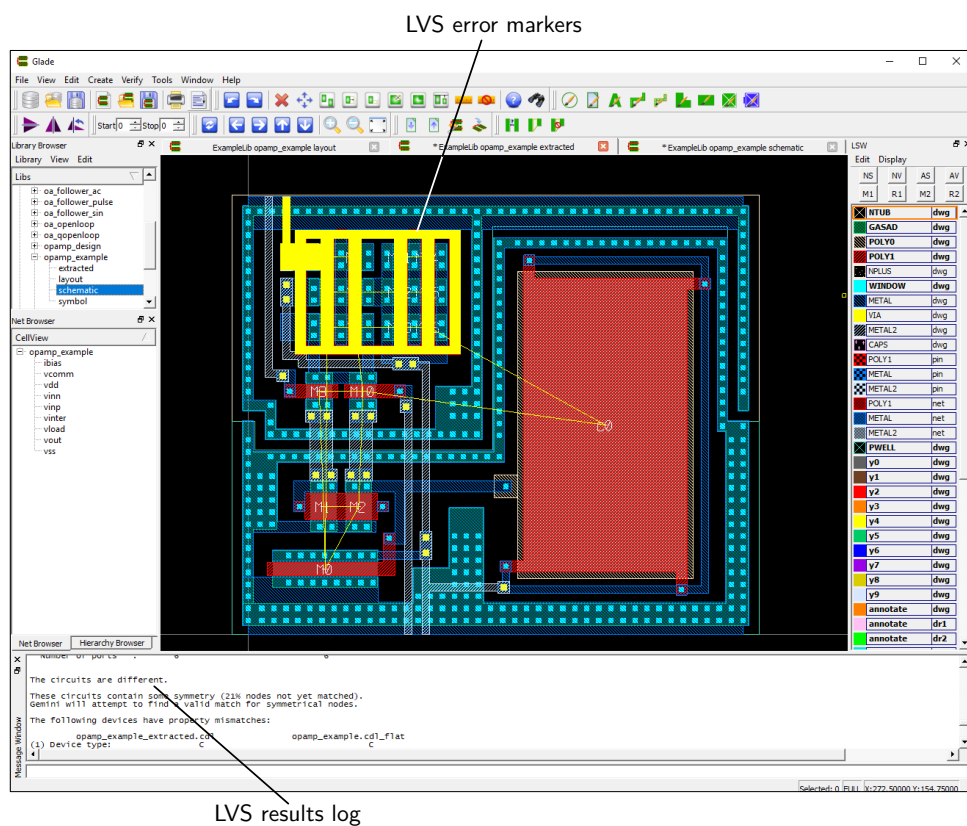


Figure 25 | Glade LVS results for cell view ExampleLib→opamp_example→extracted before updating the schematic view with layout dummy devices.

On the contrary, if the same LVS verification process is repeated **after** introducing the equivalent layout dummy devices into the schematic view of Fig. 24(b), then Gemini returns a positive matching:

```

----- Glade log file AFTER schematic dummy correction -----
-----
Netlist summary before reduction : opamp_example_extracted.cdl
-----
Number of devices :      18
Number of nets    :      9
Number of ports   :      6
-----
Netlist summary before reduction : opamp_example.cdl_flat
-----
Number of devices :      10
Number of nets    :      9
Number of ports   :      6
-----
Netlist summary after reduction :
-----
                opamp_example_extracted.cdl      opamp_example.cdl_flat
Number of devices :      10                      10
Number of nets    :      9                      9
Number of ports   :      6                      6

The following devices have property mismatches:
                opamp_example_extracted.cdl      opamp_example.cdl_flat
(1) Device type:      C                          C
    Inst name  :      Cc0                        CI9
    Model     :      C                          C
    Terminals  :      vinter                      vout
                vout                          vinter
    Value (farad):      0                        0
    W/L (um)   :      64.293/156.207             100.000/100.000

1 device property error.
12 (63%) matches were found by local matching.
All nodes were matched in 3 passes.

The netlists match.

```

Two comments arise from this last example. First, Gemini effectively applies both collapsing and permutation rules like the ones illustrated in Fig. 22. Collapsing can be easily noticed by comparing the number of MOS devices between schematic and extracted netlists before reduction. Permutation allows for example to match these circuits even with the terminals of the compensation capacitor flipped between `vinter` and `vload` nets, as highlighted in each netlist.

Second, although netslits may match topologically, Gemini still performs a comparative audit of device properties according to the 10-% tolerance specified in Fig. 23. In this case, LVS output reports a mismatch in the compensation capacitor size between schematic ($100\ \mu\text{m} \times 100\ \mu\text{m}$) and layout ($\simeq 64\ \mu\text{m} \times 156\ \mu\text{m}$), which have been also highlighted in both netlists.

Q7. Execute the above **LVS verification** to your optimized OpAmp layout, review any error from Gemini output and **correct the layout** accordingly.

4.8 2D and 3D Parasitics Extraction

After validating the correct matching between the optimized schematic and the full-custom layout topologies, the next physical verification step from Fig. 1 consists on the parasitics extraction, which is required for the final electrical re-simulation of the circuit. In general, CMOS planar technologies introduce *RLC* parasitic elements in the interconnectivity between devices following Fig. 26.

 


Figure 26 | Typical *RLC* circuit interconnectivity parasitics present in CMOS planar technologies.

For simplification purposes, only capacitive parasitics will be considered here. For this purpose, the simple parallel-plate capacitor model can be taken:

$$C_{\text{par}} = A \frac{\epsilon_o \epsilon_{\text{ox}}}{t_{\text{ox}}} \quad (3)$$

where A stands for the plate area, t_{ox} and ϵ_{ox} are the insulator thickness and its relative permittivity (~ 3.9 for SiO_2), and ϵ_o is the well-known permittivity of free space (i.e. 8.8542×10^{-12} F/m). Even with this very simplistic capacitive model, it is clear that some technology information is needed regarding the spacing (t_{ox}) between conductors. While horizontal spacing must be directly extracted from the specific layout pattern, the PDK includes also numerical data about the fixed vertical spacing between routing layers. In the particular case of CNM25, and under the assumption of ideal CMOS process planarization and thin metal layers, insulator thickness values are depicted in Fig. 27. Basically, the field oxide is 1060nm thick, while the inter-metal oxide insulator height is around 1300nm.

In practice, the extraction of parasitic elements is probably one of the most EDA time consuming steps of the whole physical verification part of Fig. 1, even considering only an small layout block like your OpAmp. The complexity of this process can be clearly understood with Fig. 28, where the 3D exploded view of the OpAmp layout example of Fig. 17 is rendered. This section will evaluate both 2D and 3D extraction techniques for estimating the capacitive parasitics of your CMOS circuit.

 


Figure 27 | Simplified CNM25 cross section used for the interconnectivity parasitic capacitance model. Units in nm. Not to scale.

 


Figure 28 | 3D exploded view of ExampleLib→opamp_example→layout based on the simplified CNM25 cross section model of Fig. 27. Rendered by the EDA tool GDS3D from the University of Twente. More information about GDS3D can be found at <http://sourceforge.net/projects/gds3d>.

The first approach relies on 2D analysis, much like the method used in Section 4.6 for the extraction of native CNM25 devices (i.e. `cnm25modn`, `cnm25modp` and `cnm25cpoly`). For this reason, the PDK includes the Python script `damics-kit/glade/verification/cnm25xtr_par2d.py`, which is very similar to the regular extraction code `damics-kit/glade/verification/cnm25xtr_lvs.py` but adding here the specific functions for the computation of overlapping capacitance. In fact, Glade can also extract the perimeter of these overlapping regions in order to estimate fringing capacitance effects.

The sequential procedure to generate 2D parasitics extraction netlists is as follows:

1. Open your OpAmp layout
ExampleLib→opamp_design→layout.
2. Execute Verify→Extract→Run (shift+y).
3. Select the extraction script `damics-kit/glade/verification/cnm25xtr_par2d.py` and launch the extraction process.
4. Regenerate the OpAmp test-bench netlists (*.cir) of Fig. 6 but using the following CDL export configuration:
 - (a) Select *Use Model Name* option for passive devices.
 - (b) Set the parasitic capacitance threshold to 1 fF.
 - (c) Choose to *Merge parasitic caps*.
 - (d) Select *SPICE lyt* switch-list name.

 


Figure 29 | Glade CDL export options for extracted views with parasitics.

```

1  # CNM25 2M extraction deck
2  # with parasitic capacitances
3
4  # Initialise boolean package & Loading pcells
5  See damics-kit/glade/verification/cnm25xtr_lvs.py
6
7  # Parasitic capacitance density [F/um2]
8  e0 = 8.854187817e-12 # [F/m]
9  er = 3.9             # SiO2
10 c0 = e0 * er * 1e-6  # Normalized to 1um thickness
11 cpoly0sub            = c0 / 1.060
12 cpoly1sub            = c0 / 1.060
13 cmetal1poly1         = c0 / 1.300
14 cmetal1poly0         = c0 / 1.300
15 cmetal1diff          = c0 / 1.300
16 cmetal1sub           = c0 / 2.360
17 cmetal2metal1        = c0 / 1.300
18 cmetal2poly1         = c0 / 2.600
19 cmetal2poly0         = c0 / 2.600
20 cmetal2diff          = c0 / 3.660
21 cmetal2sub           = c0 / 3.660
22
23 # Get raw layers & Form derived layers & Extract pin and net names before geomConnect
24 # Form connectivity & Save interconnect & Extracting devices
25 See damics-kit/glade/verification/cnm25xtr_lvs.py
26
27 # Extracting parasitics
28 print "# Extract Poly0 parasitics"
29 extractParasitic2(pwell, polycap, cpoly0sub, 0)
30 extractParasitic2(nwell, polycap, cpoly0sub, 0)
31
32 print "# Extract Poly1 parasitics"
33 extractParasitic2(pwell, polygate, cpoly1sub, 0)
34 extractParasitic2(nwell, polygate, cpoly1sub, 0)
35
36 print "# Extract Metal1 parasitics"
37 extractParasitic2(polygate, metal1, cmetal1poly1, 0)
38 extractParasitic2(polycap, metal1, cmetal1poly0, 0)
39 extractParasitic3(pdifff, metal1, cmetal1diff, 0, [polygate, polycap])
40 extractParasitic3(ndifff, metal1, cmetal1diff, 0, [polygate, polycap])
41 extractParasitic3(pwell, metal1, cmetal1sub, 0, [polygate, polycap, pdifff, ndifff])
42 extractParasitic3(nwell, metal1, cmetal1sub, 0, [polygate, polycap, pdifff, ndifff])
43
44 print "# Extract Metal2 parasitics"
45 extractParasitic2(metal1, metal2, cmetal2metal1, 0)
46 extractParasitic3(polygate, metal2, cmetal2poly1, 0, [metal1])
47 extractParasitic3(polycap, metal2, cmetal2poly0, 0, [metal1, polygate])
48 extractParasitic3(pdifff, metal2, cmetal2diff, 0, [metal1, polygate, polycap])
49 extractParasitic3(ndifff, metal2, cmetal2diff, 0, [metal1, polygate, polycap])
50 extractParasitic3(pwell, metal2, cmetal2sub, 0, [metal1, polygate, polycap, pdifff, ndifff])
51 extractParasitic3(nwell, metal2, cmetal2sub, 0, [metal1, polygate, polycap, pdifff, ndifff])
52
53 print "# Ending circuit extraction"
54 geomEnd()
55
56 # Opening extracted view
57 ui.openCellView(libxtrpar.libName(), cv.cellName(), "extracted")
58
damics-kit/glade/verification/cnm25xtr_par2d.py

```

For instance, the 2D parasitics for the OpAmp example of Fig. 17 are listed as follows:

```
*****
* Library Name: ExampleLib
* Cell Name:    opamp_example
* View Name:    extracted
*****

.SUBCKT opamp_example vinn vinp vout vdd vss ibias
*.PININFO vss:B vinp:B vdd:B vinn:B ibias:B vout:B

MM2 vinter vload vss vss cnm25modn w=1.2e-05 l=1.2e-05 as=6.6e-11 ps=3.5e-05 ad=6.6e-11 pd=3.5e-05
MM0 vout vinter vss vss cnm25modn w=4.8e-05 l=6e-06 as=2.64e-10 ps=0.000107 ad=2.64e-10 pd=0.000107
MM14 vout ibias vdd vdd cnm25modp w=1.2e-05 l=6e-06 as=7.8e-11 ps=3.7e-05 ad=6.6e-11 pd=3.5e-05
MM12 vdd ibias vout vdd cnm25modp w=1.2e-05 l=6e-06 as=7.8e-11 ps=3.7e-05 ad=6.6e-11 pd=3.5e-05
MM4 vdd ibias ibias vdd cnm25modp w=1.2e-05 l=6e-06 as=7.8e-11 ps=3.7e-05 ad=6.6e-11 pd=3.5e-05
MM6 vdd ibias vcomm vdd cnm25modp w=1.2e-05 l=6e-06 as=7.8e-11 ps=3.7e-05 ad=6.6e-11 pd=3.5e-05
Cc0 vinter vout cnm25cpoly w=6.42928e-05 l=0.000156207
MM11 vdd ibias vout vdd cnm25modp w=1.2e-05 l=6e-06 as=7.8e-11 ps=3.7e-05 ad=6.6e-11 pd=3.5e-05
MM16 vout ibias vdd vdd cnm25modp w=1.2e-05 l=6e-06 as=7.8e-11 ps=3.7e-05 ad=6.6e-11 pd=3.5e-05
MM9 vcomm ibias vdd vdd cnm25modp w=1.2e-05 l=6e-06 as=7.8e-11 ps=3.7e-05 ad=6.6e-11 pd=3.5e-05
MM15 vout ibias vdd vdd cnm25modp w=1.2e-05 l=6e-06 as=7.8e-11 ps=3.7e-05 ad=6.6e-11 pd=3.5e-05
MM5 vdd ibias vout vdd cnm25modp w=1.2e-05 l=6e-06 as=7.8e-11 ps=3.7e-05 ad=6.6e-11 pd=3.5e-05
MM3 vload vinn vcomm vdd cnm25modp w=1.2e-05 l=6e-06 as=6.6e-11 ps=3.5e-05 ad=6.6e-11 pd=3.5e-05
MM8 vout ibias vdd vdd cnm25modp w=1.2e-05 l=6e-06 as=7.8e-11 ps=3.7e-05 ad=6.6e-11 pd=3.5e-05
MM7 vdd ibias vdd vdd cnm25modp w=1.2e-05 l=6e-06 as=7.8e-11 ps=3.7e-05 ad=6.6e-11 pd=3.5e-05
MM13 vdd ibias vout vdd cnm25modp w=1.2e-05 l=6e-06 as=7.8e-11 ps=3.7e-05 ad=6.6e-11 pd=3.5e-05
MM1 vload vload vss vss cnm25modn w=1.2e-05 l=1.2e-05 as=6.6e-11 ps=3.5e-05 ad=6.6e-11 pd=3.5e-05
MM10 vinter vinp vcomm vdd cnm25modp w=1.2e-05 l=6e-06 as=6.6e-11 ps=3.5e-05 ad=6.6e-11 pd=3.5e-05
CP0 vinter vdd C=1.39453e-15
CP1 vinn vdd C=6.18331e-15
CP2 vload vdd C=1.39453e-15
CP3 vinter vss C=3.8582e-13
CP5 vout ibias C=3.33692e-15
CP7 ibias vdd C=7.53437e-14
CP8 vinp vss C=1.85938e-15
CP9 vinp vdd C=5.88887e-15
CP11 vcomm ibias C=2.72266e-15
CP12 vload vss C=1.59238e-14
CP13 vdd ibias C=3.05469e-15
CP14 vout vcomm C=2.0918e-15
CP16 vout vss C=3.37819e-13
.ENDS
```

Depending on the particular IC application, like radio frequency (RF) communications, more accurate parasitics estimations may be required. For such cases, Glade integrates FastCap² [8], the classic 3D finite-element tool capable of extracting self and mutual capacitances between ideal conductors of arbitrary shapes, orientations and sizes. The CNM25 PDK already incorporates the geometrical cross-section information in the technological file to exploit this fast but accurate extraction tool. Indeed, the procedure to perform the 3D capacitance extraction and generate the corresponding netlist is exactly the same as for the 2D case of page 53 but selecting the script file `damics-kit/glade/verification/cnm25xtr_par3d.py` instead. In this sense, Fig. 30 presents its usage for the same OpAmp layout example.

²More information can be found at http://www.rle.mit.edu/cpg/research_codes.htm.

It is important to note that this PDK is configured to annotate all the FastCap coupling contributions to bulk and to infinite boundaries into a predefined node named vss. This preset and the rest of FastCap configuration parameters highlighted in green below can be easily changed by listing them as switch variables in the extraction dialogue Verify→Extract→Run of Fig. 21.

```

1  # CNM25 2M extraction deck
2  # with 3D parasitic capacitances
3
4  # Initialise boolean package & Loading pcells
5  # Get raw layers & Form derived layers
6  # Extract pin and net names before geomConnect
7  # Form connectivity & Save interconnect & Extracting devices
8
9  See damics-kit/glade/verification/cnm25xtr_lvs.py
10
11 # Extracting devices
12
13 if geomNumShapes(ngate) > 0 :
14     print "# Extract NMOS transistors"
15     extractMOS("cnm25modn", ngate, polygate, ndiff, pwell)
16
17 if geomNumShapes(pgate) > 0 :
18     print "# Extract PMOS transistors"
19     extractMOS("cnm25modp", pgate, polygate, pdiff, nwell)
20
21 if geomNumShapes(cpoly) > 0 :
22     print "# Extract PiP capacitors"
23     extractDevice("cnm25cpoly", cpoly, [[polygate, "T"], [polycap, "B"]])
24
25 # Extracting 3D parasitics with Fastcap
26
27 print "# Extract 3D cap parasitics using switch values:"
28
29 if 'bulk_name' not in globals() :
30     bulk_name = "vss"
31 print " bulk_name = ", bulk_name
32
33 if 'ref_name' not in globals() :
34     ref_name = "vss"
35 print " ref_name = ", ref_name
36
37 if 'fastcap_tol' not in globals() :
38     fastcap_tol = 0.01
39 print " fastcap_tol = ", fastcap_tol
40
41 if 'fastcap_order' not in globals() :
42     fastcap_order = 3
43 print " fastcap_order = ", fastcap_order
44
45 extractParasitic3D(bulk_name, ref_name, fastcap_tol, fastcap_order)
46
47 print "# Ending circuit extraction"
48 geomEnd()
49
50 # Opening extracted view
51 ui.openCellView(libxtrpar.libName(), cv.cellName(), "extracted")
52
damics-kit/glade/verification/cnm25xtr_par3d.py


```


For instance, the 3D parasitics for the OpAmp example of Fig. 17 are listed as follows:

```
*****
* Library Name: ExampleLib
* Cell Name:    opamp_example
* View Name:    extracted
*****

.SUBCKT opamp_example vinn vinp vout vdd vss ibias
*.PININFO vss:B vinp:B vdd:B vinn:B ibias:B vout:B

MM2 vinter vload vss vss cnm25modn w=1.2e-05 l=1.2e-05 as=6.6e-11 ps=3.5e-05 ad=6.6e-11 pd=3.5e-05
MM0 vout vinter vss vss cnm25modn w=4.8e-05 l=6e-06 as=2.64e-10 ps=0.000107 ad=2.64e-10 pd=0.000107
MM14 vout ibias vdd vdd cnm25modp w=1.2e-05 l=6e-06 as=7.8e-11 ps=3.7e-05 ad=6.6e-11 pd=3.5e-05
MM12 vdd ibias vout vdd cnm25modp w=1.2e-05 l=6e-06 as=7.8e-11 ps=3.7e-05 ad=6.6e-11 pd=3.5e-05
MM4 vdd ibias ibias vdd cnm25modp w=1.2e-05 l=6e-06 as=7.8e-11 ps=3.7e-05 ad=6.6e-11 pd=3.5e-05
MM6 vdd ibias vcomm vdd cnm25modp w=1.2e-05 l=6e-06 as=7.8e-11 ps=3.7e-05 ad=6.6e-11 pd=3.5e-05
Cc0 vinter vout cnm25cpoly w=6.42928e-05 l=0.000156207
MM11 vdd ibias vout vdd cnm25modp w=1.2e-05 l=6e-06 as=7.8e-11 ps=3.7e-05 ad=6.6e-11 pd=3.5e-05
MM16 vout ibias vdd vdd cnm25modp w=1.2e-05 l=6e-06 as=7.8e-11 ps=3.7e-05 ad=6.6e-11 pd=3.5e-05
MM9 vcomm ibias vdd vdd cnm25modp w=1.2e-05 l=6e-06 as=7.8e-11 ps=3.7e-05 ad=6.6e-11 pd=3.5e-05
MM15 vout ibias vdd vdd cnm25modp w=1.2e-05 l=6e-06 as=7.8e-11 ps=3.7e-05 ad=6.6e-11 pd=3.5e-05
MM5 vdd ibias vout vdd cnm25modp w=1.2e-05 l=6e-06 as=7.8e-11 ps=3.7e-05 ad=6.6e-11 pd=3.5e-05
MM3 vload vinn vcomm vdd cnm25modp w=1.2e-05 l=6e-06 as=6.6e-11 ps=3.5e-05 ad=6.6e-11 pd=3.5e-05
MM8 vout ibias vdd vdd cnm25modp w=1.2e-05 l=6e-06 as=7.8e-11 ps=3.7e-05 ad=6.6e-11 pd=3.5e-05
MM7 vdd ibias vdd vdd cnm25modp w=1.2e-05 l=6e-06 as=7.8e-11 ps=3.7e-05 ad=6.6e-11 pd=3.5e-05
MM13 vdd ibias vout vdd cnm25modp w=1.2e-05 l=6e-06 as=7.8e-11 ps=3.7e-05 ad=6.6e-11 pd=3.5e-05
MM1 vload vload vss vss cnm25modn w=1.2e-05 l=1.2e-05 as=6.6e-11 ps=3.5e-05 ad=6.6e-11 pd=3.5e-05
MM10 vinter vinp vcomm vdd cnm25modp w=1.2e-05 l=6e-06 as=6.6e-11 ps=3.5e-05 ad=6.6e-11 pd=3.5e-05
CP1 vinn vdd C=5.378e-15
CP2 vinn vout C=1.433e-15
CP4 vout vss C=1.6182e-13
CP8 vss vdd C=2.9485e-15
CP9 vss vss C=4.10208e-13
CP10 vload vss C=2.164e-14
CP11 vss vout C=1.6651e-15
CP14 vinter vdd C=2.313e-15
CP16 vinp vout C=3.227e-15
CP18 vinp vdd C=1.327e-15
CP27 vinter vout C=2.122e-15
CP30 vinter vss C=3.7989e-14
CP32 ibias vdd C=2.687e-15
CP33 vdd vss C=2.78947e-13
CP34 vinp vss C=1.2754e-14
CP37 vout vdd C=4.388e-15
CP38 vinn vss C=9.51276e-15
CP39 vinp vinter C=3.258e-15
CP40 vcomm vout C=8.066e-15
CP41 vcomm vss C=2.45168e-14
CP42 vload vdd C=2.399e-15
CP44 ibias vss C=1.0712e-14
.ENDS
```

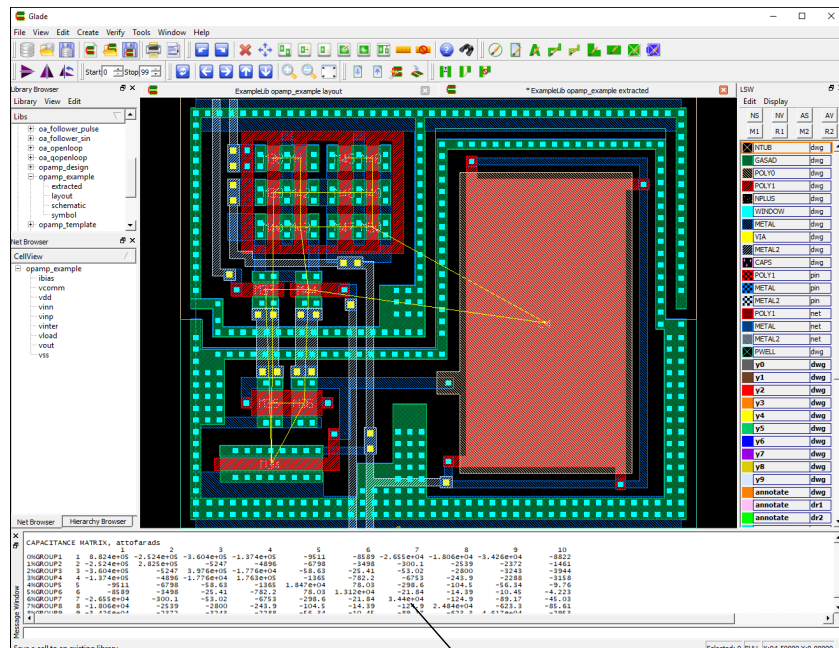

(a)

Report on 3D extraction results...

 


Figure 30 | Glade 3D extraction results for ExampleLib→opamp_example→extracted cell view (a) and FastCap equivalent finite-element mesh (b).

- Q8.** Execute the 2D and 3D parasitics extraction procedure to your optimized OpAmp layout following Fig. 29:
- Which are the **top 3** parasitic caps of your layout?
 - What are the quantitative differences between **2D** and **3D** cap values?
 - Qualitatively speaking, what **impact** do you expect in OpAmp performance?

4.9 Post-Layout Simulation

According to Fig. 1, the last physical verification step of your full-custom layout consists on the electrical re-simulation of the circuit extracted in the previous section to evaluate the effects of parasitics. Thanks to the SpiceOpus netlist hierarchy of Fig. 8, this post-layout simulation only requires the substitution of the subcircuit netlist file before redoing the OpAmp datasheet.

Q9. Build a **summary datasheet** of your OpAmp following Table 5 with 3 performance columns: optimized schematic, extracted layout with 2D and 3D parasitics. Which OpAmp figures are the most affected by the layout parasitics? What are the main differences between 2D and 3D post-layout simulation results?

4.10 Tape-Out

Finally, your full-custom CMOS layout design is ready for fabrication at the IC foundry! The process of transferring the layout from the design house to the semiconductor manufacturer is called tape-out, from the time when the physical media support used for sending the EDA database was a magnetic tape itself. Although several database standards exist specifically for IC mask design transfer, the commonly accepted choice is the GDSII file format. Glade can generate this file format through File→Export→Export GDS2 and choosing the options of Fig. 31.

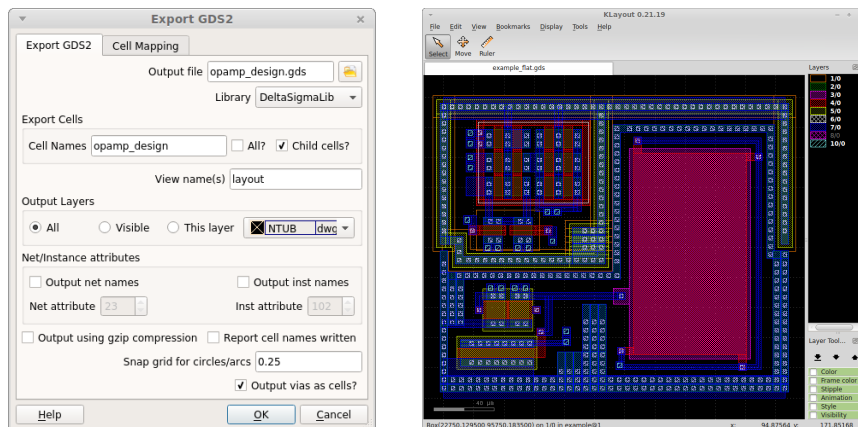


Figure 31 | Glade GDSII export options and ExampleLib→opamp_example→layout GDSII file example viewed with KLayout. More information about KLayout can be found at <http://www.klayout.de>.

Q10. Export your OpAmp layout to damics-kit/glade/opamp_design.gds.

Glossary

BSIM3v3 Berkeley Short-channel IGFET Model version 3.3

CDL circuit description language

CNM25 2.5 μm 2-polySi 2-metal CMOS technology from IMB-CNM(CSIC)

CMOS complementary metal-oxide-semiconductor

CMRR common-mode rejection ratio

DRC design rule checker

DRD design rule driven

EDA electronic design automation

ERC electrical rule checker

GDSII graphic database system II

MPP MultiPartPath

MOS metal-oxide-semiconductor

MOSFET MOS field-effect transistor

NMOS N-type MOS

PDK physical design kit

PMOS P-type MOS

IC integrated circuit

I/O input/output

LSW layer selection window

LVS layout versus schematic

OpAmp operational amplifier

OS operative system

PCell parameterized cell

PDF portable document format

PiP polySi-insulator-polySi

PVT process, supply voltage and temperature

RF radio frequency

SPICE Simulation Program with Integrated Circuit Emphasis

References

- [1] T. Tuma and Á. Bűrmen. *Circuit Simulation with SPICE OPUS: Theory and Practice*. Modeling and Simulation in Science, Engineering and Technology. Birkhäuser Boston, 2009. ISBN 978-0-8176-4867.
- [2] Yuhua Cheng, Mansun Chan, Kelvin Hui, Min chie Jeng, Zhihong Liu, Jianhui Huang, Kai Chen, James Chen, Robert Tu, Ping K. Ko, and Chenming Hu. BSIM3v3 Manual. Technical report, University of California, Berkeley, CA 94720, USA, 1996. damics-kit/doc/bib/BSIM3v3_Manual.pdf.
- [3] M. J. M. Pelgrom, A. C. J. Duinmaijer, and A. P. G. Welbers. Matching Properties of MOS transistors. *IEEE Journal of Solid-State Circuits*, 24(5):1433–1440, Oct 1989. <https://doi.org/10.1109/JSSC.1989.572629>.
- [4] P. E. Allen and D. R. Holberg. *CMOS Analog Circuit Design*. Oxford University Press, 2002. <http://www.aicdesign.org>.
- [5] T. Quarles, A. R. Newton, D. O. Pederson, and A. Sangiovanni-Vincentelli. *SPICE3 Version 3f3 User's Manual*. University of California, Berkeley CA 94720, May 1993. damics-kit/doc/bib/Spice3f3_Users_Manual.pdf.
- [6] A. Hastings. *The Art of Analog Layout*. Prentice Hall, 2005.
- [7] C. Ebeling, N. McKenzie, and L. McMurchie. *The Gemini Users Guide*. University of Washington, Dec 1993. damics-kit/doc/bib/The_Gemini_Users_Guide.pdf.
- [8] K. Nabors, S. Kim, J. White, and S. Senturia. *FastCap User's Guide*. Massachusetts Institute of Technology, Sep 1992. damics-kit/doc/bib/FastCap_Users_Guide.pdf.