

1. Introduction to Integrated Heterogeneous Systems

Francesc Serra Graells

francesc.serra.graells@uab.cat

Departament de Microelectrònica i Sistemes Electrònics
Universitat Autònoma de Barcelona

paco.serra@imb-cnm.csic.es


Integrated Circuits and Systems
IMB-CNM(CSIC)

- 1 Evolution of CMOS Technologies
- 2 Trends in Analog and Mixed IC Design
- 3 A/D and D/A Conversion Principles
- 4 ADC and DAC Figures of Merit
- 5 Lab proposal

- 1 Evolution of CMOS Technologies
- 2 Trends in Analog and Mixed IC Design
- 3 A/D and D/A Conversion Principles
- 4 ADC and DAC Figures of Merit
- 5 Lab proposal


Moore's Law

 - ▲ Number of transistors per chip **doubles** every **24 months**





➤ Gordon E. Moore
Cramming More Components onto Integrated Circuits
 Electronics Magazine, 38(8):114–117, Apr 1965
doi.org/10.1109/N-SSC.2006.4785860

 ➤ Plot built from tabulated data available in
wikipedia.org/wiki/Transistor_count




Moore's Law

  - ▲ Number of transistors per chip **doubles** every **24** months
- ▲ Thanks to **scaling**, not at chip (yield!), but at transistor (litho) level





Moore's Law

 - ▲ Number of transistors per chip **doubles** every **24** months
- ▲ Thanks to **scaling**, not at chip (yield!), but at transistor (litho) level




Technology nodes

  


More Moore

 - ▲ Number of transistors per chip **doubles** every **24** months
- ▲ Thanks to **scaling**, not at chip (yield!), but at transistor (litho) level




Technology nodes

 


➤ [tsmc.com](https://www.tsmc.com)


3D FinFET + SOI + multiple patterning

 

Planar FET

 


FinFET

 

Nanosheet/Gate-All-Around FET

 
➤ Samuel K. Moore
*Intel's Stacked Nanosheet Transistors
 Could Be the Next Step in Moore's Law*
 IEEE Spectrum, Dec 2020
spectrum.ieee.org



>10M, ultra low-k

More Moore

 - ▲ Number of transistors per chip **doubles** every **24** months
- ▲ Thanks to **scaling**, not at chip (yield!), but at transistor (litho) level



➤ Gwendolyn Rak
Intel Hopes to Leapfrog Its Competitors
 IEEE Spectrum, Jan 2024
spectrum.ieee.org





Future 3D technologies



➤ Luc Van den hove
20-Year Semiconductor Roadmap: Tearing Down the Walls
 IMEC International Technology Forum, July 2022
imec-int.com



More Moore

    - ▲ Number of transistors per chip **doubles** every **24** months
- ▲ Thanks to **scaling**, not at chip (yield!), but at transistor (litho) level
- ▲ **Cut-off frequency** increases, but not exploited due to RF and **power** limitations → parallelism



More Moore

  
- ▲ Number of transistors per chip **doubles** every **24** months
- ▲ Thanks to **scaling**, not at chip (yield!), but at transistor (litho) level
- ▲ **Cut-off frequency** increases, but not exploited due to RF and **power** limitations → parallelism
- ▲ **Cost/transistor** improved also due to wafer scaling (capacity)



More Moore

- ▲ Number of transistors per chip **doubles** every **24** months
- ▲ Thanks to **scaling**, not at chip (yield!), but at transistor (litho) level
- ▲ **Cut-off frequency** increases, but not exploited due to RF and **power** limitations → parallelism
- ▲ **Cost/transistor** improved also due to wafer scaling (capacity)
- ▼ Small is beautiful, but what to do with so **many**, **inexpensive** and super **fast** devices?

apple.com

 

Apple M3 Max processor with 12 P-cores 4 E-cores and 40 GPU cores in 15-metal 3-nm FinFET TSMC technology featuring **92 billion transistors**

More than Moore

► Diversification of technology **applications**


▲ **Ubiquitous** computing

▲ Not only signal processing but:

- Smart **sensing**
- Wireless **communications**
- **Power** control

▲ **Multi-domain** integrated systems:

 - Physics
- Chemistry
- Biology
- Medicine




More than Moore

- Diversification of technology **applications**

- ▲ **Ubiquitous** computing

- ▲ Not only signal processing but:
 - Smart **sensing**
 - Wireless **communications**
 - **Power** control

 - ▲ **Multi-domain** integrated systems:
 - Physics
 - Chemistry
 - Biology
 - Medicine





- ▼ **New challenges** (beside miniaturization):


- CMOS technologies with extra process **modules**
- **Heterogeneous** circuit design (A/D/RF/MEMS/power...)
- Application-specific **packaging**

Silicon Wafer

 
 
- ▶ Polished **monocrystalline** slice
- ▶ **Periodic** atomic lattice




~5Å lattice spacing

 

CMOS technologies

  



Bipolar technologies

 

- Doping type
- Crystalline plane

Silicon Wafer

  - ▶ Polished **monocrystalline** slice
- ▶ **Periodic** atomic lattice
- ▶ Obtained from cylindrical **ingots**




Czocharalski method



Silicon Wafer

 - ▶ Polished **monocrystalline** slice
- ▶ **Periodic** atomic lattice
- ▶ Obtained from cylindrical **ingots**
- ▶ Grinding, slicing and polishing




Flat side

- 200- μm to 750- μm thickness
- Bulk, epitaxial, Silicon-on-insulator (SOI)



Diameter grinding




Flat grinding

 


Wafer slicing

  


Edge rounding

 

Two-side lapping

 


Chemical etching

 

Surface polishing

Wafer Processing

 - **Patterning** areas using photolithography




Wafer Processing


► Patterning areas using photolithography




1. Vapor prime

 

2. Spin coat

 


3. Soft bake

 


4. **Alignment** and exposure




5. Post-exposure bake

 

6. Develop

 


7. Hard bake

 

 8. Inspection

Wafer Processing

- **Patterning** areas using photolithography



- ▲ Simple equipment
- ▼ Limited mask lifetime


- ▲ No direct contact
- ▼ Resolution $> 3\mu\text{m}$

- ▲ High resolution
- ▼ Expensive and slower

Wafer Processing

- **Patterning** areas using photolithography

Stepper equipment

 

Wafer Processing

- **Patterning** areas
using photolithography

UV Light source	Name	Wavelength (nm)	Application feature size (μm)
Mercury Lamp	G-line	436	0.50
	H-line	405	
	I-line	365	0.35 to 0.25
Excimer Laser	XeF	351	
	XeCl	308	
	KrF (DUV)	248	0.25 to 0.15
	ArF	193	0.18 to 0.13
Fluorine Laser	F ₂	157	0.13 to 0.1

124

10

EUV

Wafer Processing




► **Patterning** areas
using photolithography

► **Adding** materials:


■ Ion implantation

▲ Depth control

▼ Lattice damage

   

▼ Lateral effect

 


▼ Shadowing

Wafer Processing

- **Patterning** areas using photolithography
- **Adding** materials:
 - Ion implantation

Doping applications

 


Wafer Processing

► **Patterning** areas
using photolithography



► **Adding** materials:

- Ion implantation
- Diffusion
- Thin-film growing
- Thin-film deposition

e.g. Si doping (hours, 800°C to 1200°C)


 


  e.g. SiO_2 oxidation (hours, 700°C to 1200°C)




Wafer Processing

  - **Patterning** areas using photolithography
- **Adding** materials:
 - Ion implantation
 - Diffusion
 - Thin-film growing
 - Thin-film deposition
- **Removing** materials:
 - Cleaning
 - Etching



 e.g. physical/chemical
reactive ion etching (RIE)
for micromachining



Wafer Processing

► **Patterning** areas using photolithography

► **Adding** materials:



- Ion implantation
- Diffusion
- Thin-film growing
- Thin-film deposition

► **Removing** materials:

- Cleaning
- Etching
- Chemical-mechanical planarization (**CMP**)

► **Thermal** treatment:

- Annealing
- Reflowing
- Alloying

  

e.g. 6-metal 0.18μm BEOL


CNM25 Technology Example

► **2.5- μm polySi-insulator-polySi (PiP) 1M** twin-well CMOS process:

- 4-inch wafers
- 22-mm x 22-mm (484mm²) stepper reticle
- 8-mask layout design

► **FEOL** stages:

- N and P wells

 

Initial pad oxidation (314Å to 415Å)
Nitride deposition (1050Å to 1300Å)
NTUB photolithography

➤ M. Zabala and A. Sánchez, IMB-CNM(CSIC)


CNM25 Technology Example

► 2.5- μm polySi-insulator-polySi (PiP) 1M twin-well CMOS process:

- 4-inch wafers
- 22-mm x 22-mm (484mm²) stepper reticle
- 8-mask layout design

► FEOL stages:

- N and P wells

 

➤ M. Zabala and A. Sánchez, IMB-CNM(CSIC)


CNM25 Technology Example

► 2.5- μm polySi-insulator-polySi (PiP) 1M twin-well CMOS process:

- 4-inch wafers
- 22-mm x 22-mm (484mm²) stepper reticle
- 8-mask layout design

► FEOL stages:

- N and P wells

 

Well-oxide grow (3500Å to 4500Å)
Nitride stripping
P-well implantation

➤ M. Zabala and A. Sánchez, IMB-CNM(CSIC)



CNM25 Technology Example

► 2.5- μm polySi-insulator-polySi (PiP) 1M twin-well CMOS process:

- 4-inch wafers
- 22-mm x 22-mm (484mm²) stepper reticle
- 8-mask layout design

► FEOL stages:

- N and P wells

  

Oxide stripping
P-well (7 μm) N-well (5 μm) drive-in
and oxide grow (1500Å to 1750Å)
Oxide stripping

➤ M. Zabala and A. Sánchez, IMB-CNM(CSIC)


CNM25 Technology Example

► **2.5- μm polySi-insulator-polySi (PiP) 1M** twin-well CMOS process:

- 4-inch wafers
- 22-mm x 22-mm (484mm²) stepper reticle
- 8-mask layout design

► **FEOL** stages:

- N and P wells
- Active areas

 

Pad oxidation (150Å to 225Å)
Nitride deposition (1050Å to 1300Å)
GASAD photolithography

➤ M. Zabala and A. Sánchez, IMB-CNM(CSIC)


CNM25 Technology Example

► 2.5- μm polySi-insulator-polySi (PiP) 1M twin-well CMOS process:

- 4-inch wafers
- 22-mm x 22-mm (484mm²) stepper reticle
- 8-mask layout design

► FEOL stages:

- N and P wells
- Active areas

 

Nitride etching
Field implantation

➤ M. Zabala and A. Sánchez, IMB-CNM(CSIC)



CNM25 Technology Example

► 2.5- μm polySi-insulator-polySi (PiP) 1M twin-well CMOS process:

- 4-inch wafers
- 22-mm x 22-mm (484mm²) stepper reticle
- 8-mask layout design

► FEOL stages:

- N and P wells
- Active areas

  

LOCOS* (10000Å to 11200Å)
Nitride etching

*LOCal Oxidation of Silicon

➤ M. Zabala and A. Sánchez, IMB-CNM(CSIC)


CNM25 Technology Example

► 2.5- μm polySi-insulator-polySi (PiP) 1M twin-well CMOS process:

- 4-inch wafers
- 22-mm x 22-mm (484mm²) stepper reticle
- 8-mask layout design

► FEOL stages:

- N and P wells
- Active areas

 

Sacrificial oxidation (850Å to 1050Å)
Gate implantation
Pre-poly cleaning

➤ M. Zabala and A. Sánchez, IMB-CNM(CSIC)


CNM25 Technology Example

► 2.5- μm polySi-insulator-polySi (PiP) 1M twin-well CMOS process:

- 4-inch wafers
- 22-mm x 22-mm (484mm²) stepper reticle
- 8-mask layout design

► FEOL stages:

 - N and P wells
- Active areas
- PiP capacitor



PolySi deposition
(3200Å to 3800Å)
N-type doping

➤ M. Zabala and A. Sánchez, IMB-CNM(CSIC)



CNM25 Technology Example

► 2.5- μm polySi-insulator-polySi (PiP) 1M twin-well CMOS process:

- 4-inch wafers
- 22-mm x 22-mm (484mm²) stepper reticle
- 8-mask layout design

► FEOL stages:

  - N and P wells
- Active areas
- PiP capacitor



POLY0 photolithography

➤ M. Zabala and A. Sánchez, IMB-CNM(CSIC)



CNM25 Technology Example

► 2.5- μm polySi-insulator-polySi (PiP) 1M twin-well CMOS process:

- 4-inch wafers
- 22-mm x 22-mm (484mm²) stepper reticle
- 8-mask layout design

► FEOL stages:

  - N and P wells
- Active areas
- PiP capacitor



PolySi etching
Sacrificial oxide stripping

➤ M. Zabala and A. Sánchez, IMB-CNM(CSIC)



CNM25 Technology Example

► 2.5- μm polySi-insulator-polySi (PiP) 1M twin-well CMOS process:

- 4-inch wafers
- 22-mm x 22-mm (484mm²) stepper reticle
- 8-mask layout design

► FEOL stages:

  - N and P wells
- Active areas
- PiP capacitor
- MOS gate



Gate-oxide growing (340Å to 390Å)

➤ M. Zabala and A. Sánchez, IMB-CNM(CSIC)



CNM25 Technology Example

► 2.5- μm polySi-insulator-polySi (PiP) 1M twin-well CMOS process:

- 4-inch wafers
- 22-mm x 22-mm (484mm²) stepper reticle
- 8-mask layout design

► FEOL stages:

  - N and P wells
- Active areas
- PiP capacitor
- MOS gate



PolySi deposition (4500Å to 5100Å)
POLY1 photolithography

➤ M. Zabala and A. Sánchez, IMB-CNM(CSIC)



CNM25 Technology Example

► 2.5- μm polySi-insulator-polySi (PiP) 1M twin-well CMOS process:

- 4-inch wafers
- 22-mm x 22-mm (484mm²) stepper reticle
- 8-mask layout design

► FEOL stages:

  - N and P wells
- Active areas
- PiP capacitor
- MOS gate



PolySi etching

➤ M. Zabala and A. Sánchez, IMB-CNM(CSIC)


CNM25 Technology Example

► 2.5- μm polySi-insulator-polySi (PiP) 1M twin-well CMOS process:

- 4-inch wafers
- 22-mm x 22-mm (484mm²) stepper reticle
- 8-mask layout design

► FEOL stages:

 - N and P wells
- Active areas
- PiP capacitor
- MOS gate
- MOS source and drain



NPLUS photolithography
N-type doping

➤ M. Zabala and A. Sánchez, IMB-CNM(CSIC)


CNM25 Technology Example

► 2.5- μm polySi-insulator-polySi (PiP) 1M twin-well CMOS process:

- 4-inch wafers
- 22-mm x 22-mm (484mm²) stepper reticle
- 8-mask layout design

► FEOL stages:

 - N and P wells
- Active areas
- PiP capacitor
- MOS gate
- MOS source and drain



➤ M. Zabala and A. Sánchez, IMB-CNM(CSIC)

CNM25 Technology Example

► 2.5- μm polySi-insulator-polySi (PiP) 1M twin-well CMOS process:




- 4-inch wafers
- 22-mm x 22-mm (484mm²) stepper reticle
- 8-mask layout design

► FEOL stages:

- N and P wells
- Active areas
- PiP capacitor
- MOS gate
- MOS source and drain

► BEOL stages:

- Interlevel oxide

   

TEOS* deposition (12000Å to 13000Å)
N⁺⁺(1 μm) and P⁺⁺(3 μm) D/S diffusion

*TEtraethyl O_rthoSilicate

► M. Zabala and A. Sánchez, IMB-CNM(CSIC)

CNM25 Technology Example

► 2.5- μm polySi-insulator-polySi (PiP) 1M twin-well CMOS process:




- 4-inch wafers
- 22-mm x 22-mm (484mm²) stepper reticle
- 8-mask layout design

► FEOL stages:

- N and P wells
- Active areas
- PiP capacitor
- MOS gate
- MOS source and drain

► BEOL stages:

- Interlevel oxide
- Contacts

   

WINDOW photolithography

➤ M. Zabala and A. Sánchez, IMB-CNM(CSIC)

CNM25 Technology Example

► 2.5- μm polySi-insulator-polySi (PiP) 1M twin-well CMOS process:



- 4-inch wafers
- 22-mm x 22-mm (484mm²) stepper reticle
- 8-mask layout design

► FEOL stages:

- N and P wells
- Active areas
- PiP capacitor
- MOS gate
- MOS source and drain

► BEOL stages:

- Interlevel oxide
- Contacts
- Metal

  

Al metalization
METAL photolithography

➤ M. Zabala and A. Sánchez, IMB-CNM(CSIC)

CNM25 Technology Example

► 2.5- μm polySi-insulator-polySi (PiP) 1M twin-well CMOS process:


- 4-inch wafers
- 22-mm x 22-mm (484mm²) stepper reticle
- 8-mask layout design

► FEOL stages:

- N and P wells
- Active areas
- PiP capacitor
- MOS gate
- MOS source and drain

► BEOL stages:

- Interlevel oxide
- Contacts
- Metal

 

Al etching

► M. Zabala and A. Sánchez, IMB-CNM(CSIC)

CNM25 Technology Example

► 2.5- μm polySi-insulator-polySi (PiP) 1M twin-well CMOS process:



- 4-inch wafers
- 22-mm x 22-mm (484mm²) stepper reticle
- 8-mask layout design

► FEOL stages:

- N and P wells
- Active areas
- PiP capacitor
- MOS gate
- MOS source and drain

► BEOL stages:

  - Interlevel oxide
- Contacts
- Metal
- Passivation and pads



Oxidation (4000Å)
Nitride deposition (4000Å)
CAPS photolithography

► M. Zabala and A. Sánchez, IMB-CNM(CSIC)

CNM25 Technology Example

► 2.5- μm polySi-insulator-polySi (PiP) 1M twin-well CMOS process:


- 4-inch wafers
- 22-mm x 22-mm (484mm²) stepper reticle
- 8-mask layout design

► FEOL stages:

- N and P wells
- Active areas
- PiP capacitor
- MOS gate
- MOS source and drain

► BEOL stages:

 
- Interlevel oxide
- Contacts
- Metal
- Passivation and pads



► M. Zabala and A. Sánchez, IMB-CNM(CSIC)


Modern Technologies

► Advanced **MOSFET** device structure

 

Modern Technologies

 - ▶ Advanced **MOSFET** device structure
- ▶ Device **isolation**




Pad oxide growth + nitride deposition




Pattern and etch Si_3N_4 and SiO_2



Trench etch into Si

 

 Deposition of trench filling oxide (No thermal growth!)



Oxide CMP polish step with stop on nitride



Field oxide recess (HF dip)

Removal of nitride layer (H_3PO_4)



Modern Technologies


- ▶ Advanced **MOSFET** device structure
- ▶ Device **isolation**
- ▶ **Cu** interconnections
 - Lower resistivity
 - Higher melting point
 - Lower thermal expansion
 - Lower electromigration

Classical Al metallisation


1) metal deposition



2) etching of metal lines

 

3) oxide gapfill + oxide CMP

 


Damascene Cu metallisation

1) etching of oxide trenches



2) metal deposition

 


3) metal CMP



Mixed-Signal Technology Modules


► CMOS process **options** for each IC application:

■ Twin vs **triple** well

 

▲ **Gate-bootstrapping** in SC circuits (e.g. input samplers, charge pumps)

▲ **Isolation** against substrate noise

 

Mixed-Signal Technology Modules

► CMOS process **options** for each IC application:

- Twin vs **triple** well
- Several MOSFET **threshold-voltage** families




Family	V_{TN}	V_{TP}	Purpose
	[V]	[V]	
LP	0.50	-0.55	+1.8-V low-leakage core
LV	0.33	-0.33	Low-voltage supply
TH	0.70	-0.63	+3.3-V I/O interface

e.g. 0.18- μm 1P6M CMOS technology

Mixed-Signal Technology Modules


► CMOS process **options** for each IC application:

   - Twin vs **triple** well
- Several MOSFET **threshold-voltage** families
- Metal-insulator-metal (**MIM**) and metal-oxide-metal (**MOM**) linear capacitors
- High-resistance polySi (**HIPO**) linear and low-TC resistors
- **Thick top metal** for high-Q RF inductors



Mixed-Signal Technology Modules


- ▶ CMOS process **options** for each IC application:
 - Twin vs **triple** well
 - Several MOSFET **threshold-voltage** families
 - Metal-insulator-metal (**MIM**) and metal-oxide-metal (**MOM**) linear capacitors
 - High-resistance polySi (**HIPO**) linear and low-TC resistors
 - **Thick top metal** for high-Q RF inductors
 - Linear **varactors** for continuous RF tuning
 - High-voltage (**HV**) and **LDMOS** transistors for power management
 - Lateral and vertical **bipolar** transistors for bandgap references
 - **Anti-reflective** coating and optimum **doping profiles** for CMOS image sensors (**CIS**)
 - Non-volatile memory (**NVM**) for chip ID, configuration, tuning...

 

▼ **Many** modules = higher mask/process **costs** + difficult circuit design **migration**

Hybrid-Packaging Alternatives


- ▶ Classic **wire-bonding** approach:

 

- **Monolithic** solution (signal integrity, production)
- Sensor needs to be CMOS **compatible**
- **Area** costs
- Wire-bonding costs for **large arrays**


Hybrid-Packaging Alternatives

► Classic **wire-bonding** approach:

 

- **Monolithic** solution (signal integrity, production)
- Sensor needs to be CMOS **compatible**
- **Area** costs
- Wire-bonding costs for **large arrays**


► **Bump-bonding** flip-chip:

 


- **Heterogeneous** sensor/CMOS technologies
- Sensor **area** can be reused for circuits
- **Back-side** sensing
- Wire-bonding costs for **large arrays**

Hybrid-Packaging Alternatives

 ► 3D stacking with through-Silicon vias (**TSV**):



 
- Height/diameter < 20
- Typ. diameter $50\mu\text{m}$ to $100\mu\text{m}$
- pF-range parasitic capacitance
- $< 1\text{-}\Omega$ series resistance



- **Heterogeneous** sensor/CMOS technologies
- Sensor **area** can be reused for circuits
- **Front-side** sensing
- Wire-bonding free


Hybrid-Packaging Alternatives

 ▶ 3D stacking with through-Silicon vias (TSV):



- Height/diameter < 20
- Typ. diameter $50\mu\text{m}$ to $100\mu\text{m}$
- pF-range parasitic capacitance
- $< 1\text{-}\Omega$ series resistance

 
▲ TSV downscaling by wafer chemical-mechanical polishing (CMP):



imec-int.com

IC Development


► Typical project **scheduling**:

 

▼ Alignment with foundry fixed **run calendar**


▼ Long design **iterations** (typ. 6M)

▼ **First** complete prototype >18M

 


CMOS Technology Costs

► Full-mask regular run

 

e.g. 0.15- μm 1P6M CMOS technology

 - Die size: < **625 mm²**
- Mask costs: **100 k€**
- Processing costs: **2 k€/wafer**
- Samples: > **50 die/wafer**
- Intended for **full production** (> 200 wafer/year)





CMOS Technology Costs

- ▶ **Full-mask** regular run
- ▶ Multi-project wafer (**MPW**) run

e.g. 0.15- μm 1P6M CMOS technology

  - Die size: $> 4 \text{ mm}^2$
- Mask and processing costs: **1 k€/mm²**
- Samples: < 100 **die**
- Intended for **prototyping**




CMOS Technology Costs

- ▶ **Full-mask** regular run
- ▶ Multi-project wafer (**MPW**) run
- ▶ Multi-layer mask (**MLM**) engineering run

e.g. 0.15- μm 1P6M CMOS technology

 - Die size: < **156 mm²**
- Mask costs: **25 k€**
- Processing costs: **2 k€/wafer** (6-wafer lots)
- Samples: > **200 die/wafer**
- Intended for **small series** (< 100 wafer/year)



CMOS Technology Costs



- ▶ **Full-mask** regular run
- ▶ Multi-project wafer (**MPW**) run
- ▶ Multi-layer mask (**MLM**) engineering run

e.g. 0.15- μm 1P6M CMOS technology

- Die size: < **69 mm²**
- Mask costs: **12 k€**
- Processing costs: **2 k€/wafer** (6-wafer lots)
- Samples: > **450 die/wafer**
- Intended for **small series** (< 100 wafer/year)

9-MLM

9 layer/mask
4-mask set

 
 


CMOS Technology Costs


- ▶ **Full-mask** regular run
- ▶ Multi-project wafer (**MPW**) run
- ▶ Multi-layer mask (**MLM**) engineering run
- ▶ Wafer-scale **stitching** run

e.g. 0.15- μm 1P6M CMOS technology

  - Die size: **150x150 mm²**
- Mask costs: **100 k€**
- Processing costs: **2 k€/wafer**
- Samples: **1 die/wafer**
- Intended for **limited series**
- **Low yield** (acceptable for imagers)




imagesensors.org

 

- 1 Evolution of CMOS Technologies
- 2 Trends in Analog and Mixed IC Design
- 3 A/D and D/A Conversion Principles
- 4 ADC and DAC Figures of Merit
- 5 Lab proposal

IC Design Scenario

► Synthesis vs analysis:

 

Specifications

Parameter	Comments	Spec.	Units
TR			mV _{pp}
CMR	Upper Lower	>4 <1	V
OR		>3	V _{op}
V _{dr}	±0	<10	mV _{rms}
P _d	V _{in} = 2.5V	<1.5	mW
G _{dc}		>60	dB
CMRR _{DC}		>50	dB
PSRR _{DC}	+	>50	dB
	-	>50	dB
SR	+	>1.5	V/μs
	-	>1.5	V/μs
t _b (1%)	V _{out} = 2 → 3V V _{out} = 3 → 2V	<1500 <1500	ns
f _{max}	V _{out} = OR	<1500	KHz
THD	V _{out} = OR/2@10KHz	<1	%
BW	-3dB		Hz
GBW		>1	MHz
Φ _m		>50	deg
V _{in}	100Hz to 10MHz	<1	mV _{rms}
Area		<0.025	mm ²


Synthesis

Circuit



Analysis

Schematics

 


Synthesis

Physical



Analysis

Layout

 


▼ EDA tools do **not** design ICs!

Analog vs Digital

► *If it can be done by digital, don't use analog!*

▼ Analog IC design is **complex**...

 - **Background** in physics, electronics, information and control theory, signal processing, communications
- Variety of **state-of-the-art** solutions
- High dependence from **technology**
- **Modeling** skills
- Complex **EDA** tools




Analog vs Digital

► *If it can be done by digital, don't use analog!*

▼ Analog IC design is **complex**...

- **Background** in physics, electronics, information and control theory, signal processing, communications
- Variety of **state-of-the-art** solutions
- High dependence from **technology**
- **Modeling** skills
- Complex **EDA** tools

▲ ...but still **necessary**!

 

Analog vs Digital



► *If it can be done by digital, don't use analog!*

▼ Analog IC design is **complex**...

- **Background** in physics, electronics, information and control theory, signal processing, communications
- Variety of **state-of-the-art** solutions
- High dependence from **technology**
- **Modeling** skills
- Complex **EDA** tools

▲ ...but still **necessary**!

  ► Most modern ICs are really **mixed-signal**



IC vs PCB

- ▶ What can mixed IC design offer compared to PCB?



IC vs PCB

► What can mixed IC design offer compared to PCB?

Good	Bad
▲ Small size and high density ▲ Complex systems ▲ High speed operation ▲ Low power consumption ▲ Heterogeneous SoC (A/D/RF/MEMS/Power) ▲ Low production costs	

IC vs PCB

► What can mixed IC design offer compared to PCB?

Good	Bad
▲ Small size and high density	▼ Low observability/controllability
▲ Complex systems	▼ Few device primitives
▲ High speed operation	▼ Technology variability (process and mismatching)
▲ Low power consumption	▼ Complex modeling
▲ Heterogeneous SoC (A/D/RF/MEMS/Power)	▼ High design costs (EDA/personnel)
▲ Low production costs	▼ High prototyping costs
	▼ Long design cycles



IC Flavors

- Each **application** may require a different IC solution:

	Full-custom
Density	
Flexibility	
Performance	
Design time	
EDA tools	
Prototype costs	
Target volume	High
Mixed-mode	A and D

- **Hand-drawn** geometry
- **All** layers customized
- Application-specific IC (**ASIC**) result
  
```
cnm25modn(w=28,
l=6,
mx=4,
my=2,
common_d=False,
common_g=False,
common_s=True)
```




IC Flavors

- Each **application** may require a different IC solution:

	Full-custom	Macro-cell
Density		
Flexibility		
Performance		
Design time		
EDA tools		
Prototype costs		
Target volume	High	High
Mixed-mode	A and D	A and D

- Configurable **IP** blocks (ADC, memory...)
- Automated **routing**
- **All** layers customized
- Still an **ASIC**

 


Magali 65-nm SoC for 4G communication with 22 IPs

IC Flavors

► Each **application** may require a different IC solution:

	Full-custom	Macro-cell	Standard-cell
Density			
Flexibility			
Performance			
Design time			
EDA tools			
Prototype costs			
Target volume	High	High	High
Mixed-mode	A and D	A and D	D

 - Gate level cells + automated **routing**
- Regular **floorplan**
- **All** layers customized
- Still an **ASIC**







IC Flavors

- Each **application** may require a different IC solution:

	Full-custom	Macro-cell	Standard-cell	Gate-array
Density				
Flexibility				
Performance				
Design time				
EDA tools				
Prototype costs				
Target volume	High	High	High	Medium
Mixed-mode	A and D	A and D	D	D

    - **Pre-built** transistors/gates/IPs
- **Only routing** layers customized
- **Structured** ASIC





IC Flavors

- Each **application** may require a different IC solution:

	Full-custom	Macro-cell	Standard-cell	Gate-array	FPGA
Density					
Flexibility					
Performance					
Design time					
EDA tools					
Prototype costs					
Target volume	High	High	High	Medium	Low
Mixed-mode	A and D	A and D	D	D	D (A)

- **Programmable** logic blocks
- **Programmable** routing
- Not an **ASIC**

Altera
Cyclone III

  

IC Flavors


- Each **application** may require a different IC solution:

	Full-custom	Macro-cell	Standard-cell	Gate-array	FPGA
Density					
Flexibility					
Performance					
Design time					
EDA tools					
Prototype costs					
Target volume	High	High	High	Medium	Low
Mixed-mode	A and D	A and D	D	D	D (A)

Full-Custom Design


▼ Fixed CMOS technology:

 - Materials and processes
- Vertical dimensions





▲ Mixed design space:

 - Circuit **topology**
- Device **horizontal sizing**
- Device **biasing**



$$C \propto M \times \left\{ \frac{WL}{W+L} \right\}$$


Width
Length
Multiplicity

  

Full-Custom Design

▼ Fixed CMOS technology:

 - Materials and processes
- Vertical dimensions





▲ Mixed design space:

- Circuit **topology**
- Device **horizontal sizing**
- Device **biasing**



  
$$R \propto \frac{1}{M} \times \frac{L}{W}$$



other device cases:

 
Number of turns
Inner **D**iameter
Spacing
Width



$$L = f(N, D, S, W)$$

Bulk Enhancement MOSFET


► Intrinsic and extrinsic model parts

 


▲ **Accurate** results from electrical simulation

▼ **Too complex** for hand design!

 ► Analytical (physical) vs numerical (fitting) modeling




Process	.MODEL MY_NMOS BSIM3V3 TYPE=N + VERSION=3.2 PARAMCHK=1 + NSUB=2.161E+19 NCH=1.280E+17 XJ=1.500E-07 LINT=7.639E-04 + WINT=3.669E-04 LL=0 LLN=0 LW=0 LWN=0 LWL=0 WL=-1.253E-10 + WLN=1 WW=-2.595E-07 WWN=4.475E-01 WWL=0 DWG=0 DWB=0 + TOX=3.800E-08 TOXM=3.800E-08 XT=1.000E-07 RDSW=3.580E+02 + PRWB=6.678E-03 PRWG=4.740E-04 WR=4.148E-01
Threshold voltage	+ VTH0=7.874E-01 K1=1.233E+03 K2=-6.791E-02 K3=8.227E+03 + K3B=-5.071E-01 W0=2.500E-06 NLX=0 DVT0=5.820E+00 DVT1=5.168E-01 + DVT2=-2.594E-01 DVTOW=0 DVT1W=5.300E+06 DVT2W=-3.200E-02 + A0=8.010E-01 B0=0 B1=0 A1=0 A2=1 AGS=1.006E-01 KETA=-1.385E-02
Mobility	+ MOBMOD=1 U0=6.020E+02 VSAT=1.746E+08 + UA=9.395E-07 UB=2.828E-15 UC=5.191E-08
Output resistance	+ DROUT=5.600E-01 PCLM=3.178E+03 PDIBLC1=4.811E+03 + PDIBLC2=8.600E-03 PDIBLCB=0 PSCBE1=4.240E+08 + PSCBE2=1.000E-05 PVAG=0 DELTA=1.000E-02
Subthreshold	+ CDSC=2.953E-02 CDSCB=7.380E-03 CDSCD=-2.864E-03 + NFACTOR=6.727E-01 CIT=0 VOFF=-6.277E-02 + DSUB=5.600E-01 ETA0=0 ETAB=-1.653E-01
Charge model	+ CAPMOD=3 DWC=3.669E-04 DLC=0 CLC=1.000E-07 + CLE=6.000E-01 CF=0 ELM=2 ACDE=1 MOIN=15 + NOFF=1 VOFFCV=0 XPART=6.000E-01 LLC=0 + LWC=0 LWLC=0 WLC=-1.253E-10 WWC=-2.595E-07 WWLC=0
Substrate	+ ALPHA0=2.725E-03 ALPHA1=-7.804E-01 BETA0=3.180E+01
Junction diode	+ JS=1.000E-04 JSW=0 NJ=1 IJTH=1.000E-01 + CJ=5.000E-04 MJ=5.000E-01 PB=1 + CJSW=5.000E-10 MJSW=3.300E-01 PBSW=1 + CJSWG=5.000E-10 MJSWG=3.300E-01 PBSWG=1
Overlap cap.	+ CGSO=0 CGDO=0 CGBD=0 CGSL=0 CGDL=0 CKAPPA=6.000E-01
Thermal model	+ TNOM=27 KT1=-1.100E-01 KT1L=0 KT2=2.200E-02 AT=3.300E+04 + UA1=4.310E-09 UB1=-7.610E-18 UC1=-5.600E-11 PRT=0 UTE=-1.5 + XTI=3 TPB=0 TPBSW=0 TPBSWG=0 TCJ=0 TCJSW=0 TCJSWG=0
Noise model	+ NOIMOD=1 KF=1.000E-17 AF=1.5 EF=1.5 NOIA=2.000E+29 + NOIB=2.000E+29 NOIC=2.000E+29 EM=4.100E+07
Scaling	+ XL=0 XW=0 PK1=1.711E-01 PK2=-6.688E-02 + PUA=6.246E-04 PUB=-3.418E-12 LUC=1.519E-05 + PUC=-5.063E-05 PAGS=2.532E-01 PRDSW=-1.071E+04 + WVSAT=0 PVSAT=-1.800E+05 PVTH0=-1.644E-01

 

Bulk Enhancement MOSFET

► Classic large signal I/V model:

 

Non linear

$$I_D = \begin{cases} \beta \left[(V_{GS} - V_{TH}) V_{DS} - \frac{1}{2} V_{DS}^2 \right] & V_{DS} \leq V_{DSsat} \\ \frac{\beta}{2} (V_{GS} - V_{TH})^2 [1 + \lambda (V_{DS} - V_{DSsat})] & V_{DS} \geq V_{DSsat} \end{cases}$$



Channel length modulation (CLM):
negligible for large signal, but critical in **small signal** $\lambda \propto \frac{1}{L}$

$$\beta \doteq M \frac{W}{L} K$$

$K = \mu C_{ox}$
Current factor


$$V_{DSsat} \doteq V_{GS} - V_{TH}$$

Pinch-off voltage

  

Bulk Enhancement MOSFET

► Classic large signal I/V model:

 

Non linear

$$I_D = \begin{cases} \beta \left[(V_{GS} - V_{TH}) V_{DS} - \frac{1}{2} V_{DS}^2 \right] & V_{DS} \leq V_{DSsat} \\ \frac{\beta}{2} (V_{GS} - V_{TH})^2 [1 + \lambda (V_{DS} - V_{DSsat})] & V_{DS} \geq V_{DSsat} \end{cases}$$

Channel length modulation (CLM):
negligible for large signal, but critical in **small signal** $\lambda \propto \frac{1}{L}$

$$\beta \doteq M \frac{W}{L} K$$


$K = \mu C_{ox}$
Current factor

$$V_{DSsat} \doteq V_{GS} - V_{TH}$$

Pinch-off voltage

▲ Simple enough for hand design


▼ Body effect in stacked circuits?
 
$$V_{TH} = V_{TH0} + \gamma \left(\sqrt{|2\Phi_F - V_{BS}|} - \sqrt{|2\Phi_F|} \right)$$


$$\gamma = \frac{\sqrt{2q\epsilon_{Si}N_{sub}}}{C_{ox}}$$

Body effect coefficient

▼ Asymmetrical D/S model!

 

▼ Subthreshold operation?


▼ Single expression wanted for all regions with continuous derivatives (small signal)...

Bulk Enhancement MOSFET

► EKV large signal I/V model:

ekv.epfl.ch

Enz
Krummenacher
Vittoz

 

$$F(x) \doteq \ln^2(1 + e^{\frac{x}{2}}) \equiv \begin{cases} e^x & x \ll 0 \\ \left(\frac{x}{2}\right)^2 & x \gg 0 \end{cases}$$

$$I_D = I_{DF} - I_{DR} = I_S \left[F\left(\frac{V_P - V_{SB}}{U_t}\right) - F\left(\frac{V_P - V_{DB}}{U_t}\right) \right]$$

Forward Reverse

■ Specific current

$$I_S \doteq 2n\beta U_t^2$$

Subthreshold slope
($1 < n < 2$)

$$M \frac{W}{L} \underbrace{\mu C_{ox}}_K$$

■ Pinch-off voltage

$$V_P \doteq \frac{V_{GB} - V_{TH}}{n} \equiv V_{sat}$$

■ Inversion coefficient

$$IC \doteq \frac{I_D}{I_S}$$


	Weak inversion (subthreshold) $V_{SB} \text{ and } V_{DB} \gg \frac{V_{GB} - V_{TH}}{n}$	Strong inversion $V_{SB} \text{ or } V_{DB} \ll \frac{V_{GB} - V_{TH}}{n}$
Conduction	$I_S e^{\frac{V_{GB} - V_{TH}}{nU_t}} \left(e^{-\frac{V_{SB}}{U_t}} - e^{-\frac{V_{DB}}{U_t}} \right)$ $ V_{DB} - V_{SB} \ll U_t$	$\beta \left[(V_{GB} - V_{TH}) - \frac{n}{2} (V_{DB} + V_{SB}) \right] (V_{DB} - V_{SB})$ $V_{SB} \text{ and } V_{DB} \ll \frac{V_{GB} - V_{TH}}{n}$
Saturation (forward)	$I_S e^{\frac{V_{GB} - V_{TH}}{nU_t}} e^{-\frac{V_{SB}}{U_t}} [1 + \lambda (V_{DB} - V_{SB})]$ $(V_{DB} - V_{SB}) \gg U_t$	$\frac{\beta}{2n} (V_{GB} - V_{TH} - nV_{SB})^2 [1 + \lambda (V_{DB} - V_{sat})]$ $V_{SB} \ll \frac{V_{GB} - V_{TH}}{n} \text{ and } V_{DB} \gg V_{sat}$

Bulk Enhancement MOSFET

► EKV large signal I/V model:


ekv.epfl.ch

Enz
Krummenacher
Vittoz

 

- ▲ **Simple** enough for hand design
- ▲ **Symmetrical** D/S expressions
- ▲ Explicit **body effect**
- ▲ **Single expression** from strong to weak inversion and from conduction to saturation
- ▲ **Continuous derivatives** for small signal parameters

 
Forward saturation example
(neglecting CLM):



$$I_D(V_{GB}, V_{SB}, V_{DB})|_{\text{PMOS}} \equiv -I_D(-V_{GB}, -V_{SB}, -V_{DB})|_{\text{NMOS}}$$

Bulk Enhancement MOSFET

 
► Classic small signal transconductance model:



Non-linear
operating point

Small signal
increments only
 
$$\begin{aligned} V_{GS} &= V_{GS0} + v_{gs} \\ V_{DS} &= V_{DS0} + v_{ds} \\ V_{BS} &= V_{BS0} + v_{bs} \\ I_D &= I_{D0} + i_d \end{aligned}$$



Linear
equivalent circuit

$$I_D = \begin{cases} \beta \left[(V_{GS} - V_{TH}) V_{DS} - \frac{1}{2} V_{DS}^2 \right] & V_{DS} \leq V_{DSsat} \\ \frac{\beta}{2} (V_{GS} - V_{TH})^2 [1 + \lambda (V_{DS} - V_{DSsat})] & V_{DS} \geq V_{DSsat} \end{cases}$$

$$V_{TH} = V_{TH0} + \gamma \left(\sqrt{|2\Phi_F - V_{BS}|} - \sqrt{|2\Phi_F|} \right)$$


$$\begin{aligned} g_m &\doteq \frac{\partial I_D}{\partial V_{GS}} \equiv \frac{i_d}{v_{gs}} \Big|_{v_{ds}=v_{bs}=0} \\ g_{ds} &\doteq \frac{\partial I_D}{\partial V_{DS}} \equiv \frac{i_d}{v_{ds}} \Big|_{v_{gs}=v_{bs}=0} \\ g_{mb} &\doteq \frac{\partial I_D}{\partial V_{BS}} \equiv \frac{i_d}{v_{bs}} \Big|_{v_{gs}=v_{ds}=0} \end{aligned}$$

$$g_m \simeq \begin{cases} \beta V_{DS} & V_{DS} \leq V_{DSsat} \\ \beta (V_{GS} - V_{TH}) \equiv \sqrt{2\beta I_D} & V_{DS} \geq V_{DSsat} \end{cases}$$

▲ Analog circuits biased through current sources → **op** as a function of **drain current**

Bulk Enhancement MOSFET

 
► Classic small signal transconductance model:



Non-linear
operating point

Small signal
increments only
 
$$\begin{aligned} V_{GS} &= V_{GS0} + v_{gs} \\ V_{DS} &= V_{DS0} + v_{ds} \\ V_{BS} &= V_{BS0} + v_{bs} \\ I_D &= I_{D0} + i_d \end{aligned}$$



Linear
equivalent circuit

$$I_D = \begin{cases} \beta \left[(V_{GS} - V_{TH}) V_{DS} - \frac{1}{2} V_{DS}^2 \right] & V_{DS} \leq V_{DSsat} \\ \frac{\beta}{2} (V_{GS} - V_{TH})^2 [1 + \lambda (V_{DS} - V_{DSsat})] & V_{DS} \geq V_{DSsat} \end{cases}$$

$$V_{TH} = V_{TH0} + \gamma \left(\sqrt{|2\Phi_F - V_{BS}|} - \sqrt{|2\Phi_F|} \right)$$


$$\begin{aligned} g_m &\doteq \frac{\partial I_D}{\partial V_{GS}} \equiv \frac{i_d}{v_{gs}} \Big|_{v_{ds}=v_{bs}=0} \\ g_{ds} &\doteq \frac{\partial I_D}{\partial V_{DS}} \equiv \frac{i_d}{v_{ds}} \Big|_{v_{gs}=v_{bs}=0} \\ g_{mb} &\doteq \frac{\partial I_D}{\partial V_{BS}} \equiv \frac{i_d}{v_{bs}} \Big|_{v_{gs}=v_{ds}=0} \end{aligned}$$

$$g_{ds} \simeq \begin{cases} \beta (V_{GS} - V_{TH}) & V_{DS} \leq V_{DSsat} \\ \frac{\beta}{2} (V_{GS} - V_{TH})^2 \lambda \equiv \lambda I_D & V_{DS} \geq V_{DSsat} \end{cases}$$

▲ Analog circuits biased through current sources → **op** as a function of **drain current**

Bulk Enhancement MOSFET

 
► Classic small signal transconductance model:



Non-linear
operating point

Small signal
increments only
 
$$\begin{aligned} V_{GS} &= V_{GS0} + v_{gs} \\ V_{DS} &= V_{DS0} + v_{ds} \\ V_{BS} &= V_{BS0} + v_{bs} \\ I_D &= I_{D0} + i_d \end{aligned}$$



Linear
equivalent circuit

$$I_D = \begin{cases} \beta \left[(V_{GS} - V_{TH}) V_{DS} - \frac{1}{2} V_{DS}^2 \right] & V_{DS} \leq V_{DSsat} \\ \frac{\beta}{2} (V_{GS} - V_{TH})^2 [1 + \lambda (V_{DS} - V_{DSsat})] & V_{DS} \geq V_{DSsat} \end{cases}$$

$$V_{TH} = V_{TH0} + \gamma \left(\sqrt{|2\Phi_F - V_{BS}|} - \sqrt{|2\Phi_F|} \right)$$

$$g_m \doteq \frac{\partial I_D}{\partial V_{GS}} \equiv \frac{i_d}{v_{gs}} \Big|_{v_{ds}=v_{bs}=0}$$

$$g_{ds} \doteq \frac{\partial I_D}{\partial V_{DS}} \equiv \frac{i_d}{v_{ds}} \Big|_{v_{gs}=v_{bs}=0}$$

$$g_{mb} \doteq \frac{\partial I_D}{\partial V_{BS}} \equiv \frac{i_d}{v_{bs}} \Big|_{v_{gs}=v_{ds}=0}$$


$$g_{mb} \equiv \eta g_m$$

$$\eta = \frac{\gamma}{2\sqrt{|2\Phi_F - V_{BS}|}}$$

▼ **Asymmetrical** parameters and non-explicit expressions...

Bulk Enhancement MOSFET

 
► EKV small signal transconductance model:



Non-linear
operating point

Small signal
increments only
 
$$\begin{aligned} V_{GB} &= V_{GB0} + v_{gb} \\ V_{DB} &= V_{DB0} + v_{db} \\ V_{SB} &= V_{SB0} + v_{sb} \\ I_D &= I_{D0} + i_d \end{aligned}$$



Linear
equivalent circuit


$$g_{mg} \doteq \frac{\partial I_D}{\partial V_{GB}} \equiv \left. \frac{i_d}{v_{gb}} \right|_{v_{sb}=v_{db}=0} \quad g_{md} \doteq \frac{\partial I_D}{\partial V_{DB}} \equiv \left. \frac{i_d}{v_{db}} \right|_{v_{gb}=v_{sb}=0}$$

$$g_{ms} \doteq -\frac{\partial I_D}{\partial V_{SB}} \equiv -\left. \frac{i_d}{v_{sb}} \right|_{v_{gb}=v_{db}=0} \equiv n g_{mg}$$

	Weak inversion (subthreshold)	Strong inversion
Conduction	$g_{mg} = \frac{I_D}{nU_t}$ $g_{ms} = \frac{I_{DF}}{U_t}$ $g_{md} = \frac{I_{DR}}{U_t}$	$g_{mg} = \beta (V_{DB} - V_{SB})$ $g_{ms} = \sqrt{2n\beta I_{DF}}$ $g_{md} = \sqrt{2n\beta I_{DR}}$
Saturation (forward)	$g_{mg} = \frac{I_D}{nU_t}$ $g_{ms} = \frac{I_D}{U_t}$ $g_{md} = \lambda I_D$	$g_{mg} = \sqrt{\frac{2\beta I_D}{n}}$ $g_{ms} = \sqrt{2n\beta I_D}$ $g_{md} = \lambda I_D \propto \frac{1}{L}$

Bulk Enhancement MOSFET

 
► EKV small signal transconductance model:



Non-linear
operating point

Small signal
increments only
 
$$\begin{aligned} V_{GB} &= V_{GB0} + v_{gb} \\ V_{DB} &= V_{DB0} + v_{db} \\ V_{SB} &= V_{SB0} + v_{sb} \\ I_D &= I_{D0} + i_d \end{aligned}$$



Linear
equivalent circuit

$$g_{mg} \doteq \frac{\partial I_D}{\partial V_{GB}} \equiv \frac{i_d}{v_{gb}} \Big|_{v_{sb}=v_{db}=0} \quad g_{md} \doteq \frac{\partial I_D}{\partial V_{DB}} \equiv \frac{i_d}{v_{db}} \Big|_{v_{gb}=v_{sb}=0}$$

$$g_{ms} \doteq -\frac{\partial I_D}{\partial V_{SB}} \equiv -\frac{i_d}{v_{sb}} \Big|_{v_{gb}=v_{db}=0} \equiv n g_{mg}$$


► Equivalence between models:

$$g_m \doteq \frac{\partial I_D}{\partial V_{GS}} \equiv g_{mg}$$

$$g_{mb} \doteq \frac{\partial I_D}{\partial V_{BS}} \equiv g_{ms} - g_{mg} - g_{md}$$


$$g_{ds} \doteq \frac{\partial I_D}{\partial V_{DS}} \equiv g_{md}$$

▲ Continuity between operating regions:

 

Bulk Enhancement MOSFET

► Quasi-static transcapacitance model:

 


Small signal
increments only

$$\begin{aligned} V_{GB} &= V_{GB0} + v_{gb} \\ V_{DB} &= V_{DB0} + v_{db} \\ V_{SB} &= V_{SB0} + v_{sb} \end{aligned}$$

$$c_{xy} \doteq \left. \frac{\partial Q_X}{\partial V_Y} \right|_{v_{rest}=0}$$

$$c_{xy} \neq c_{yx}$$

Non-reciprocal!


 


► Input only elements:

■ Gate oxide cap.


$$3.9 (\text{SiO}_2) \rightarrow \epsilon_r \epsilon_o$$
  
$$C_{ox} \doteq \frac{\epsilon_{ox}}{t_{ox}} WL$$



Bulk Enhancement MOSFET

Small signal noise model:

 

Thermal (white) component:

$$\frac{di_{nth}^2}{df} = 4KTg_{ms}K_{th} \quad K_{th} = \begin{cases} 1 & \text{w.i. and s.i. conduction} \\ \frac{1}{2} \text{ or } \frac{2}{3} & \text{w.i. or s.i. saturation} \end{cases}$$

$$U_t = \frac{KT}{q}$$

Flicker (pink) component:

$$\frac{dv_{nfk}^2}{df} = \frac{K_{fk}}{WL} \frac{1}{f}$$


Technology dependent (NMOS >> PMOS)

Memory effect

Uncorrelated phenomena:

$$\frac{di_{ntot}^2}{df} = 4KTg_{ms}K_{th} + g_{mg}^2 \frac{K_{fk}}{WL} \frac{1}{f}$$


Power spectral density (PSD) statistics:

 

$$f_c \doteq \frac{g_{mg}^2}{g_{ms}} \frac{K_{fk}}{K_{th}} \frac{1}{4KTWL}$$

Bulk Enhancement MOSFET

Small signal noise model:

 

Thermal (white) component:

$$\frac{di_{nth}^2}{df} = 4KTg_{ms}K_{th} \quad K_{th} = \begin{cases} 1 & \text{w.i. and s.i. conduction} \\ \frac{1}{2} \text{ or } \frac{2}{3} & \text{w.i. or s.i. saturation} \end{cases}$$

$$U_t = \frac{KT}{q}$$

Flicker (pink) component:

$$\frac{dv_{nfk}^2}{df} = \frac{K_{fk}}{WL} \frac{1}{f}$$

Technology dependent (NMOS >> PMOS)

Memory effect

Noise-aware analog IC design:

Signal-to-noise ratio

$$SNR \doteq \frac{V_{max}^2}{\int_{BW} \frac{dv_{ntot}^2}{df} df}$$

Signal full scale

$$\frac{di_{nth}^2}{df} = 4KTg_{ms}K_{th} + g_{mg}^2 \frac{K_{fk}}{WL} \frac{1}{f}$$

$$\frac{dv_{ntot}^2}{df} = \frac{4KTnK_{th}}{g_{mg}} + \frac{K_{fk}}{WL} \frac{1}{f}$$

$\propto I_D$ or $\sqrt{I_D}$

Dynamic Range

Power

▼ Low-power circuit design



Dynamic Range

Area

▼ Circuit design scalability

Bulk Enhancement MOSFET

► Extrinsic D/S diffusion diodes:

  

■ Geometry parameters:

$$\begin{cases} A_D = WL_D & \text{Area} \\ P_D = 2(W + L_D) & \text{Perimeter} \end{cases}$$

$$A_J = \underbrace{A_D}_{\text{Bottom plate}} + \underbrace{P_D X_D}_{\text{Side walls}}$$

■ Reverse leakage current:

$$I_D = A_D JS \left(e^{-\frac{V_{DB}}{U_t}} - 1 \right) + P_D X_D JSW \left(e^{-\frac{V_{DB}}{U_t}} - 1 \right)$$

■ Depletion capacitance:

$$C_D = A_D \frac{C_J}{\left(1 - \frac{V_{DB}}{P_B}\right)^{M_J}} + P_D X_D \frac{C_{JSW}}{\left(1 - \frac{V_{DB}}{P_{BSW}}\right)^{M_{JSW}}}$$


EKV Model Extraction

➤ M.Baucher et al.


An Efficient Parameter Extraction Methodology for the EKV MOST Model
IEEE ICMTS, Mar 1996

doi.org/10.1109/ICMTS.1996.535636

 ➤ **Sequential** methodology to minimize errors:



 ➤ W/L array of transistors to adjust model scalability




EKV Model Extraction

➤ M.Baucher et al.


An Efficient Parameter Extraction Methodology for the EKV MOST Model
IEEE ICMTS, Mar 1996

doi.org/10.1109/ICMTS.1996.535636

 ➤ **Sequential** methodology to minimize errors:



 ➤ W/L array of transistors to adjust model scalability




EKV Model Extraction

➤ M.Baucher et al.

An Efficient Parameter Extraction Methodology for the EKV MOST Model
IEEE ICMTS, Mar 1996

doi.org/10.1109/ICMTS.1996.535636

► e.g. **specific-current** estimation:

 

$$\frac{g_{ms} \times U_t}{I_D} = \frac{1}{\sqrt{\frac{1}{4} + IC + \frac{1}{2}}} = \begin{cases} 1 & IC \ll 1 \\ 0.618 & IC \equiv 1 \end{cases}$$

EKV Model Extraction


➤ M.Baucher et al.

An Efficient Parameter Extraction Methodology for the EKV MOST Model

IEEE ICMTS, Mar 1996



doi.org/10.1109/ICMTS.1996.535636

➤ e.g. **specific-current** estimation:

 

$$\frac{g_{ms} \times U_t}{I_D} = \frac{1}{\sqrt{\frac{1}{4} + IC + \frac{1}{2}}} = \begin{cases} 1 & IC \ll 1 \\ 0.618 & IC \equiv 1 \end{cases}$$



➤ e.g. **threshold-voltage** estimation:

  

$$I_B = \frac{I_S}{2} = n\beta U_t^2$$

Passive Components

► Coplanar capacitors:

  

 C.P.Yuan and T.N.Trick
A Simple Formula for the Estimation of the Capacitance of Two-Dimensional Interconnects in VLSI Circuits
 IEEE Electron Device Letters, 3(12):391-3, Dec 1982
doi.org/10.1109/EDL.1982.25610

- **Overlap + fringing** capacitance:

Overlap + fringing capacitance:

Electrical permittivity [F/m]

$$C = M \left[\frac{\epsilon}{H} WL + \frac{4\pi\epsilon(W+L)}{\ln\left(1 + \frac{2H}{T} + \sqrt{\frac{2H}{T}\left(\frac{2H}{T} + 2\right)}\right)} \right]$$

$$C = M [C_{ua}A + C_{up}P] \quad \left\{ \begin{array}{l} C_{ua} \text{ [F/m}^2\text{]} \\ C_{up} \text{ [F/m]} \end{array} \right. \begin{array}{l} \text{Process} \\ \text{dependent} \end{array}$$

- Typ. available **CMOS** structures:



available **CMOS** structures:

	C_{ua} [fF/ μm^2]	Voltage linearity	Temp. indep.
MOS	>1		
PiP or MiM PolySi-insulator-PolySi Metal-insulator-Metal	1~10		

Sandwich techniques...

Passive Components

► Serpentine resistors:

  

■ Square resistance:

$$R_{\square} \doteq \frac{\rho}{H} \quad [\Omega/\square]$$

$$R = N \frac{L}{W} R_{\square}$$

Process dependent

Design aspect ratio
e.g. $\frac{L}{W} = 8.5 \square$

■ Typ. available CMOS structures:

	$R_{\square}$ [Ω/□]	Voltage linearity	Temp. indep.
Well	~1k		
Diffusion	~100		
PolySi	~10		
Metal	~1m		
HiPo	1k~10k		

Highly
resistive
PolySi


Technological Mismatching

► Statistical Gaussian model:

General
Pelgrom Law

$$\sigma^2(\Delta P) = \underbrace{\frac{A_P^2}{WL}}_{\text{Local e.g. dopant non-uniformity}} + \underbrace{B_P^2 D}_{\text{Global e.g. thickness gradient}}$$
 
$$\sigma(\Delta P) \simeq \frac{A_P}{\sqrt{WL}} \quad \text{CMOS process dependent}$$



► M.J.M. Pelgrom et al.
Matching Properties of MOS Transistors
 IEEE Journal Solid-State Circuits, 24(5):1433-9, Oct 1989
doi.org/10.1109/JSSC.1989.572629

Technological Mismatching

► Statistical Gaussian model:

General Pelgrom Law

$$\sigma^2(\Delta P) = \underbrace{\frac{A_P^2}{WL}}_{\text{Local e.g. dopant non-uniformity}} + \underbrace{B_P^2 D}_{\text{Global e.g. thickness gradient}}$$

Standard deviation

$$\sigma(\Delta P) \simeq \frac{A_P}{\sqrt{WL}}$$

CMOS process dependent


► e.g. MOS differential pair:

$$V_{off} \doteq V_{inp} - V_{inn} |_{I_{D1} \equiv I_{D2}}$$

small-signal uncorrelated phenomena

$$\sigma^2(V_{off}) = \sigma^2(\Delta V_{TH}) + \frac{\sigma^2(\Delta \beta)}{g_{m0}^2}$$
 
$$\sigma(V_{off}) \simeq \sigma(\Delta V_{TH}) \simeq \frac{A_{VTH}}{\sqrt{(WL)_{1,2}}}$$



► M.J.M. Pelgrom et al.
Matching Properties of MOS Transistors
 IEEE Journal Solid-State Circuits, 24(5):1433-9, Oct 1989
doi.org/10.1109/JSSC.1989.572629

Technological Mismatching

► Statistical Gaussian model:

General Pelgrom Law

$$\sigma^2(\Delta P) = \underbrace{\frac{A_P^2}{WL}}_{\text{Local e.g. dopant non-uniformity}} + \underbrace{B_P^2 D}_{\text{Global e.g. thickness gradient}}$$

Standard deviation

$$\sigma(\Delta P) \simeq \frac{A_P}{\sqrt{WL}}$$


CMOS process dependent

► e.g. MOS current mirror:


small-signal uncorrelated phenomena

$$\sigma^2(\Delta I_D) = \sigma^2(\Delta \beta) + g_{mg}^2 \sigma^2(\Delta V_{TH})$$
 
$$\sigma^2\left(\frac{\Delta I_D}{I_D}\right) = \frac{1}{WL} \left[\left(\frac{A_\beta}{\beta}\right)^2 + \left(\frac{g_{mg}}{I_D}\right)^2 A_{VTH}^2 \right]$$



 
► M.J.M. Pelgrom et al.
Matching Properties of MOS Transistors
 IEEE Journal Solid-State Circuits, 24(5):1433-9, Oct 1989
doi.org/10.1109/JSSC.1989.572629



► Typically, V_{TH} mismatch is dominant...


Mixed IC Design

 - ▶ Must deal with several **hierarchy** and **abstraction** levels





Mixed IC Design

 - ▶ Must deal with several **hierarchy** and **abstraction** levels



Mixed IC Design

 
 
- ▶ Must deal with several **hierarchy** and **abstraction** levels
- ▶ **Combining** abstraction levels during design



- ▲ Simulation **speed up**
- ▲ Study of circuit **non-ideal** effects
- ▼ **Multi-level** and **multi-domain** simulation needed (single engine or glue approach)


IC Optimization

▲ Quantitative design comparison

  


IC Optimization

▲ Quantitative design comparison

 

 - **Power** consumption (lifetime, range...)
- **Silicon area** (costs, packaging...)




► Circuit **specific**...

$$FOM_{OpAmp} \equiv \begin{cases} \frac{C_{load}SR}{P_D} & \text{e.g. line buffer} \\ \frac{1}{P_D v_{neq}^2 A_{Si}} & \text{e.g. pre-amplifier} \\ \frac{C_{load}GBW}{P_D} & \text{e.g. RF amplifier} \end{cases}$$


Impact of Technology Scaling

 - ▼ Increase of **process variability**
demands robust design techniques



Impact of Technology Scaling

 - ▼ Increase of **process variability** demands robust design techniques
- ▼ **Supply-voltage** downscaling can reduce signal dynamic range or require larger area




Thermal noise:

$$v_{nout}^2 \equiv \frac{KT}{C_s}$$

Dynamic range:
 
$$DR \doteq \left(\frac{V_{FS}}{v_{nout}} \right)^2 \propto V_{DD}^2 C_s$$




Impact of Technology Scaling

- ▼ Increase of **process variability** demands robust design techniques
- ▼ **Supply-voltage** downscaling can reduce signal dynamic range or require larger area
- ▼ **Matching** parameters do rule area savings vs circuit precision

$$\sigma(\Delta V_{TH}) \simeq \frac{A_{VTH}}{\sqrt{MWL}}$$

$$A_{VTH} = \sqrt{2} \frac{q \sqrt{N_A X_D}}{C_{ox}} \quad \begin{array}{l} \text{Depletion layer} \\ 1/t_{ox} \end{array}$$

 Rule of thumb: $A_{VTH} \sim 1 \text{mV}\mu\text{m} \times t_{ox}[\text{nm}]$





Impact of Technology Scaling

- ▼ Increase of **process variability** demands robust design techniques
- ▼ **Supply-voltage** downscaling can reduce signal dynamic range or require larger area
- ▼ **Matching** parameters do rule area savings vs circuit precision
- ▼ **Noise** statistics (time/freq) may be modified at atomic scale

$$\frac{dv_{nfk}^2}{df} = \frac{K_{fk}}{MWL} \frac{1}{f}$$

Classic flicker "macro" noise PSD

  


Modern Trends

- **All-MOS** techniques for circuit implementation

e.g. MOS resistive circuit (**MRC**):

 supposing matched devices operating in strong inversion and non-saturation:



- ▲ **Compact** area
- ▲ **Tunable** resistance
- ▼ **Technology sensitivity**
- ▼ **Distortion** due to worse **mismatching**


$$I_p = \beta \left[V_{tun1} - V_{TO} - \frac{n}{2} \left(\frac{V_{in}}{2} \right) \right] \left(\frac{V_{in}}{2} \right) + \beta \left[V_{tun2} - V_{TO} - \frac{n}{2} \left(-\frac{V_{in}}{2} \right) \right] \left(-\frac{V_{in}}{2} \right)$$

$$\left. \begin{aligned} I_p &= \beta \left(V_{tun1} - V_{tun2} - n \frac{V_{in}}{2} \right) \frac{V_{in}}{2} \\ I_n &= \beta \left(V_{tun2} - V_{tun1} - n \frac{V_{in}}{2} \right) \frac{V_{in}}{2} \end{aligned} \right\} \quad I_{in} = I_p - I_n = \beta (V_{tun1} - V_{tun2}) V_{in}$$



$$R \equiv \frac{1}{\beta (V_{tun1} - V_{tun2})}$$

Modern Trends

 - ▶ **All-MOS** techniques for circuit implementation
- ▶ **IC-based low-power** circuits
 - Low-current
 - Low-voltage


  
$$IC_X = \frac{I_{DX}}{I_{SX}} \propto \frac{I_{bias}}{(W/L)_X}$$




- Simple bias design by **current** and **sizing** selection
- Independent from **technology** if $I_{bias} \propto I_S = 2n\beta U_t^2$


Modern Trends

- ▶ **All-MOS** techniques for circuit implementation
- ▶ **IC-based low-power** circuits
 - Low-current
 - Low-voltage
- ▶ **Time/frequency** domain processing

e.g. **all-digital** flash ADC:

 

 
- ▲ Benefit of **high-speed** CMOS technologies
- ▼ **Non-linearity**
- ▼ Technology **sensitivity**



Modern Trends

- ▶ **All-MOS** techniques for circuit implementation
- ▶ **IC-based low-power** circuits
 - Low-current
 - Low-voltage
- ▶ **Time/frequency** domain processing
- ▶ **Digitally assisted** analog minimalist

 e.g. dynamic element matching (**DEM**) in SC flash DAC:




▼ Capacitor mismatching = binary weight non-linearity = **harmonic distortion**

▼ Increase of **circuit area** according to **Pelgrom's Law** $\sigma\left(\frac{\Delta C}{C}\right) \propto \frac{1}{\sqrt{WL}}$

Modern Trends

- ▶ **All-MOS** techniques for circuit implementation
- ▶ **IC-based low-power** circuits
 - Low-current
 - Low-voltage
- ▶ **Time/frequency** domain processing
- ▶ **Digitally assisted** analog minimalist

 e.g. dynamic element matching (**DEM**) in SC flash DAC:




- ▲ Thermometric scrambling = harmonic **power spreading**
- ▲ Frequency selective algorithm = **mismatch shaping**
- ▲ **Dynamic range** improvement (or **silicon area** saving)

Modern Trends

- ▶ **All-MOS** techniques for circuit implementation
- ▶ **IC-based low-power** circuits
 - Low-**current**
 - Low-**voltage**
- ▶ **Time/frequency** domain processing
- ▶ **Digitally assisted** analog minimalist
- ▶ **Technology independent** tuning strategies

e.g. **master-slave**
tuning strategy:

 


- ▲ **PVT** (process, supply voltage, temperature) compensation
- ▼ **Area** and **power** overheads


- 1 Evolution of CMOS Technologies
- 2 Trends in Analog and Mixed IC Design
- 3 A/D and D/A Conversion Principles
- 4 ADC and DAC Figures of Merit
- 5 Lab proposal

Signal Domains

 - ▶ **Analog** is related with external world, like:
 - Sensor read-out
 - Wireless RF signal
- ▶ **Digital** is common inside electronic systems, like:
 - Computation
 - Stored memory




e.g. switched-capacitor (SC) filters

 


		Amplitude	
		Continuous	Discrete
Time	Continuous	Analog	Quantized
	Discrete	Sampled	Digital

 e.g. pulse-width
modulation (PWM)
in Class-D audio
amplifiers




Signal Domains

 - ▶ **Analog** is related with external world, like:
 - Sensor read-out
 - Wireless RF signal
- ▶ **Digital** is common inside electronic systems, like:
 - Computation
 - Stored memory
- ▶ **Intermediate** domains present in A/D and D/A interfaces
- ▶ Always finite **dynamic range** and **bandwidth**!



Quantization

 - ▶ Intrinsic error called **quantization noise**
- ▶ **Uniform** distribution probability
- ▶ Signal **uncorrelated**




estimated power:

$$Q_N = \frac{1}{\Delta} \int_{-\frac{\Delta}{2}}^{+\frac{\Delta}{2}} \epsilon^2 d\epsilon = \frac{1}{\Delta} \frac{\epsilon^3}{3} \Big|_{-\frac{\Delta}{2}}^{+\frac{\Delta}{2}} = \frac{\Delta^2}{12} \quad [\text{rms}]$$

independent from sampling frequency

Quantization

 
- ▶ Intrinsic error called **quantization noise**
- ▶ **Uniform** distribution probability
- ▶ Signal **uncorrelated**
- ▶ **N-bit** quantization (2^N-1 decision levels)
- ▶ **Harmonic** signal full-scale occupancy



estimated power:


$$QN = \frac{\Delta^2}{12} \quad [\text{rms}]$$
 
$$A_{FS} = 2^N \Delta \quad [\text{peak-to-peak}]$$



Quantization

 - ▶ Intrinsic error called **quantization noise**
- ▶ **Uniform** distribution probability
- ▶ Signal **uncorrelated**
- ▶ **N-bit** quantization ($2^N - 1$ decision levels)
- ▶ **Harmonic** signal full-scale occupancy
- ▶ Signal-to-quantization-noise **ratio**



estimated power:

$$QN = \frac{\Delta^2}{12} \quad [\text{rms}]$$

$$A_{FS} = 2^N \Delta \quad [\text{peak-to-peak}]$$


harmonic analysis:

$$S_{max} = \left(\frac{A_{FS}}{2\sqrt{2}} \right)^2 \quad [\text{rms}]$$

$$SQNR_{max} \doteq \frac{S_{max}}{QN} = (2^N \sqrt{1.5})^2$$


$$SQNR_{max} = 6.02N + 1.76 \quad [\text{dB}]$$
 
$$\pm 1 \text{ bit} \equiv \pm 6 \text{ dB}$$



Quantization

 - ▶ Intrinsic error called **quantization noise**
- ▶ **Uniform** distribution probability
- ▶ Signal **uncorrelated**
- ▶ **N-bit** quantization (2^N-1 decision levels)
- ▶ **Harmonic** signal full-scale occupancy
- ▶ Signal-to-quantization-noise **ratio**
- ▶ **Dynamic range** considerations



Only when **no distortion** is considered: $DR \equiv SQNR_{max}$

Sampling

► Nyquist rate

$$f_{nyq} = 2BW$$



► Sub-Nyquist rate generates **aliasing**

- Signal distortion
- Noise folding

► Oversampling relaxes **pre-filter** sharpness and stop-band attenuation

▲ More **compact circuits**



▼ Higher **clock frequencies**

  


Sampling

- ▶ Switched capacitor **sampler** model

- ▶ **Thermal noise** equivalent circuit

  

$$\frac{dv_{nin}^2}{df} = 4KTR_s$$

 

$$BW = \frac{1}{2\pi R_s C_s}$$

$$v_{nout}^2 = \frac{\pi}{2} \frac{1}{2\pi R_s C_s} 4KTR_s$$


- ▲ Capacitance only driven design (**KT/C**)

- ▼ Large **passive** devices

- ▼ Low **impedance** loads

$$v_{nout}^2 \equiv \frac{KT}{C_s}$$
 
$$DR \propto \frac{1}{v_{nout}^2} \propto C_s \dots +3\text{dB/oct} \\ +0.5\text{bit/oct}$$





Sampling



- ▶ Switched capacitor **sampler** model

- ▶ **Clock jitter** causes amplitude errors

- ▶ **Harmonic analysis**

  
  
$$\epsilon \simeq \frac{dV_{in}}{dt} \Delta t_s$$



$$V_{in} = \frac{A_{FS}}{2} \sin(2\pi BWt)$$

$$\epsilon = A_{FS}\pi BW \cos(2\pi BWt)\Delta t_s$$


estimated power:

$$JN = (\sigma_j A_{FS}\pi BW)^2 \left[2BW \int_0^{\frac{1}{2BW}} \cos^2(2\pi BWt) dt \right] = \frac{1}{2} (\sigma_j A_{FS}\pi BW)^2$$

$$\int_0^{\pi} \cos^2(x) dx = \frac{\pi}{2}$$

Sampling

 - ▶ Switched capacitor **sampler** model
- ▶ **Clock jitter** causes amplitude errors
- ▶ **Harmonic** analysis




$$JN = \frac{1}{2}(\sigma_j A_{FS} \pi BW)^2$$

if jitter effect is **dominant**:

$$SJNR_{max} = 2 \left(\frac{A_{FS}/2\sqrt{2}}{\sigma_j A_{FS} \pi BW} \right)^2 = \frac{1}{(2\sigma_j \pi BW)^2}$$

–6dB/oct
–1bit/oct

 


▲ Negligible for **low frequency**

▼ **High accuracy** clock generator



Sampling and Quantization

 - Constant (**white**) error spectrum profile



Sampling and Quantization

  - Constant (**white**) error spectrum profile




Sampling and Quantization

- Constant (**white**) error spectrum profile

$$QN(f) = \frac{\Delta^2/12}{f_s/2} = \frac{1}{6} \frac{\Delta^2}{f_s} \quad [\text{W/Hz}]$$

- **Spread** across spectrum ($f_s/2$)

 

Sampling and Quantization

- ▶ Constant (**white**) error spectrum profile

$$QN(f) = \frac{\Delta^2/12}{f_s/2} = \frac{1}{6} \frac{\Delta^2}{f_s} \quad [\text{W/Hz}]$$


- ▶ **Spread** across spectrum ($f_s/2$)

- ▶ **Oversampling** ratio

$$OSR \doteq \frac{f_s}{f_{nyq}} \equiv \frac{f_s}{2BW}$$

- ▲ Lower **in-band** noise

- ▼ Higher **clock** frequencies

 


$$QN = \frac{\Delta^2}{12} \frac{1}{OSR}$$

$$SQNR_{max} = \left(2^N \sqrt{1.5}\right)^2 OSR$$







$$SQNR_{max} = 6.02N + 1.76 + 10 \log OSR \quad [\text{dB}]$$

+3dB/oct
 +0.5bit/oct

 


Reconstruction

      - ▶ Signal **interpolation**
from discrete to
continuous time
- ▶ Zero-order **hold**
(S/H like)
- ▶ Continuous-time **low-pass**
filtering for
alias rejection
- ▼ Distortion due
to upper band
amplitude loss
- ▼ High-frequency
residual contents
- ▲ Attenuation by
oversampling



A/D and D/A Converters

 - Typical **pre** and **post** signal processing stages around ADC and DAC...



...out of the scope of this course!

- 1 Evolution of CMOS Technologies
- 2 Trends in Analog and Mixed IC Design
- 3 A/D and D/A Conversion Principles
- 4 ADC and DAC Figures of Merit
- 5 Lab proposal

Static FoMs


- ▶ Least significant bit (**LSB**):

$$1LSB \doteq \frac{A_{FS}}{2^N - 1}$$

except for
full-scale
boundaries!

- ▶ **Absolute accuracy** is $\pm 0.5LSB$

- ▶ DC transfer curve

 

Static FoMs


- ▶ Least significant bit (**LSB**):

$$1\text{LSB} \doteq \frac{A_{FS}}{2^N - 1}$$

- ▶ **Absolute accuracy** is $\pm 0.5\text{LSB}$

- ▶ DC transfer curve

- ▼ **Gain** and **offset** errors

 

Static FoMs

- ▶ Least significant bit (**LSB**):


$$1LSB \doteq \frac{A_{FS}}{2^N - 1}$$

- ▶ **Absolute accuracy** is $\pm 0.5LSB$

- ▶ DC transfer curve

- ▼ **Gain** and **offset** errors

 - ▼ **Non-monotonicity**
and **missing codes**



Static FoMs

- ▶ Least significant bit (**LSB**):

$$1LSB \doteq \frac{A_{FS}}{2^N - 1}$$

- ▶ **Absolute accuracy** is $\pm 0.5LSB$



- ▶ DC transfer curve

- ▼ **Gain** and **offset** errors

- ▼ **Non-monotonicity** and **missing codes**

- ▶ Differential non-linearity (**DNL**)

$$DNL(c) \doteq A(c) - A(c-1) - 1LSB$$

  

Static FoMs

- ▶ Least significant bit (**LSB**):

$$1\text{LSB} \doteq \frac{A_{FS}}{2^N - 1}$$

- ▶ **Absolute accuracy** is $\pm 0.5\text{LSB}$

- ▶ DC transfer curve

- ▼ **Gain** and **offset** errors

- ▼ **Non-monotonicity**
and **missing codes**



- ▶ Differential non-linearity (**DNL**)

$$\text{DNL}(c) \doteq A(c) - A(c-1) - 1\text{LSB}$$

- ▶ Integral non-linearity (**INL**)

$$\text{INL}(c) \doteq A(c) - A(0) - m \cdot c$$
  
$$m \doteq \frac{A(c_{max}) - A(0)}{c_{max}}$$



Dynamic FoMs

- ▶ Based on single or multiple **harmonic** stimulus

- ▶ **Sampling rate:**

$$f_s \geq f_{nyq} = 2BW$$


- ▶ **Oversampling ratio (OSR):**

$$OSR = \frac{f_s}{f_{nyq}}$$

- ▶ Signal to noise and distortion ratio (**SNDR** or **SINAD**)

- ▶ Effective number of bits (**ENOB**):
 
$$ENOB = \frac{SNDR_{max}[dB] - 1.76}{6.02}$$



- ▶ **Dynamic range (DR):**

$$DR \doteq 20 \log \frac{A_{max}}{A_{min}} \quad [dB] \quad \geq \quad SNDR_{max}$$

Combined FoMs


- ▶ **Quantitative** expression
- ▶ **Performance** and **resources** mixed
- ▲ Objective rule for design **comparison** purposes
- ▶ Examples for **ADC**:

- R.H. Walden (1999)

$$FOM_W \doteq \frac{P_D}{f_{nyq} \cdot 2^{ENOB}} \quad [\text{J/conv-step}]$$

- R. Schreier (2005)
 
$$FOM_S \doteq SNDR_{max} + 10 \log \frac{f_{nyq}}{2P_D} \quad [\text{dB}]$$






➤ B. Murmann
ADC Performance Survey 1997-2022
github.com/bmurmann/ADC-survey

- 1 Evolution of CMOS Technologies
- 2 Trends in Analog and Mixed IC Design
- 3 A/D and D/A Conversion Principles
- 4 ADC and DAC Figures of Merit
- 5 Lab proposal

My $\Delta\Sigma$ in CNM25

   
- ▶ Second-order single-bit A/D $\Delta\Sigma$ modulator design case
- ▲ Simple 2.5 μm 2P2M CMOS technology (CNM25)



My $\Delta\Sigma$ in CNM25

- ▶ Second-order single-bit A/D $\Delta\Sigma$ modulator design case
- ▲ Simple 2.5 μm 2P2M CMOS technology (CNM25)
- ▶ From system HDL simulation...
...to full-custom layout

Architectural
HDL simulation

 


Initial specs

```
void cm_zinteg2lim(ARGS) {
  inp = INPUT(inp);
  clk = INPUT_STATE(clk);
  pos_edge = PARAM(pos_edge);
  out_max = PARAM(out_ax);
  ...
  switch (ANALYSIS) {
    case TRANSIENT:
      if ((*clk_mem==ONE)&&(clk==ZERO))
        if (pos_edge==FALSE)
          action = SAMPLING_INTEGRATION;
      } else {
        if ((*clk_mem==ZERO)&&(clk==ONE))
          if (pos_edge==TRUE)
            action = SAMPLING_INTEGRATION;
        } else {
          action = HOLDING;
        }
      }
    }
}
```


Block
HDL specs



Automatic
circuit optimization

 

My layout

 

PCell-based
layout design

Physical
verification



My $\Delta\Sigma$ in CNM25

- ▶ Second-order single-bit A/D $\Delta\Sigma$ modulator design case
- ▲ Simple 2.5 μ m 2P2M CMOS technology (CNM25)
- ▶ From **system HDL** simulation...
...to **full-custom layout**
- ▲ **Freeware and multi-OS**
(MS Windows, Linux) EDA tools:
 - **Glade** (schematic/layout edition and physical verification with Python user language)
peardrop.co.uk
 - **SpiceOpus** (SPICE/XSpice mixed-signal simulation and circuit optimization with NUTMEG user language)
fides.fe.uni-lj.si/spice
- ▲ Work at **home** and tutorial at **lab!**

