

3. DAC Architectures and CMOS Circuits

Francesc Serra Graells

francesc.serra.graells@uab.cat

Departament de Microelectrònica i Sistemes Electrònics
Universitat Autònoma de Barcelona

paco.serra@imb-cnm.csic.es


Integrated Circuits and Systems
IMB-CNM(CSIC)

- 1 DAC Classification
- 2 Flash Converters
- 3 Pulse-Width Modulation
- 4 Delta-Sigma Modulation

- 1 DAC Classification
- 2 Flash Converters
- 3 Pulse-Width Modulation
- 4 Delta-Sigma Modulation

DAC Families

 - Classification based on **architecture** approach:




- Distinctive **characteristics**:

- Feedforward vs feedback control
- Single vs multiple stages
- Amplitude vs time domains

- Typically **mixed** solutions...

DAC vs ADC Design

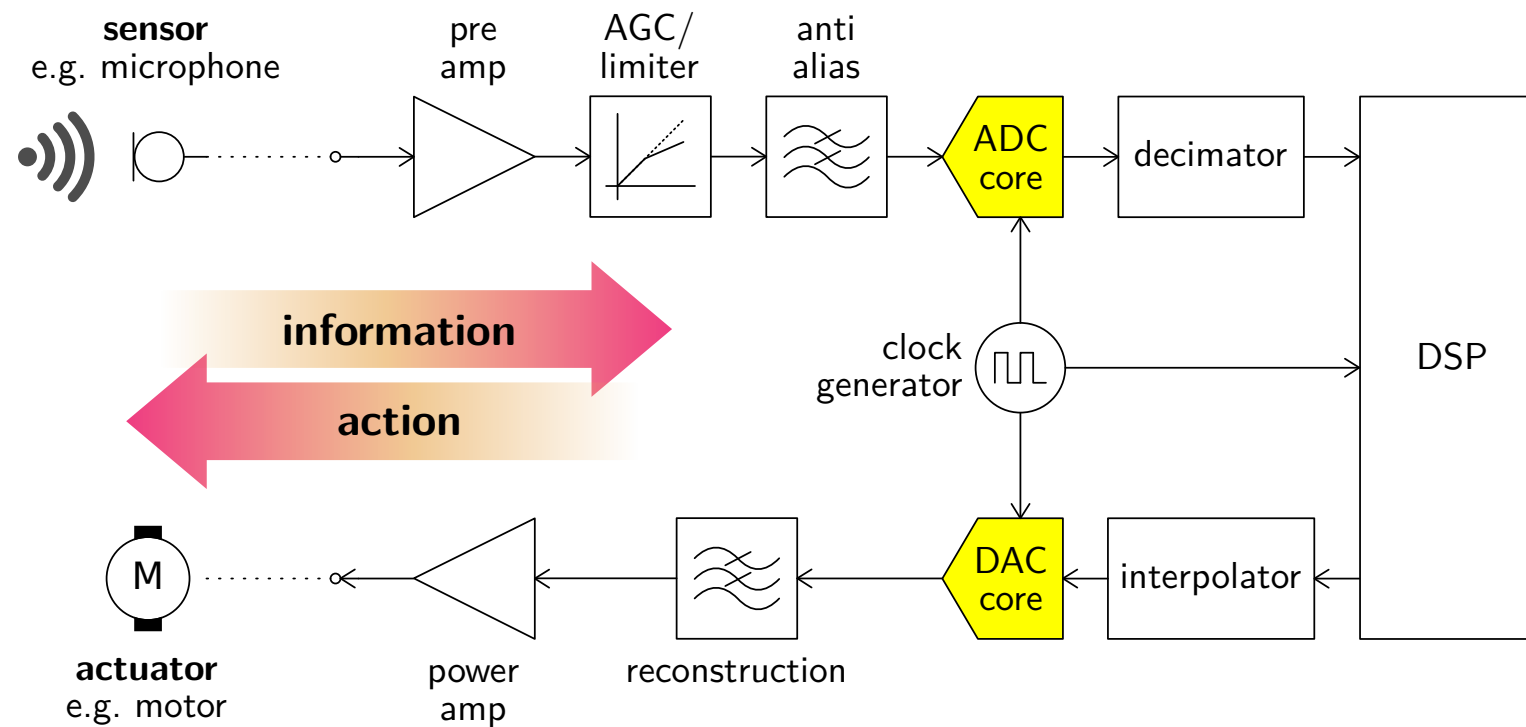- **Asymmetrical** system architecture and signal purpose:





...typically **ADC** is more performance demanding!

- 1 DAC Classification
- 2 Flash Converters
- 3 Pulse-Width Modulation
- 4 Delta-Sigma Modulation


Basic Flash Architecture

  - ▶ All **parallel** and **segmented** (unitary) resistive ladder:




Basic Flash Architecture

 - All **parallel** and **segmented** (unitary) resistive ladder:





$$V_{out} = V_{low} + \frac{R_{sel}}{R_{total}} V_{FS}$$

e.g. **single-ended**
10-bit flash DAC

 


Basic Flash Architecture

  - All **parallel** and **segmented** (unitary) resistive ladder:




Basic Flash Architecture

 - All **parallel** and **segmented** (unitary) resistive ladder:





 ▼ Distortion due to **switch** on-resistance variability



Switch Optimization

  ► Thermometric switched-resistor flash DAC:





$$\begin{cases} I_f = (-1)^{th_{sign}} \frac{V_{FS}/2}{R_{th}} \sum th_{mag} \\ V_{out} = I_f R_f \end{cases}$$

$$V_{out} = \frac{R_f}{R_{th}} \frac{V_{FS}}{2} (-1)^{th_{sign}} \sum th_{mag}$$

Switch Optimization

  ► Thermometric switched-resistor flash DAC:




$$\frac{dv_{nout}^2}{df} = 4KT \left[R_f + th_{mag} R_{th} \left(\frac{R_f}{R_{th}} \right)^2 \right]$$

$$\frac{dv_{nout}^2}{df} = 4KTR_f \left(1 + th_{mag} \frac{R_f}{R_{th}} \right) \leq 8KTR_f$$

▲ Switch non-linearity minimized thanks to its **signal independent** bias point

CMOS Circuits

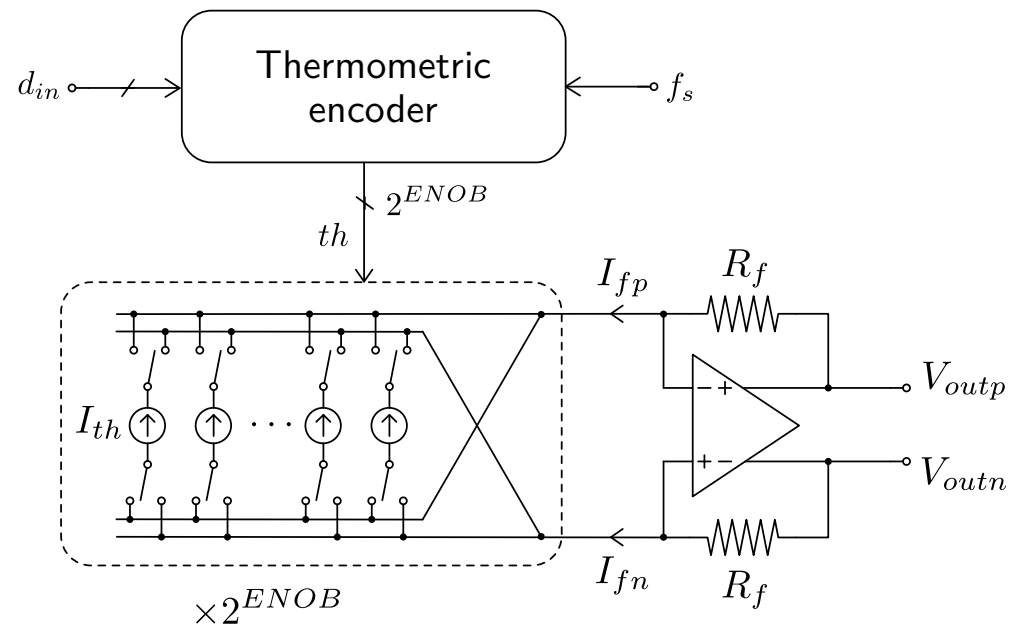- Thermometric switched-current (**SI**) **fully-differential** flash DAC:



continuous-time
waveform!


$$V_{out} = V_{outp} - V_{outn}$$

$$\frac{V_{FS}}{2} = 2^{ENOB+1} I_{th} R_f$$

- ▼ MOSFET **noise** contributions!
- ▲ Always-on SI cell to reduce **glitches**

CMOS Circuits

 
► Thermometric switched-current (SI) fully-differential flash DAC:



▲ Good current control thanks to...


OpAmp virtual ground + cascode topologies

► SI CMOS modular cell:

 


CMOS Circuits

 - ▶ Regular versus return-to-zero (**RTZ**) digital signalling:




- ▼ Inter-symbol interference depends on input code, so it generates **signal distortion**!

- ▶ SI **CMOS** modular cell:

 


CMOS Circuits

 ► Regular versus return-to-zero (**RTZ**) digital signalling:




- ▲ RTZ minimizes inter-symbol interference
- ▼ Full-scale reduction due to RTZ **duty cycle**
- ▼ Poor **scalability** with ENOB

► SI **CMOS** modular cell:

 

Sub-Ranging Architectures

 - Mixed **segmented** (coarse) and **binary weighted** (fine) solutions:





- ▲ Unlike in sub-ranging ADCs, still a **single step** conversion!
- ▲ Good ENOB **scalability**

- 1 DAC Classification
- 2 Flash Converters
- 3 Pulse-Width Modulation
- 4 Delta-Sigma Modulation


Digital Pulse Width Modulation

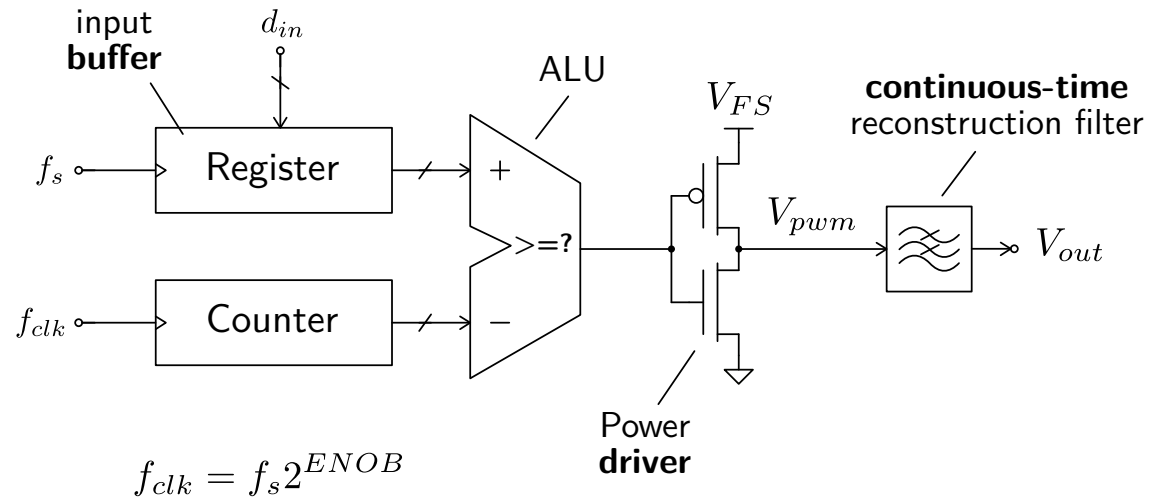 ► Discrete amplitude and continuous-time domains:




$$V_{out} = t_{pwm} f_s V_{FS} = \frac{d_{in}}{f_{clk}} f_s V_{FS}$$
 
$$V_{out} = \frac{d_{in}}{2^{ENOB}} V_{FS}$$





Digital Pulse Width Modulation

 ► **Discrete amplitude** and **continuous-time** domains:



$$f_{clk} = f_s 2^{ENOB}$$

  ▲ Output **actuator** can be reused as reconstruction filter:




▼ **Overclocking**

▼ Output filter **selectivity**



Digital Pulse Width Modulation

 - **Discrete amplitude and continuous-time domains:**




$$f_{clk} = f_s 2^{ENOB}$$

  - ▲ **Relaxing** output filter selectivity through non-monotonic counters, e.g. linear-feedback shift registers (LFSRs)




Dual-Ramp Analog Integration

► Sub-ranging PDM DAC architecture:

 

Dual-Ramp Analog Integration


► Sub-ranging PDM DAC architecture:

 

$$f_{clk} = 2^{\frac{ENOB}{2}} f_s$$

$$I_{coarse} = 2^{\frac{ENOB}{2}} I_{fine}$$
 
$$V_{out} = \frac{d_{in}}{2^{ENOB}} \underbrace{\frac{I_{coarse} + I_{fine}}{C_i f_s}}_{V_{FS}}$$




- ▲ Relaxing output filter selectivity
- ▲ Strong reduction of **clock speed** requirements
- ▼ Coarse-fine **matching**

e.g. **16-bit** dual ramp DAC

$$\begin{cases} f_{clk} = 256 f_s \\ I_{coarse} = 256 I_{fine} \end{cases}$$

- 1 DAC Classification
- 2 Flash Converters
- 3 Pulse-Width Modulation
- 4 Delta-Sigma Modulation




Analog vs Digital DSM

 

high-pass filter
(quantization noise shaping)

$$D_{out}(z) = z^{-N} V_{in}(z) + (1 - z^{-1})^N E_{quant}(z)$$

Analog vs Digital DSM

   


▲ Flash output DAC with **reduced** number of levels

▼ Possibility of loop **instability** for $N > 2$


Multi-Stage Noise Shaping (MASH)

 - ▶ Cascade of 1st-order DSM
- ▶ **Forward** digital cancellation
- ▲ Intrinsically **stable**



Multi-Stage Noise Shaping (MASH)

 - Cascade of 1st-order DSM
- Forward digital cancellation
- ▲ Intrinsically **stable**




$$D_{out} = z^{-2} [z^{-1} D_{in} + (1 - z^{-1}) E_1] + (1 - z^{-1}) z^{-1} [-z^{-1} E_1 + (1 - z^{-1}) E_2] + (1 - z^{-1})^2 [-z^{-1} E_2 + (1 - z^{-1}) E_N]$$

Multi-Stage Noise Shaping (MASH)

- ▶ **Cascade** of 1st-order DSM
- ▶ **Forward** digital cancellation
- ▲ Intrinsically **stable**
- ▶ Each DSM **cancels** quantization errors of previous one
- ▼ Not suitable for ADC DSM due to **mismatching** at cancellation stage
- ▲ **N-order noise shaping**:

 
$$D_{out} = z^{-N} D_{in} + (1 - z^{-1})^N E_N$$



$$D_{out} = z^{-2} [z^{-1} D_{in} + \cancel{(1 - z^{-1}) E_1}] + (1 - z^{-1}) z^{-1} [\cancel{-z^{-1} E_1} + \cancel{(1 - z^{-1}) E_2}] + (1 - z^{-1})^2 [\cancel{-z^{-1} E_2} + (1 - z^{-1}) E_N]$$


Multi-Stage Noise Shaping (MASH)

 - Example for **1-bit quantization** 1st-order DSM stage:




$$Y = X + (1 - z^{-1}) E$$

- ▲ **Compact** solution:

 


Multi-Stage Noise Shaping (MASH)

 ► Example for **1-bit quantization** 1st-order DSM stage:




$$Y = X + (1 - z^{-1}) E$$

▲ **Compact solution:**




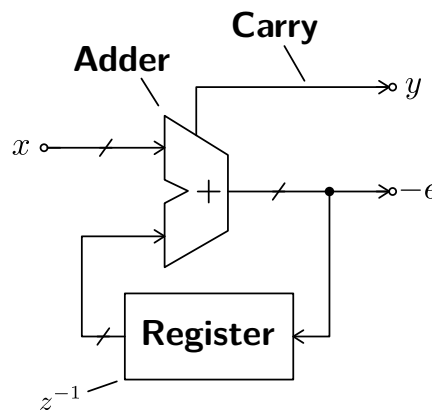


$$Y_1 = D_{in} + (1 - z^{-1}) E_1$$

$$Y_2 = -E_1 + (1 - z^{-1}) E_2$$

 

 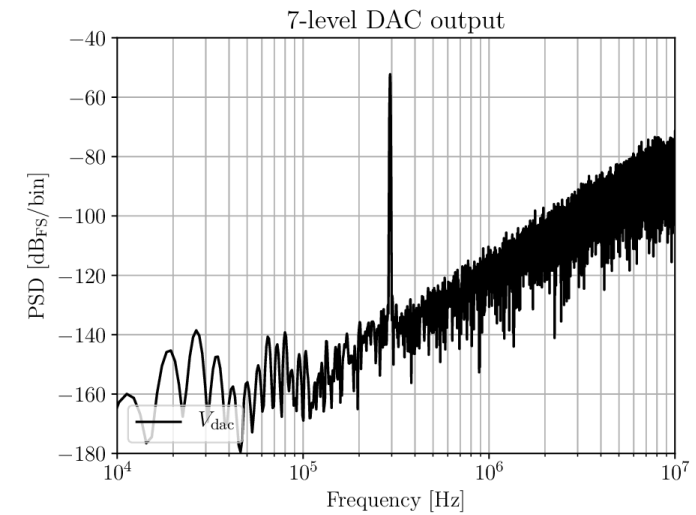  Example of Application: Periodic Function Generator



Example of Application: Periodic Function Generator

