

4. Full-Custom IC Design Methodology

Francesc Serra Graells

francesc.serra.graells@uab.cat

Departament de Microelectrònica i Sistemes Electrònics
Universitat Autònoma de Barcelona

paco.serra@imb-cnm.csic.es

Integrated Circuits and Systems
IMB-CNM(CSIC)


- 1 Mixed-Signal Design Flow
- 2 AMS Hardware Description Languages
- 3 Device Sizing
- 4 Process and Mismatching Simulation
- 5 The Art of Analog Layout
- 6 Physical Verification
- 7 Parasitics Extraction
- 8 DFM Techniques

- 1 Mixed-Signal Design Flow
- 2 AMS Hardware Description Languages
- 3 Device Sizing
- 4 Process and Mismatching Simulation
- 5 The Art of Analog Layout
- 6 Physical Verification
- 7 Parasitics Extraction
- 8 DFM Techniques

Full-Custom Analog IC Design Flow


► From circuit **idea** to **layout** masks...

▲ **EDA-assisted** methodology

 


Full-Custom Schematic Design

 - **Architecture** selection according to system and application specifications:



 e.g. $\Delta\Sigma$ modulation ADC architecture



- Signal processing performance
- Communications standards
- Power constraints
- Testability requirements
- ... and many more!

Full-Custom Schematic Design

- System modeling through any hardware description language (**HDL**):



```

----- zinteg2lim.mod -----
void cm_zinteg2lim(ARGS) {
  inp = INPUT(inp);          /* Retriving input values */
  clk = INPUT_STATE(clk);
  pos_edge = PARAM(pos_edge); /* Retrieving parameters */
  out_max = PARAM(out_ax);
  ...
  switch (ANALYSIS) {
    case TRANSIENT:
      if ((*clk_mem==ONE)&&(clk==ZERO)) { /* Neg. clk edge */
        if (pos_edge==FALSE)
          action = SAMPLING_INTEGRATION;
      } else {
        if ((*clk_mem==ZERO)&&(clk==ONE)) { /* Pos. clk edge */
          if (pos_edge==TRUE)
            action = SAMPLING_INTEGRATION;
        } else {
          /* No clock edge */
          action = HOLDING;
        }
      }
    ...
    switch (action) {
      case SAMPLING_INTEGRATION:
        *inp_mem = inp;
        out = *out_mem+*inp_mem;
        if (out<out_min) { out = out_min; } /* Limiter */
        if (out>out_max) { out = out_max; }
        *out_mem = out;
        break;
      case HOLDING:
        out = *out_mem;
    }
  }
}

```

e.g. XSpice

  - Architecture description
- **Simplified** functional modeling of each block
- Second-order circuit effects still **neglected**





Full-Custom Schematic Design

- ▶ HDL numerical simulation of the full system using **event-based** engines:


- Architecture evaluation
- Simulation **speed-up** by orders of magnitude!
- **Ideal** response (maximum possible performance)

e.g. SpiceOpus

  

```


dsm-arch.sub
.subckt dsm_arch vin dclk dout
asumin [%v(vin) %v(vdac)] %v(verr) msumin
.model msumin usummer(sign=[1.0 -1.0])
aki1 %v(verr) %v(vintlout) mki1
.model mki1 kgain(k=0.3)
azint1 %v(vintlout) %d(dclk) %v(vintlout) mzint1
.model mzint1 zinteg2lim(pos_edge=0 out_ic=0.0
+ out_min=-5.0 out_max=5.0)
aki2 %v(vintlout) %v(vint2in) mki2
.model mki2 kgain(k=0.7)
azint2 %v(vint2in) %d(dclk) %v(vint2out) mzint2
.model mzint2 zinteg2lim(pos_edge=0 out_ic=0.0
+ out_min=-5.0 out_max=5.0)
akff %v(vint2out) %v(vkffout) mkff
.model mkff kgain(k=2.0)
asumout [%v(vint2out) %v(vkffout) %v(vin)]
+ %v(vquantin) msumout
.model msumout usummer(sign=[1.0 1.0 1.0])
aquant %v(vquantin) %d(~dclk) %d(dout) mquant
.model mquant quant2lsh(inp_th=0.0 out_ic=0 pos_edge=0
+ t_rise=1e-9 t_fall=1e-9)
adac %d(dout) %v(vdac) mdac
.model mdac dac2lsym(out_level=2.0)
.ends
  
```

 



Full-Custom Schematic Design

► Choosing most suitable **circuit technique** according to:

 - **CMOS** technology options
- Circuit sensitivity against process, supply and temperature (**PVT**)
- IC **operation** conditions (calibration, testability...)
- **External** components available




  e.g. switched-capacitor (**SC**) technique




Full-Custom Schematic Design

 - **Splitting** system design problem into independent **blocks**:



- Modeling **second-order** effects due to limited circuit performance
- Electrical simulation of each individual **block** is feasible
- Transistor-level **final** simulation of overall system is still required!

 e.g. limited {G,GBW,SR} in **Opamp** model



```

opamp.ifs


NAME_TABLE:
Spice_Model_Name: opamp
C_Function_Name:  cm_opamp
Description:      "OpAmp macro"

PORT_TABLE:
Port_Name:       inp      inn      out
Description:     "pos. input" "neg. input" "output"
Direction:       in       in       out
Default_Type:    v        v        v
...

PARAMETER_TABLE:
Parameter_Name:  G        GBW      SR
Description:     "DC OL gain" "GBW"  "slew-rate"
Data_Type:       real      real   real
Default_Value:   1000     1e6   1e6
Limits:          [0 -]    [0 -]  [0 -]
...


PARAMETER_TABLE:
Parameter_Name:  out_min  out_max
Description:     "lower out limit" "upper out limit"
Data_Type:       real      real
Default_Value:   0         5.0
Limits:          [0 5.0]   [0 5.0]
...

```

 



Full-Custom Schematic Design

 - Choosing the particular **circuit topology** for each system block:





e.g. fully-differential
cascode and
folded **OpAmp**

  - **Separated** block testbenches
- **Target specs** from previous step
e.g. {G,GBW,SR}
- Fast and accurate **electrical simulations**
- **Several** circuit topologies can be easily investigated for each functional block
- Inter-block **coupled** effects not covered!



Full-Custom Schematic Design

  ► Device size optimization at block level:




SpiceOpus Command Window

Device	Units	Before	After
M1 M2	[um/um]	2x32/6	2x10.02/6
M3 M4	[um/um]	1x24/6	2x24/6
M6	[um/um]	8x24/6	4x24/6
M8	[um/um]	1x12/6	1x12/6
M5	[um/um]	8x12/6	9x12/6
M7	[um/um]	2x12/6	8x12/6
Ccomp	[umxum]	1x100x100	1x61.18x61.18


Param	Units	Spec	Before	After
G	[dB]	60	76.1	64.2
GBW	[MHz]	2	2.12	4.37
PM	[deg]	60	72.9	60
SR+	[V/us]	12	3.9	14.3
SR-	[V/us]	12	4.1	19.3
PD	[mW]	1.5	0.55	0.78
Area	[mm2]	0.025	0.022	0.015

e.g. OpAmp
automatic
optimization

 

```
opamp_optimize.sp3

optimize
  parameter 0 @m1:xopamp[w] low 6u high 120u initial 32u
  " parameter 1 @m6:xopamp[m] low 1 high 10 initial 8
  " parameter 3 @ccomp:xopamp[w] low 25u high 250u
  ...
  " analysis 25 ac dec 50 10 10e6
  " analysis 26 let gmag=20*log10(mag(v(vout)))
  " analysis 27 let gph=phase(v(vout))
  " analysis 28 cursor c right gmag 0
  " analysis 29 let gbw=abs(frequency[%c])/1e6
  " analysis 30 let pm=180+gph[%c]
  ...
  " analysis 46 tran 1n 5u
  " analysis 47 cursor c right vout 2.1
  " analysis 48 let t1=time[%c]
  " analysis 49 cursor c right vout 2.9
  " analysis 50 let t2=time[%c]
  " analysis 51 let srpos=0.8/(t2-t1)*1e-6
  ...
  " implicit 0 op2.pd lt 1.5
  " implicit 1 op2.area lt 0.025
  " implicit 4 ac2.pm gt 60
  " implicit 5 tran2.srpos gt 12
  ...
  " cost 1/tran2.srneg+1/tran2.srpos+abs(60-ac2.pm)
  " method genetic elitism yes maxgen 1000
```

 

System-level
schematic entry

Architecture HDL
simulation

Block HDL
specification

Circuit-level
schematic entry


Automatic
circuit optimization

$$M \times \frac{W}{L}$$

- 1 Mixed-Signal Design Flow
- 2 **AMS Hardware Description Languages**
- 3 Device Sizing
- 4 Process and Mismatching Simulation
- 5 The Art of Analog Layout
- 6 Physical Verification
- 7 Parasitics Extraction
- 8 DFM Techniques

Electrical vs Event Simulation

 
► Circuit as network of **physical devices**:




- **Electrical** modeling
- **Impedance** coupling
- Any change requires resolving the **full net**
- **Accurate** results
- **Time consuming** simulation

Electrical vs Event Simulation

 ► Circuit as network of **physical devices**:



► Circuit as chain of **black boxes**:

 


$$V_{out} = k_A V_A + k_B V_B + k_C V_C$$

- **Electrical** modeling
- **Impedance** coupling
- Any change requires resolving the **full net**
- **Accurate** results
- **Time consuming** simulation


Electrical vs Event Simulation

 ► Circuit as network of **physical devices**:



- **Electrical** modeling
- **Impedance** coupling
- Any change requires resolving the **full net**
- **Accurate** results
- **Time consuming** simulation

► Circuit as chain of **black boxes**:


 


$$V_{out} = k_A V_A + k_B V_B + k_C V_C$$

- **Behavioral** modeling
- Cause-effect **event** generation
- Only resolving event **propagation**
- **Fast** simulation
- **Simplified** predictions



Electrical vs Behavioral Modeling

► Example: **voltage comparator**

  

Electrical vs Behavioral Modeling

► Example: **voltage comparator**

  

behavioral macro-model
explicit equations:


$$d_{out} = \begin{cases} H & V_{in} \geq V_{ref} \\ L & V_{in} < V_{ref} \end{cases}$$

► Specific hardware description language (**HDL**) required...

Simulink Engine


► Created in 1984

▲ **Multi** data type

 


Simulink Engine

 - ▶ Created in 1984
- ▲ **Multi** data type
- ▲ Several **libraries** of predefined blocks




blocksets:

 


Simulink Engine

 - Created in 1984
- ▲ **Multi** data type
- ▲ Several **libraries** of predefined blocks




blocksets:

 


Simulink Engine

 - Created in 1984
- ▲ **Multi** data type
- ▲ Several **libraries** of predefined blocks




blocksets:

 


Simulink Engine

 - Created in 1984
- ▲ **Multi** data type
- ▲ Several **libraries** of predefined blocks




blocksets:

 


Simulink Engine

 - Created in 1984
- ▲ **Multi** data type
- ▲ Several **libraries** of predefined blocks




blocksets:

 


Simulink Engine

 - Created in 1984
- ▲ **Multi** data type
- ▲ Several **libraries** of predefined blocks




blocksets:

 


Simulink Engine

 - Created in 1984
- ▲ **Multi** data type
- ▲ Several **libraries** of predefined blocks




blocksets:

 

Simulink Engine

- ▶ Created in 1984
- ▲ **Multi** data type
- ▲ Several **libraries** of predefined blocks


 
- ▲ **Variable** and **fixed** step ordinary differential equation (**ODE**) solvers
- ▲ Continuous-time (**CT**) and discrete-time (**DT**) systems




e.g. phase-locked loop (**PLL**)
for frequency synthesis

Simulink Engine

  - ▶ Created in 1984
- ▲ **Multi** data type
- ▲ Several **libraries** of predefined blocks
- ▲ **Variable** and **fixed** step ordinary differential equation (**ODE**) solvers
- ▲ Continuous-time (**CT**) and discrete-time (**DT**) systems



 e.g. phase-locked loop (PLL)
for frequency synthesis



Simulink Engine

- ▶ Created in 1984
- ▲ **Multi** data type
- ▲ Several **libraries** of predefined blocks
- ▲ **Variable** and **fixed** step ordinary differential equation (**ODE**) solvers
- ▲ Continuous-time (**CT**) and discrete-time (**DT**) systems
- ▲ Linked to **Matlab** scripting for the analysis of results
- ▼ Limited types of analysis

```

Block {
    BlockType      Reference
    Name           "Continuous-Time\nVCO"
    SID            3
    Ports          [1, 1]
    Position       [655, 357, 745, 403]
    BlockMirror    on
    NamePlacement  "alternate"
    LibraryVersion "1.37"
    FontName       "Arial"
    SourceBlock    "commsynccomp2/Continuous-Time\nVCO"
    SourceType     "Continuous-Time VCO"
    ShowPortLabels "FromPortIcon"
    SystemSampleTime "-1"
    FunctionWithSeparateData off
    RTWMemSecFuncInitTerm "Inherit from model"
    RTWMemSecFuncExecute  "Inherit from model"
    RTWMemSecDataConstants "Inherit from model"
    RTWMemSecDataInternal  "Inherit from model"
    RTWMemSecDataParameters "Inherit from model"
    Ac                    "1"
    Fc                    "1e6"
    Kc                    "1e5"
    Ph                    "0"
}

```

Verilog Analog and Mixed Signal (AMS)

- ▶ Created in 1998
- ▶ Superset of Verilog digital HDL (**IEEE 1364**)
- ▶ Same as Verilog-A (1996), the AMS extension of Cadence Spectre
- ▲ **Analog/digital** circuits
- ▲ **Continuous/discrete** time
- ▲ All **SPICE analysis** supported (DC, AC, TRAN...)
- ▲ New **primitives** can be added in **C**

```
`include "constants.vams"
`include "disciplines.vams"
```

```
module example(a,b,c,d)
```

```
    parameter real cap = 1p;
    parameter integer gain = 2;
```

```
    input a;
    output b;
    inout c,d;
```


```
    electrical a,b,c,d;
```

```
    analog begin
```

```
        //Capacitor
        I(c,d) <+ cap * ddt(V(c,d));
```

```
        // Simple amplifier
        // Voltages referenced to ground if no second node is given
        V(b) <+ gain * V(a);
```

```
    end
endmodule
```

 

Verilog Analog and Mixed Signal (AMS)

- ▶ Created in 1998
- ▶ Superset of Verilog digital HDL (**IEEE 1364**)
- ▶ Same as Verilog-A (1996), the AMS extension of Cadence Spectre
- ▲ **Analog/digital** circuits
- ▲ **Continuous/discrete** time
- ▲ All **SPICE analysis** supported (DC, AC, TRAN...)
- ▲ New **primitives** can be added in **C**

```
`include "constants.vams"
`include "disciplines.vams"

module dac_simple(aout, clk, din, vref);

    parameter integer bits = 4 from [1:24];
    parameter integer td = 1n from [0:inf);


    input clk, vref; // Define input/output
    input [bits-1:0] din;
    output aout;

    logic clk; //Define port types
    logic [bits-1:0] din;
    electrical aout, vref;

    real aout_new, ref; // Internal variables
    integer i;

    analog begin
        ...
    end

endmodule
```

 

Verilog Analog and Mixed Signal (AMS)

- ▶ Created in 1998
- ▶ Superset of Verilog digital HDL (**IEEE 1364**)
- ▶ Same as Verilog-A (1996), the AMS extension of Cadence Spectre
- ▲ **Analog/digital** circuits
- ▲ **Continuous/discrete** time
- ▲ All **SPICE analysis** supported (DC, AC, TRAN...)
- ▲ New **primitives** can be added in **C**


```
`include "constants.vams"
`include "disciplines.vams"

module dac_simple(aout, clk, din, vref);

...

analog begin
    @(initial_step) V(aout) <+ 0; // Initialization
    @(posedge clk) begin // Change only for rising clock edge
        aout_new = 0;
        ref = V(vref);
        for(i=0; i<bits; i=i+1) begin
            ref = ref/2;
            aout_new = aout_new + ref * din[i];
        end
    end
    V(aout) <+ transition(aout_new, td, 5n); // Smoothing
end


endmodule
```

 

VHDL-AMS

- ▶ Created in 1999
- ▶ Incorporated into VHDL (**IEEE 1076**)
- ▲ **Similar** features to Verilog-AMS
 
```
library IEEE;  
use IEEE.math_real.all;  
use IEEE.electrical_systems.all;
```




```
-- this is the interface  
entity DIODE is  
    generic (is : current := 1.0e-14; -- Saturation current  
            rs : real    := 0.0);    -- Series resistance  
    port (terminal anode, cathode : electrical);  
end entity DIODE;
```

VHDL-AMS

- ▶ Created in 1999
- ▶ Incorporated into VHDL (**IEEE 1076**)
- ▲ **Similar** features to Verilog-AMS
- ▲ Splitting between interface (**entity**) and implementation (**architecture**)
 
```
library IEEE;
use IEEE.math_real.all;
use IEEE.electrical_systems.all;
```




```
-- this is the interface
entity DIODE is
    generic (is : current := 1.0e-14; -- Saturation current
            rs : real    := 0.0);    -- Series resistance
    port (terminal anode, cathode : electrical);
end entity DIODE;

-- this is the implementation
architecture IV_CONTINUOUS of DIODE is
    quantity vd across id through anode to cathode;
    constant vt : voltage := 0.0258;    -- Thermal voltage at 300K
    begin

        id == is * (exp((vd-rs*id)/vt) - 1.0);

    end architecture IV_CONTINUOUS;
```

 


▶ IEEE 1076.1 Standard
standards.ieee.org

VHDL-AMS

- ▶ Created in 1999
- ▶ Incorporated into VHDL (**IEEE 1076**)
- ▲ **Similar** features to Verilog-AMS
- ▲ Splitting between interface (**entity**) and implementation (**architecture**)
- ▲ Same entity can hold **several** architectures...
 
```
library IEEE;
use IEEE.math_real.all;
use IEEE.electrical_systems.all;
```




```
-- this is the interface
entity DIODE is
    generic (is : current := 1.0e-14; -- Saturation current
            rs : real := 0.0); -- Series resistance
    port (terminal anode, cathode : electrical);
end entity DIODE;

-- this is the implementation
architecture IV_PIECEWISE of DIODE is
    quantity vd across id through anode to cathode;
    variable vdo : real := 0.0; -- Equivalent threshold
    begin

        vdo == ...;
        if (vd > vdo) use
            id == (vd - vdo) / rs;
        else
            id == 0;
        end use;

    end architecture IV_PIECEWISE;
```

 


SystemC-AMS

- ▶ Created in 2010
- ▶ Incorporated into SystemC (**IEEE 1666**)
- ▶ Hierarchically, **on top** of Verilog-AMS and VHDL-AMS
- ▲ Based on **C++** class libraries:
 - Timed data flow (**TDF**)
 - Linear signal flow (**LSF**)
 - Electrical linear networks (**ELN**)
- ▲ **Concurrency** is optimized for simulation multithreading

```
SC_MODULE(mylsfmodel)    // model using LSF primitives
{
    sca_lsf::sca_in  in;    // LSF input port
    sca_lsf::sca_out out;  // LSF output port
    sca_lsf::sca_signal sig; // LSF signal

    sca_lsf::sca_dot* dot1; // declare module instances
    sca_lsf::sca_sub* sub1;

     mylsfmodel(sc_module_name, double fc=1.0e3)
    {
        // instantiate predefined primitives
        dot1 = new sca_lsf::sca_dot("dot1", 1.0/(2.0*M_PI*fc));
        dot1->x(out);
        dot1->y(sig);    // parameters
        sub1 = new sca_lsf::sca_sub("sub1");
        sub1->x1(in);
        sub1->x2(sig);
        sub1->y(out);
    }
};
```



XSpice HDL

- ▶ Created in 1992
- ▶ Extension of SPICE (a-elements)
- ▲ Analog/digital circuits
- ▲ Continuous/discrete time
- ▲ New **primitives** can be added in **C** and compiled separately (**modular**):
 - Interface file specification (**IFS**)

NAME_TABLE:

Spice_Model_Name: zinteg2lim
 C_Function_Name: cm_zinteg2lim
 Description: "Z-domain integrator with limited output"

PORT_TABLE:


Port_Name:	inp	clk	out
Description:	"input"	"clock"	"output"
Direction:	in	in	out
Default_Type:	v	d	v
Allowed_Types:	[v]	[d]	[v]
Vector:	no	no	no
Vector_Bounds:	-	-	-
Null_Allowed:	no	no	no

PARAMETER_TABLE:

Parameter_Name:	pos_edge	out_ic
Description:	"L->H edge output sync?"	"output initial condition"
Data_Type:	int	real
Default_Value:	0	0.0
Limits:	[0 1]	-
Vector:	no	no
Vector_Bounds:	-	-
Null_Allowed:	no	no

PARAMETER_TABLE:

Parameter_Name:	out_min	out_max
Description:	"lower output limit"	"upper output limit"
Data_Type:	real	real
Default_Value:	-1.0	1.0
Limits:	-	-
...		

 

➤ F. L. Cox et al.
Code-level Modeling in XSPICE
 IEEE ISCAS, May 1992
doi.org/10.1109/ISCAS.1992.230083


XSpice HDL

- ▶ Created in 1992
- ▶ Extension of SPICE (a-elements)
- ▲ Analog/digital circuits
- ▲ Continuous/discrete time
- ▲ New **primitives** can be added in **C** and compiled separately (**modular**):
 - Interface file specification (**IFS**)
 - Code model (**CM**)

```
#define SAMPLING_INTEGRATION 1
#define HOLDING 0

void cm_zinteg2lim(ARGS)
{
    double inp,      /* analog voltage input */
           out,      /* analog voltage output */
           *inp_mem, /* sampled input */
           *out_mem, /* integrated output */
           out_ic,   /* output initial condition */
           out_min,  /* minimum output limit */
           out_max;  /* maximum output limit */
    Digital_State_t clk, /* current clock level */
                  *clk_mem, /* previous clock level*/
                  pos_edge; /* L->H edge clock output? */
    int action; /* action type */
    char *error; /* error message */

     inp = INPUT(inp);          /* Retriving input values */
    clk = INPUT_STATE(clk);
    pos_edge = PARAM(pos_edge); /* Retriving parameters */
    out_ic = PARAM(out_ic);
    out_min = PARAM(out_min);
    out_max = PARAM(out_max);
    ...
}
```




➤ F. L. Cox et al.
Code-level Modeling in XSPICE
 IEEE ISCAS, May 1992
doi.org/10.1109/ISCAS.1992.230083

XSpice HDL

- ▶ Created in 1992
- ▶ Extension of SPICE (a-elements)
- ▲ Analog/digital circuits
- ▲ Continuous/discrete time
- ▲ New **primitives** can be added in **C** and compiled separately (**modular**):
 - Interface file specification (**IFS**)
 - Code model (**CM**)

```
...  
  
if (INIT==1) { /* Static storage allocation and checking */  
  
    cm_analog_alloc(1,sizeof(double));  
    cm_analog_alloc(2,sizeof(double));  
    cm_event_alloc(3,sizeof(Digital_State_t));  
  
    if (out_min>out_max) {  
        error = "\n*** zinteg2lim error: out_min>out_max !\n";  
        cm_message_send(error);  
    }  
    if ((out_ic>out_max)|| (out_ic<out_min)) {  
        error = "\n*** zinteg2lim error: out_ic exceeds  
                [out_min,out_max] !\n";  
        cm_message_send(error);  
    }  
}  
  
...
```

 

➤ F. L. Cox et al.
Code-level Modeling in XSPICE
IEEE ISCAS, May 1992
doi.org/10.1109/ISCAS.1992.230083

XSpice HDL

- ▶ Created in 1992
- ▶ Extension of SPICE (a-elements)
- ▲ Analog/digital circuits
- ▲ Continuous/discrete time
- ▲ New **primitives** can be added in **C** and compiled separately (**modular**):
 - Interface file specification (**IFS**)
 - Code model (**CM**)

```

...
switch (ANALYSIS) {
  case TRANSIENT: /* Transient analysis */

    inp_mem = cm_analog_get_ptr(1,0); /* Previous state */
    out_mem = cm_analog_get_ptr(2,0);
    clk_mem = cm_event_get_ptr(3,0);


    if (TIME==0) { /* Initialization */

      *inp_mem = inp;
      *out_mem = out_ic;
      out = out_ic;

    } else { /* Regular operation */

      if ((*clk_mem==ONE)&&(clk==ZERO)) { /* Neg clk edge */
        if (pos_edge==FALSE)
          action = SAMPLING_INTEGRATION;
      } else {
        if ((*clk_mem==ZERO)&&(clk==ONE)) { /* Pos edge */
          if (pos_edge==TRUE)
            action = SAMPLING_INTEGRATION;
        } else { /* No clock edge */
          action = HOLDING;
        }
      }
    }
  }
}
...

```

 

↗ F. L. Cox et al.
Code-level Modeling in XSPICE
 IEEE ISCAS, May 1992
doi.org/10.1109/ISCAS.1992.230083

XSpice HDL

- ▶ Created in 1992
- ▶ Extension of SPICE (a-elements)
- ▲ Analog/digital circuits
- ▲ Continuous/discrete time
- ▲ New **primitives** can be added in **C** and compiled separately (**modular**):
 - Interface file specification (**IFS**)
 - Code model (**CM**)

```

...
    switch (action) {
        case SAMPLING_INTEGRATION: /* Samp and integ */
            *inp_mem = inp;
            out = *out_mem+*inp_mem;
            if (out<out_min) { out = out_min; } /* Limiter */
            if (out>out_max) { out = out_max; }
            *out_mem = out;
            break;
        case HOLDING: /* Holding */
            out = *out_mem;
    }


    *clk_mem = clk;
    OUTPUT(out) = out;

    break;

case DC: /* DC analysis */
    OUTPUT(out) = out_ic;
    break;

default: /* Analysis not supported */
    error = "\n*** zinteg2lim error: analysis not
            supported !\n";
    cm_message_send(error);
}}

```

 

↗ F. L. Cox et al.
Code-level Modeling in XSPICE
 IEEE ISCAS, May 1992
doi.org/10.1109/ISCAS.1992.230083

XSpice HDL

- ▶ Created in 1992
- ▶ Extension of SPICE (a-elements)
- ▲ **Analog/digital** circuits
- ▲ **Continuous/discrete** time
- ▲ New **primitives** can be added in **C** and compiled separately (**modular**):
 - Interface file specification (**IFS**)
 - Code model (**CM**)
- ▲ XSpice + SPICE3 co-simulation

```

vin 1 0 sin(0 1 1e4 0 0 90)
vctl 2 0 dc=1
aclk %v(2) %d(3) myclock
.model myclock d_osc(cntl_array=[0 1] freq_array=[0 1e6])

azinteg2lim %v(1) %d(3) %v(5) myzinteg2lim
.model myzinteg2lim zinteg2lim(pos_edge=0 out_ic=0.0
out_min=-1.0 out_max=1.0)



aprobe [%d(3)] [%v(4)] myprobe
.model myprobe dac_bridge(out_low=0 out_high=1 t_rise=1e-9
t_fall=1e-9)
.end
  
```

```

.control

source test_zinteg2lim.cir
let @@myzinteg2lim[out_min]=-10
let @@myzinteg2lim[out_max]=10
tran 1e-9 1e-4
let vin=v(1)
let vclk=v(4)
let vout=v(5)
plot create plot1 vin vclk vout vs time xlabel 'Time [s]'
ylabel 'Output Voltage [V]' xlimit 0 1e-4 ylimit -20 20
...



.endc
.end
  
```

  

▶ F. L. Cox et al.
Code-level Modeling in XSPICE
 IEEE ISCAS, May 1992
doi.org/10.1109/ISCAS.1992.230083

XSpice HDL

  - ▶ Created in 1992
- ▶ Extension of SPICE (**a**-elements)
- ▲ **Analog/digital** circuits
- ▲ **Continuous/discrete** time
- ▲ New **primitives** can be added in **C** and compiled separately (**modular**):
 - Interface file specification (**IFS**)
 - Code model (**CM**)
- ▲ XSpice + SPICE3 co-simulation



➤ F. L. Cox et al.
Code-level Modeling in XSPICE
 IEEE ISCAS, May 1992
doi.org/10.1109/ISCAS.1992.230083

XSpice HDL

► Macro definitions for **circuit data**:

Name	Description	Example
ARGS	Passing arguments to the CM.	<code>void dsm_opamp(ARGS)</code>
CALL_TYPE	Returns the simulator type used for the CM (EVENT or ANALOG).	<code>if (CALL_TYPE==ANALOG) {...}</code>
INIT	Returns 1 when first call of the CM.	<code>if (INIT==1) {...}</code>
ANALYSIS	Returns the current analysis type (AC, DC or TRANSIENT).	<code>if (ANALYSIS!=AC) {...}</code>
FIRST_TIMEPOINT	Returns 1 when first call of CM during the current analysis step.	<code>if (FIRST_TIMEPOINT==0) {...}</code>
TIME	Double returning current time point of TRANSIENT analysis in s.	<code>t2 = TIME-t1;</code>
T(n)	Double vector returning [current previous] time points of TRANSIENT analysis.	<code>dt = T(0)-T(1);</code>
RAD_FREQ	Double returning current frequency of AC analysis in rad/s.	<code>f = RAD_FREQ/(2*pi);</code>
TEMPERATURE	Double vector returning current analysis temperature in °C.	<code>TK = TEMPERATURE+273;</code>

 F. L. Cox et al.
Code-level Modeling in XSPICE
 IEEE ISCAS, May 1992
doi.org/10.1109/ISCAS.1992.230083

XSpice HDL

► Macro definitions for **parameter** and **port data**:

Name	Description	Example
PARAM(param)	Returns CM parameter value.	k = PARAM(gain);
PARAM_SIZE(param)	Returns CM parameter vector size.	num_coeff = PARAM_SIZE(coeff);
PARAM_NULL(param)	Returns 1 when no value specified.	if (PARAM_NULL(gain)==1) {...}
PORT_SIZE(a)	Returns port size.	num_out = PORT_SIZE(out);
PORT_NULL(a)	Returns 1 when port is not connected.	if (PORT_NULL(inp)==1) {...}
LOAD(a)	Adds load capacitance in F to digital port.	LOAD(inp) = 1e-12;
TOTAL_LOAD(a)	Reads total load capacitance in F at digital port due to all attached CMs.	delay = TOTAL_LOAD(out)*...

► Macro definitions for **partial derivatives**, **gains** and **static variables**:

Name	Description	Example
PARTIAL(y,x)	Sets the partial derivative of output port y with respect to input port x. Needed by the simulator to solve non-linear equations. The cm_analog_auto_partial() function of Table 10 may be used instead.	PARTIAL(out,in) = 1;
AC_GAIN(y,x)	Sets the gain from input port x to output port y in AC analysis. Gain follows the complex data structure Complex_t defined in Table 11.	AC_GAIN(out,in) = gain_complex;
STATIC_VAR(a)	Provides access to the static variables defined in the IFS file.	last_x = STATIC_VAR(x); STATIC_VAR(x) = x;

 F. L. Cox et al.
Code-level Modeling in XSPICE
 IEEE ISCAS, May 1992
doi.org/10.1109/ISCAS.1992.230083

XSpice HDL


► Macro definitions for I/O data:

Name	Description	Example
INPUT(x)	Reads value from input port.	<code>signal = INPUT(inp);</code>
INPUT_STATE(x)	Reads the state of a digital input port (ZERO, ONE or UNKNOWN).	<code>if (INPUT_STATE(inp) != ONE) {...}</code>
INPUT_STRENGTH(x)	Reads the strength with which a digital input port is externally driven (STRONG, RESISTIVE, HI_IMPEDANCE or UNDETERMINATED).	<code>if (INPUT_STRENGTH(inp) != HI_IMPEDANCE) {...}</code>
OUTPUT(y)	Writes value to output port.	<code>OUTPUT(out) = result;</code>
OUTPUT_CHANGED(y)	Flags a digital output port as modified. If TRUE (default) then state, strength and delay need to be defined.	<code>OUTPUT_CHANGED(out) = FALSE;</code>
OUTPUT_DELAY(y)	Defines the delay in s (>0) of a digital output port.	<code>OUTPUT_DELAY(out) = 1e-9;</code>
OUTPUT_STATE(y)	Writes the state of a digital output port (ZERO, ONE or UNKNOWN).	<code>OUTPUT_STATE(out) = ZERO;</code>
OUTPUT_STRENGTH(y)	Writes the strength with which a digital output port is internally driven (STRONG, RESISTIVE, HI_IMPEDANCE or UNDETERMINATED).	<code>OUTPUT_STRENGTH(out) == STRONG;</code>

 F. L. Cox et al.
Code-level Modeling in XSPICE
 IEEE ISCAS, May 1992
doi.org/10.1109/ISCAS.1992.230083

XSpice Examples

► Simple **gain** block:

 

■ Interface file specification

NAME_TABLE:

Spice_Model_Name: kgain

C_Function_Name: cm_kgain

Description: "Scalar gain"

PORT_TABLE:


Port_Name:	inp	out
Description:	"input"	"output"
Direction:	in	out
Default_Type:	v	v
Allowed_Types:	[v]	[v]
Vector:	no	no
Vector_Bounds:	-	-
Null_Allowed:	no	no

PARAMETER_TABLE:

Parameter_Name:	k
Description:	"gain factor"
Data_Type:	real
Default_Value:	1.0
Limits:	-

XSpice Examples

► Simple **gain** block:

 

- Interface file specification
- Code model


```
void cm_kgain(ARGS)
{
    double inp, /* analog voltage input */
           out, /* analog voltage output */
           k; /* gain factor */
    Complex_t k_ac; /* AC gain factor */

    inp = INPUT(inp); /* Retriving input values */
    k = PARAM(k); /* Retrieving parameters */

    if (ANALYSIS!=AC) { /* DC and TRANSIENT analysis */
        OUTPUT(out) = k*inp;
        PARTIAL(out,inp) = k;
    } else { /* AC analysis */
        k_ac.real = k;
        k_ac.imag = 0.0;
        AC_GAIN(out,inp) = k_ac;
    }
}
```

XSpice Examples

► Simple **gain** block:

 

- Interface file specification
- Code model
- Simulation example

```
test_kgain.sp3

* Test script for kgain CM
* Requires cmload deltasigma.cm

.control

delcirc all
destroy all
delete all
save all

source test_kgain.cir
let @@mykgain[k]=5
tran 1e-9 1e-4
let vin=v(1)
let vout=v(2)
plot create plot1 vin vout vs time xlabel 'Time [s]'
ylabel 'Output Voltage [V]' xlimit 0 1e-4 ylimit -6 6

.endc


.end
```

```
test_kgain.cir
* Test circuit for kgain CM

vin 1 0 sin(0 1 1e4)


akgain %v(1) %v(2) mykgain
.model mykgain kgain(k=10)

.end
```

 

XSpice Examples

► Unity-gain summer/subtractor:

 

■ Interface file specification

```
NAME_TABLE:

Spice_Model_Name: usummer
C_Function_Name:  cm_usummer
Description:      "Unity-gain summer/subtractor"

PORT_TABLE:


Port_Name:        inp          out
Description:      "input array" "output"
Direction:        in           out
Default_Type:     v            v
Allowed_Types:    [v]          [v]
Vector:           yes          no
Vector_Bounds:    [2 -]        -
Null_Allowed:     no           no

PARAMETER_TABLE:

Parameter_Name:   sign
Description:       "input sign array {-1,1}"
Data_Type:         int
Default_Value:     1
Limits:            [-1 1]
```

XSpice Examples

► Unity-gain summer/subtractor:

 

- Interface file specification
- Code model


```
void cm_usummer(ARGS)
{
    double acc; /* summation accumulator */
    Complex_t k_ac; /* equivalent AC gain factor */
    int ninp, /* number of inputs */
        i; /* generic loop counter */

    ninp = PORT_SIZE(inp);

    if (ANALYSIS!=AC) { /* DC and TRANSIENT analysis */
        acc = 0.0;
        for (i=0; i<ninp; i++) {
            if (PARAM(sign[i])<0) {
                acc = acc-INPUT(inp[i]);
                PARTIAL(out,inp[i]) = -1.0;
            } else {
                acc = acc+INPUT(inp[i]);
                PARTIAL(out,inp[i]) = 1.0;
            }
        }
        OUTPUT(out) = acc;
    } else { /* AC analysis */
        for (i=0; i<ninp; i++) {
            if (PARAM(sign[i])<0) {
                k_ac.real = -1;
            } else {
                k_ac.real = 1;
            }
            k_ac.imag = 0.0;
            AC_GAIN(out,inp[i]) = k_ac;
        }
    }
}
```

XSpice Examples

► Unity-gain summer/subtractor:

 

- Interface file specification
- Code model
- Simulation example

```
test_usummer.sp3
* Test script for usummer CM
* Requires cmload deltasigma.cm

.control

delcirc all
destroy all
delete all
save all

source test_usummer.cir
let @@myusummer[sign]=(-1;1)
tran 1e-9 1e-4
let vin1=v(1)
let vin2=v(2)
let vout=v(3)
plot create plot1 vin1 vin2 vout vs time xlabel 'Time
[s]' ylabel 'Output Voltage [V]'

.endc


.end
```

```
test_usummer.cir
* Test circuit for usummer CM

vin1 1 0 sin(0 1 1e4)
vin2 2 0 sin(0 1 1e4 0 0 90)


ausummer [%v(1) %v(2)] %v(3) myusummer
.model myusummer usummer(sign=[1 -1])

.end
```

 

XSpice Examples

► 2-level quantizer with S/H:

 

■ Interface file specification

NAME_TABLE:

```
Spice_Model_Name: quant2lsh
C_Function_Name:  cm_quant2lsh
Description:      "2-level quantizer with S/H"
```

PORT_TABLE:

Port_Name:	inp	clk	out
Description:	"input"	"clock"	"output"
Direction:	in	in	out
Default_Type:	v	d	d
Allowed_Types:	[v]	[d]	[d]
Vector:	no	no	no
Vector_Bounds:	-	-	-
Null_Allowed:	no	no	no

PARAMETER_TABLE:


Parameter_Name:	inp_th	out_ic
Description:	"input threshold"	"output initial condition"
Data_Type:	real	int
Default_Value:	0.0	0
Limits:	-	[0 1]
Vector:	no	no
Vector_Bounds:	-	-
Null_Allowed:	no	no

PARAMETER_TABLE:

Parameter_Name:	pos_edge	t_rise	t_fall
Description:	"L->H edge out?"	"rise delay"	"fall delay"
Data_Type:	int	real	real
Default_Value:	0	1.0e-9	1.0e-9
Limits:	[0 1]	[1e-12 -]	[1e-12 -]
Vector:	no	no	no

XSpice Examples

► 2-level quantizer with S/H:

 

- Interface file specification
- Code model

```
#define SAMPLING_QUANTIZATION 1
#define HOLDING 0

void cm_quant2lsh(ARGs)
{
    double inp,          /* analog voltage input */
          *inp_mem, /* sampled input */
          inp_th, /* input threshold */
          t_rise, /* output rise time */
          t_fall; /* output fall time */


    Digital_State_t out, /* digital output */
                  *out_mem, /* holded output */
                  clk, /* current clock level */
                  *clk_mem, /* previous clock level*/
                  out_ic, /* output initial condition */
                  pos_edge; /* L->H edge clock output? */
    int action; /* action type */
    char *error; /* error message */

    inp = INPUT(inp);          /* Retriving input values */
    clk = INPUT_STATE(clk);
    inp_th = PARAM(inp_th);    /* Retrieving parameters */
    t_rise = PARAM(t_rise);
    t_fall = PARAM(t_fall);
    out_ic = PARAM(out_ic);
    pos_edge = PARAM(pos_edge);

    if (INIT==1) { /* Static storage allocation and checking */
        cm_analog_alloc(1,sizeof(double));
        cm_event_alloc(2,sizeof(Digital_State_t));
        cm_event_alloc(3,sizeof(Digital_State_t));
        if (t_rise<1e-12) {
            error = "\n*** quant2lsh error: t_rise<1ps !\n";
            cm_message_send(error);
        }
        if (t_fall<1e-12) {
            error = "\n*** quant2lsh error: t_fall<1ps !\n";
            cm_message_send(error);
        }
    }
}
```

XSpice Examples

► 2-level quantizer with S/H:

 

- Interface file specification
- Code model

```
switch (ANALYSIS) {

case TRANSIENT: /* Transient analysis */

    inp_mem = cm_analog_get_ptr(1,0); /* Retriving previous state */
    out_mem = cm_event_get_ptr(2,0);
    clk_mem = cm_event_get_ptr(3,0);

    if (TIME==0) { /* Initialization */


        *inp_mem = inp;
        *out_mem = out_ic;
        out = out_ic;
        OUTPUT_CHANGED(out) = TRUE;
        OUTPUT_STATE(out) = out;
        OUTPUT_STRENGTH(out) = STRONG;

    } else { /* Regular operation */

        if ((*clk_mem==ONE)&&(clk==ZERO)) { /* Negative clk edge */
            if (pos_edge==FALSE)
            {
                action = SAMPLING_QUANTIZATION;
            }
        } else {
            if ((*clk_mem==ZERO)&&(clk==ONE)) { /* Positive clk edge */
                if (pos_edge==TRUE)
                {
                    action = SAMPLING_QUANTIZATION;
                }
            } else { /* No clock edge */
                action = HOLDING;
            }
        }
    }
}
```

XSpice Examples

► 2-level quantizer with S/H:

 

- Interface file specification
- Code model

```

switch (action) {
case SAMPLING_QUANTIZATION: /* Quantization action */
    OUTPUT_CHANGED(out) = TRUE;
    *inp_mem = inp;
    if (*inp_mem > inp_th) {
        out = ONE;
        OUTPUT_DELAY(out) = t_rise;
    } else {
        out = ZERO;
        OUTPUT_DELAY(out) = t_fall;
    }
    OUTPUT_STATE(out) = out;
    OUTPUT_STRENGTH(out) = STRONG;
    *out_mem = out;
    break;
case HOLDING: /* Holding action */
    OUTPUT_CHANGED(out) = FALSE;
}

*clk_mem = clk;

break;


case DC: /* DC analysis */
    OUTPUT_STATE(out) = out_ic;
    OUTPUT_STRENGTH(out) = STRONG;
    break;

default: /* Analysis not supported */
    error = "\n*** quant2lsh error: analysis not supported !\n";
    cm_message_send(error);
}
}

```

XSpice Examples

► 2-level quantizer with S/H:

 

- Interface file specification
- Code model
- Simulation example

```
test_quant2lsh.cir
* Test circuit for quant2lsh CM

vin 1 0 sin(0 1 1e4)
vctl 2 0 dc=1

aclk %v(2) %d(3) myclock
.model myclock d_osc(cntl_array=[0 1] freq_array=[0 1e5])

aquant2lsh %v(1) %d(3) %d(4) myquant2lsh
.model myquant2lsh quant2lsh(inp_th=0.5 out_ic=0 pos_edge=0 t_rise=1e-9
t_fall=1e-9)

aprobe1 [%d(3)] [%v(5)] myprobe
aprobe2 [%d(4)] [%v(6)] myprobe
.model myprobe dac_bridge(out_low=0 out_high=1 t_rise=1e-9 t_fall=1e-9)

.end
```

```
test_quant2lsh.sp3
* Test script for quant2lsh CM


.control
delcirc all
destroy all
delete all
save all

source test_quant2lsh.cir
let @myquant2lsh[t_rise]=1e-6
let @myquant2lsh[t_fall]=1e-6
tran 1e-9 1e-4
let vin=v(1)
let vclk=v(5)
let vout=v(6)
plot create plot1 vin vclk vout vs time xlabel 'Time [s]' ylabel 'Output ...

.endc
.end
```

XSpice Examples

- ▶ 2-level quantizer with S/H:

 

- Interface file specification
- Code model
- Simulation example

```
test_quant2lsh.cir
* Test circuit for quant2lsh CM

vin 1 0 sin(0 1 1e4)
vctl 2 0 dc=1

aclk %v(2) %d(3) myclock
.model myclock d_osc(cntl_array=[0 1] freq_array=

aquant2lsh %v(1) %d(3) %d(4) myquant2lsh
.model myquant2lsh quant2lsh(inp_th=0.5 out_ic=0
t_fall=1e-9)


aprobe1 [%d(3)] [%v(5)] myprobe
aprobe2 [%d(4)] [%v(6)] myprobe
.model myprobe dac_bridge(out_low=0 out_high=1 t_

.end
```

```
test_quant2lsh.sp3
* Test script for quant2lsh CM
.control
delcirc all
destroy all
delete all
save all

source test_quant2lsh.cir
let @myquant2lsh[t_rise]=1e-6
let @myquant2lsh[t_fall]=1e-6
tran 1e-9 1e-4
let vin=v(1)
let vclk=v(5)
let vout=v(6)
plot create plot1 vin vclk vout vs time xlabel 'Time [s]' ylabel 'Output ...

.endc
.end
```

 


- 1 Mixed-Signal Design Flow
- 2 AMS Hardware Description Languages
- 3 Device Sizing
- 4 Process and Mismatching Simulation
- 5 The Art of Analog Layout
- 6 Physical Verification
- 7 Parasitics Extraction
- 8 DFM Techniques

Full-Custom Analog IC Design Flow

► From circuit **idea** to **layout** masks...


▲ **EDA-assisted** methodology

 

► **Device sizing** is an intermediate key point!

MOSFET Sizing Analog Guidelines

 - ▶ Transistor (also other devices) matching **ratios**:



multiplicity (**M**)
design for a common
channel aspect
ratio (W/L)

- ▶ Device output **impedance**:

$$\lambda \propto \frac{1}{L} \downarrow$$

- ▶ MOS **transconductance**:

$$M \frac{W}{L} \uparrow \quad g_{m,g,s} \uparrow$$

non-minimum
channel length (**L**)
above design rules
for a given W/L

overall
M and **W/L**
design for a given
absolute L value

$$M \times \frac{W}{L}$$

- ▶ **Bandwidth**, technology **mismatching** and **flicker** noise:


$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} MWL$$

device area (**MWL**)
design for a given
M and W/L

$$\sigma(\Delta P) \simeq \frac{A_P}{\sqrt{MWL}}$$

$$\frac{dv_{nfk}^2}{df} = \frac{K_{fk}}{MWL} \frac{1}{f}$$

- ▶ Physical **layout** considerations:

 

M integer
design for an
overall MW/L


e.g. **M even** values for common centroid layout techniques

- 1 Mixed-Signal Design Flow
- 2 AMS Hardware Description Languages
- 3 Device Sizing
- 4 Process and Mismatching Simulation
- 5 The Art of Analog Layout
- 6 Physical Verification
- 7 Parasitics Extraction
- 8 DFM Techniques

Process Simulation

► Global deviations of model parameters:

 - Same change in **all devices** of the ASIC
- Worse-case **corner** analysis: (t)yp, (f)ast, (s)low...



```

cnm25proc.lib

* CNM25 process corners


.lib common
.model cnm25modn nmos LEVEL = 2
+ TOX = 380E-10 VTO = {vton} NSUB = 2.64E16 UO = {uon}
+ UCRIT = 1E4 UEXP = 6.86E-2 NFS = 7.11E11
+ DELTA = 2.20 RS = 93.8 LD = 9.13E-7 XJ = 8.24E-8
+ VMAX = 5.96E4 NEFF = 1.48 CJ = 3.50E-4 MJ = .40
+ CJSW = 5.95E-10 MJSW = .29 PB = .65
+ AF =1.33 KF =1e-29
.model cnm25modp pmos LEVEL = 2
+ TOX = 380E-10 VTO = {vtop} NSUB = 1.36E16 UO = {uop}
+ UCRIT = 1E4 UEXP = 1.16E-1 NFS = 6.62E11
+ DELTA = 1.82 RS = 134.9 LD = 8.10E-7 XJ = 2.78E-9
+ VMAX = 1.20E5 NEFF = 6.67E-2 CJ = 3.82E-4 MJ = .35
+ CJSW = 7.38E-10 MJSW = .39 PB = .56
+ AF =1.33 KF =1e-29
.model cnm25cpoly c CJ= 4.227E-4 CJSW=0.0
.endl

.lib tt
.param vton=.942
.param vtop=-1.139
.param uon=648
.param uop=213
.lib 'cnm25proc.lib' common
.endl

.lib ss
.param vton=1.1 VTH ↑ slow
.param vtop=-1.3 β ↓
.param uon=415
.param uop=131
.lib 'cnm25proc.lib' common
.endl

.lib ff
.param vton=0.7 VTH ↓ fast
.param vtop=-0.9 β ↑
.param uon=881
.param uop=295
.lib 'cnm25proc.lib' common
.endl


```

 


Process Simulation

► Global deviations of model parameters:

 - Same change in **all devices** of the ASIC
- Worse-case **corner** analysis: (t)yp, (f)ast, (s)low...
- Combined corners: process/voltage/temperature (**PVT**)



■ Montecarlo statistical analysis:

 

```

cnm25proc.lib

* CNM25 process corners

.lib common
.model cnm25modn nmos LEVEL = 2
+ TOX = 380E-10 VTO = {vton} NSUB = 2.64E16 UO = {uon}
+ UCRIT = 1E4 UEXP = 6.86E-2 NFS = 7.11E11
+ DELTA = 2.20 RS = 93.8 LD = 9.13E-7 XJ = 8.24E-8
+ VMAX = 5.96E4 NEFF = 1.48 CJ = 3.50E-4 MJ = .40
+ CJSW = 5.95E-10 MJSW = .29 PB = .65
+ AF =1.33 KF =1e-29
.model cnm25modp pmos LEVEL = 2
+ TOX = 380E-10 VTO = {vtop} NSUB = 1.36E16 UO = {uop}
+ UCRIT = 1E4 UEXP = 1.16E-1 NFS = 6.62E11
+ DELTA = 1.82 RS = 134.9 LD = 8.10E-7 XJ = 2.78E-9
+ VMAX = 1.20E5 NEFF = 6.67E-2 CJ = 3.82E-4 MJ = .35
+ CJSW = 7.38E-10 MJSW = .39 PB = .56
+ AF =1.33 KF =1e-29
.model cnm25cpoly c CJ= 4.227E-4 CJSW=0.0
.endl

.lib tt
.param vton=.942
.param vtop=-1.139
.param uon=648
.param uop=213
.lib 'cnm25proc.lib' common
.endl

.lib ss
.param vton=1.1
.param vtop=-1.3
.param uon=415
.param uop=131
.lib 'cnm25proc.lib' common
.endl

.lib ff
.param vton=0.7
.param vtop=-0.9
.param uon=881
.param uop=295
.lib 'cnm25proc.lib' common
.endl

```

supply voltage


temp.

N/PMOS

$V_{TH} \uparrow$ slow
 $\beta \downarrow$

$V_{TH} \downarrow$ fast
 $\beta \uparrow$


ss sf tt fs ff

 

Mismatching Simulation

► Local deviations of model parameters:

 - Different change for **each device** of the ASIC
- **Pelgrom Law**
- **Montecarlo** statistical analysis:




```

cnm25match.lib

.param avto=30e-9
.param rauo=5e-8
.param rac=7.3e-8

.subckt cnm25modn d g s b param: w=3u l=3u
+ ad=0 as=0 pd=0 ps=0 m=1
.param vton=.942+rndgauss(avto/sqrt(m*w*l))
.param uon=648*(1+rndgauss(rauo/sqrt(m*w*l)))
.model modnlocal nmos level=2 vto={vton} uo={uon} tox=...
mn d g s b modnlocal w={w} l={l}
+ ad={ad} as={as} pd={pd} ps={ps} m={m}
.ends

 .subckt cnm25cpoly t b param: w=30u l=30u m=1
.param cj=4.227E-4*(1+rndgauss(rac/sqrt(m*w*l)))
.model cpolylocal c cj={cj} cjsw=0.0
cpip t b cpolylocal w={w} l={l} m={m}
.ends
  
```




- 1 Mixed-Signal Design Flow
- 2 AMS Hardware Description Languages
- 3 Device Sizing
- 4 Process and Mismatching Simulation
- 5 The Art of Analog Layout
- 6 Physical Verification
- 7 Parasitics Extraction
- 8 DFM Techniques

General Matching Rules

► Unitary elements

e.g. 1 : 2 ratio

 


- Play with **multiplicity** only
- Same ratio for **second order** effects also (e.g. area and perimeter ratio in caps)
- **Larger area** for the overall array

General Matching Rules

- ▶ **Unitary** elements
- ▶ Large **area** devices

e.g. 1 : 1 ratio

 




■ Technology local **granularity**
(e.g. distribution of dopants)

■ **Pelgrom Law** $\propto \frac{1}{\sqrt{WL}}$

General Matching Rules

- ▶ **Unitary** elements
- ▶ Large **area** devices
- ▶ Minimum **distance**


e.g. 1 : 1 ratio

   

- Technology global **drifts**
(e.g. gate oxide thickness slope)
- **Design rule** spacing limits

General Matching Rules

 
- ▶ **Unitary** elements
- ▶ Large **area** devices
- ▶ Minimum **distance**
- ▶ Same **orientation**



- **Anisotropic** materials
(e.g. wafer crystal lattice orientation)
- Longer **routing** may be required...

General Matching Rules

 
- ▶ **Unitary** elements
- ▶ Large **area** devices
- ▶ Minimum **distance**
- ▶ Same **orientation**
- ▶ Same **surround**




- Attenuation of **proximity** effects
- **Inter-device** second order effects (e.g. parasitic RLC)
- **Larger area** for the overall array

General Matching Rules

 - ▶ **Unitary** elements
- ▶ Large **area** devices
- ▶ Minimum **distance**
- ▶ Same **orientation**
- ▶ Same **surround**
- ▶ Same **symmetry**




 
interference
source
(thermal drift,
radio coupling,
power ripple,
mechanical stress)



- **Differential** circuits
(common mode interference)
- **Complex floorplan**

General Matching Rules

  - ▶ **Unitary** elements
- ▶ Large **area** devices
- ▶ Minimum **distance**
- ▶ Same **orientation**
- ▶ Same **sorround**
- ▶ Same **symmetry**




- Compensation of **linear** gradients (and non-linear at short distance)
- **Longer routing** is usually required...

Common Centroid Arrays

- ▼ Difficult to achieve for **large** and **multiple groups** of unitary elements

e.g. A : B : C : D ratios
8 4 2 2

 

Common Centroid Arrays

▼ Difficult to achieve for **large** and **multiple groups** of unitary elements


► Centroid as a **center-of-mass** concept, but with area weights...

$$\sum_{i=1}^M \overbrace{A_i}^{\text{each element area}} \overbrace{(C_i - C_0)}^{\text{center-of-mass coordinates}} = 0$$

$$\text{centroid coordinates } C_0 = \frac{\sum_{i=1}^M A_i C_i}{\sum_{i=1}^M A_i}$$

If all elements are of **same area**:
 
$$C_0 \equiv \frac{1}{M} \sum_{i=1}^M C_i$$



Common Centroid Arrays

▼ Difficult to achieve for **large** and **multiple groups** of unitary elements


► Centroid as a **center-of-mass** concept, but with area weights...

$$\sum_{i=1}^M \overset{\substack{\text{each element} \\ \text{area}}}{A_i} \overset{\substack{\text{center-of-mass} \\ \text{coordinates}}}{(C_i - C_0)} = 0$$

$$\overset{\substack{\text{centroid} \\ \text{coordinates}}}{C_0} = \frac{\sum_{i=1}^M A_i C_i}{\sum_{i=1}^M A_i}$$

If all elements are of **same area**:
 
$$C_0 \equiv \frac{1}{M} \sum_{i=1}^M C_i$$



Center-of-area is the **average** of elements positions...

Common Centroid Arrays


▼ Difficult to achieve for **large** and **multiple groups** of unitary elements

► Centroid as a **center-of-mass** concept, but with area weights...

▲ **Centroid**-based golden rules:

■ **Coincidence** of all centroids

e.g. A : B : C : D ratios
8 4 2 2

 

Not a common centroid arrangement!

Common Centroid Arrays



▼ Difficult to achieve for **large** and **multiple groups** of unitary elements

► Centroid as a **center-of-mass** concept, but with area weights...

▲ **Centroid**-based golden rules:

- **Coincidence** of all centroids
- **Symmetry** for X and Y axes

e.g. A : B : C : D ratios
8 4 2 2

  

Common Centroid Arrays

▼ Difficult to achieve for **large** and **multiple groups** of unitary elements

► Centroid as a **center-of-mass** concept, but with area weights...

▲ **Centroid**-based golden rules:

- **Coincidence** of all centroids
- **Symmetry** for X and Y axes
- **Dispersion** of groups as uniformly as possible

e.g. A : B : C : D ratios
8 4 2 2

A	A	B	C	D	B	A	A
A	A	B	D	C	B	A	A

A	B	A	C	A	D	A	B
B	A	D	A	C	A	B	A

Common Centroid Arrays

▼ Difficult to achieve for **large** and **multiple groups** of unitary elements

► Centroid as a **center-of-mass** concept, but with area weights...

▲ **Centroid**-based golden rules:

- **Coincidence** of all centroids
- **Symmetry** for X and Y axes
- **Dispersion** of groups as uniformly as possible
- **Compactness** of overall array to ideal square shape


e.g. A : B : C : D ratios
8 4 2 2

A	B	A	C	A	D	A	B
B	A	D	A	C	A	B	A

A	B	A	B
C	A	D	A
A	D	A	C
B	A	B	A


PCell-Based Layout

 - ▲ Unitary elements
- ▲ Regular geometry
- ▲ Design rule compliant




Decoupling Guidelines

 - **Signal integrity** between analog, digital, RF... domains






Decoupling Guidelines

 - ▶ **Signal integrity** between analog, digital, RF... domains




   - ▶ Avoiding signal coupling through **power rails**





Decoupling Guidelines


 
- ▶ **Signal integrity** between analog, digital, RF... domains







 
 
- ▶ Avoiding signal coupling through **power rails**







 
 
- ▶ Investing peripheral free area for on-chip **decoupling capacitors**



      OpAmp Layout Examples (real cases from past students)



      OpAmp Layout Examples (real cases from past students)




- 1 Mixed-Signal Design Flow
- 2 AMS Hardware Description Languages
- 3 Device Sizing
- 4 Process and Mismatching Simulation
- 5 The Art of Analog Layout
- 6 Physical Verification**
- 7 Parasitics Extraction
- 8 DFM Techniques


Geometrical Rules

► Basic 2D concepts


e.g. MOSFET gate

 


e.g. MiM capacitor

 

e.g. signal routing

 


e.g. serpentine resistor

 

Geometrical Rules

► Technology rules set

e.g. 2.5um 2P2M CMOS (CNM25)

 


0.0	Design grid is 0.25um x 0.25um
1.1	N-well width $\geq 8\mu\text{m}$
1.2	N-well spacing and notch $\geq 8\mu\text{m}$
2.1	GASAD width $\geq 2\mu\text{m}$
2.2	GASAD spacing and notch $\geq 4\mu\text{m}$
2.3	N-well enclosure of P-plus active $\geq 5\mu\text{m}$
2.4	N-well spacing to N-plus active $\geq 5\mu\text{m}$
3.1	Poly0 width $\geq 2.5\mu\text{m}$
3.2	Poly0 spacing and notch $\geq 6\mu\text{m}$
3.3	Poly0 spacing to GASAD $\geq 6\mu\text{m}$
4.1.a	Poly1 width inside GASAD $\geq 3\mu\text{m}$
4.1.b	Poly1 width outside GASAD $\geq 2.5\mu\text{m}$
4.2	Poly1 spacing and notch $\geq 3\mu\text{m}$
4.3	GASAD extension of Poly1 $\geq 3\mu\text{m}$
4.4	Poly1 extension of GASAD $\geq 2.5\mu\text{m}$
4.5	Poly1 spacing to GASAD $\geq 1.25\mu\text{m}$
4.6	Poly0 enclosure of Poly1 $\geq 3\mu\text{m}$
5.1	N-plus enclosure of GASAD $\geq 2.5\mu\text{m}$
5.2	N-plus spacing to P-plus active $\geq 2.5\mu\text{m}$
5.3	N-plus spacing to Poly1 inside P-plus active $\geq 2\mu\text{m}$
5.4	N-plus extension of Poly1 inside N-plus active $\geq 1.5\mu\text{m}$
5.5	N-plus width $\geq 2.5\mu\text{m}$
5.6	N-plus spacing and notch $\geq 2.5\mu\text{m}$
6.1	Exact contact size = $2.5\mu\text{m} \times 2.5\mu\text{m}$
6.2	Contact spacing $\geq 3\mu\text{m}$
6.3	GASAD enclosure of Contact $\geq 1\mu\text{m}$
6.4	Poly1 enclosure of Contact $\geq 1.25\mu\text{m}$
6.5	Poly1 Contact spacing to GASAD $\geq 2.5\mu\text{m}$
6.6	Contact spacing to Poly1 inside GASAD $\geq 2\mu\text{m}$
6.9	Poly0 enclosure of Contact $\geq 4\mu\text{m}$
6.10	Contact spacing to Poly1 & Poly0 $\geq 4\mu\text{m}$
7.1	Metal1 width $\geq 2.5\mu\text{m}$
7.2	Metal1 spacing and notch $\geq 3\mu\text{m}$
7.3	Metal1 enclosure of Contact $\geq 1.25\mu\text{m}$
8.1	Exact via size = $3\mu\text{m} \times 3\mu\text{m}$
8.2	Via spacing $\geq 3.5\mu\text{m}$
8.3	Metal1 enclosure of Via $\geq 1.25\mu\text{m}$
8.4	Via spacing to Contact $\geq 2.5\mu\text{m}$
8.5	Via spacing to Poly1 $\geq 2.5\mu\text{m}$
9.1	Metal2 width $\geq 3.5\mu\text{m}$
9.2	Metal2 spacing and notch $\geq 3.5\mu\text{m}$
9.3	Metal2 enclosure of Via $\geq 1.25\mu\text{m}$
10.1	Exact passivation window size = $100\mu\text{m} \times 100\mu\text{m}$

Geometrical Rules

► Technology rules set

Process
flow

 

Front end of line (**FEOL**)

Back end of line (**BEOL**)

0.0	Design grid is 0.25um x 0.25um
1.1	N-well width $\geq 8\mu\text{m}$
1.2	N-well spacing and notch $\geq 8\mu\text{m}$
2.1	GASAD width $\geq 2\mu\text{m}$
2.2	GASAD spacing and notch $\geq 4\mu\text{m}$
2.3	N-well enclosure of P-plus active $\geq 5\mu\text{m}$
2.4	N-well spacing to N-plus active $\geq 5\mu\text{m}$
3.1	Poly0 width $\geq 2.5\mu\text{m}$
3.2	Poly0 spacing and notch $\geq 6\mu\text{m}$
3.3	Poly0 spacing to GASAD $\geq 6\mu\text{m}$
4.1.a	Poly1 width inside GASAD $\geq 3\mu\text{m}$
4.1.b	Poly1 width outside GASAD $\geq 2.5\mu\text{m}$
4.2	Poly1 spacing and notch $\geq 3\mu\text{m}$
4.3	GASAD extension of Poly1 $\geq 3\mu\text{m}$
4.4	Poly1 extension of GASAD $\geq 2.5\mu\text{m}$
4.5	Poly1 spacing to GASAD $\geq 1.25\mu\text{m}$
4.6	Poly0 enclosure of Poly1 $\geq 3\mu\text{m}$
5.1	N-plus enclosure of GASAD $\geq 2.5\mu\text{m}$
5.2	N-plus spacing to P-plus active $\geq 2.5\mu\text{m}$
5.3	N-plus spacing to Poly1 inside P-plus active $\geq 2\mu\text{m}$
5.4	N-plus extension of Poly1 inside N-plus active $\geq 1.5\mu\text{m}$
5.5	N-plus width $\geq 2.5\mu\text{m}$
5.6	N-plus spacing and notch $\geq 2.5\mu\text{m}$
6.1	Exact contact size = $2.5\mu\text{m} \times 2.5\mu\text{m}$
6.2	Contact spacing $\geq 3\mu\text{m}$
6.3	GASAD enclosure of Contact $\geq 1\mu\text{m}$
6.4	Poly1 enclosure of Contact $\geq 1.25\mu\text{m}$
6.5	Poly1 Contact spacing to GASAD $\geq 2.5\mu\text{m}$
6.6	Contact spacing to Poly1 inside GASAD $\geq 2\mu\text{m}$
6.9	Poly0 enclosure of Contact $\geq 4\mu\text{m}$
6.10	Contact spacing to Poly1 & Poly0 $\geq 4\mu\text{m}$
7.1	Metal1 width $\geq 2.5\mu\text{m}$
7.2	Metal1 spacing and notch $\geq 3\mu\text{m}$
7.3	Metal1 enclosure of Contact $\geq 1.25\mu\text{m}$
8.1	Exact via size = $3\mu\text{m} \times 3\mu\text{m}$
8.2	Via spacing $\geq 3.5\mu\text{m}$
8.3	Metal1 enclosure of Via $\geq 1.25\mu\text{m}$
8.4	Via spacing to Contact $\geq 2.5\mu\text{m}$
8.5	Via spacing to Poly1 $\geq 2.5\mu\text{m}$
9.1	Metal2 width $\geq 3.5\mu\text{m}$
9.2	Metal2 spacing and notch $\geq 3.5\mu\text{m}$
9.3	Metal2 enclosure of Via $\geq 1.25\mu\text{m}$
10.1	Exact passivation window size = $100\mu\text{m} \times 100\mu\text{m}$

Design Rule Checker


► Programming a rules set...

boolean operations

derived layers

```
cnm25drc.py
...
active = geomGetShapes("GASAD", "drawing")
polygate = geomGetShapes("POLY1", "drawing")
polycap = geomGetShapes("POLY0", "drawing")
gate = geomAnd(polygate, active)
cpoly = geomAnd(polygate, polycap)
geomOffGrid(polygate, 0.25, 1, "0.0. Design grid is ...")
geomWidth(gate, 3, "4.1.a. Poly1 width inside GASAD >= ...")
geomSpace(polygate, 3, diffnet, "4.2. Poly1 spacing...")
geomNotch(polygate, 3, "4.2. Poly1 notch >= 3um")
geomExtension(polygate, active, 2.5, "4.4. Poly1 ext...")
geomEnclose(polycap, cpoly, 3, "4.6. Poly0 enclosure...")
...
```

e.g. 2.5um 2P2M CMOS (CNM25)

 

Design Rule Checker

► Using assisted DRC tools

Run DRC

DRC rules file: ./cnm25drc.py

Help OK Cancel

Library Browser

Libraries

- OpAmpLib
 - template
 - path_test
 - example
 - edit_test
 - drc_test
 - layout
 - cnm25modp_m
 - cnm25modn_m
 - cnm25cpoly_m

Hierarchy Browser

CellView

- drc_test

Message Window

5.X. Checking N-plus...

6.X. Checking contact...

7.X. Checking Metal1...

8.X. Checking Via...

9.X. Checking Metal2...

10.X. Checking Pad...

** Total error count = 110

Report on total DRC error count

Properties for object POLYGON in cell drc_test view layout

Properties Polygon

Name	Type	Value
drcWhy	string	WINDOW POLY0 : 6.9. Poly0 enclosure of Contact >= 4um

Change all selected objects

< Previous Next > Delete Apply OK Cancel

View DRC errors

L2051 NTUB : 2.3. N-well enclosure of P-plus active >= 5um

NTUB L2050 : 2.4. N-well spacing to N-plus active (different net) >= 5um

POLY1 GASAD : 4.3. GASAD extension of Poly1 >= 3um

METAL : 7.2. Metal1 spacing (different net) >= 3um

METAL : 7.1. Metal1 width >= 2.5um

WINDOW GASAD : 6.3. GASAD enclosure of Contact >= 1um

GASAD NPLUS : 5.1. N-plus enclosure of GASAD >= 2.5um

POLY1 : notch < 3.000

VIA POLY1 : 8.5. Via spacing to Poly1 (different net) >= 2.5um

WINDOW : 6.1. Exact contact size = 2.5um x 2.5um

6.0. Contact requires Metal1

CAPS : 10.1. Exact passivation size = 100um x 100um

NPLUS : 5.3. N-plus spacing to Poly1 inside P-plus active (same net) >= 2um

WINDOW POLY1 : 6.4. Poly1 enclosure of Contact >= 1.25um

0.0. Design grid is 0.25um x 0.25um

VIA WINDOW : 8.4. Via spacing to contact (different net) >= 2.5um

WINDOW POLY0 : 6.9. Poly0 enclosure of Contact >= 4um

WINDOW METAL : 7.3. Metal1 enclosure of Contact >= 1.25um

GASAD POLY1 : 4.4. Poly1 extension of GASAD >= 2.5um

4.1 a. Poly1 width inside GASAD >= 3um

GASAD : 2.2. GASAD spacing (same net) >= 4um

WINDOW : 6.10. Contact spacing to Poly1 & Poly0 (different net) >= 4um

NPLUS L2051 : 5.2. N-plus spacing to P-plus active (same net) >= 2.5um

4.1 b. Poly1 width outside GASAD >= 2.5um

Viewed

1

Remaining

2

Help OK Cancel

Layer: POLY1 drawing Selected: 0 FULL X:22.7500 Y:-72.7500




e.g. **glade**
and **CNM25**

- 1 Mixed-Signal Design Flow
- 2 AMS Hardware Description Languages
- 3 Device Sizing
- 4 Process and Mismatching Simulation
- 5 The Art of Analog Layout
- 6 Physical Verification
- 7 Parasitics Extraction
- 8 DFM Techniques

Motivation

► Planar technology parasitics



(2D layout view)

   



Motivation

► Planar technology parasitics

(2D layout view)

  

(2D cross section view)

 
 


Motivation



► Planar technology parasitics

▼ **R** and **L** require node **splitting**!



(2D layout view)

  

(2D cross section view)

  


(3D view)

  

Extraction Tools

 - **Programming** a simple rules set for parasitic overlap capacitance only...



```


...
geomLabel(polygate, "POLY1", "pin", 1)
geomLabel(polygate, "POLY1", "net", 0)
geomConnect([
    [cont, ndiff, pdiff, polygate, polycap, metal1],
    [via12, metal1, metal2]... ])
extractMOS("cnm25modn", ngate, polygate, ndiff, pwell)
extractParasitic3(pdiff, metal2, cmetal2diff, 0,
    [metal1, polygate, polycap])
...

```

e.g. 2.5um 2P2M CMOS (CNM25)

Extraction Tools

 - ▶ Programming a simple rules set for parasitic overlap capacitance only...
- ▶ Using assisted extraction tools...



opamp_par.sub

```
.SUBCKT opamp vinn vinp vout vdd vss ibias
MM0 vdd ibias vdd vdd cnm25modp w=1.2e-05 l=6e-06 as=...
MM1 vdd ibias vout vdd cnm25modp w=1.2e-05 l=6e-06 as=...
Cc0 vinter vout cnm25cpoly w=6.42928e-05 l=0.000156207
MM8 vout ibias vdd vdd cnm25modp w=1.2e-05 l=6e-06 as=...
...
CP1 vinter vss C=3.8582e-13
CP2 vout ibias C=3.33692e-15
CP3 vinp vss C=1.85938e-15
CP4 vout vcomm C=2.0918e-15
...
.ENDS
```

Run Extraction

Extraction rules file: /cnm25xtr_lvs.py

☐ Multithreaded? Max number of threads: []

Help OK Cancel

Glade

File View Edit Create Verify Floorplan Tools Window Help

Start 0 Stop 99

Library Browser

Libraries

- OpAmpLib
 - template
 - path_test
 - example
 - layout
 - extracted
 - edit_test
 - drc_test
 - cnm25modp_m
 - cnm25modn_m
 - cnm25modn
 - cnm25cpoly_m
 - cnm25cpoly

Net Browser

CellView

- example
 - ibias
 - vcomm
 - vdd
 - vinn
 - vinp
 - vinter
 - vload
 - vout
 - vss

Hierarchy Browser

Net Browser

Message

```
>>> # INFO: Cell example contains no nets!
>>> # INFO: Opened cell example view extracted
>>> ** Total device count = 18
# INFO: LPE run completed.
```

Properties for object INST in cell example view extracted

Name	Type	Value
plist	string	[[0.0],[3000.0],[3000.4500],[0.4500]]
type	string	mos
w	float	12
l	float	6
as	float	78
ps	float	37
ad	float	66
pd	float	35

Change all selected objects

< Previous Next > Delete Apply OK Cancel

Properties for object POLYGON in cell example view extracted

Properties Net Polygon

Net Name: vinter

Pin Name(s):

Pin Direction: INOUT

NonDefault Rule:

Special Net: ☐

Pin shapes: 0

Inst pins: 10

Net Use: SIGNAL


Inst Name	Cell Name	Pin Name	Special?
c0	cnm25cpoly\$[[3001.8001],[1,...	B	false
M10	cnm25modp\$[[12000.6000],[...]	D	false
M2	cnm25modn\$[[12000.12000],[...]	B	false

e.g. glade and CNM25


- 1 Mixed-Signal Design Flow
- 2 AMS Hardware Description Languages
- 3 Device Sizing
- 4 Process and Mismatching Simulation
- 5 The Art of Analog Layout
- 6 Physical Verification
- 7 Parasitics Extraction
- 8 DFM Techniques

Going Into Production

 - ▶ From few IC **prototypes** to small and medium **series**
- ▶ Design for manufacturing (**DFM**) layout rules to increase manufacturing **yield**
- ▶ Some **examples**:
 - Dummy **filling**




non-uniform
layer area =
etching
issues

 


Going Into Production

- ▶ From few IC **prototypes** to small and medium **series**
- ▶ Design for manufacturing (**DFM**) layout rules to increase manufacturing **yield**
- ▶ Some **examples**:


- Dummy **filling**

 

 Using few shapes also simplifies optical proximity correction (**OPC**)



non-uniform
layer area =
etching
issues

 



floating
dummy
structures

automatic
filling for
a target
% coverage

Going Into Production


- ▶ From few IC **prototypes** to small and medium **series**
- ▶ Design for manufacturing (**DFM**) layout rules to increase manufacturing **yield**
- ▶ Some **examples**:
 - Dummy **filling**
 - **Antenna** reduction

  charge stored during metal patterning can **break** thin gate oxide:




Going Into Production

 - ▶ From few IC **prototypes** to small and medium **series**
- ▶ Design for manufacturing (**DFM**) layout rules to increase manufacturing **yield**
- ▶ Some **examples**:
 - Dummy **filling**
 - **Antenna** reduction
 - Metal **slotting**
 - **Multiple** contacts
 - Extra **guard rings**



 large
metal area =
mechanical
stress issues



stress-relief
holes