

## 5. CMOS Operational Amplifiers

Francesc Serra Graells

[francesc.serra.graells@uab.cat](mailto:francesc.serra.graells@uab.cat)

Departament de Microelectrònica i Sistemes Electrònics  
Universitat Autònoma de Barcelona

[paco.serra@imb-cnm.csic.es](mailto:paco.serra@imb-cnm.csic.es)


Integrated Circuits and Systems  
IMB-CNM(CSIC)

- 1 OpAmp Figures of Merit
- 2 The Mono-Transistor Amplifier
- 3 Differential Circuits with CMFB
- 4 Folded Amplifiers
- 5 Cascode Topologies
- 6 Gain Enhancement Techniques
- 7 Multi-Stage OpAmps

- 1 OpAmp Figures of Merit
- 2 The Mono-Transistor Amplifier
- 3 Differential Circuits with CMFB
- 4 Folded Amplifiers
- 5 Cascode Topologies
- 6 Gain Enhancement Techniques
- 7 Multi-Stage OpAmps

# Universal Analog Building Block
 
## ► Operational voltage amplifier (OpAmp)




Single ended  
case study

$$V_{out} = GV_{din} + \cancel{G_{cm}V_{cm}}_0$$


with  $G \rightarrow \infty$
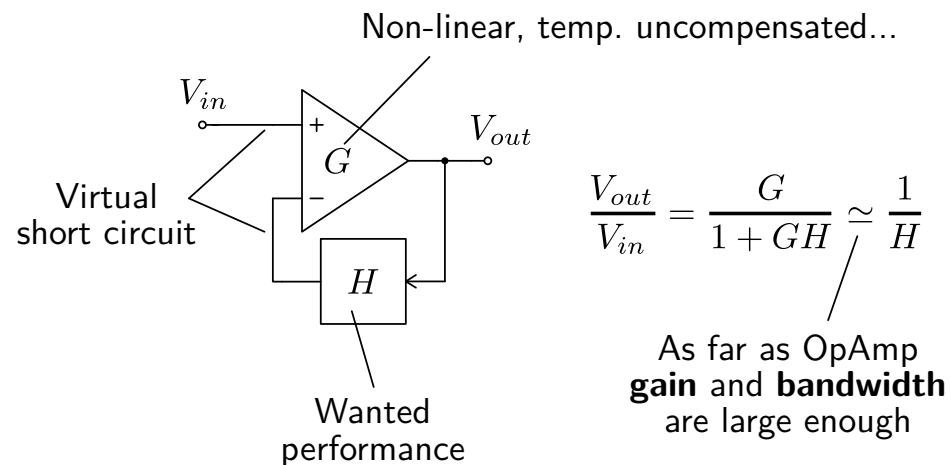
## ▲ Analog computing **operations** in closed loop:




# Universal Analog Building Block

 
## ► Operational voltage amplifier (OpAmp)


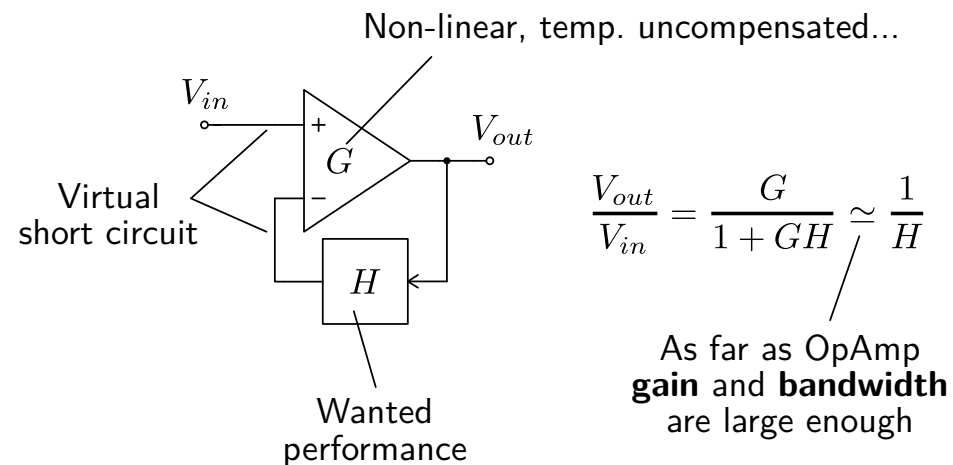
## ▲ Analog computing **operations** in closed loop:




e.g. Instrumentation amplifier

 


$$\frac{V_{out}}{V_{in}} = \left(1 + \frac{2R_2}{R_1}\right) \frac{R_4}{R_3}$$

e.g. I/V converter

 


# Universal Analog Building Block

 
## ► Operational voltage amplifier (OpAmp)


 
## ▲ Analog computing **operations** in closed loop:



 
## ► CMOS OpAmp known as operational transconductance amplifier (OTA)



OpAmp or OTA naming depends on the load conditions...


e.g. switched capacitor (SC) filters

 


# OpAmp Performance Parameters
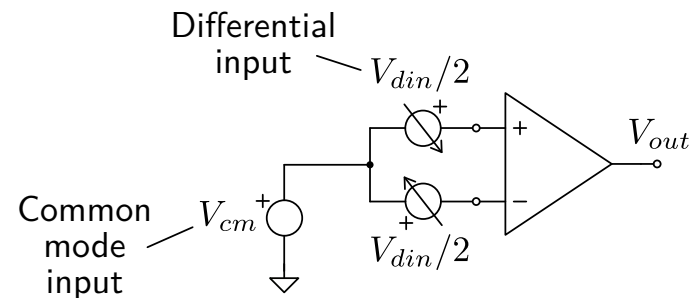
## ► Large signal static figures (ideal):

- Input range  $IR \rightarrow 0$
- Output range  $OR \rightarrow V_{DD}$
- Equivalent input offset  $V_{off} \rightarrow 0$
- Open loop differential DC gain  $G(DC) \rightarrow \infty$



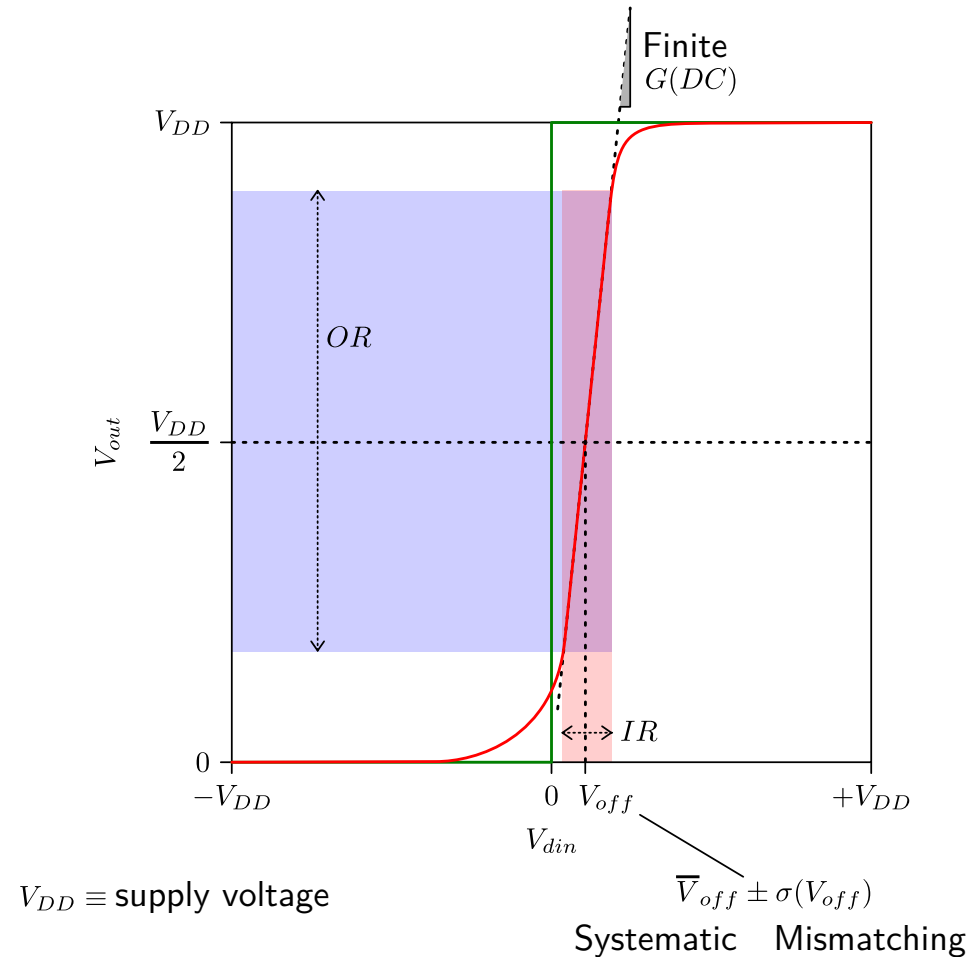
## ► Open-loop differential DC voltage transfer curve (**VTC**) at constant common mode:



# OpAmp Performance Parameters
 
## ► Large signal static figures (ideal):


- Input range  $IR \rightarrow 0$
- Output range  $OR \rightarrow V_{DD}$
- Equivalent input offset  $V_{off} \rightarrow 0$
- Open loop differential DC gain  $G(DC) \rightarrow \infty$
- Common mode range  $CMR_{l,h} \rightarrow 0, V_{DD}$



$$V_{out} = \frac{G}{1+G} V_{in}$$


$$\begin{cases} V_{din} = V_{inp} - V_{inn} \\ V_{cm} = \frac{V_{inp} + V_{inn}}{2} \end{cases} \quad V_{cm} = \frac{1}{2} \frac{1+2G}{1+G} V_{in} \simeq V_{in}$$

Depending on feedback topology!

 

$$V_{cm} \simeq 0$$

## ► Input common-mode DC sweep:

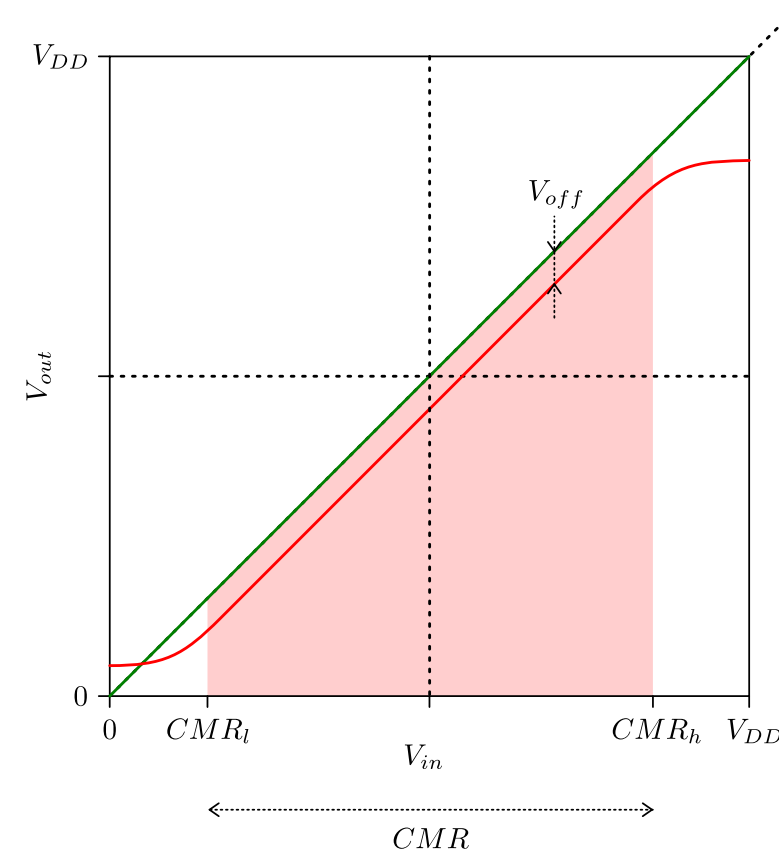





# OpAmp Performance Parameters
 
## ► Small signal dynamic figures (ideal):

- Open loop differential DC gain  $G(DC)$  ( $\rightarrow \infty$ )
- Bandwidth  $BW$  ( $\rightarrow \infty$ )
- Gain-bandwidth product  $GBW$  ( $\rightarrow \infty$ )
- Phase margin  $m_\phi$  ( $\rightarrow 90^\circ$ )
- Equivalent input noise  $v_{neq}$  ( $\rightarrow 0$ )




## ► AC Bode diagram:

 


# OpAmp Performance Parameters
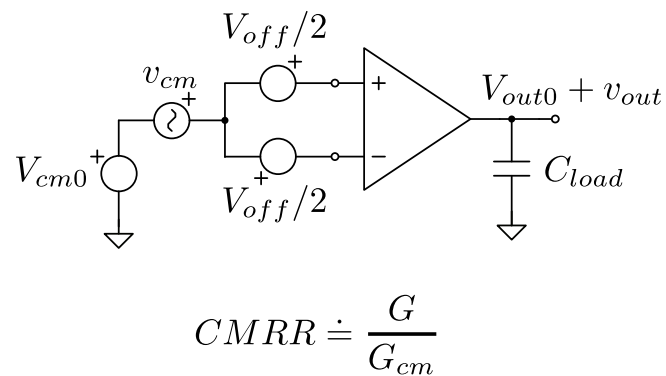
## ► Small signal dynamic figures (ideal):

- Open loop differential DC gain  $G(DC)$  ( $\rightarrow \infty$ )
- Bandwidth  $BW$  ( $\rightarrow \infty$ )
- Gain-bandwidth product  $GBW$  ( $\rightarrow \infty$ )
- Phase margin  $m_\phi$  ( $\rightarrow 90^\circ$ )
- Equivalent input noise  $v_{neq}$  ( $\rightarrow 0$ )
- Common mode rejection ratio  $CMRR$  ( $\rightarrow \infty$ )




## ► AC Bode diagram:

 


# OpAmp Performance Parameters
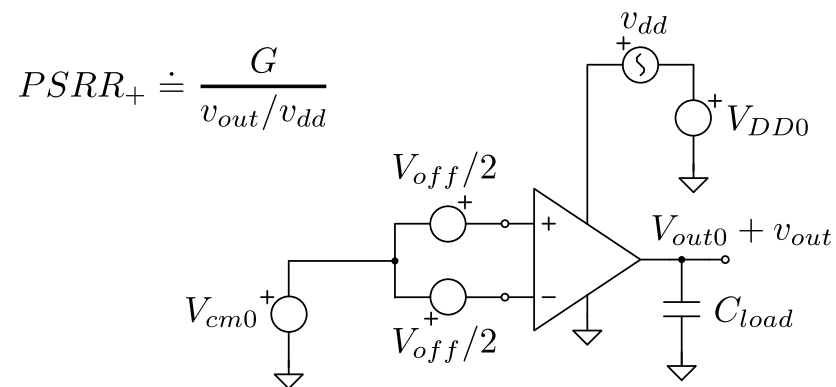
## ► Small signal dynamic figures (ideal):

- Open loop differential DC gain  $G(DC)$  ( $\rightarrow \infty$ )
- Bandwidth  $BW$  ( $\rightarrow \infty$ )
- Gain-bandwidth product  $GBW$  ( $\rightarrow \infty$ )
- Phase margin  $m_\phi$  ( $\rightarrow 90^\circ$ )
- Equivalent input noise  $v_{neq}$  ( $\rightarrow 0$ )
- Common mode rejection ratio  $CMRR$  ( $\rightarrow \infty$ )
- Power supply rejection ratio  $PSRR_{+/-}$  ( $\rightarrow \infty$ )




## ► AC Bode diagram:

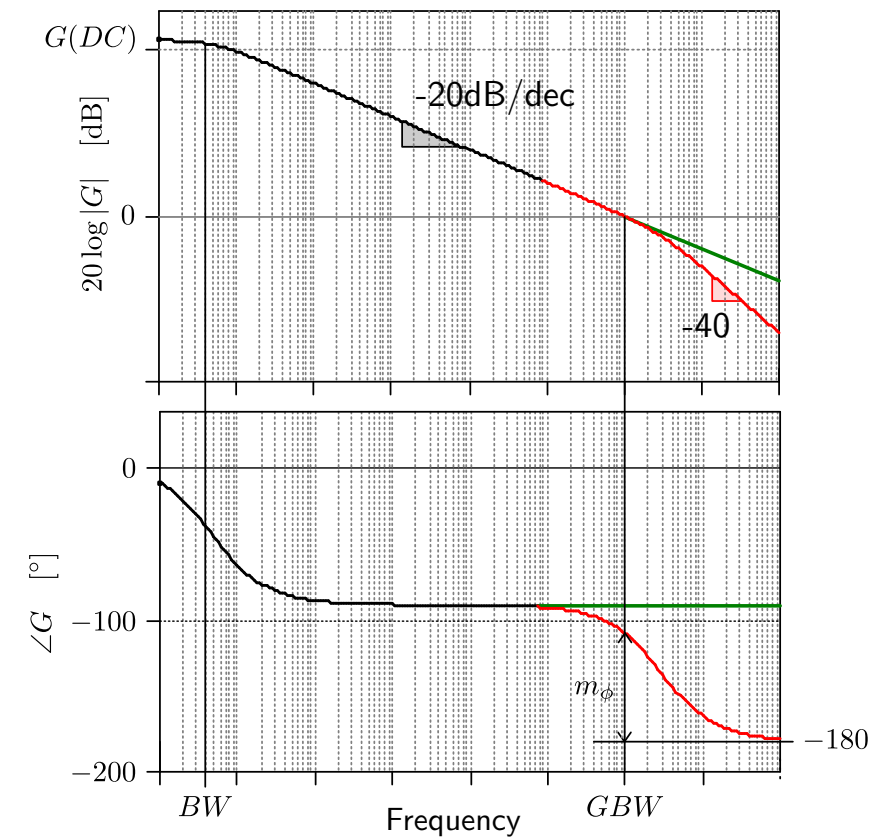


# OpAmp Performance Parameters
 
## ► Large signal dynamic figures (ideal)

- Settling time  $t_s(x\%) \rightarrow 0$




## ► Transient step response:

 



# OpAmp Performance Parameters
 
## ► Large signal dynamic figures (ideal)

- Settling time  $t_s(x\%) \rightarrow 0$
- Slew rate  $SR_{+/-} \rightarrow \infty$




## ► Transient step response:

  

# OpAmp Performance Parameters
 
## ► Large signal dynamic figures (ideal)



- Settling time  $t_s(x\%) \rightarrow 0$
- Slew rate  $SR_{+/-} \rightarrow \infty$
- Maximum frequency  $f_{max} \rightarrow \infty$



$$f_{max} = \frac{SR}{\pi CMR} \ll GBW$$

$$V_{max} = \frac{SR}{2\pi GBW} \ll CMR \quad SR \doteq \min(SR_+, SR_-)$$


## ► Transient harmonic response:

  


# OpAmp Performance Parameters
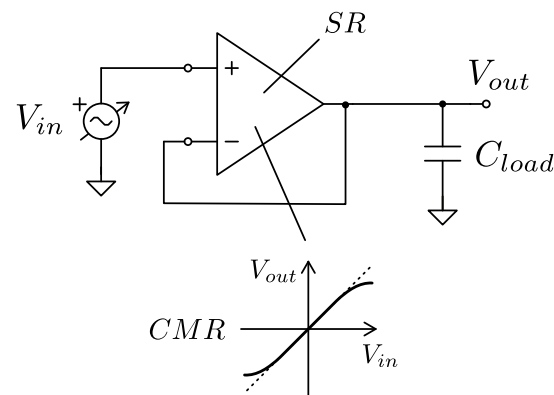
## ► Large signal dynamic figures (ideal)

- Settling time  $t_s(x\%) \rightarrow 0$
- Slew rate  $SR_{+/-} \rightarrow \infty$
- Maximum frequency  $f_{max} \rightarrow \infty$
- Total harmonic distortion  $THD \rightarrow 0$




## ► Transient harmonic response:

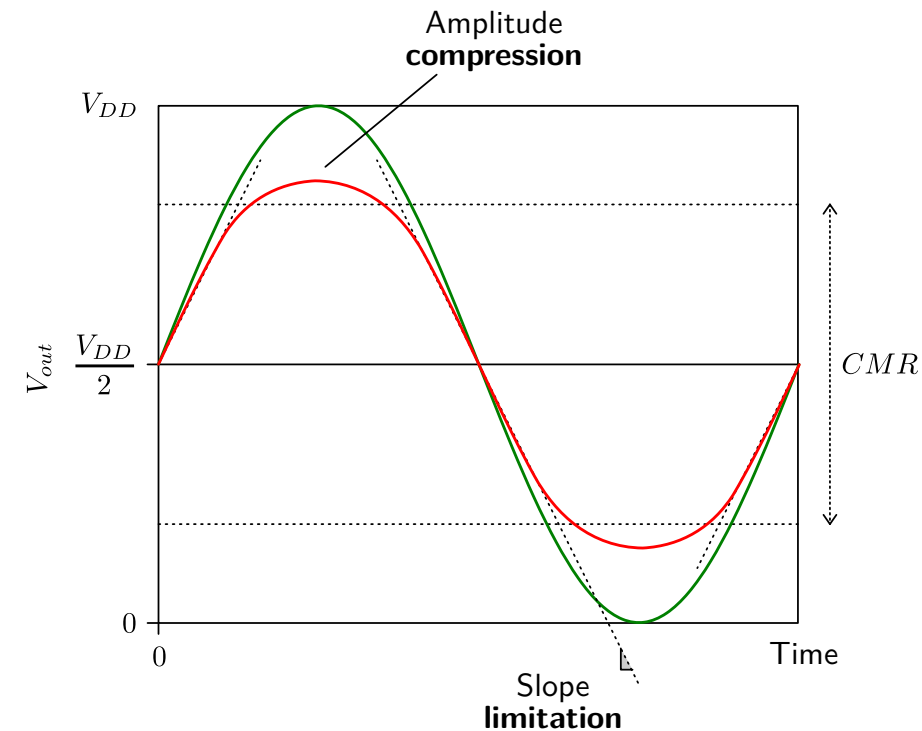

## ► Both static and dynamic non-linearity = **signal distortion**
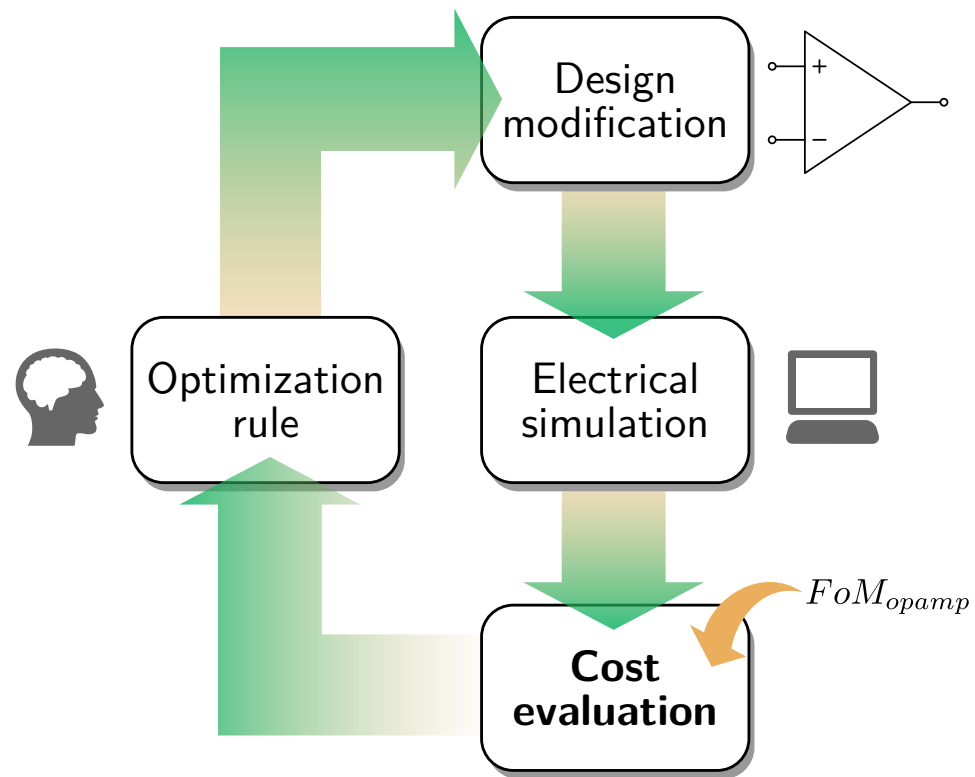
# OpAmp FoMs

- ▲ **Quantitative** design comparison
- ▲ Useful in circuit **optimization**:







# OpAmp FoMs

▲ **Quantitative** design comparison

▲ Useful in circuit **optimization**:

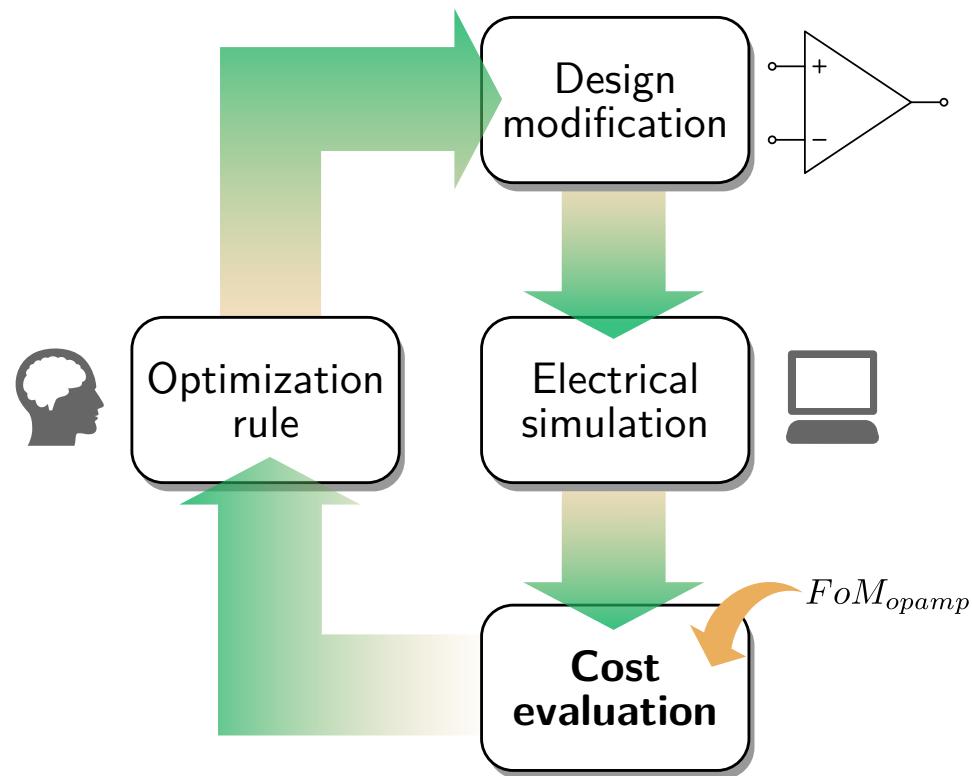

▼ **Too many** performance parameters!

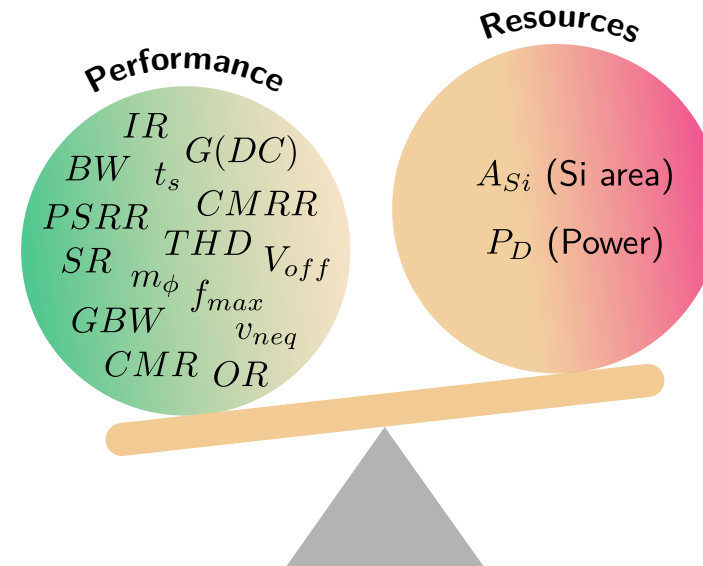




▼ Application **specific** FoMs...

$$FoM_{opamp} \equiv \begin{cases} \frac{C_{load}SR}{P_D} & \text{e.g. line buffer} \\ \frac{1}{P_D v_{neq}^2 A_{Si}} & \text{e.g. pre-amplifier} \\ \frac{C_{load}GBW}{P_D} & \text{e.g. RF amplifier} \end{cases}$$

- 1 OpAmp Figures of Merit
- 2 The Mono-Transistor Amplifier
- 3 Differential Circuits with CMFB
- 4 Folded Amplifiers
- 5 Cascode Topologies
- 6 Gain Enhancement Techniques
- 7 Multi-Stage OpAmps

# Single-Transistor Topologies
  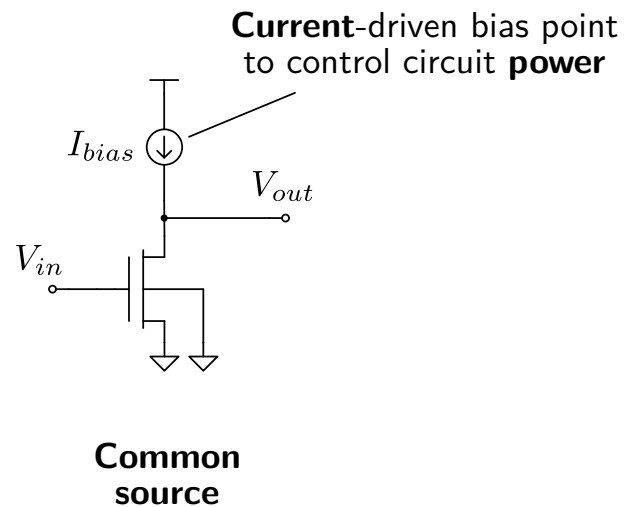
## ► Operational voltage amplifier (OpAmp)?




Supposing **forward saturation**,  
**drain** is selected as output port  
due to its **high impedance (CLM)**:

# Single-Transistor Topologies
 
## ► Operational voltage amplifier (OpAmp)?


Supposing **forward saturation**, **drain** is selected as output port due to its **high impedance (CLM)**:




**Common source**

$$\Delta V_{SB} \equiv n \Delta V_{GB}$$

$$1 < n < 2$$

 

**Common gate**

 

**Back gate**


Power efficiency

► Moderate  $G_m/I_D$

▲ High input **impedance**

▲ **Inverting** amplifier

Easier feedback

 

▲ Highest  $G_m/I_D$

▼ Low input **impedance**

▼ **Non-inverting** amplifier


▼ Lowest  $G_m/I_D$

▼ Low input **impedance**

▲ **Inverting** amplifier

▼ **Latchup**


▼ **Triple-well** required

 

# Voltage Transfer Curve
 
## ► Large signal analysis of common source amplifier:

M1 operating in **strong inversion** and **forward saturation**:




$$I_D = \frac{\beta}{2n} (V_{GB} - V_{TH})^2 [1 + \lambda (V_{DB} - V_{sat})]$$


$$I_{bias} \equiv \frac{\beta}{2n} (V_{bias} - V_{TH})^2$$

$$V_{bias} = \sqrt{\frac{2nI_{bias}}{\beta}} + V_{TH}$$

CLM negligible in large signal

 


e.g. auto-biasing

 

$$V_{sat} = \frac{V_{GB} - V_{TH}}{n} = \frac{V_{bias} - V_{TH}}{n} = \sqrt{\frac{2I_{bias}}{n\beta}}$$
 
# Gain and Frequency Response



► Common source **small signal** analysis:




$$V_{GB} = V_{bias} + v_{in}$$

$$V_{DB} = \frac{V_{DD}}{2} + v_{out}$$

$$V_{SB} \equiv 0$$

  

► **Incremental** equivalent circuit:

 

M1 **strong inversion**  
and forward **saturation**  
bias point

$$I_{bias} \gg I_S = 2n\beta U_t^2$$


$$V_{bias} \gg V_{TH}$$

$$V_{out} \gg V_{sat}$$

$$\begin{cases} g_{mg} = \sqrt{\frac{2\beta I_D}{n}} \equiv \sqrt{\frac{2\beta I_{bias}}{n}} \\ g_{md} = \lambda I_D \equiv \lambda I_{bias} \end{cases}$$

# Gain and Frequency Response

## ► Incremental equivalent circuit:

 

M1 **strong inversion** and forward **saturation** bias point

$$\begin{cases} g_{mg} = \sqrt{\frac{2\beta I_D}{n}} \equiv \sqrt{\frac{2\beta I_{bias}}{n}} \\ g_{md} = \lambda I_D \equiv \lambda I_{bias} \end{cases}$$

$\propto \frac{1}{L}$

## ► DC voltage gain

$$G \doteq \frac{v_{out}}{v_{in}}$$

$$G(DC) = -\frac{g_{mg}}{g_{md}}$$

$$G(DC) = -\frac{1}{\lambda} \sqrt{\frac{2\beta}{nI_{bias}}} \left( \frac{W}{L} \right) \uparrow 3\text{dB/oct}$$

6dB/oct  $L \uparrow$   $I_{bias} \downarrow$  3dB/oct


In general, for **CMOS** amplifiers:

$$|G(DC)| = g_{in} r_{out}$$

input transconductance  $v \rightarrow i$       output resistance  $i \rightarrow v$

# Gain and Frequency Response

## ► Incremental equivalent circuit:

 


M1 **strong inversion** and forward **saturation** bias point

$$\begin{cases} g_{mg} = \sqrt{\frac{2\beta I_D}{n}} \equiv \sqrt{\frac{2\beta I_{bias}}{n}} \\ g_{md} = \lambda I_D \equiv \lambda I_{bias} \end{cases} \begin{matrix} (\frac{W}{L}) \\ \propto \frac{1}{L} \end{matrix}$$

## ► Spectral bandwidth

$$G(DC) = -\frac{g_{mg}}{g_{md}}$$

 


$$BW = \frac{g_{md}}{2\pi c_{load}}$$

$$GBW = \frac{g_{mg}}{2\pi c_{load}} = \frac{1}{2\pi c_{load}} \sqrt{\frac{2\beta I_{bias}}{n}} \begin{matrix} I_{bias} \uparrow 0.5\text{oct/oct} \\ (\frac{W}{L}) \uparrow 0.5\text{oct/oct} \end{matrix}$$



# Dynamic Range

## ► Noise equivalent circuit:

 


$$\frac{dv_{nfk}^2}{df} = \frac{K_{fk}}{WL} \frac{1}{f} \quad \frac{di_{nth}^2}{df} = \frac{8}{3} K T n g_{mg}$$

Uncorrelated phenomena and low-frequency:


$$\frac{dv_{nout}^2}{df} = \frac{8}{3} K T n \frac{g_{mg}}{g_{md}^2} + \frac{K_{fk}}{WL} \left( \frac{g_{mg}}{g_{md}} \right)^2 \frac{1}{f} |G(DC)|^2$$

$$v_{nout}^2 = \frac{8}{3} K T n \frac{g_{mg}}{g_{md}^2} \underbrace{(f_2 - f_1)}_{BW} + \frac{K_{fk}}{WL} \left( \frac{g_{mg}}{g_{md}} \right)^2 \ln \frac{f_2}{f_1}$$
 
## ► Thermal noise contribution only ( $f >$ flicker corner):



Equivalent input noise:

 


$$v_{out} = v_{nout} + G(v_{in} - v_{out})$$

$$v_{out} = \frac{G v_{in} + v_{nout}}{1 + G} \simeq v_{in} + \underbrace{\frac{v_{nout}}{G}}_{v_{nin}}$$


# Dynamic Range

## ► Noise equivalent circuit:

 


$$\frac{dv_{nfk}^2}{df} = \frac{K_{fk}}{WL} \frac{1}{f} \quad \frac{di_{nth}^2}{df} = \frac{8}{3} K T n g_{mg}$$
 
$$v_{nout}^2 = \frac{8}{3} K T n \frac{g_{mg}}{g_{md}^2} \underbrace{(f_2 - f_1)}_{BW} + \frac{K_{fk}}{WL} \left( \frac{g_{mg}}{g_{md}} \right)^2 \ln \frac{f_2}{f_1}$$


 
## ► Thermal noise contribution only ( $f >$ flicker corner):




$$v_{nin}^2 \doteq \frac{v_{nout}^2}{|G(DC)|^2} = \frac{8}{3} \frac{K T n}{g_{mg}} BW = \frac{8}{3} \frac{K T n^{3/2}}{\sqrt{2\beta}} \frac{BW}{\sqrt{I_{bias}}}$$

$$DR = \left( \frac{V_{FS}/2\sqrt{2}}{v_{nin}} \right)^2 = \frac{3\sqrt{2}}{64} \frac{(V_{DD} - 2V_{sat})^2}{K T BW} \sqrt{\frac{\beta I_{bias}}{n^3}} \uparrow$$

$V_{DD} \uparrow$  (1.5dB/oct)  
 $(\frac{W}{L}) \uparrow$   
 $T \downarrow$  (3dB/oct)  
 $I_{bias} \uparrow$

# Full CMOS Circuit


► Similar performance analysis:

 

All operating in **strong inversion** and forward **saturation** bias points:

$$V_{sat1} = \sqrt{\frac{2I_{bias}}{n\beta_1}} \quad V_{sat2} = \sqrt{\frac{2I_{bias}}{n\beta_2}} \quad \left(\frac{W}{L}\right)_2$$


► Large signal **VTC**:

 

$$OR = V_{DD} - V_{sat1} - V_{sat2}$$

# Full CMOS Circuit

► Similar performance analysis:

 

All operating in **strong inversion** and forward **saturation** bias points:

$$\left(\frac{W}{L}\right)_x \begin{cases} g_{mx} = \sqrt{\frac{2\beta_x I_{bias}}{n}} \\ L_x \end{cases} \quad \begin{cases} g_{mdx} = \lambda_x I_{bias} \end{cases}$$

► Small signal **gain** and **bandwidth**:

$$G(DC) = -\frac{g_{m1}}{g_{md1} + g_{md2}} \quad \left(\frac{W}{L}\right)_1 \uparrow 3\text{dB/oct}$$

$$G(DC) = -\frac{1}{\lambda_1 + \lambda_2} \sqrt{\frac{2\beta_1}{nI_{bias}}} \quad \begin{matrix} 6\text{dB/oct} & L_{1,2} \uparrow & I_{bias} \uparrow 3\text{dB/oct} \end{matrix}$$


$$BW = \frac{g_{m1} + g_{m2}}{2\pi C_{load}} \quad I_{bias} \uparrow 0.5\text{oct/oct}$$

$$GBW = \frac{g_{m1}}{2\pi C_{load}} = \frac{1}{2\pi C_{load}} \sqrt{\frac{2\beta_1 I_{bias}}{n}} \quad \begin{matrix} \left(\frac{W}{L}\right)_1 \uparrow 0.5\text{oct/oct} \end{matrix}$$

- 1 OpAmp Figures of Merit
- 2 The Mono-Transistor Amplifier
- 3 Differential Circuits with CMFB
- 4 Folded Amplifiers
- 5 Cascode Topologies
- 6 Gain Enhancement Techniques
- 7 Multi-Stage OpAmps

# Fully-Differential vs Single-Ended

## ► Single-ended OpAmps:

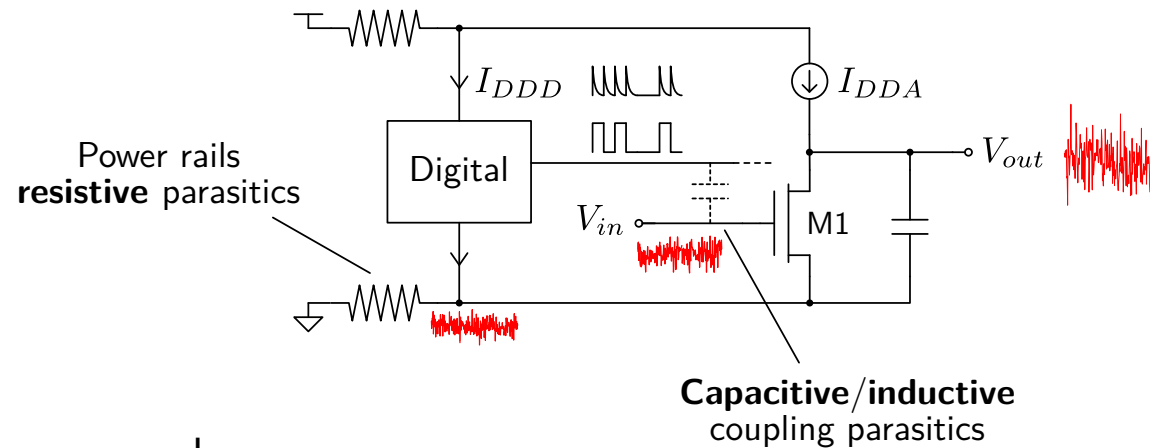

▲ Compact **area** and **power**

▼ Poor **signal integrity**

## ► Dynamic sources of **interference**:

- Large signals (e.g. digital states)
- Power supply currents
- EM fields
- Temperature gradients
- Mechanical stress


# Fully-Differential vs Single-Ended

## ► Pseudo-differential OpAmps:

Signal **true info**

$$\begin{cases} V_{ind} \doteq V_{inp} - V_{inn} \\ V_{inc} \doteq \frac{V_{inp} + V_{inn}}{2} \end{cases}$$

Signal **baseline** only

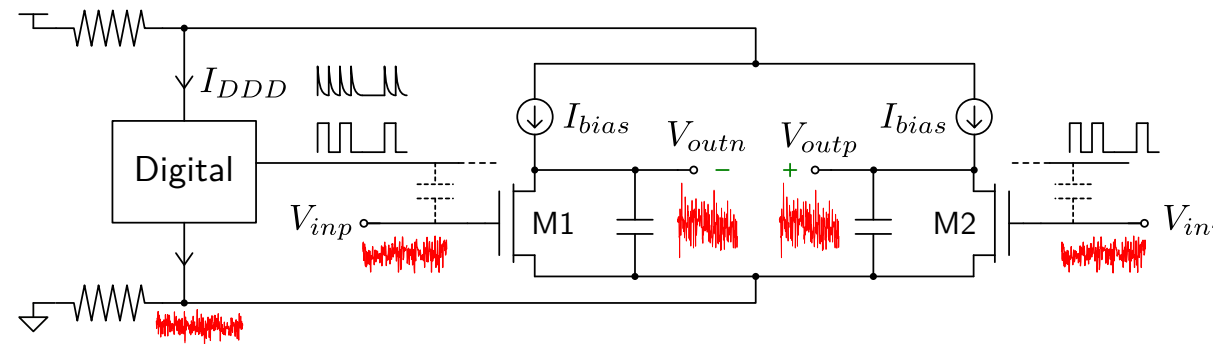

$$\begin{cases} V_{outd} \doteq V_{outp} - V_{outn} \\ V_{outc} \doteq \frac{V_{outp} + V_{outn}}{2} \end{cases}$$

## ▲ Interference **rejection**

## ▼ **Area** and **power** overheads (x2)


# Fully-Differential vs Single-Ended

## ► Pseudo-differential OpAmps:

Signal **true info**

$$\begin{cases} V_{ind} \doteq V_{inp} - V_{inn} \\ V_{inc} \doteq \frac{V_{inp} + V_{inn}}{2} \end{cases}$$

Signal **baseline** only

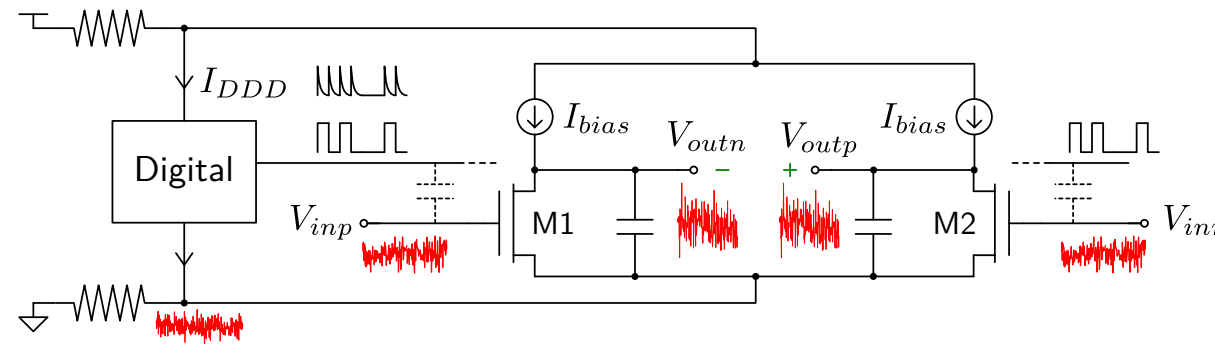


$$\begin{cases} V_{outd} \doteq V_{outp} - V_{outn} \\ V_{outc} \doteq \frac{V_{outp} + V_{outn}}{2} \end{cases}$$

▲ Interference **rejection**

▼ **Area** and **power** overheads (x2)

 ▲ **Full-scale** extension (+6dB) } SNR  
▼ **Noise** increase (+3dB) } (+3dB)






# Fully-Differential vs Single-Ended

## ► Pseudo-differential OpAmps:

Signal **true info**

$$\begin{cases} V_{ind} \doteq V_{inp} - V_{inn} \\ V_{inc} \doteq \frac{V_{inp} + V_{inn}}{2} \end{cases}$$

Signal **baseline** only

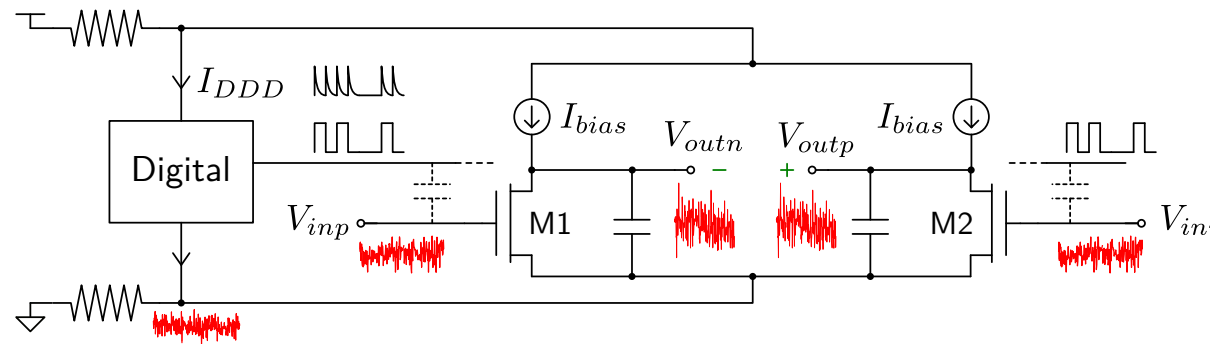

$$\begin{cases} V_{outd} \doteq V_{outp} - V_{outn} \\ V_{outc} \doteq \frac{V_{outp} + V_{outn}}{2} \end{cases}$$


▲ Interference **rejection**

▼ **Area** and **power** overheads (x2)

▲ **Full-scale** extension (+6dB) } SNR  
▼ **Noise** increase (+3dB) } (+3dB)


▲ **Distortion** cancellation (even harm.)

▼ Limited by device **matching**

 

# Fully-Differential OpAmps

► **Basic CMOS topology:**

 

$$\left\{ \begin{array}{l} V_{ind} \doteq V_{inp} - V_{inn} \\ V_{inc} \doteq \frac{V_{inp} + V_{inn}}{2} \end{array} \right.$$

device  
multiplicity


$$M \times \frac{W}{L}$$

same  
aspect  
ratio

$$\left\{ \begin{array}{l} V_{outd} \doteq V_{outp} - V_{outn} \\ V_{outc} \doteq \frac{V_{outp} + V_{outn}}{2} \end{array} \right.$$

# Fully-Differential OpAmps


## ► Basic CMOS topology:

 

$$\begin{cases} V_{ind} \doteq V_{inp} - V_{inn} \\ V_{inc} \doteq \frac{V_{inp} + V_{inn}}{2} \end{cases} \quad \begin{array}{l} \text{device} \\ \text{multiplicity} \\ M \times \frac{W}{L} \end{array}$$


$$\begin{cases} V_{outd} \doteq V_{outp} - V_{outn} \\ V_{outc} \doteq \frac{V_{outp} + V_{outn}}{2} \end{cases} \quad \begin{array}{l} \text{same} \\ \text{aspect} \\ \text{ratio} \end{array}$$

## ► Differential **input** only:

 

# Fully-Differential OpAmps


## ► Basic CMOS topology:

 

$$\begin{cases} V_{ind} \doteq V_{inp} - V_{inn} \\ V_{inc} \doteq \frac{V_{inp} + V_{inn}}{2} \end{cases} \quad \begin{array}{l} \text{device} \\ \text{multiplicity} \\ M \times \frac{W}{L} \end{array}$$
  

$$\begin{cases} V_{outd} \doteq V_{outp} - V_{outn} \\ V_{outc} \doteq \frac{V_{outp} + V_{outn}}{2} \end{cases} \quad \begin{array}{l} \text{same} \\ \text{aspect} \\ \text{ratio} \end{array}$$


## ► Differential **input** only:

 

- ▼ M5-6 current mirror **asymmetry**
- ▼ Not full **cancellation** of unwanted terms
- ▲ Mostly used for **single-ended** signaling

# Fully-Differential OpAmps


## Basic CMOS topology:

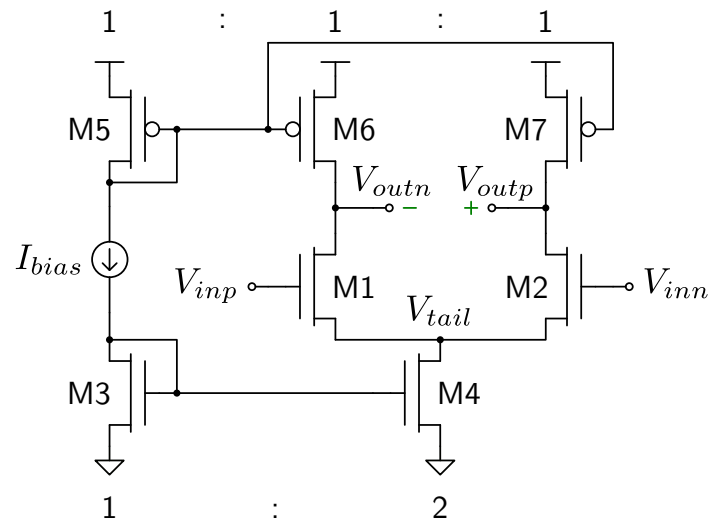

$$\begin{cases} V_{ind} \doteq V_{inp} - V_{inn} \\ V_{inc} \doteq \frac{V_{inp} + V_{inn}}{2} \end{cases}$$

$$\begin{cases} V_{outd} \doteq V_{outp} - V_{outn} \\ V_{outc} \doteq \frac{V_{outp} + V_{outn}}{2} \end{cases}$$

## Large signal VTC:

 


All operating in strong inversion  
saturation + neglecting CLM

$$V_{sat7} = \sqrt{\frac{2I_{bias}}{n\beta_7}} \quad V_{sat2} \simeq \frac{V_{inc} - V_{TH}}{n}$$

# Fully-Differential OpAmps


## Basic CMOS topology:

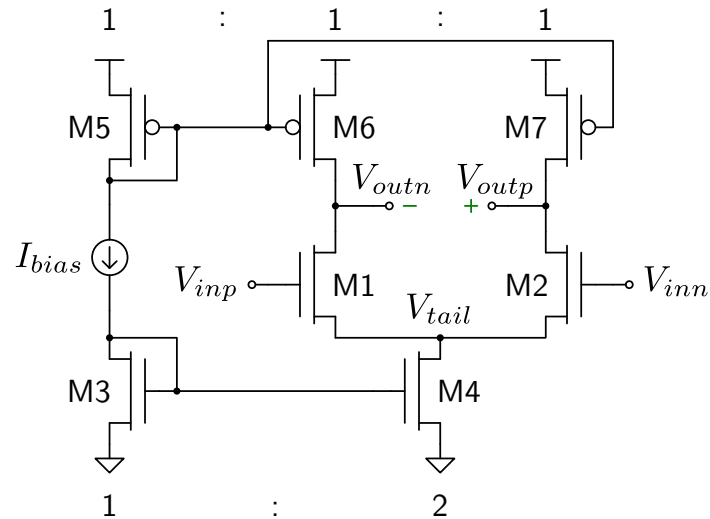

## Reduced output range

$$OR = 2V_{DD} - 4V_{sat1,2} \quad V_{sat1,2} \simeq \frac{V_{inc} - V_{TH}}{n}$$

## Large signal VTC:

 


All operating in strong inversion  
saturation + neglecting CLM


# Fully-Differential OpAmps

All operating in strong inversion  
saturation + neglecting CLM

## Basic CMOS topology:

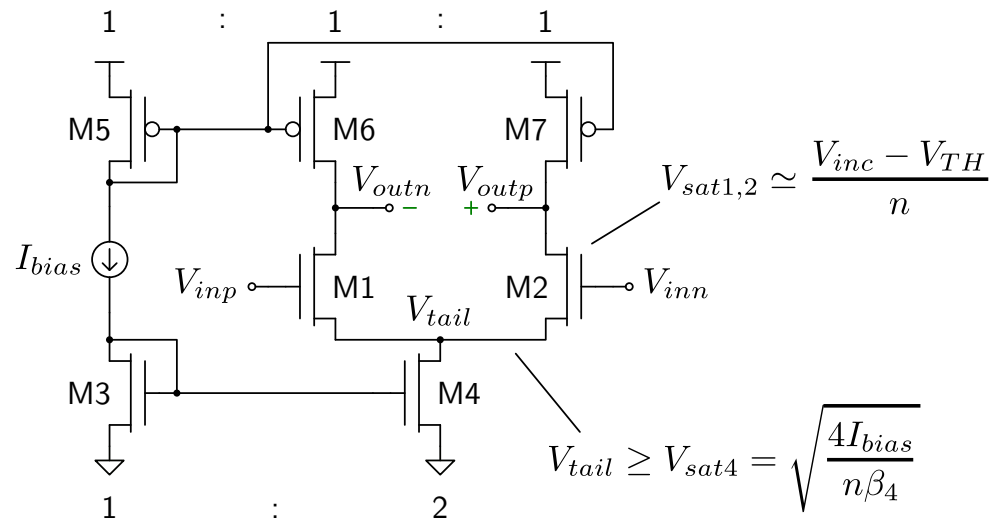

## Large signal VTC:

 

## Reduced output range


$$OR = 2V_{DD} - 4V_{sat1,2}$$

$$I_{bias} = \frac{\beta_{1,2}}{2n} (V_{inc} - V_{TH} - nV_{tail})^2$$


# Fully-Differential OpAmps

All operating in strong inversion  
saturation + neglecting CLM

## Basic CMOS topology:

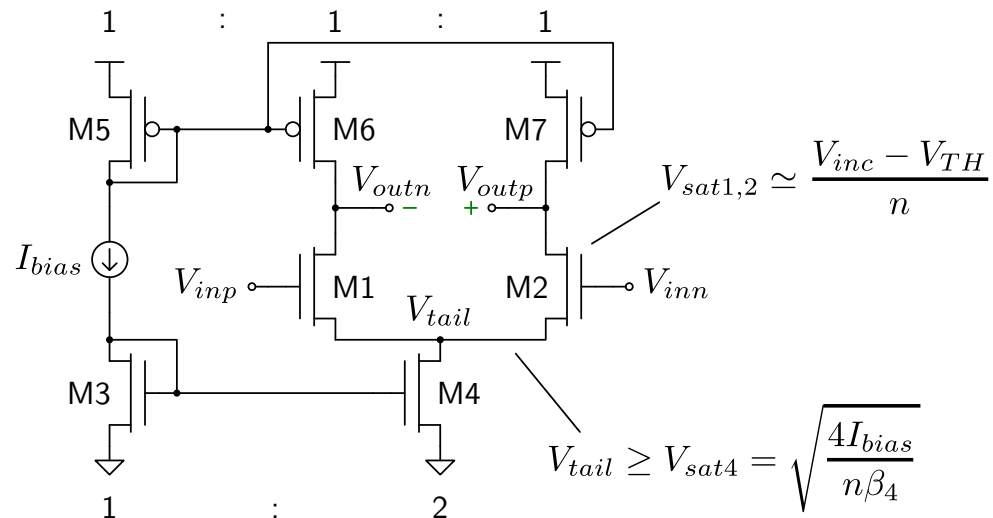

## Large signal VTC:

 

## Reduced output range

$$OR = 2V_{DD} - 4V_{sat1,2}$$

$$I_{bias} = \frac{\beta_{1,2}}{2n} (V_{inc} - V_{TH} - nV_{tail})^2$$

$$V_{sat1,2} = \sqrt{\frac{2I_{bias}}{n\beta_{1,2}}} + V_{sat4}$$


$$OR = 2V_{DD} - 4\sqrt{\frac{2I_{bias}}{n\beta_{un}}} \left[ \sqrt{\left(\frac{L}{W}\right)_{1,2}} + \sqrt{2\left(\frac{L}{W}\right)_4} \right] \uparrow \left(\frac{W}{L}\right)_{1,2} \uparrow \left(\frac{W}{L}\right)_4 \uparrow$$



# Fully-Differential OpAmps

All operating in strong inversion  
saturation + neglecting CLM


## Basic CMOS topology:

 

▼ Reduced **output range**

▼ More **offset** contributions

## Large signal **VTC**:

 


Threshold voltage  
**mismatching** only

$$\sigma^2(V_{off}) = \sigma^2(\Delta V_{TH1,2}) + \left( \frac{g_{m3,4}}{g_{m1,2}} \right)^2 \sigma^2(\Delta V_{TH6,7}) = \frac{A_{VTHN}^2}{(WL)_{1,2}} + \underbrace{\frac{\beta_{up}}{\beta_{un}} \frac{(W/L)_{6,7}}{(W/L)_{1,2}} \frac{A_{VTHP}^2}{(WL)_{6,7}}}_{\text{negligible}} \downarrow (WL)_{1,2} \uparrow$$


Pelgrom's Law

# Fully-Differential OpAmps

## Basic CMOS topology:

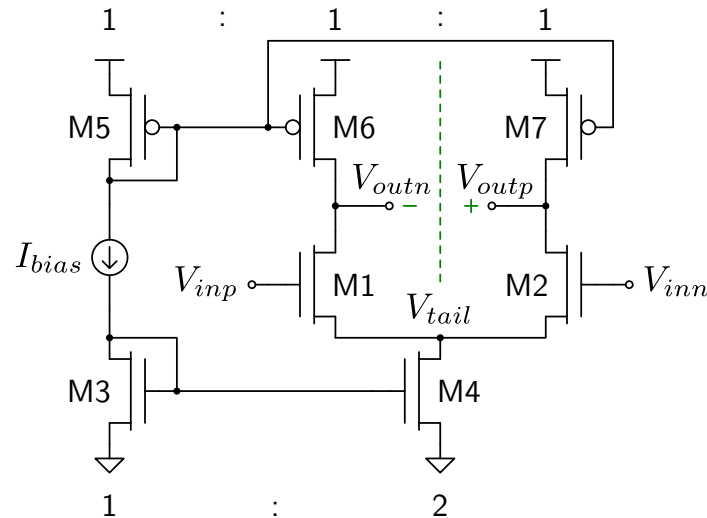
 
## Small signal differential and common DC gains:



$$\begin{cases} i_p = g_{mg2}v_{inn} - g_{ms2}v_{tail} + g_{md2}v_{outp} \\ i_n = g_{mg1}v_{inp} - g_{ms1}v_{tail} + g_{md1}v_{outn} \end{cases} \quad \begin{cases} g_{md7}v_{outp} = -i_p \\ g_{md6}v_{outn} = -i_n \end{cases}$$


$$i_n + i_p = g_{md4}v_{tail}$$

$$(g_{md7} + g_{md2})v_{outp} - (g_{md6} + g_{md1})v_{outn} + \frac{g_{ms1} - g_{ms2}}{g_{ms1} + g_{ms2} + g_{md4}}(g_{md2}v_{outp} + g_{md1}v_{outn}) =$$


$$= g_{mg1}v_{inp} - g_{mg2}v_{inn} + \frac{g_{ms2} - g_{ms1}}{g_{ms1} + g_{ms2} + g_{md4}}(g_{mg1}v_{inp} + g_{mg2}v_{inn})$$

# Fully-Differential OpAmps

## Basic CMOS topology:

 
 
## Small signal differential and common DC gains:



$$\begin{cases} i_p = g_{m2}v_{inn} - g_{m3}v_{tail} + g_{m2}v_{outp} \\ i_n = g_{m1}v_{inp} - g_{m1}v_{tail} + g_{m1}v_{outn} \end{cases} \quad \begin{cases} g_{m7}v_{outp} = -i_p \\ g_{m6}v_{outn} = -i_n \end{cases}$$

$$i_n + i_p = g_{m4}v_{tail}$$

differential output

$v_{outd}$

$$(g_{m7} + g_{m2})v_{outp} - (g_{m6} + g_{m1})v_{outn} + \frac{g_{m1} - g_{m2}}{g_{m1} + g_{m2} + g_{m4}}(g_{m2}v_{outp} + g_{m1}v_{outn}) =$$

$$= g_{m1}v_{inp} - g_{m2}v_{inn} + \frac{g_{m2} - g_{m1}}{g_{m1} + g_{m2} + g_{m4}}(g_{m1}v_{inp} + g_{m2}v_{inn})$$

$v_{ind}$   
differential input


$v_{inc}$   
common input

common output

$v_{outc}$

# Fully-Differential OpAmps


## Basic CMOS topology:

 

differential output

$$\begin{aligned}
 (g_{md7} + g_{md2})v_{outp} - (g_{md6} + g_{md1})v_{outn} + \frac{g_{ms1} - g_{ms2}}{g_{ms1} + g_{ms2} + g_{md4}}(g_{md2}v_{outp} + g_{md1}v_{outn}) &= \\
 = g_{mg1}v_{inp} - g_{mg2}v_{inn} + \frac{g_{ms2} - g_{ms1}}{g_{ms1} + g_{ms2} + g_{md4}}(g_{mg1}v_{inp} + g_{mg2}v_{inn}) &= \\
 v_{ind} &= \text{differential input}
 \end{aligned}$$
 
## Small signal differential and common DC gains:




## Perfect matching (M1=M2 and M6=M7):

$$\left. \begin{aligned} G_d &\doteq \frac{v_{outd}}{v_{ind}} = \frac{g_{mg1,2}}{g_{md1,2} + g_{md6,7}} \\ G_c &\doteq \frac{v_{outd}}{v_{inc}} \equiv 0 \end{aligned} \right\} CMRR \doteq \frac{G_d}{G_c} = \infty$$

# Fully-Differential OpAmps

## Basic CMOS topology:

 


## Real matching (e.g. $V_{TH1} \neq V_{TH2}$ ):

$$\begin{cases} g_{m1,2} = \frac{g_{m1} + g_{m2}}{2} \\ \Delta g_{m1,2} = \frac{g_{m1} - g_{m2}}{2} \end{cases}$$

Neglecting  
common output

$$(g_{md1,2} + g_{md6,7})v_{outd} = g_{m1,2}v_{ind} + 2\Delta g_{m1,2}v_{inc} - \frac{2\Delta g_{m1,2}}{2g_{m1,2} + g_{md4}/n}(2g_{m1,2}v_{inc} + \Delta g_{m1,2}v_{ind})$$
 
## Small signal differential and common DC gains:



## Perfect matching ( $M1=M2$ and $M6=M7$ ):

$$\left. \begin{aligned} G_d &\doteq \frac{v_{outd}}{v_{ind}} = \frac{g_{m1,2}}{g_{md1,2} + g_{md6,7}} \\ G_c &\doteq \frac{v_{outd}}{v_{inc}} \equiv 0 \end{aligned} \right\} CMRR \doteq \frac{G_d}{G_c} = \infty$$


$$CMRR = \frac{g_{m1,2}}{2\Delta g_{m1,2}} \left( \frac{2ng_{m1,2}}{g_{md4}} + 1 \right) \uparrow$$

Matching  $\uparrow$

Tail current sink impedance  $\uparrow$

# Fully-Differential OpAmps

## ► Basic CMOS topology:

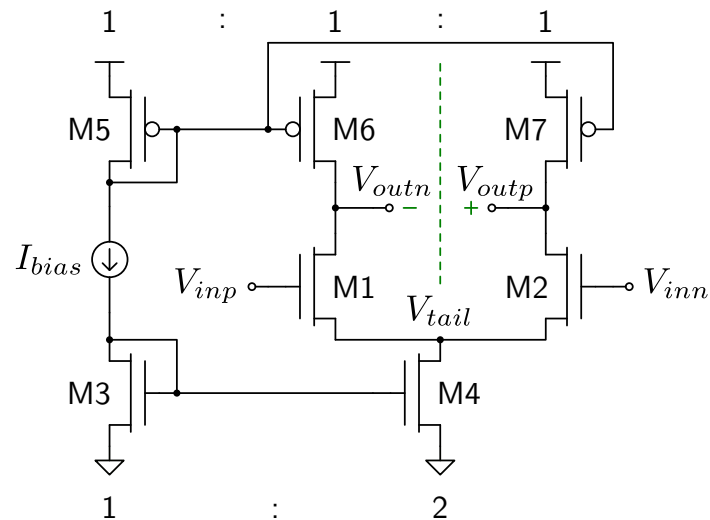


▼ Reduced **output range**

▼ **Matching** is critical

## ► Summary of **design guidelines**:



$OR \uparrow$	$\left(\frac{W}{L}\right)_{1,2} \uparrow$	$\left(\frac{W}{L}\right)_{3,4} \uparrow$	$I_{bias} \downarrow$
$\sigma(V_{off}) \downarrow$	$(WL)_{1,2} \uparrow$	$\left(\frac{W}{L}\right)_{1,2} \uparrow$	$I_{bias} \uparrow$
$G_d \uparrow$	$\left(\frac{W}{L}\right)_{1,2} \uparrow$	$L_{1,2,5,6,7} \uparrow$	$I_{bias} \downarrow$
$CMRR \uparrow$	$(WL)_{1,2} \uparrow$	$L_{3,4} \uparrow$	$I_{bias} \downarrow$
$GBW \uparrow$	$\left(\frac{W}{L}\right)_{1,2} \uparrow$		$I_{bias} \uparrow$
$v_{nin}^2 \downarrow$	$\left(\frac{W}{L}\right)_{1,2} \uparrow$		$I_{bias} \uparrow$

 

# Common-Mode Output Issue

## ► Single-ended differential OpAmps:



e.g. max.  
feedback

  

$$V_{inc} \simeq V_{out} \simeq V_{in}$$

▲ **Well-defined and stable**  
common-mode level

## ► Fully-differential OpAmps:

  


High sensitivity to  
**technology mismatching**  
(M5-M6|7 and M3-M4)!

$$V_{inc} \equiv V_{outc} = ?$$

▼ Specific auxiliary **control**  
**circuitry** is needed in practice...


# Common-Mode Output Issue

- Common-mode feedback (**CMFB**) loop:

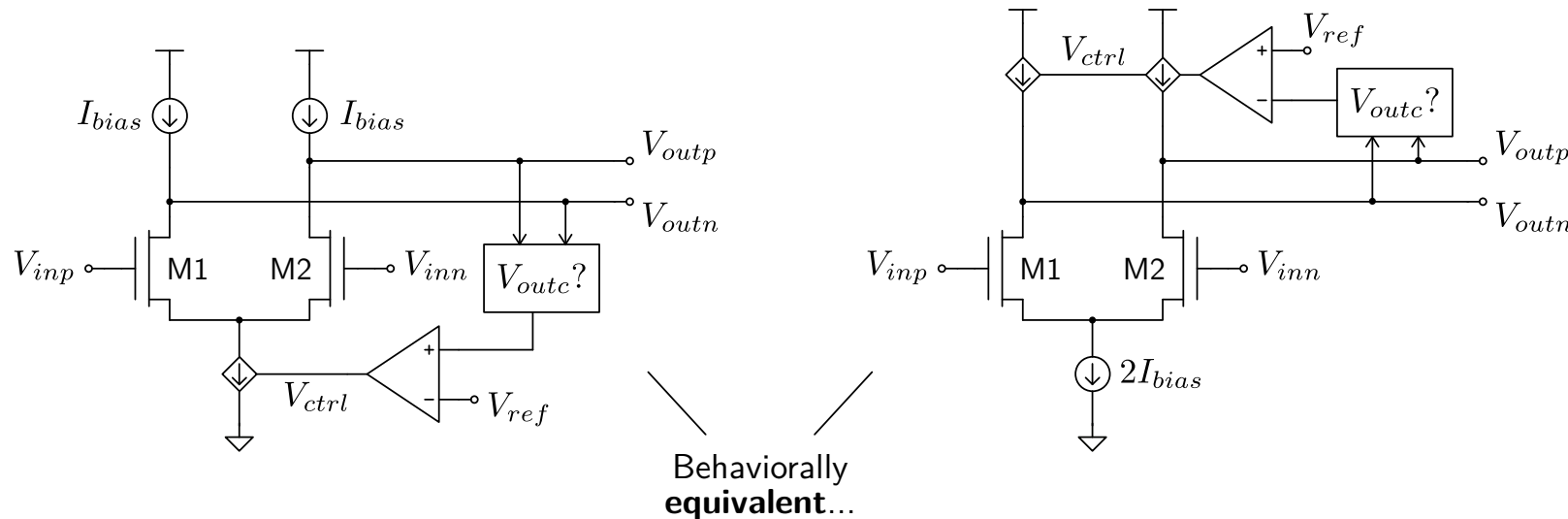

- CMFB control **functionality**:
  - Sensing common-mode output
  - Computing **error** according to **reference** level
  - Applying needed common-mode **correction**
- Not** to be confused with **CMRR**!

 
- Multi-stage OpAmps require one **CMFB** loops for **each stage**
- CMFB** control design?





# Continuous-Time CMFB

## ► Resistive-based sensing:

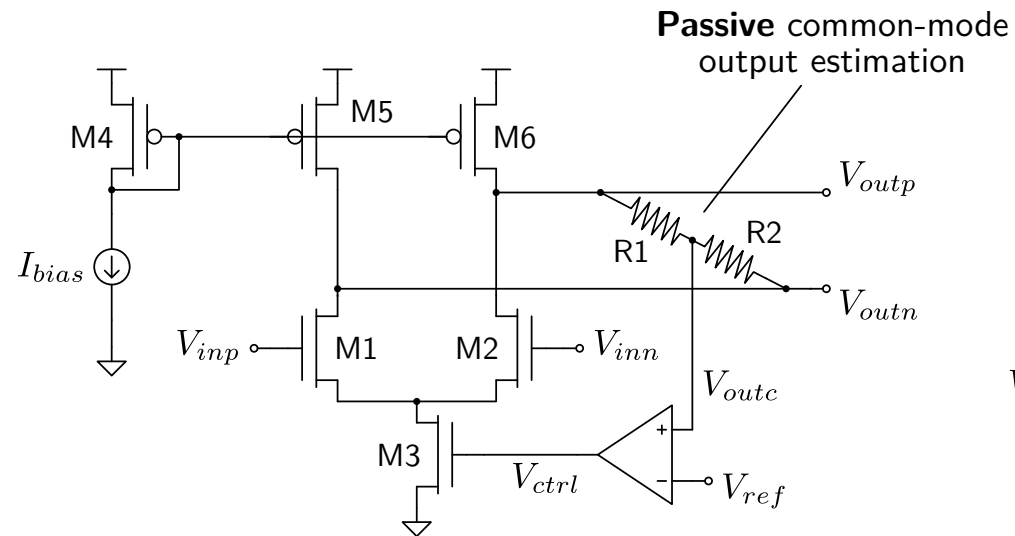


$$V_{outc} = \frac{R_2}{R_1 + R_2} V_{outp} + \frac{R_1}{R_1 + R_2} V_{outn}$$

$$V_{outc}|_{R_1 \equiv R_2} = \frac{V_{outp} + V_{outn}}{2}$$

# Continuous-Time CMFB

► **Resistive-based sensing:**

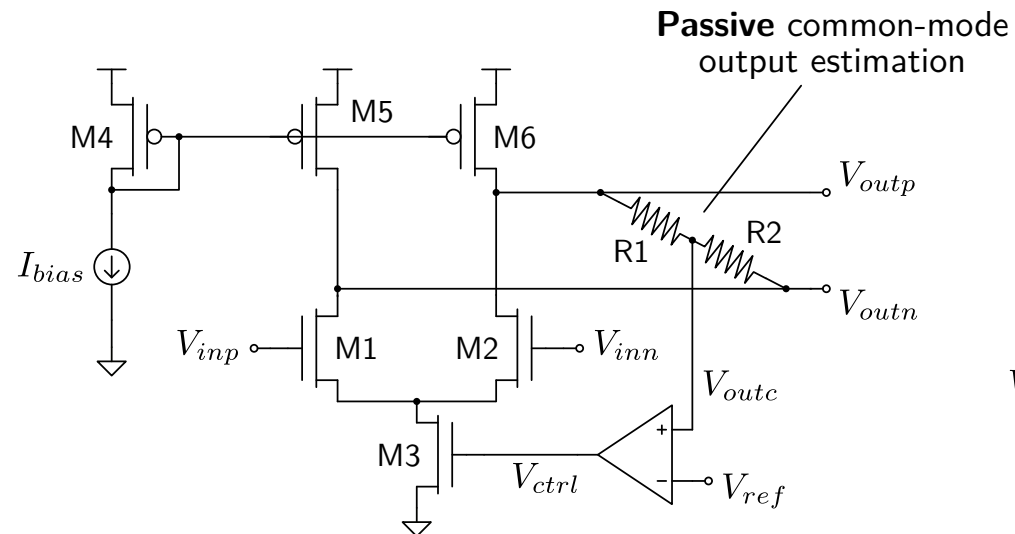

$$V_{outc} = \frac{R_2}{R_1 + R_2} V_{outp} + \frac{R_1}{R_1 + R_2} V_{outn}$$

$$V_{outc}|_{R_1 \equiv R_2} = \frac{V_{outp} + V_{outn}}{2}$$

▲ OpAmp original **OR** is preserved


▼ Resistive **extra loading**...

$$R_{1,2} \uparrow$$

...or limited  
CMFB **bandwidth**

# Continuous-Time CMFB

## ► Resistive-based sensing:

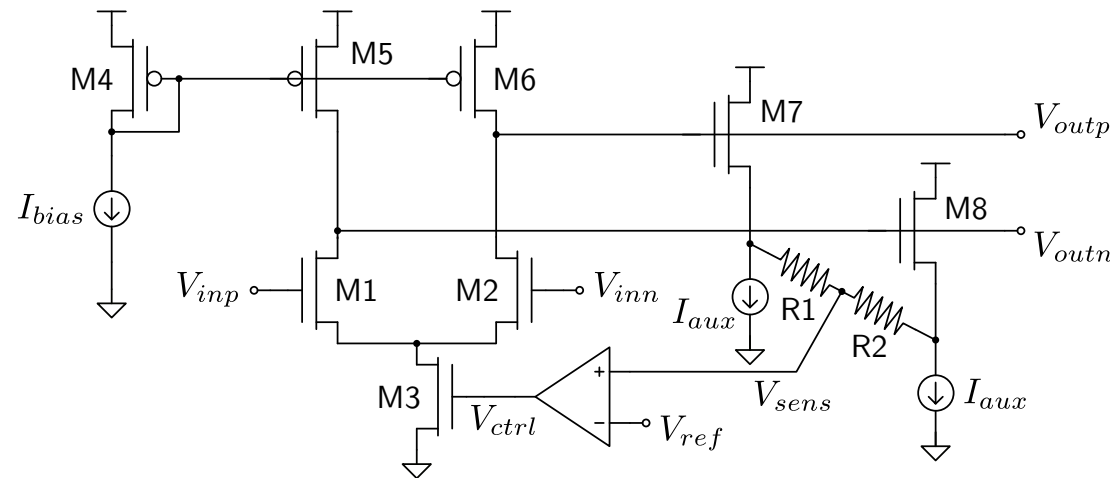

▲ Resistive **loading** is avoided

▼ **OR** severe reduction


▼ **Power** consumption overhead

▼ Common-mode output level is **technology** dependent!

$$V_{outc} = nV_{ref} + V_{TH} + \sqrt{\frac{2nI_{aux}}{\beta_{7,8}}}$$

# Continuous-Time CMFB

## ► Resistive-based sensing:

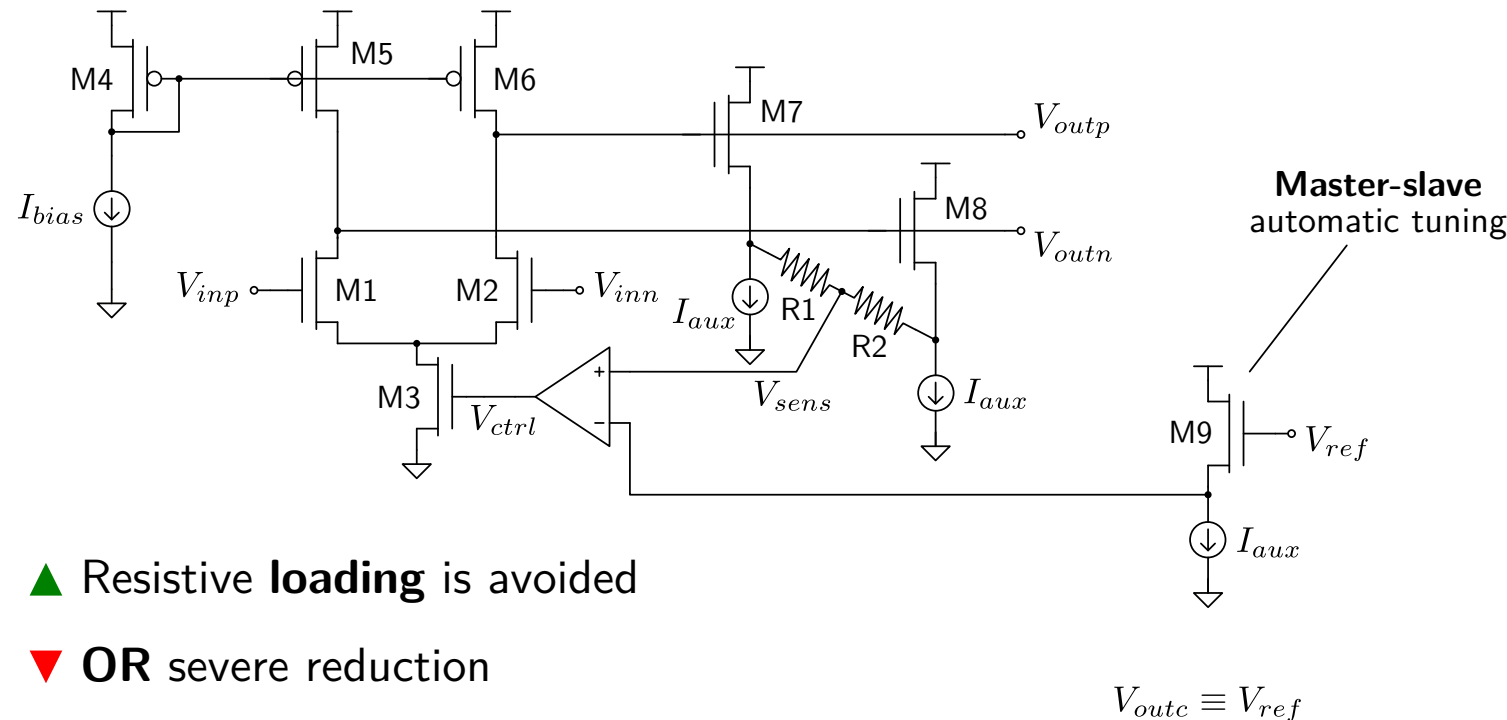

▲ Resistive **loading** is avoided


▼ **OR** severe reduction

▼ **Power** consumption overhead

▼ Common-mode output level is **technology** dependent!

# Continuous-Time CMFB

## ► Resistive-based sensing:

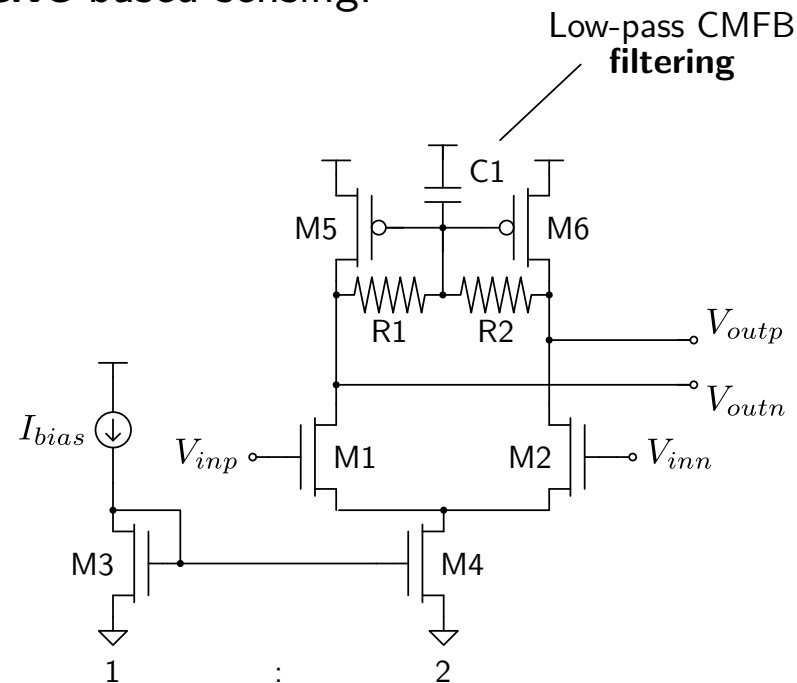

$$V_{outc} = V_{DD} - V_{TH} - \sqrt{\frac{2nI_{bias}}{\beta_{5,6}}}$$

▲ **Compact** circuit solution


▲ No **power** consumption overhead

▼ Common-mode output defined by **technology**

▼ Strong **OR** reduction

# Continuous-Time CMFB

► **MOS-based sensing:**

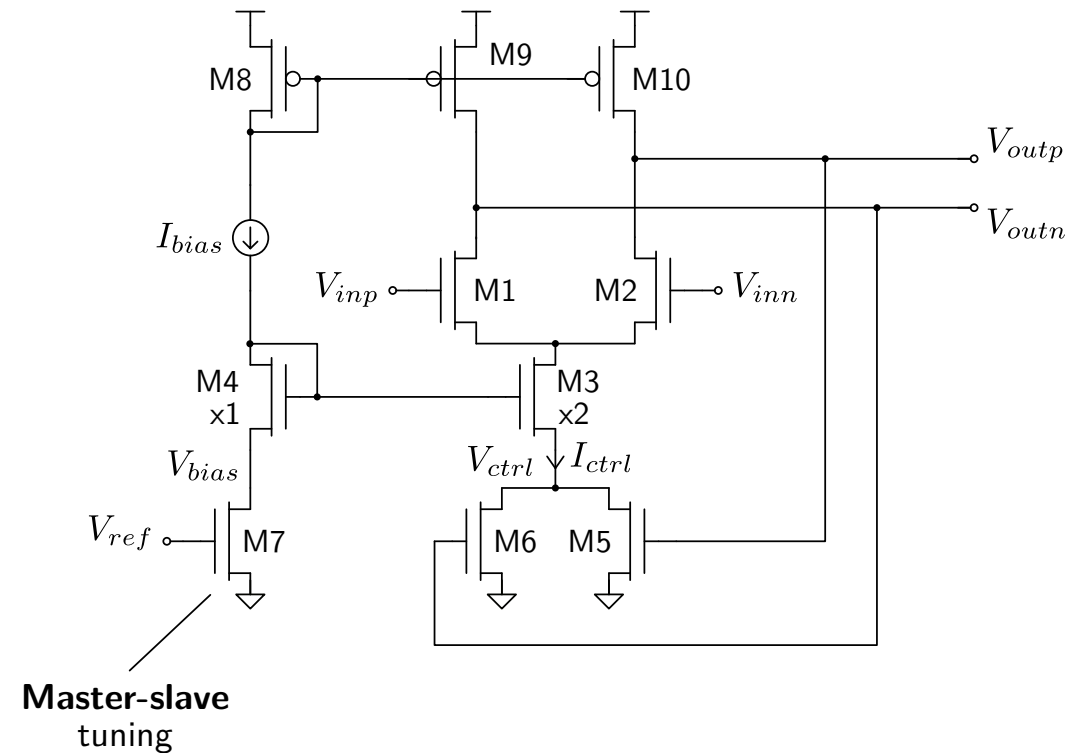

Supposing M5, M6 and M7 working in **deep conduction**:

$$I_{ctrl} = \beta_5 \left( V_{outp} - V_{TH} + n \frac{V_{ctrl}}{2} \right) V_{ctrl} + \beta_6 \left( V_{outn} - V_{TH} + n \frac{V_{ctrl}}{2} \right) V_{ctrl}$$

By **CMFB symmetry** ( $M_5=M_6$ ):


$$I_{ctrl} = f(\underbrace{V_{outp} + V_{outn}}_{\propto V_{outc}}) \quad \frac{dI_{ctrl}}{dV_{outd}} \equiv 0$$

By **bias symmetry** ( $M5|6=M7$  and  $M3=M4$ ):

$$V_{ctrl} \equiv V_{bias} \quad I_{ctrl} \equiv 2I_{bias} \quad V_{outc} \equiv V_{ref}$$

## Continuous-Time CMFB

### ► MOS-based sensing:

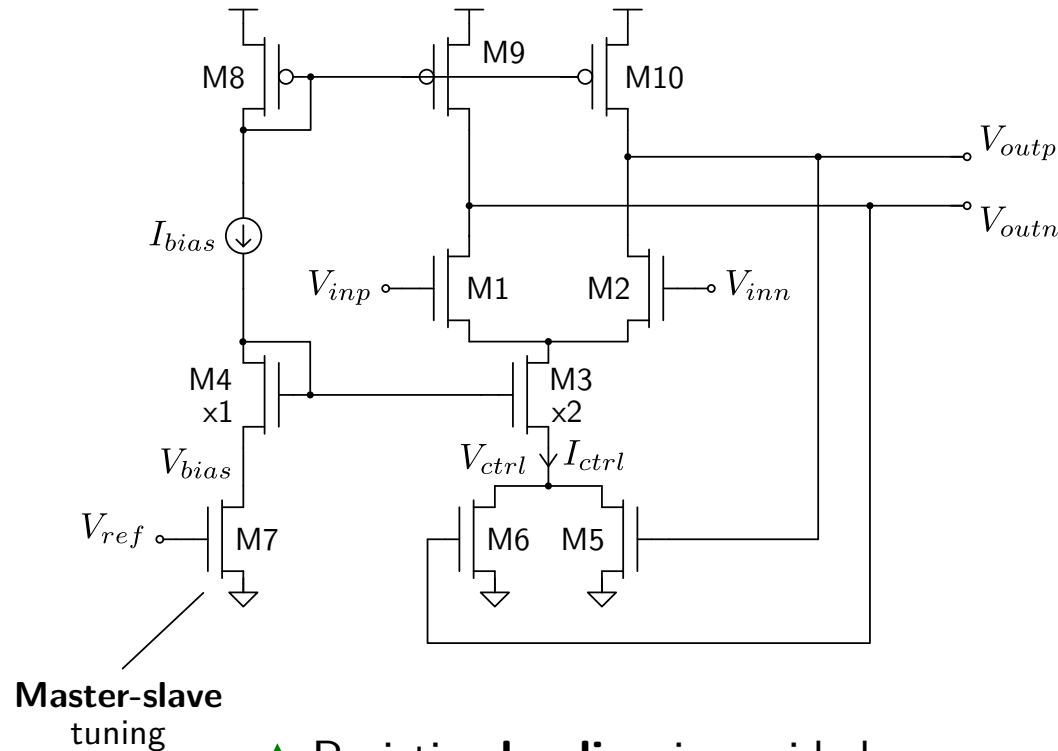

- ▲ Resistive **loading** is avoided
- ▲ No **power** consumption overhead

Supposing M5, M6 and M7 working in **deep conduction**:

$$I_{ctrl} = \beta_5 \left( V_{outp} - V_{TH} + n \frac{V_{ctrl}}{2} \right) V_{ctrl} + \beta_6 \left( V_{outn} - V_{TH} + n \frac{V_{ctrl}}{2} \right) V_{ctrl}$$

By **CMFB symmetry** (M5=M6):

$$I_{ctrl} = f(\underbrace{V_{outp} + V_{outn}}_{\propto V_{outc}}) \quad \frac{dI_{ctrl}}{dV_{outd}} \equiv 0$$

By **bias symmetry** (M5|6=M7 and M3=M4):


$$V_{ctrl} \equiv V_{bias} \quad I_{ctrl} \equiv 2I_{bias} \quad V_{outc} \equiv V_{ref}$$

- ▲ Negligible **OR** reduction
- ▲ **Technology** compensation
- ▼ Gain **non-linearity**

# Discrete-Time CMFB
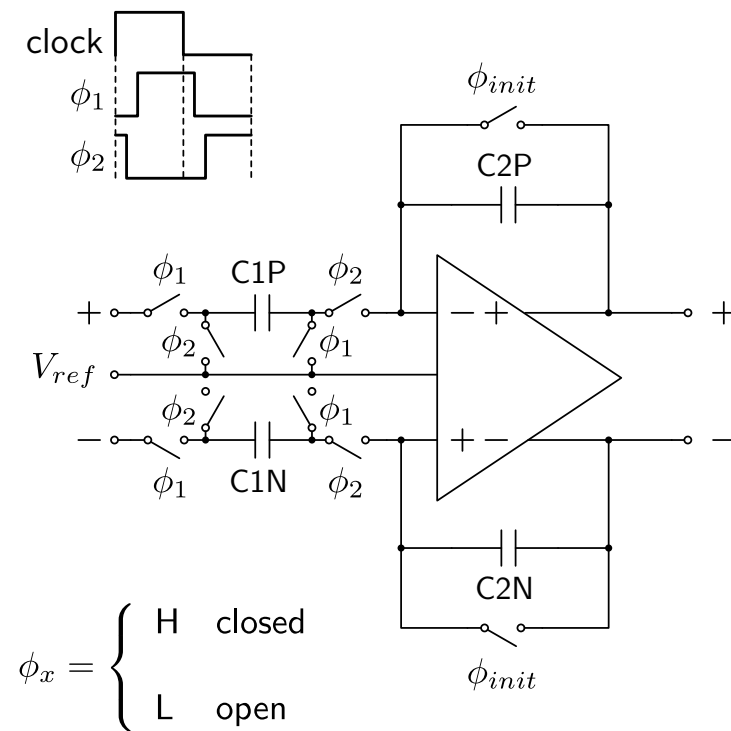
## ► Switched-capacitor (SC) implementation:

e.g. fully-differential **integrator** stage






 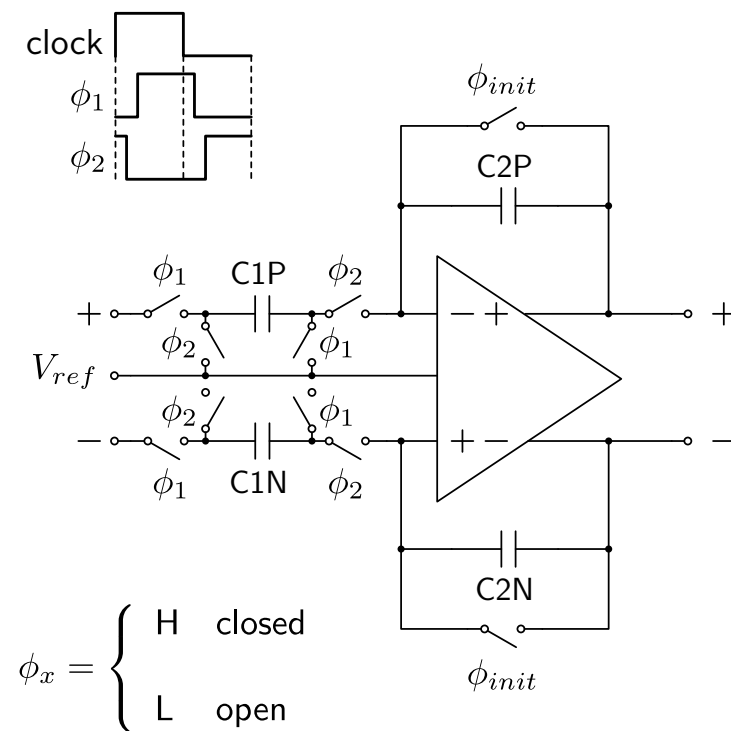
# Discrete-Time CMFB

- Switched-capacitor (**SC**) implementation:

e.g. fully-differential **integrator** stage





- ▶ **Capacitive** CMFB sensing
- ▲ Reduced **power** overheads
- ▼ Low loop-**gain**

- 1 OpAmp Figures of Merit
- 2 The Mono-Transistor Amplifier
- 3 Differential Circuits with CMFB
- 4 Folded Amplifiers
- 5 Cascode Topologies
- 6 Gain Enhancement Techniques
- 7 Multi-Stage OpAmps

## Output Range Issue

- **Basic** fully-differential topology (not showing CMFB):

$$V_{outd} \doteq V_{outp} - V_{outn}$$

 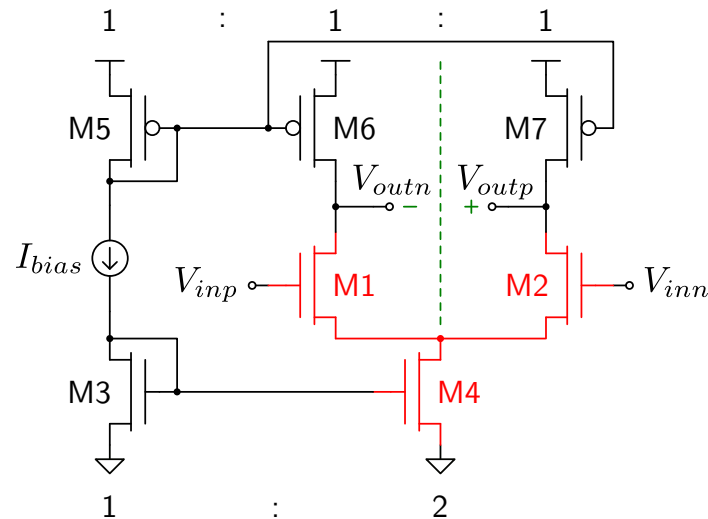


- ▼ **OR** improvement requires very large aspect ratios!
- ▼ Not compatible with other optimization rules (e.g. **CMRR**)

$$OR = 2V_{DD} - 4\sqrt{\frac{2I_{bias}}{n\beta_{un}}} \left[ \sqrt{\left(\frac{L}{W}\right)_{1,2}} + \sqrt{2\left(\frac{L}{W}\right)_4} \right] \uparrow \quad \left(\frac{W}{L}\right)_{1,2} \uparrow \quad \left(\frac{W}{L}\right)_4 \uparrow$$
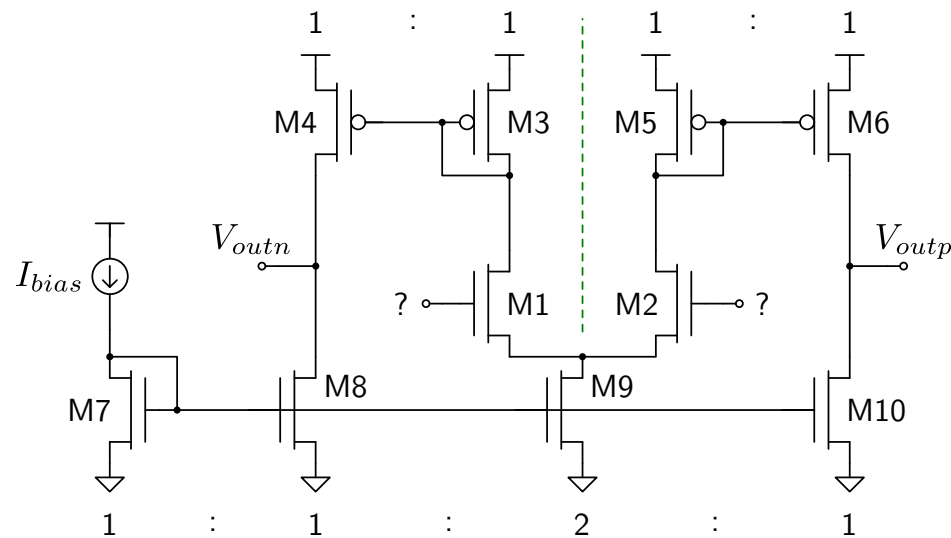
# Folded Topologies


- Fully-differential **folded** OpAmp (not showing CMFB):


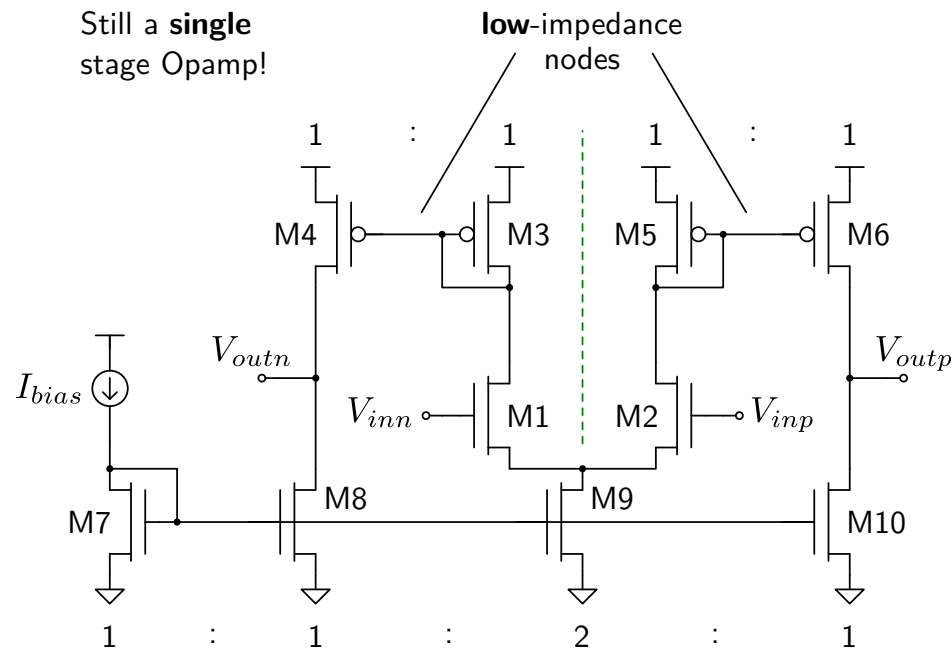
## Folded Topologies

- Fully-differential **folded** OpAmp (not showing CMFB):

All operating in strong inversion  
saturation + neglecting CLM




▼ Static **power** consumption (x2)

▼ Device silicon **area** (x2)
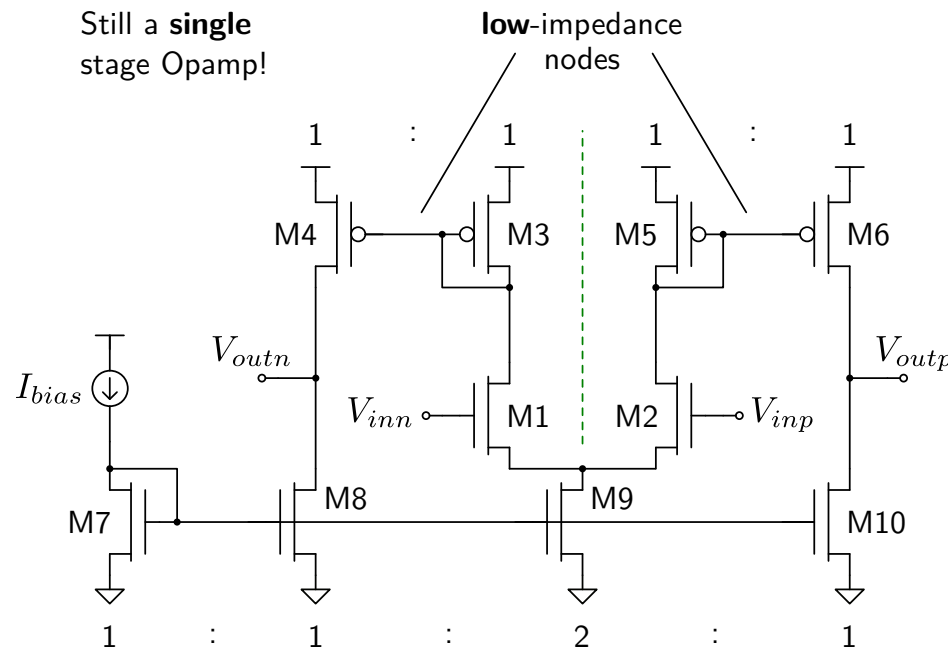
## Folded Topologies

- Fully-differential **folded** OpAmp (not showing CMFB):

All operating in strong inversion  
saturation + neglecting CLM



$$V_{sat10} < V_{outp} < V_{DD} - V_{sat6}$$

$$V_{sat10} = \sqrt{\frac{2I_{bias}}{n\beta_{10}}} \quad V_{sat6} = \sqrt{\frac{2I_{bias}}{n\beta_6}}$$

$$V_{outd} \doteq V_{outp} - V_{outn}$$

$$OR = 2V_{DD} - 4 \sqrt{\frac{2I_{bias}}{n \min \left( \beta_{un} \left( \frac{W}{L} \right)_{8,10}, \beta_{up} \left( \frac{W}{L} \right)_{4,6} \right)}}$$

▼ Static **power** consumption (x2)


▼ Device silicon **area** (x2)

▲ Full-scale **OR** optimization

## Folded Topologies
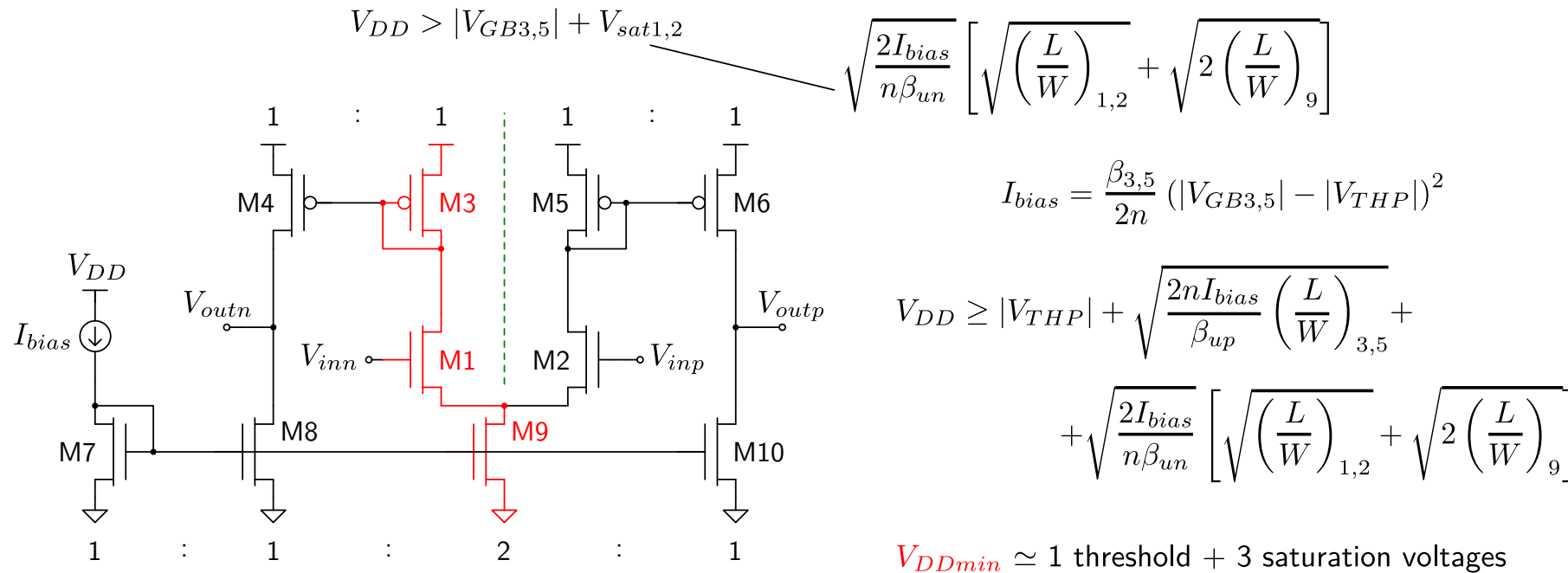
### ► Fully-differential **folded** OpAmp (not showing CMFB):

All operating in strong inversion  
saturation + neglecting CLM



▼ Static **power** consumption (x2)


▼ Device silicon **area** (x2)

▲ Full-scale **OR** optimization

▼ High **supply voltage** needed...
 
## Folded Topologies

- Fully-differential **dual folded** OpAmp (not showing CMFB):



- ▼ Static **power** consumption (x3)


- ▼ Device silicon **area** (x3)



## Folded Topologies
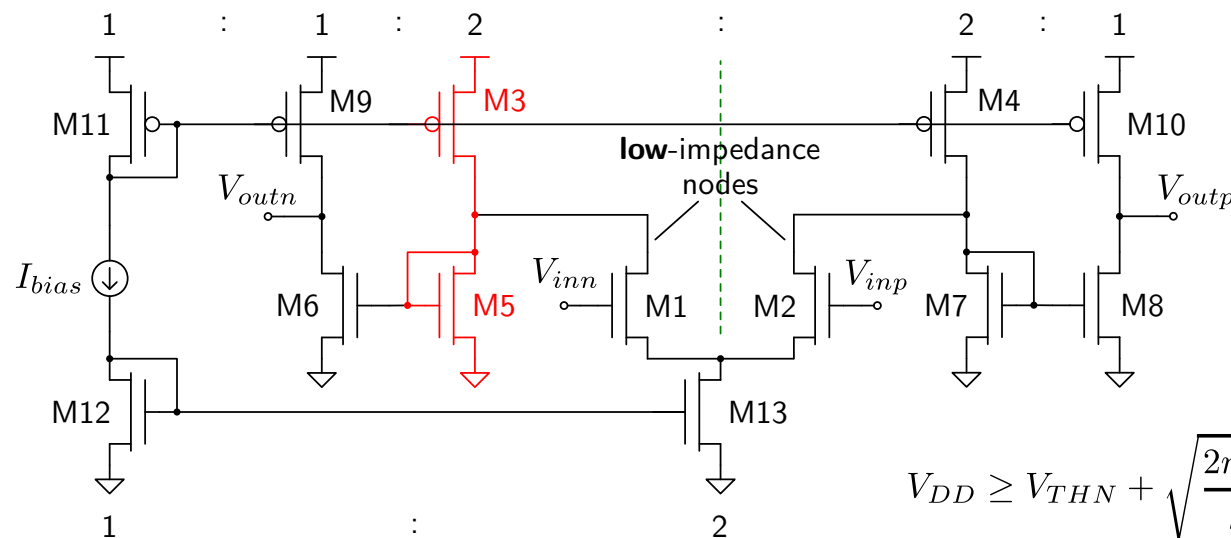
### ► Fully-differential **dual folded** OpAmp (not showing CMFB):

All operating in strong inversion  
saturation + neglecting CLM



Still a **single** stage Opamp!

Supposing:  $V_{GB5,7} \geq V_{sat1,2}$

$$V_{DD} \geq V_{GB5,7} + V_{sat3,4}$$

$$V_{DD} \geq V_{THN} + \sqrt{\frac{2nI_{bias}}{\beta_{un}} \left(\frac{L}{W}\right)_{5,7}} + \sqrt{\frac{2I_{bias}}{n\beta_{up}} \left(\frac{L}{W}\right)_{3,4}}$$

$$V_{DDmin} \simeq 1 \text{ threshold} + 2 \text{ saturation voltages}$$

▼ Static **power** consumption (x3)



▼ Device silicon **area** (x3)

▲ Same **OR** optimization

▲ Compatible with low **supply voltage**

 
 
## Folded Topologies

- Single-ended folded OpAmp counterparts:



## Folded Topologies

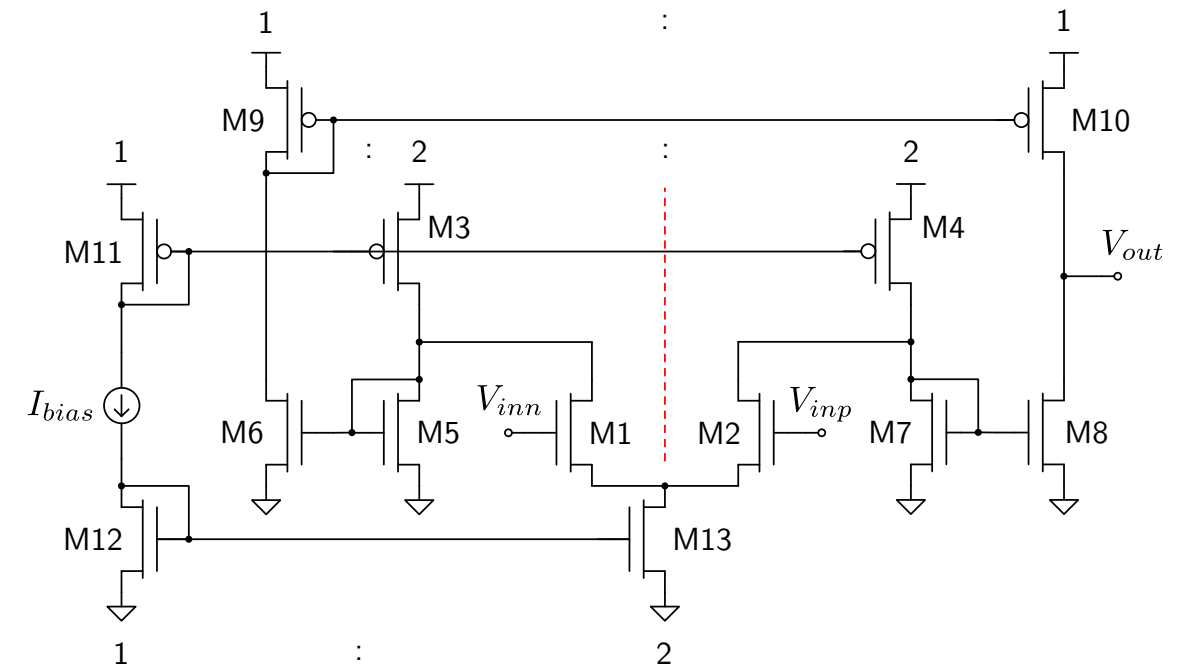 
### ► Single-ended folded OpAmp counterparts:



- 1 OpAmp Figures of Merit
- 2 The Mono-Transistor Amplifier
- 3 Differential Circuits with CMFB
- 4 Folded Amplifiers
- 5 Cascode Topologies
- 6 Gain Enhancement Techniques
- 7 Multi-Stage OpAmps

# Principle Basis

- CMOS OpAmp general **linear model**:

 

$$|G(DC)| = g_{in} r_{out}$$

input  
**transconductance**  
 $v \rightarrow i$


output  
**resistance**  
 $i \rightarrow v$

$$g_{in} \propto \begin{cases} g_{mg} \\ g_{ms} \end{cases} \quad r_{out} \propto \frac{1}{g_{md}}$$

- Enhancement by increasing MOSFET **output impedance**?

## Principle Basis
 
### ► CMOS OpAmp general **linear model**:




$$|G(DC)| = g_{in} r_{out}$$

input  
transconductance  
 $v \rightarrow i$

output  
resistance  
 $i \rightarrow v$

$$g_{in} \propto \begin{cases} g_{mg} \\ g_{ms} \end{cases} \quad r_{out} \propto \frac{1}{g_{md}}$$
 
### ► Enhancement by increasing MOSFET **output impedance**?



$$BW = \frac{1}{2\pi r_{out} c_{load}} \quad GBW = \frac{g_{in}}{2\pi c_{load}}$$


### ▲ **Gain** improvement:

- Accurate **feedback** functions
- Lower equivalent input **noise**



### ▼ No **speed** enhancement (GBW)

# Principle of Operation

## ► Output impedance **multiplier**:

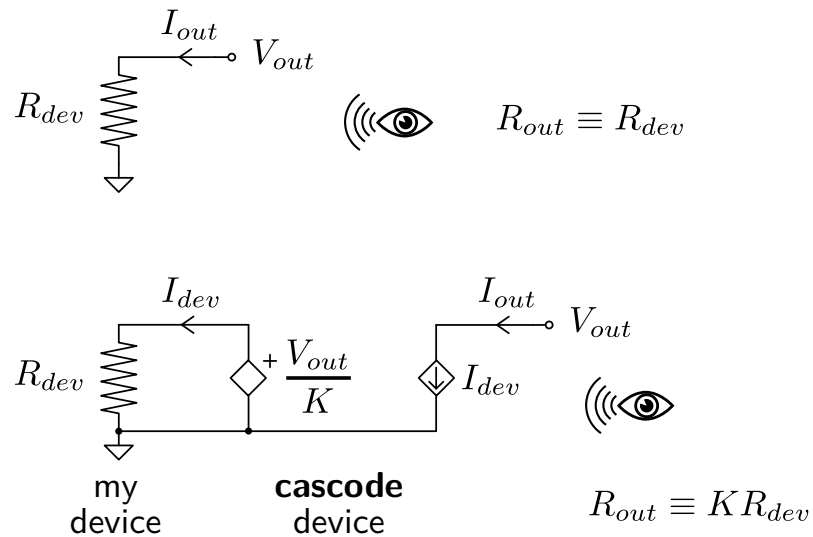

 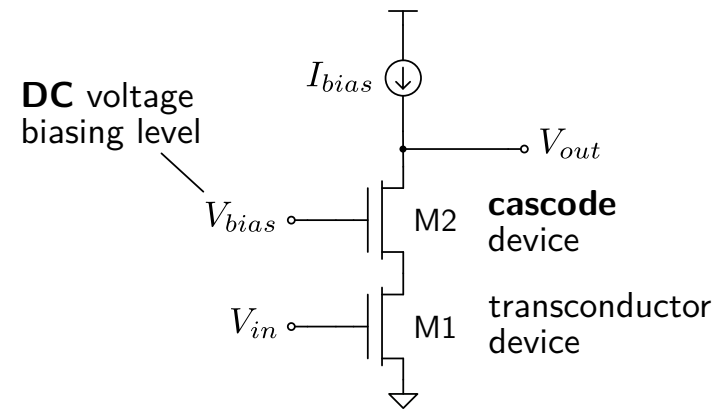
## ► Introducing cascoding in **OpAmps**:



## ► Applicable to most analog basic building **blocks** (e.g. current mirror, voltage differential pair...)

 
# Basic Cascode OpAmp

► Low-frequency **small-signal** analysis:



$$\begin{cases} i_{out} = g_{md2}v_{out} - g_{ms2}v_{cas} \\ g_{md1}v_{cas} = i_{out} - g_{mg1}v_{in} \end{cases}$$

► CMOS OpAmp **model**:

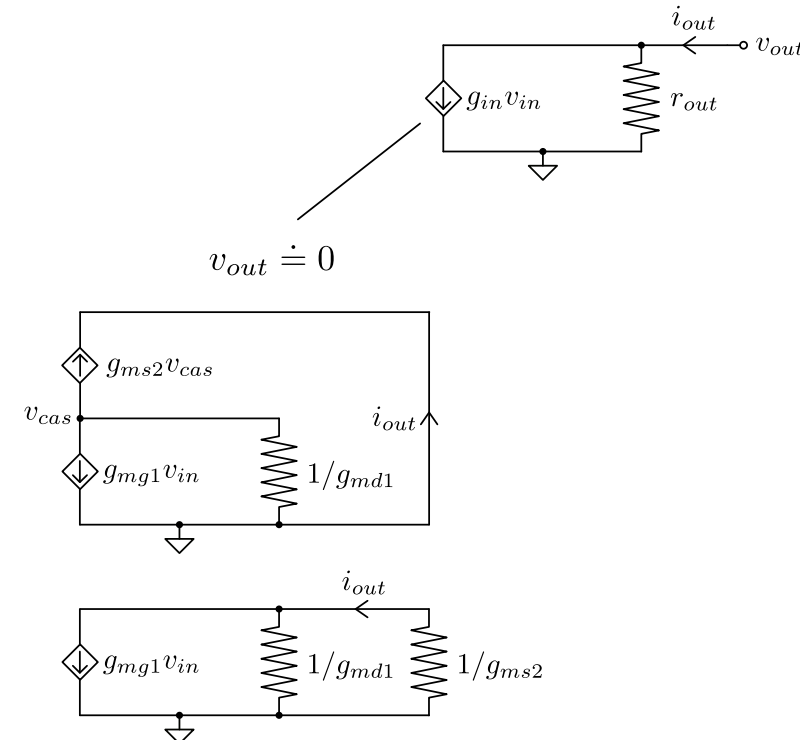


$$g_{in} \doteq \frac{i_{out}}{v_{in}} = g_{mg1} \frac{g_{ms2}}{g_{ms2} + g_{md1}}$$



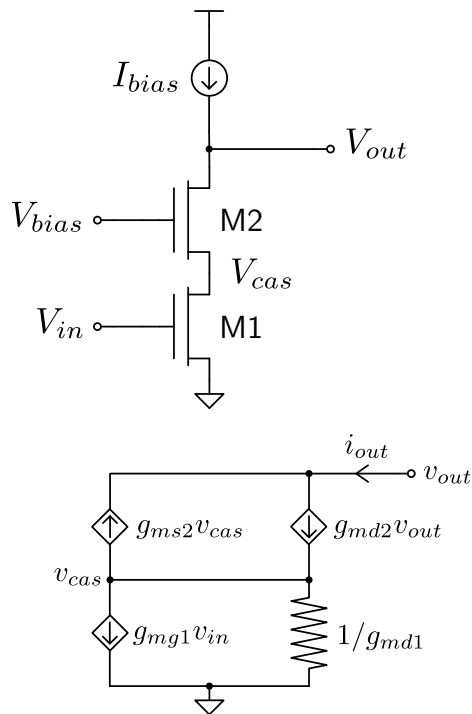
# Basic Cascode OpAmp

► Low-frequency **small-signal** analysis:



$$\begin{cases} i_{out} = g_{md2}v_{out} - g_{ms2}v_{cas} \\ g_{md1}v_{cas} = i_{out} - g_{mg1}v_{in} \end{cases}$$

► CMOS OpAmp **model**:

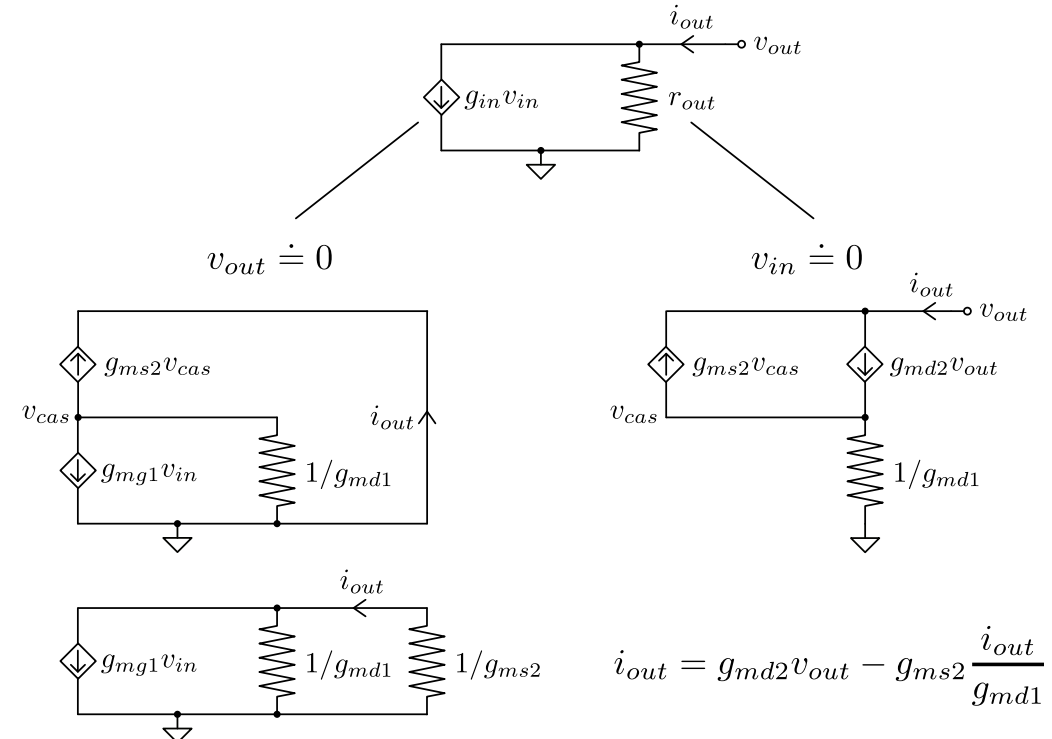


$$g_{in} \doteq \frac{i_{out}}{v_{in}} = g_{mg1} \frac{g_{ms2}}{g_{ms2} + g_{md1}}$$


$$r_{out} \doteq \frac{v_{out}}{i_{out}} = \frac{1}{g_{md2}} + \frac{1}{g_{md1}} \frac{g_{ms2}}{g_{md2}}$$
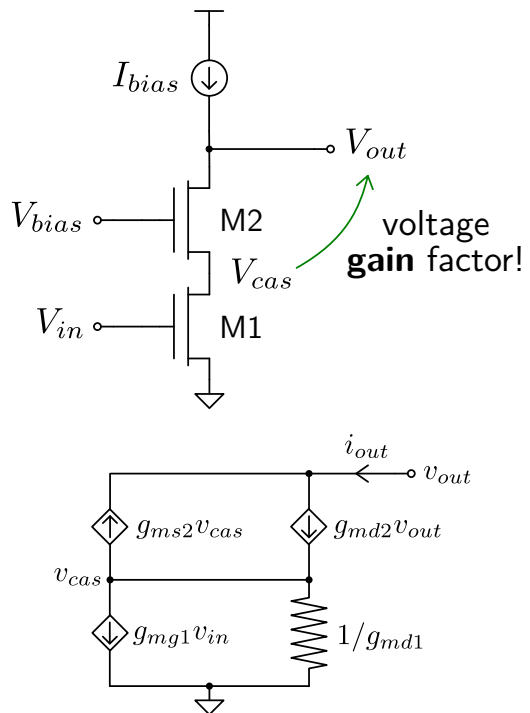
# Basic Cascode OpAmp

► Low-frequency **small-signal** analysis:



► CMOS OpAmp **model**:

 

$$g_{in} = g_{m1} \frac{g_{ms2}}{g_{ms2} + g_{md1}} \simeq \textcolor{red}{g_{m1}} \quad \text{similar transconductance}$$

$$r_{out} = \frac{1}{g_{md2}} + \frac{1}{g_{md1}} \frac{\textcolor{green}{g_{ms2}}}{\textcolor{green}{g_{md2}}} \quad \text{higher output impedance}$$

series combination



voltage gain factor!

output impedance of **cascode** device

output impedance of **transconductor** device

 
 
# Regulated Cascode OpAmp

- Low-frequency **small-signal** analysis:



  
# Regulated Cascode OpAmp

► Low-frequency **small-signal** analysis:



► CMOS OpAmp **model**:


 


$$g_{in} = g_{mg1} \frac{g_{ms2} + g_{mg2}G_{reg}}{g_{ms2} + g_{mg2}G_{reg} + g_{md1}} \simeq \textcolor{red}{g_{mg1}}$$


$$r_{out} = \frac{1}{g_{md2}} + \frac{1}{g_{md1}} \frac{g_{ms2} + g_{mg2}G_{reg}}{g_{md2}} \simeq \frac{1}{g_{md1}} \frac{\textcolor{green}{g_{mg2}}}{\textcolor{green}{g_{md2}}} G_{reg}$$

# Regulated Cascode OpAmp
  
## ► Low-frequency **small-signal** analysis:



## ► CMOS OpAmp **model**:

 


$$g_{in} = g_{mg1} \frac{g_{ms2} + g_{mg2} G_{reg}}{g_{ms2} + g_{mg2} G_{reg} + g_{md1}} \simeq \textcolor{red}{g_{mg1}}$$

$$r_{out} = \frac{1}{g_{md2}} + \frac{1}{g_{md1}} \frac{g_{ms2} + g_{mg2} G_{reg}}{g_{md2}} \simeq \frac{1}{g_{md1}} \frac{\textcolor{green}{g_{mg2}}}{\textcolor{green}{g_{md2}}} G_{reg}$$
 
## ► **Minimalist** implementation:

$$G_{reg} \equiv \frac{g_{mg3}}{g_{md3}}$$




$$|G(DC)| \simeq \frac{g_{mg1}}{g_{md1}} \frac{\textcolor{green}{g_{mg2}}}{\textcolor{green}{g_{md2}}} \frac{\textcolor{green}{g_{mg3}}}{\textcolor{green}{g_{md3}}}$$


# Output Range Optimization

All operating in strong inversion  
saturation + neglecting CLM


## Basic cascode DC biasing:

 

alternative **low-voltage** approach:

 

## Regulated cascode DC biasing:

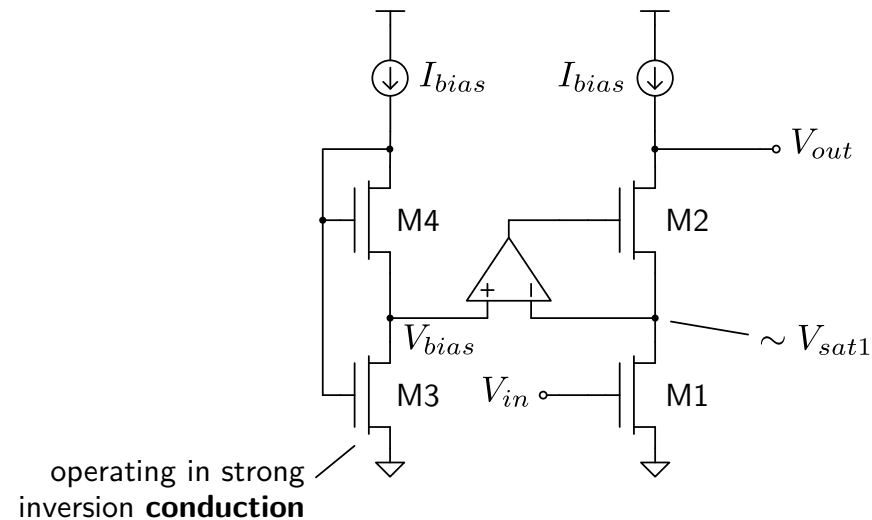


$$\begin{cases} I_{bias} = \beta_3 \left( V_{GB3,4} - V_{TH} + \frac{n}{2} V_{bias} \right) V_{bias} \\ I_{bias} = \frac{\beta_4}{2n} (V_{GB3,4} - V_{TH} - n V_{bias})^2 \end{cases}$$

$$V_{bias} \equiv V_{sat1} :$$

$$\sqrt{\frac{2}{(W/L)_4}} = \sqrt{\frac{1}{2(W/L)_3} \frac{(W/L)_1}{(W/L)_3}} - 3 \sqrt{\frac{1}{2(W/L)_1}}$$
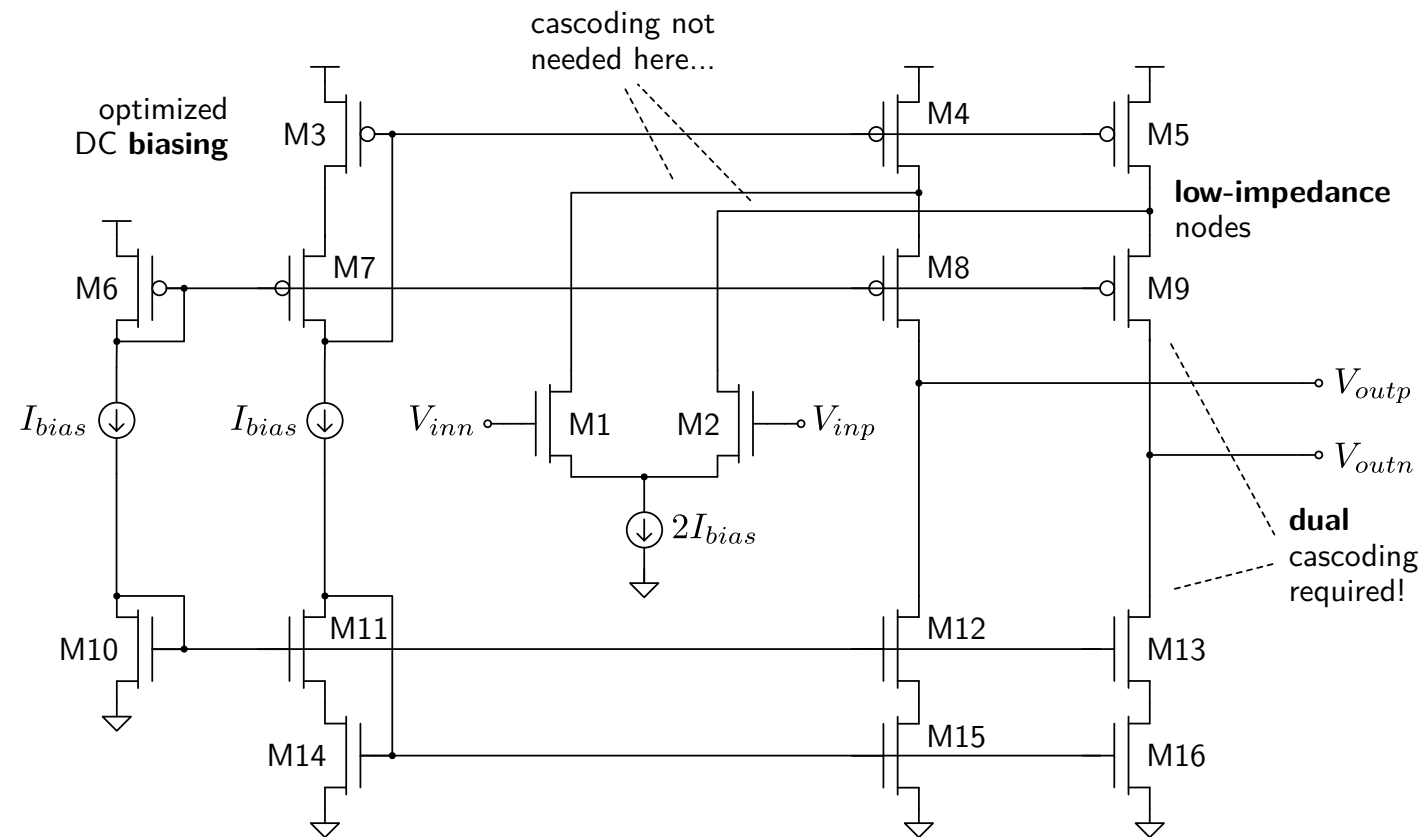
# Practical Cascode OpAmps

- Fully differential + folded + cascode topology example:




- 1 OpAmp Figures of Merit
- 2 The Mono-Transistor Amplifier
- 3 Differential Circuits with CMFB
- 4 Folded Amplifiers
- 5 Cascode Topologies
- 6 Gain Enhancement Techniques
- 7 Multi-Stage OpAmps



# Principle Basis

- CMOS OpAmp general **linear model**:

 

$$|G(DC)| = g_{in} r_{out}$$

input  
**transconductance**  
 $v \rightarrow i$


output  
**resistance**  
 $i \rightarrow v$

$$g_{in} \propto \begin{cases} g_{mg} \\ g_{ms} \end{cases} \quad r_{out} \propto \frac{1}{g_{md}}$$

- Enhancement by increasing MOSFET **input transconductance**?

# Principle Basis
 
## ► CMOS OpAmp general **linear model**:




$$|G(DC)| = g_{in} r_{out}$$

input transconductance  
 $v \rightarrow i$

output resistance  
 $i \rightarrow v$

$$g_{in} \propto \begin{cases} g_{mg} \\ g_{ms} \end{cases} \quad r_{out} \propto \frac{1}{g_{md}}$$
 
## ► Enhancement by increasing MOSFET **input transconductance**?



$$BW = \frac{1}{2\pi r_{out} c_{load}} \quad GBW = \frac{g_{in}}{2\pi c_{load}}$$


## ▲ **Gain** improvement:

- Accurate **feedback** functions
- Lower equivalent input **noise**

## ▲ **Speed** enhancement (GBW)


# Partial Positive Feedback

## ► Basic differential transconductor:

 


# Partial Positive Feedback

## ► Basic differential transconductor:

 


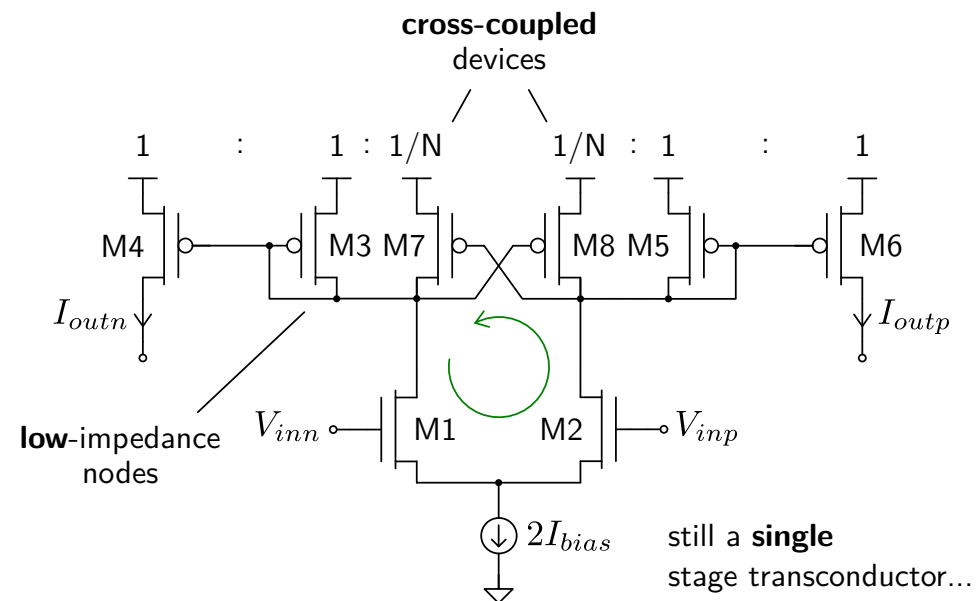
## ► Introducing **local positive feedback**:

- **Folded** structure
- **Cross-coupled** pair
- **Partial** feedback design by sizing ratio





# Partial Positive Feedback

- Small signal **transconductance**:

 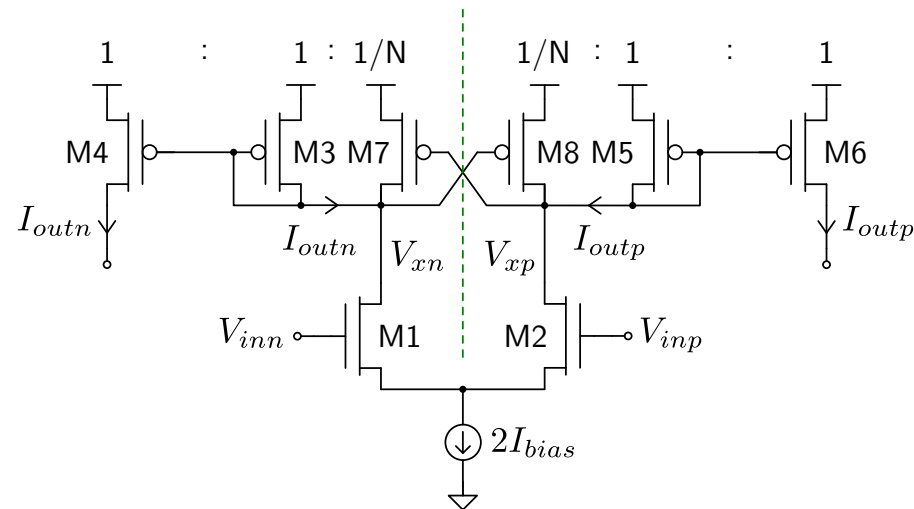



# Partial Positive Feedback

## ► Small signal transconductance:

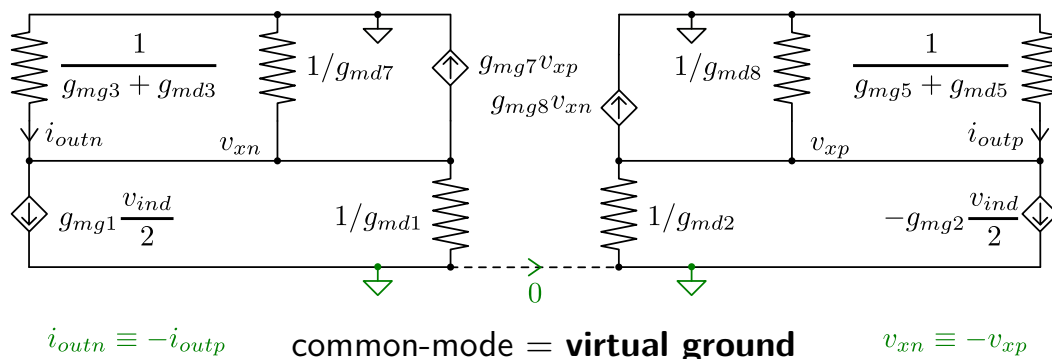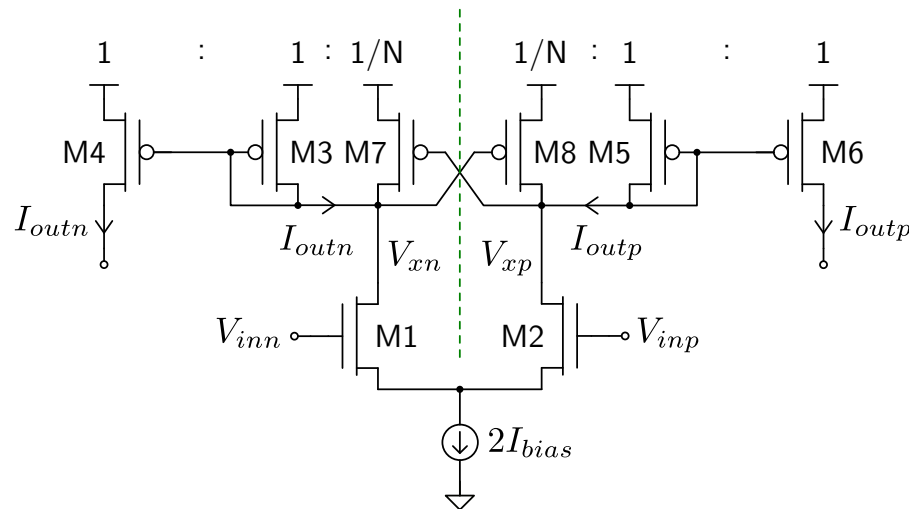
  
## ► Half-circuit analysis:

- Perfect symmetry (no mismatching)
- Infinite tail sink resistance
- Purely differential input




$$g_{inp} \doteq \frac{i_{outd}}{v_{ind}}$$

$$i_{outd} \doteq i_{outp} - i_{outn} \equiv |2i_{outn}|$$

# Partial Positive Feedback



► Small signal **transconductance**:

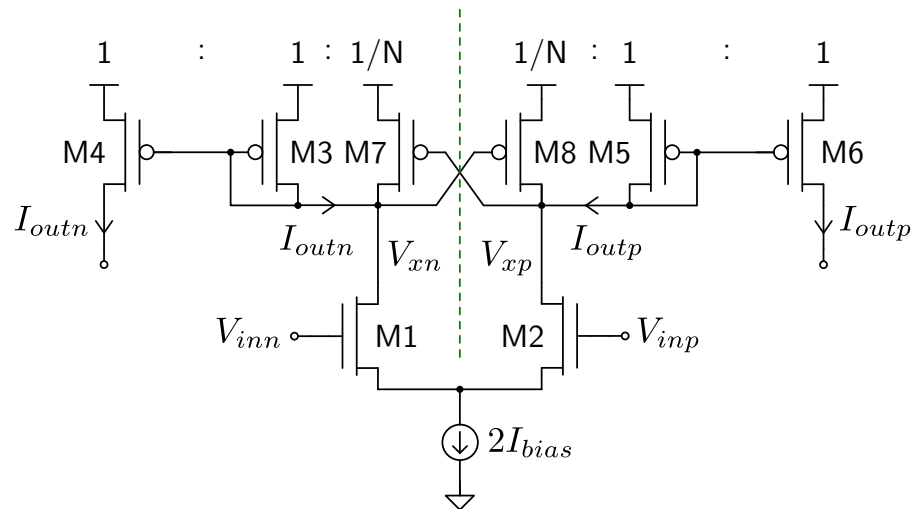

$$\left. \begin{aligned} i_{outn} &= g_{mg1} \frac{v_{ind}}{2} \frac{g_{mg3}}{g_{mg3} - g_{mg7}} \\ g_{inp} &= g_{mg1,2} \frac{g_{mg3,5}}{g_{mg3,5} - g_{mg7,8}} \uparrow \end{aligned} \right\} \begin{cases} g_{mg1,2} & N \gg 1 \\ \infty & N \equiv 1 \\ 0 & N \ll 1 \end{cases}$$

► **Half-circuit analysis:**

  - Perfect symmetry (no mismatching)
- Infinite tail sink resistance
- Purely differential input




$$g_{inp} = \frac{\dot{i}_{outd}}{v_{ind}}$$

$$i_{outd} \doteq i_{outp} - i_{outn} \equiv |2i_{outn}|$$
 
# Practical Gain Enhanced OpAmp


► **Single-ended + folded + cross-coupled** example:



▲ Larger **gain** and **GBW**


▲ Compatible with **folding** and **cascoding**

 Local **positive** feedback vs global **negative** feedback:



▼ Prone to **instability**

▼ It can generate **hysteresis**

 




- 1 OpAmp Figures of Merit
- 2 The Mono-Transistor Amplifier
- 3 Differential Circuits with CMFB
- 4 Folded Amplifiers
- 5 Cascode Topologies
- 6 Gain Enhancement Techniques
- 7 Multi-Stage OpAmps

 
# Splitting Functions

▼ **Single stage CMOS OpAmp limitations:**



 
# Splitting Functions

▼ **Single stage CMOS OpAmp limitations:**



 ► Introducing **two-stage** architectures:




▲ Improved **dynamic range** performance

▼ **Area** and **power** overheads...

▼ **Frequency compensation** required!

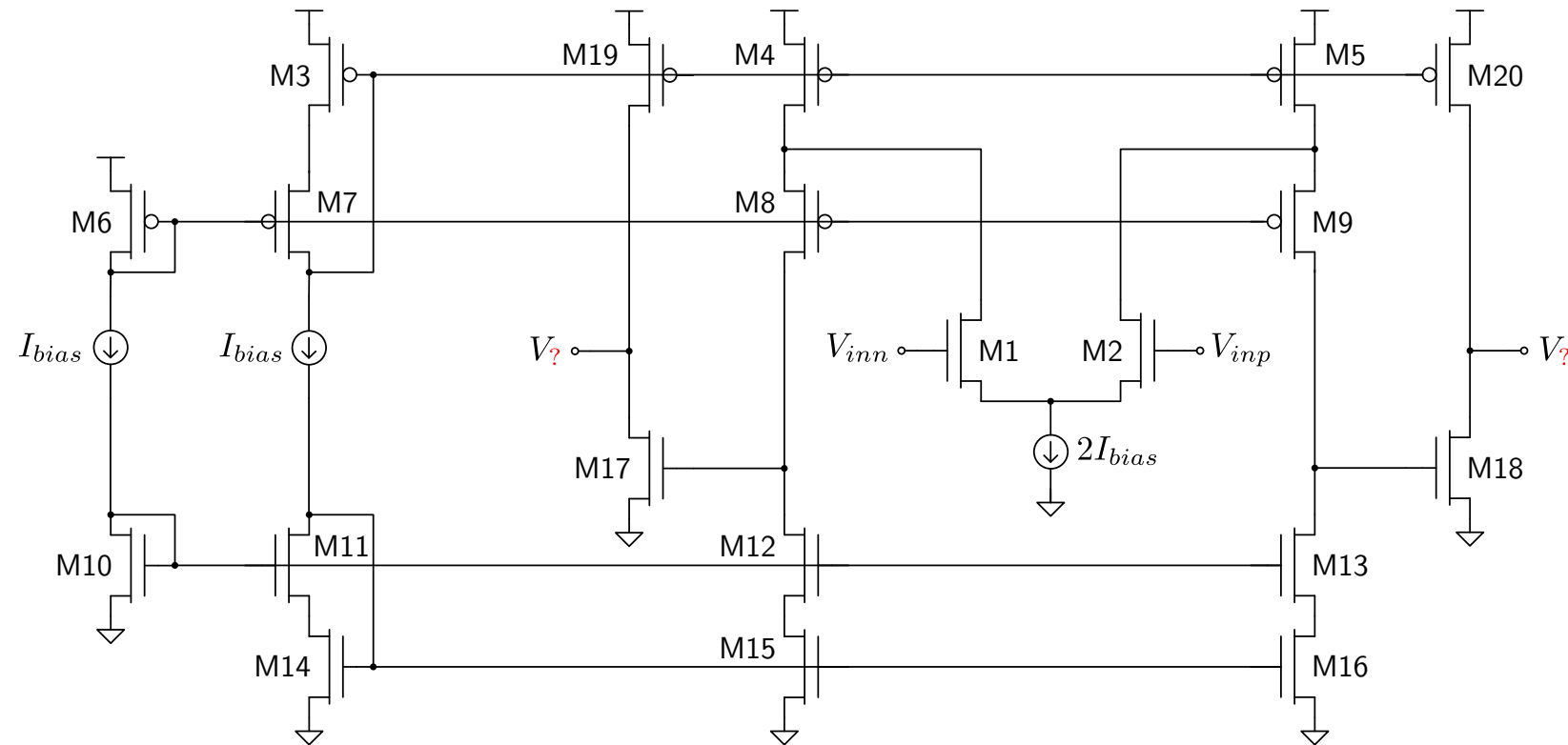
## Practical Example

- **Two-stage** fully differential folded cascode OpAmp topology:


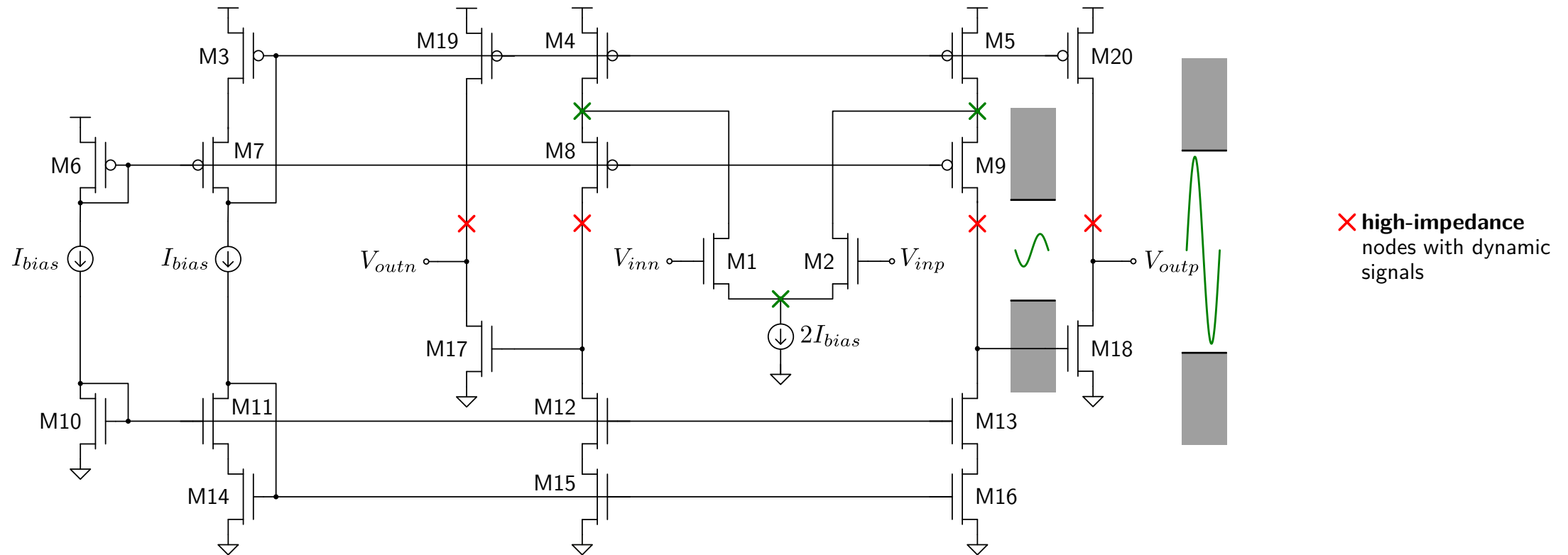
## Practical Example


- **Two-stage** fully differential folded cascode OpAmp topology:



- ▼ Frequency compensation strategy is needed under **feedback** (closed loop) operation...

# Single Stage OpAmp Case

► Basic **control** theory:

 


$$|H| = \begin{cases} 0 & \text{open loop} \\ 1 & \text{follower} \end{cases}$$

$$\frac{V_{out}}{V_{in}} = \frac{G}{1 + GH} \underset{G \rightarrow \infty}{\approx} \frac{1}{H}$$

# Single Stage OpAmp Case

## ► Basic **control** theory:

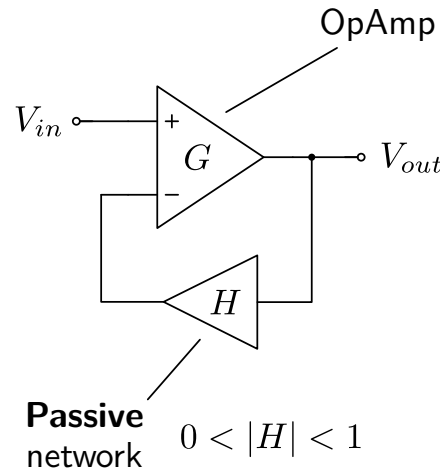

$$|H| = \begin{cases} 0 & \text{open loop} \\ 1 & \text{follower} \end{cases}$$

$$\frac{V_{out}}{V_{in}} = \frac{G}{1 + GH} \underset{G \rightarrow \infty}{\approx} \frac{1}{H}$$

## ► **Single pole** amplifier:


$$G(s) = \frac{G_0}{1 + \frac{s}{w_p}}$$

$$\frac{V_{out}}{V_{in}}(s) = \frac{\frac{G_0}{1 + \frac{s}{w_p}}}{1 + \frac{G_0}{1 + \frac{s}{w_p}} H} = \frac{G_0}{1 + \frac{s}{w_p} + G_0 H}$$

$$\frac{V_{out}}{V_{in}}(s) = \underbrace{\frac{G_0}{1 + G_0 H}}_{G'_0} \underbrace{\frac{1}{1 + \frac{s}{w_p(1 + G_0 H)}}}_{w'_p}$$

$$\frac{G'_0}{G_0} = \frac{1}{1 + G_0 H} \quad \frac{w'_p}{w_p} = 1 + G_0 H$$


# Single Stage OpAmp Case

 
 
## Single pole amplifier:

$$\frac{V_{out}}{V_{in}}(s) = \underbrace{\frac{G_0}{1 + G_0 H}}_{G'_0} \underbrace{\frac{1}{1 + \frac{s}{w_p(1 + G_0 H)}}}_{w'_p}$$

$$G'_0 \simeq \frac{1}{H} \quad \frac{w'_p}{w_p} = 1 + G_0 H$$



Barkhasuen criteria:


$$|GH(jw)| = 1 \quad \angle GH(jw) = -180^\circ$$

▲ Intrinsically stable!



## Two-Stage OpAmp Case

► Double pole analysis:

 


$$G(s) = \frac{G_0}{\left(1 + \frac{s}{w_{p1}}\right) \left(1 + \frac{s}{w_{p2}}\right)}$$

$$\frac{V_{out}}{V_{in}}(s) = \frac{G_0}{\left(1 + \frac{s}{w_{p1}}\right) \left(1 + \frac{s}{w_{p2}}\right) + G_0 H}$$

$$w'_{p1,2} = -\frac{w_{p1} + w_{p2}}{2} \pm \frac{1}{2} \sqrt{(w_{p1} + w_{p2})^2 - 4(1 + G_0 H)w_{p1}w_{p2}}$$

## Two-Stage OpAmp Case


### ► Double pole analysis:

 

$$G(s) = \frac{G_0}{\left(1 + \frac{s}{w_{p1}}\right) \left(1 + \frac{s}{w_{p2}}\right)}$$

$$\frac{V_{out}}{V_{in}}(s) = \frac{G_0}{\left(1 + \frac{s}{w_{p1}}\right) \left(1 + \frac{s}{w_{p2}}\right) + G_0 H}$$
 
$$w'_{p1,2} = -\frac{w_{p1} + w_{p2}}{2} \pm \frac{1}{2} \sqrt{(w_{p1} + w_{p2})^2 - 4(1 + G_0 H)w_{p1}w_{p2}}$$



$$G_0 H < \frac{(w_{p1} + w_{p2})^2}{4w_{p1}w_{p2}} - 1$$


$$H < \frac{1}{4G_0} \left( \frac{w_{p1}}{w_{p2}} + \frac{w_{p2}}{w_{p1}} - 2 \right) \uparrow \quad \text{in order to cover up to } \mathbf{H=1}$$

**dominant  
pole splitting  
is required!**

$$\frac{w_{p2}}{G_0 w_{p1}} \uparrow \quad \text{or} \quad \frac{w_{p1}}{G_0 w_{p2}} \uparrow$$


## Two-Stage OpAmp Case

### ► Double pole analysis:

 

**Barkhasuen**  
criteria:

$$|GH(jw)| = 1 \quad \angle GH(jw) = -180^\circ$$

 

$$G_0 H < \frac{(w_{p1} + w_{p2})^2}{4w_{p1}w_{p2}} - 1$$


$$H < \frac{1}{4G_0} \left( \frac{w_{p1}}{w_{p2}} + \frac{w_{p2}}{w_{p1}} - 2 \right) \uparrow \quad \text{in order to cover up to } H=1$$

**dominant**  
pole splitting  
is required!

$$\frac{w_{p2}}{G_0 w_{p1}} \uparrow \quad \text{or} \quad \frac{w_{p1}}{G_0 w_{p2}} \uparrow$$

# Principle of Operation


## ► Transimpedance amplifier:

 

$$\begin{cases} V_{out} = -GV_{in} \\ I_z = \frac{V_{in} - V_{out}}{Z} \end{cases}$$


# Principle of Operation

## ► Transimpedance amplifier:

 


$$\begin{cases} V_{out} = -GV_{in} \\ I_z = \frac{V_{in} - V_{out}}{Z} \end{cases}$$

## ► Miller effect:

 


 equivalent **input**  
impedance seen  
from source



$$Z_{in} \doteq \frac{V_{in}}{I_z} = \frac{V_{in}}{V_{in} - V_{out}} Z = \frac{Z}{1 + G}$$

 
equivalent **output**  
impedance seen  
from amplifier



$$Z_{out} \doteq \frac{V_{out}}{-I_z} = \frac{V_{out}}{V_{out} - V_{in}} Z = \frac{G}{1 + G} Z$$
 
# Pole Adjustment

► **Transcapacitive impedance case:**  $Z(s) \doteq \frac{1}{C_{comp}s}$






$$G_1(DC) = g_{in1}r_{out1}$$

$$G_2(DC) = -g_{in2}r_{out2}$$


two-stage OpAmp  
small signal  
model

Miller  
compensation

 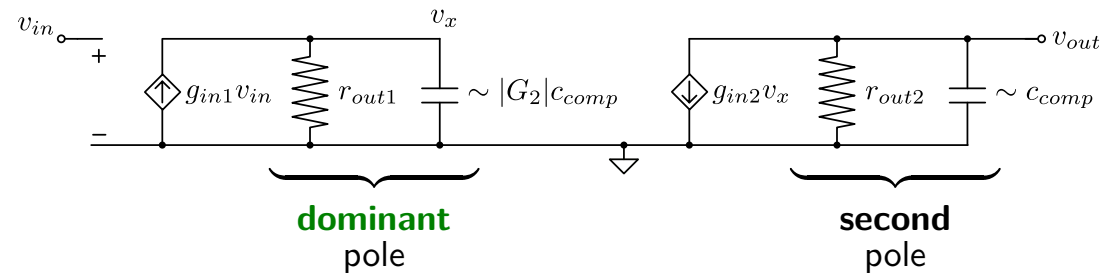 

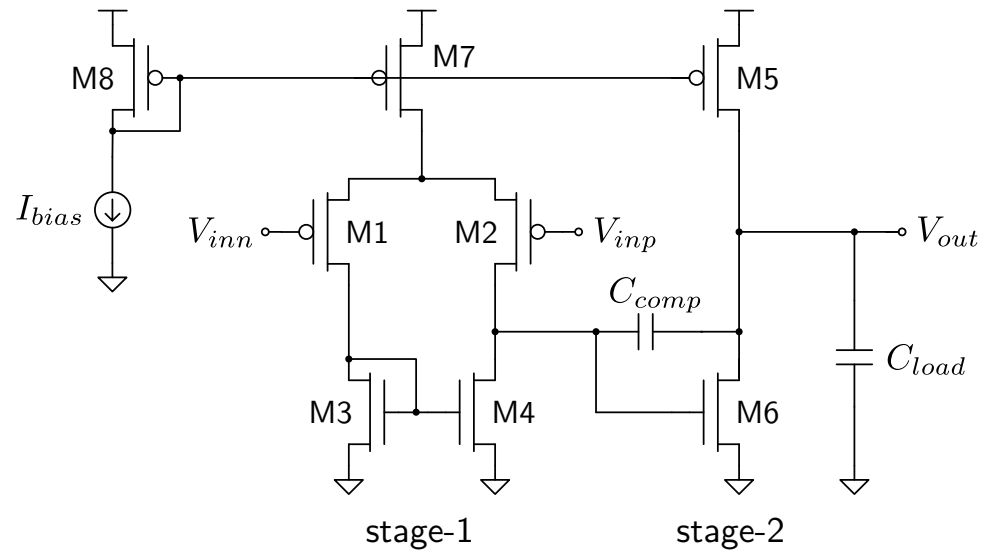
## Practical Example

- **Two-stage single-ended Miller-compensated OpAmp topology:**



## Practical Example

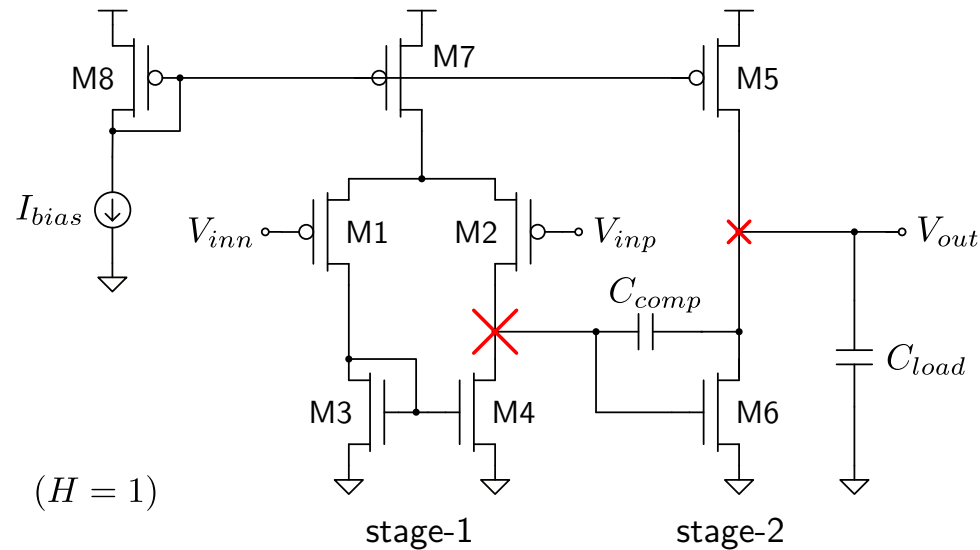
### ► Two-stage single-ended Miller-compensated OpAmp topology:



$$f'_{p1} \simeq GBW$$

$$GBW = (g_{in1} r_{out1}) (g_{in2} r_{out2}) \frac{1}{2\pi r_{out1} C_{comp}} \frac{1}{\underbrace{(g_{in2} r_{out2})}_{\text{Miller}}}$$

$$GBW = \frac{g_{m1,2}}{2\pi C_{comp}}$$

 


$$f'_{p2} = \frac{g_{m6}}{2\pi (C_{load} + C_{comp})}$$



$$\frac{g_{m6}}{g_{m1,2}} \geq 2.2 \left( 1 + \frac{C_{load}}{C_{comp}} \right)$$



# Design Variables
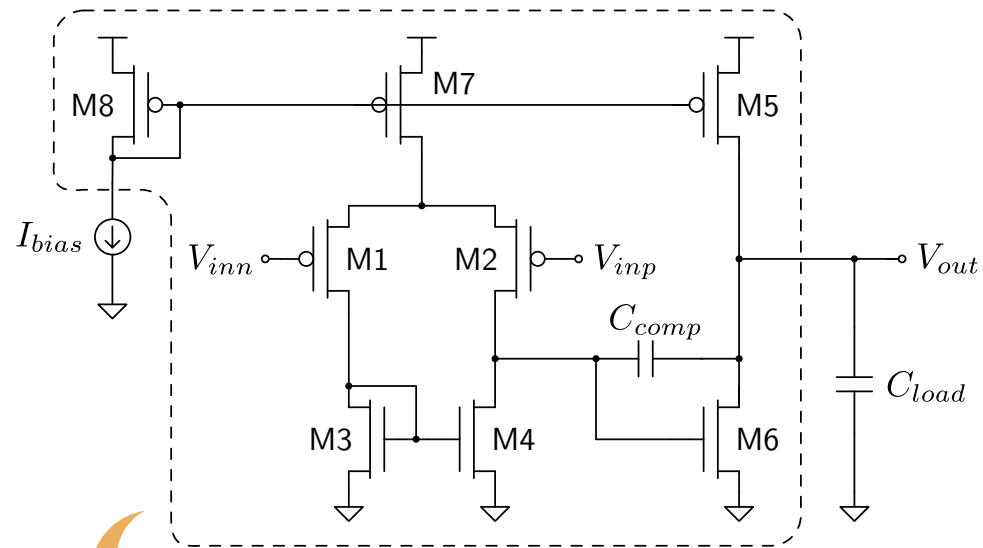
## ► Single-ended **Miller** OpAmp example:




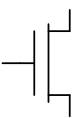
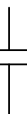
$\times 8$    $(W, L, I_D)$   
 $\times 1$    $(WL)$

$\left. \vphantom{\begin{matrix} \times 8 \\ \times 1 \end{matrix}} \right\} \text{25 design variables!}$

## Design Variables
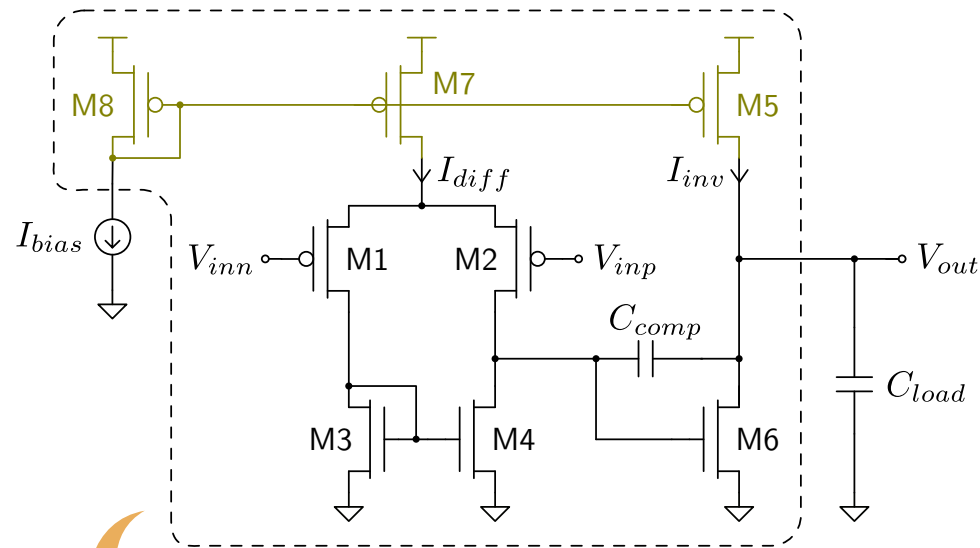
### ► Single-ended **Miller** OpAmp example:



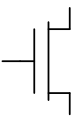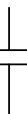$\times 8$    $(W, L, I_D)$   
 $\times 1$    $(WL)$

$\left. \begin{array}{l} (W, L, I_D) \\ (WL) \end{array} \right\} \text{25 design variables!}$


### ► Device **matching** groups:

#### ■ Current **biasing**

$$I_{diff} \doteq \underbrace{\frac{(W/L)_7}{(W/L)_8}}_{m_{diff}} I_{bias} \quad I_{inv} \doteq \underbrace{\frac{(W/L)_5}{(W/L)_8}}_{m_{inv}} I_{bias}$$

# Design Variables
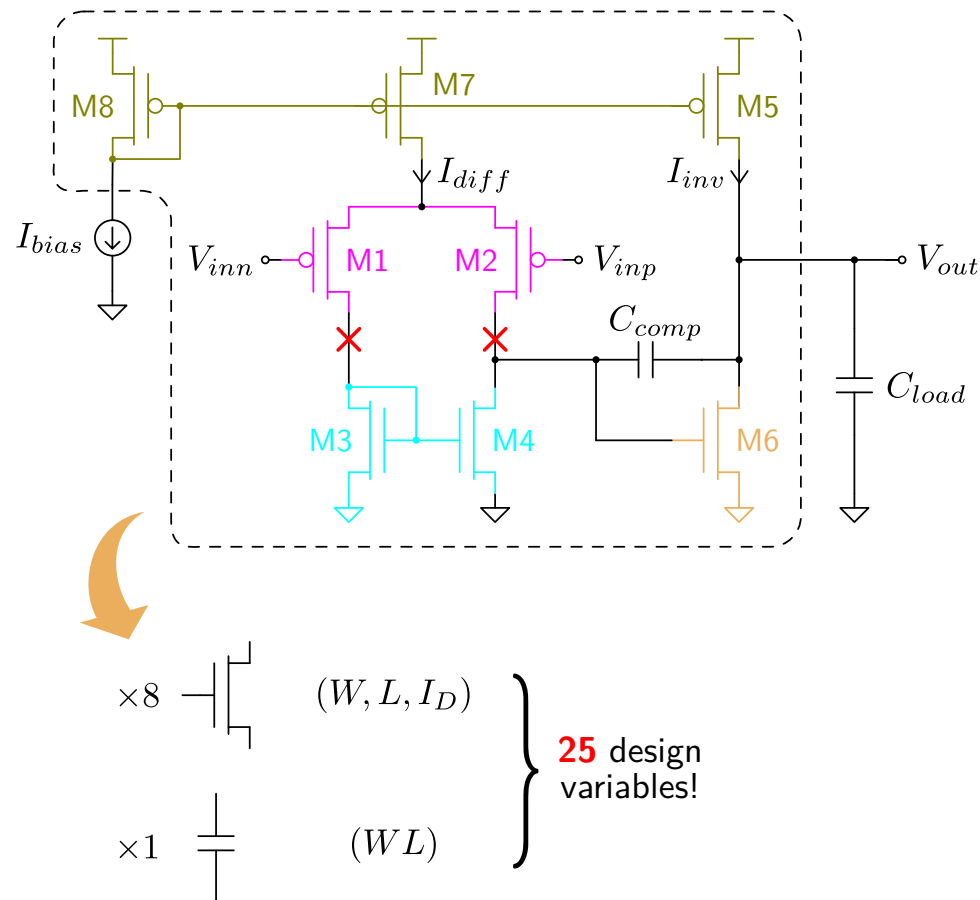
## ► Single-ended **Miller** OpAmp example:



## ► Device **matching** groups:

### ■ Current **biasing**

$$I_{diff} \doteq \underbrace{\frac{(W/L)_7}{(W/L)_8}}_{m_{diff}} I_{bias} \quad I_{inv} \doteq \underbrace{\frac{(W/L)_5}{(W/L)_8}}_{m_{inv}} I_{bias}$$

### ■ Null systematic **offset**

$$\left( \frac{W}{L} \right)_1 \equiv \left( \frac{W}{L} \right)_2 \doteq \left( \frac{W}{L} \right)_{diff}$$

$$\left( \frac{W}{L} \right)_3 \equiv \left( \frac{W}{L} \right)_4 \doteq \left( \frac{W}{L} \right)_{sing}$$



$$\frac{I_{diff}/2}{I_{inv}} \equiv \frac{(W/L)_3}{(W/L)_6}$$

**8 design variables!**


$$\left\{ \begin{array}{l} \left( \frac{W}{L} \right)_{diff} \quad \left( \frac{W}{L} \right)_{sing} \quad \left( \frac{W}{L} \right)_{inv} \\ I_{bias} \quad I_{diff} \quad I_{inv} \quad C_{comp} \quad L \end{array} \right.$$

## Design Equations
 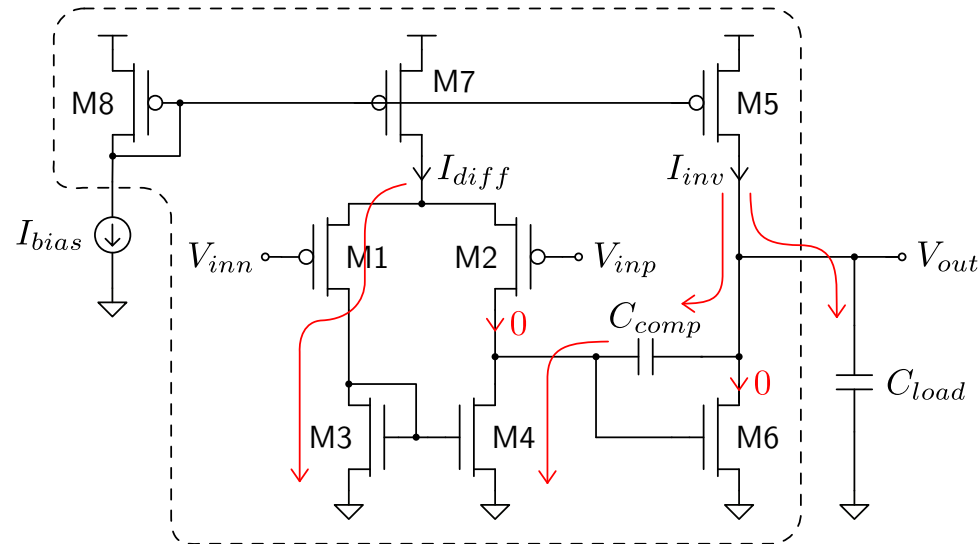
### ► Single-ended **Miller** OpAmp example:




 
$$SR_+ = \frac{I_{inv} - I_{diff}}{C_{comp} + C_{load}}$$




## Design Equations

► Single-ended **Miller** OpAmp example:

 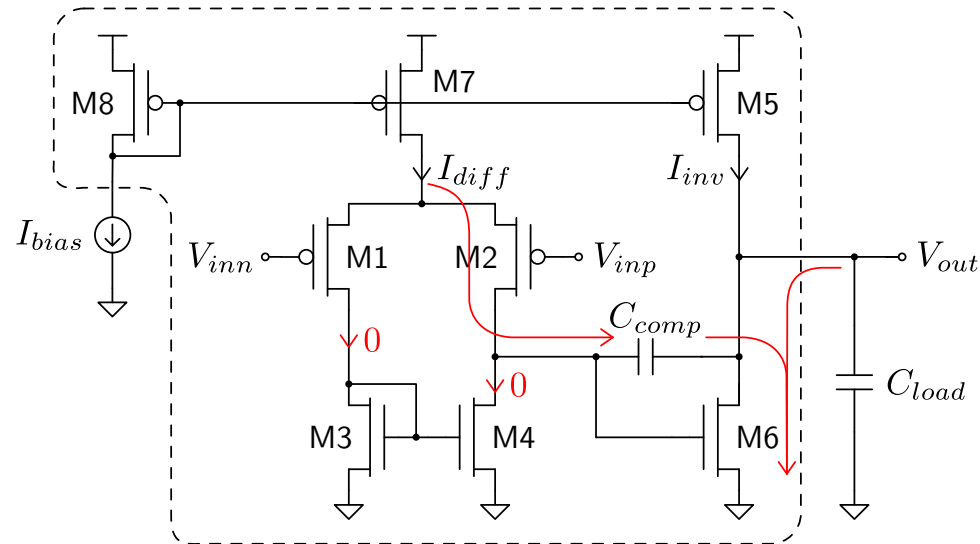

$$SR_+ = \frac{I_{inv} - I_{diff}}{C_{comp} + C_{load}}$$


$$SR_- = \frac{I_{diff}}{C_{comp}}$$

 

# Design Equations
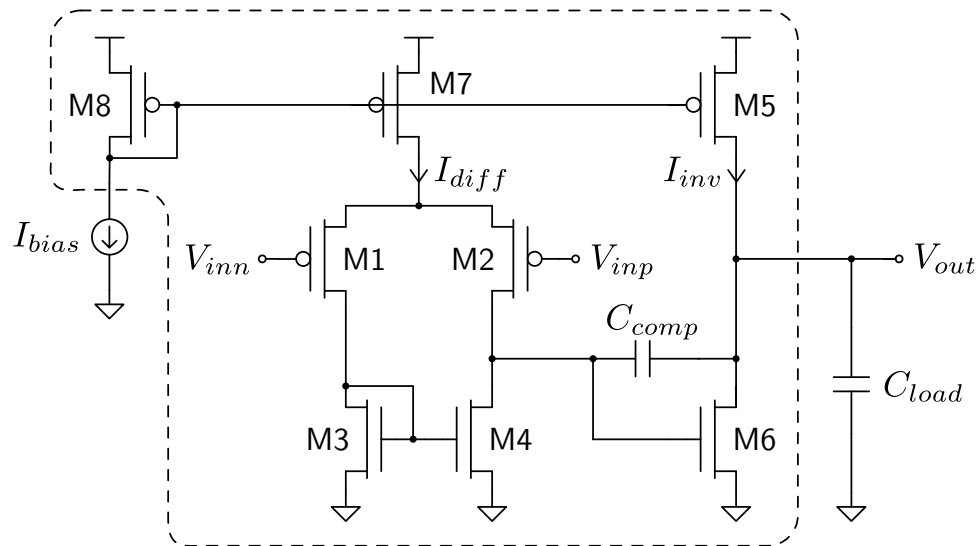
## ► Single-ended Miller OpAmp example:

**strong** inversion  
forward **saturation**  
for all transistors



$$SR_+ = \frac{I_{inv} - I_{diff}}{C_{comp} + C_{load}}$$

$$SR_- = \frac{I_{diff}}{C_{comp}}$$

$$m_\phi \geq 60^\circ : \frac{g_{m6}}{g_{m1,2}} \geq 2.2 \left( 1 + \frac{C_{load}}{C_{comp}} \right)$$

$$\sqrt{2 \frac{\beta_N}{\beta_P} \frac{(W/L)_{inv}}{(W/L)_{diff}} \frac{I_{inv}}{I_{diff}}} \geq 2.2 \left( 1 + \frac{C_{load}}{C_{comp}} \right)$$

$$GBW = \frac{g_{m1,2}}{2\pi C_{comp}} = \frac{1}{2\pi C_{comp}} \sqrt{\frac{\beta_P}{n} \left( \frac{W}{L} \right)_{diff} I_{diff}}$$

$$G(DC) = \frac{g_{m1,2}}{g_{md1,2} + g_{md3,4}} \frac{g_{m6}}{g_{md5} + g_{md6}} = \frac{2}{n(\lambda_N + \lambda_P)^2} \sqrt{\frac{2\beta_P\beta_N \left( \frac{W}{L} \right)_{diff} \left( \frac{W}{L} \right)_{inv}}{I_{diff} I_{inv}}} \propto \frac{1}{L}$$

$$\frac{I_{diff}/2}{I_{inv}} \equiv \frac{(W/L)_{sing}}{(W/L)_{inv}}$$

