

## 6. Delta-Sigma Modulators for ADC

Francesc Serra Graells

[francesc.serra.graells@uab.cat](mailto:francesc.serra.graells@uab.cat)

Departament de Microelectrònica i Sistemes Electrònics  
Universitat Autònoma de Barcelona

[paco.serra@imb-cnm.csic.es](mailto:paco.serra@imb-cnm.csic.es)

Integrated Circuits and Systems  
IMB-CNM(CSIC)


- 1 Oversampling and Noise Shaping Principles
- 2 Architecture Selection Based on Quantization Error
- 3 Switched-Capacitor CMOS Implementations
- 4 Modeling Circuit Second Order Effects
- 5 Digitally Assisted Techniques
- 6 Low-Power Circuit Topologies

- 1 Oversampling and Noise Shaping Principles
- 2 Architecture Selection Based on Quantization Error
- 3 Switched-Capacitor CMOS Implementations
- 4 Modeling Circuit Second Order Effects
- 5 Digitally Assisted Techniques
- 6 Low-Power Circuit Topologies
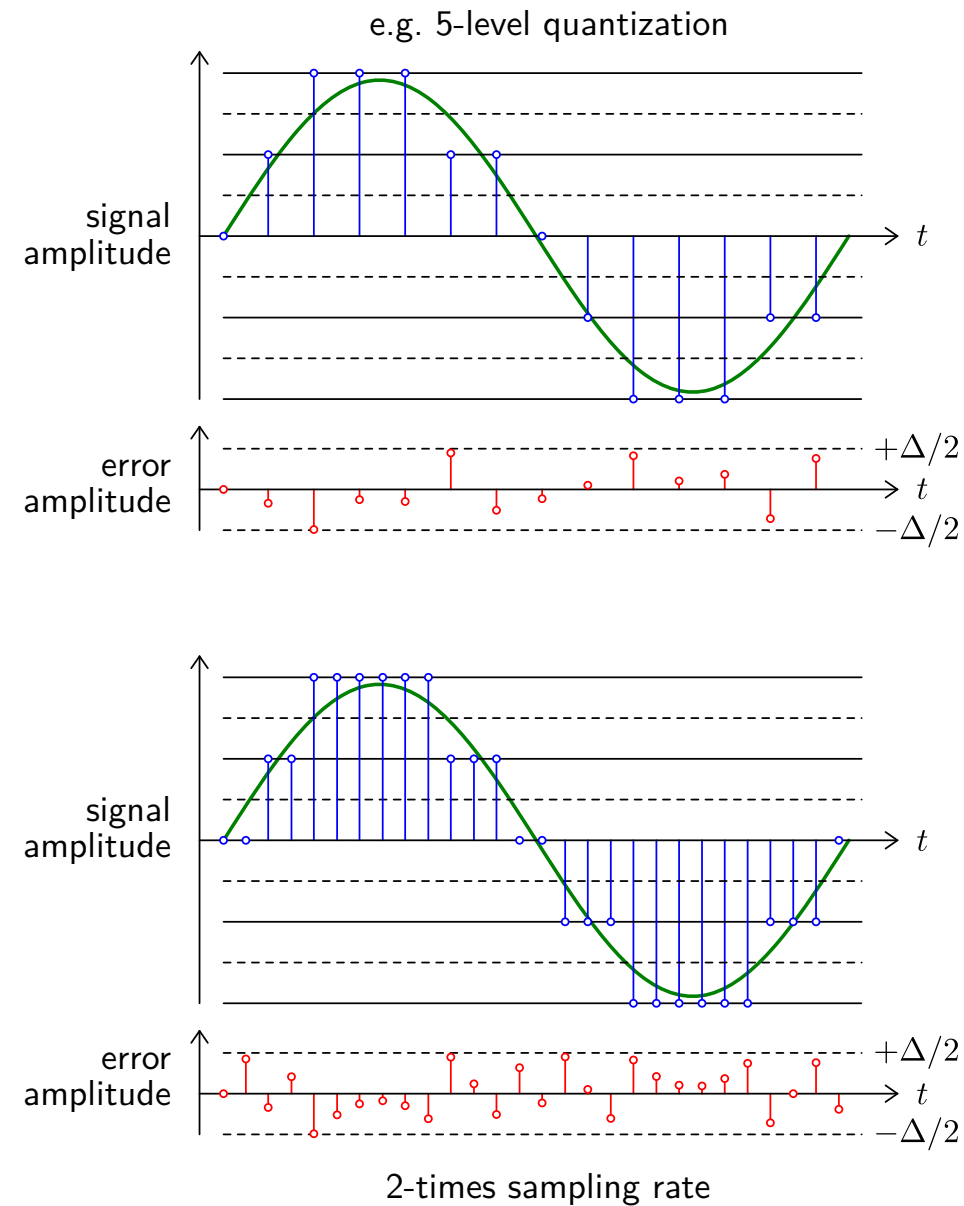
# Oversampling

- Flat (**white**) error spectrum profile

$$\Delta = \frac{V_{FS}}{2^N} \quad QN = \frac{\Delta^2}{12}$$



# Oversampling

- Flat (**white**) error spectrum profile:

$$QN(f) = \frac{1}{6} \frac{\Delta^2}{f_s} \quad [\text{W/Hz}]$$


- **Spread** across spectrum ( $f_s/2$ )

- **Oversampling** ratio:

$$OSR \doteq \frac{f_s}{f_{nyq}} \equiv \frac{f_s}{2BW}$$

- ▲ Lower **in-band** noise


- ▼ Higher **clock** frequencies

 

$$QN = \frac{\Delta^2}{12} \frac{1}{OSR} \quad S_{max} = \left( \frac{V_{FS}}{2\sqrt{2}} \right)^2 \quad SQNR_{max} \doteq \frac{S_{max}}{QN} = \left( 2^N \sqrt{1.5} \right)^2 OSR$$


$$SQNR_{max} = 6.02N + 1.76 + 10 \log OSR \quad [\text{dB}]$$

+3dB/oct  
+0.5bit/oct

 

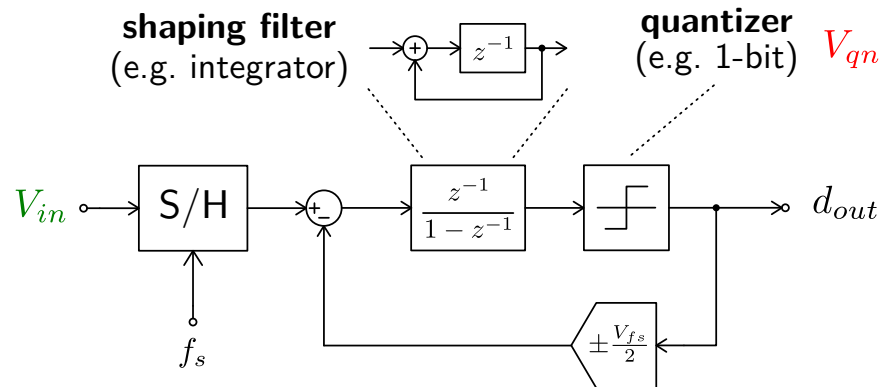
# Quantization Noise Shaping

- Basic single-loop Delta-Sigma modulator (**DSM**) for discrete time (**DT**) ADCs:




$$D_{out} = STF(z)V_{in} + NTF(z)V_{qn} \quad \left\{ \begin{array}{l} STF = \frac{H}{1+H} \rightarrow 1 \\ NTF = \frac{1}{1+H} \rightarrow 0 \end{array} \right. \quad H \rightarrow \infty$$

Equivalent **linear model**:

 

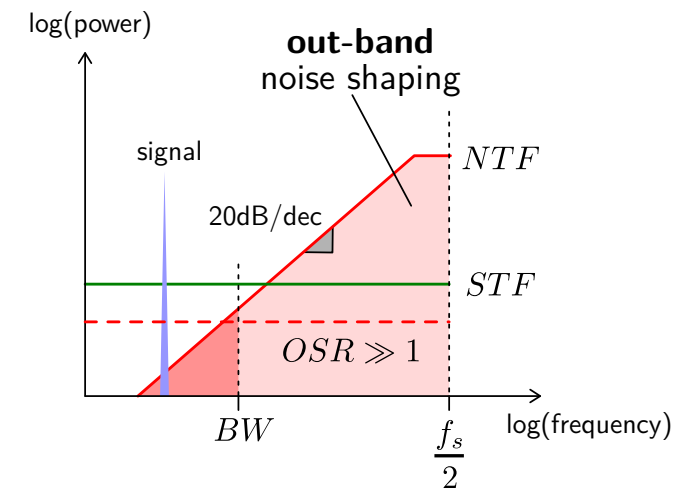
$$H(z) = \frac{z^{-1}}{1 - z^{-1}} \quad \left\{ \begin{array}{l} STF = \frac{H}{1+H} \equiv z^{-1} \text{ (all-pass)} \\ NTF = \frac{1}{1+H} \equiv 1 - z^{-1} \text{ (high-pass shaping)} \end{array} \right.$$



# Quantization Noise Shaping
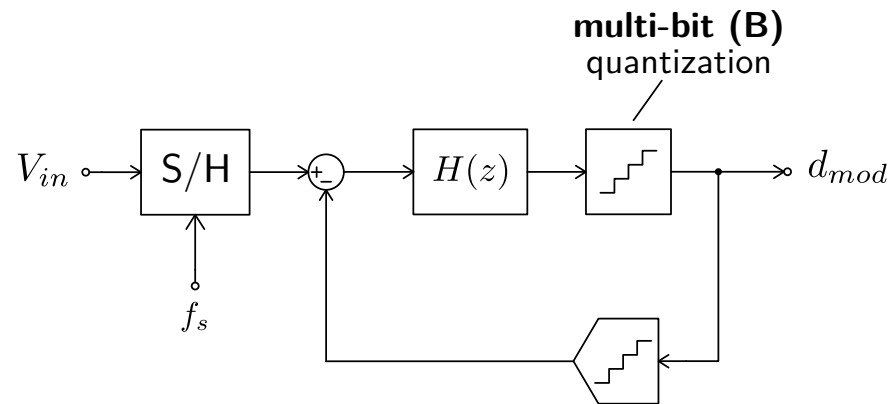
## ► N-order B-bit single loop architecture:



## ► Multi-bit quantization:

- Resolution added to overall DR
- Internal full-scale reduction
- Feedback DAC **not intrinsically linear**

## ► High-order filtering:


- Sharper noise shaping
- **Stability** issues

## ► Ideal dynamic range:

$$DR = \frac{3\pi}{2} (2^B - 1)^2 (2N + 1) \left( \frac{OSR}{\pi} \right)^{2N+1}$$

$$DR[\text{dB}] = 6.7 + 20 \log (2^B - 1) + 10 \log (2N + 1) + 20 (N + 0.5) \log \frac{OSR}{\pi}$$

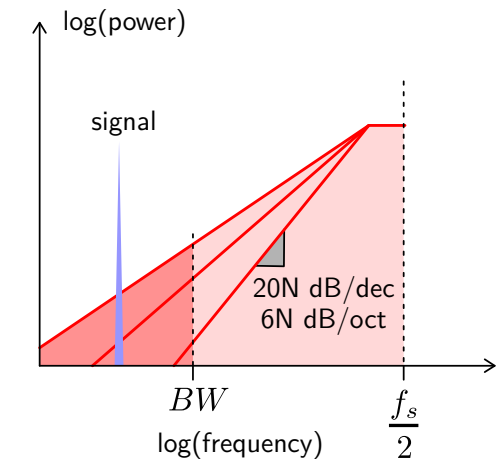shaping order    oversampling only  
 (N+0.5)-bit/oct(OSR)  
 direct improvement




- 1 Oversampling and Noise Shaping Principles
- 2 Architecture Selection Based on Quantization Error
- 3 Switched-Capacitor CMOS Implementations
- 4 Modeling Circuit Second Order Effects
- 5 Digitally Assisted Techniques
- 6 Low-Power Circuit Topologies



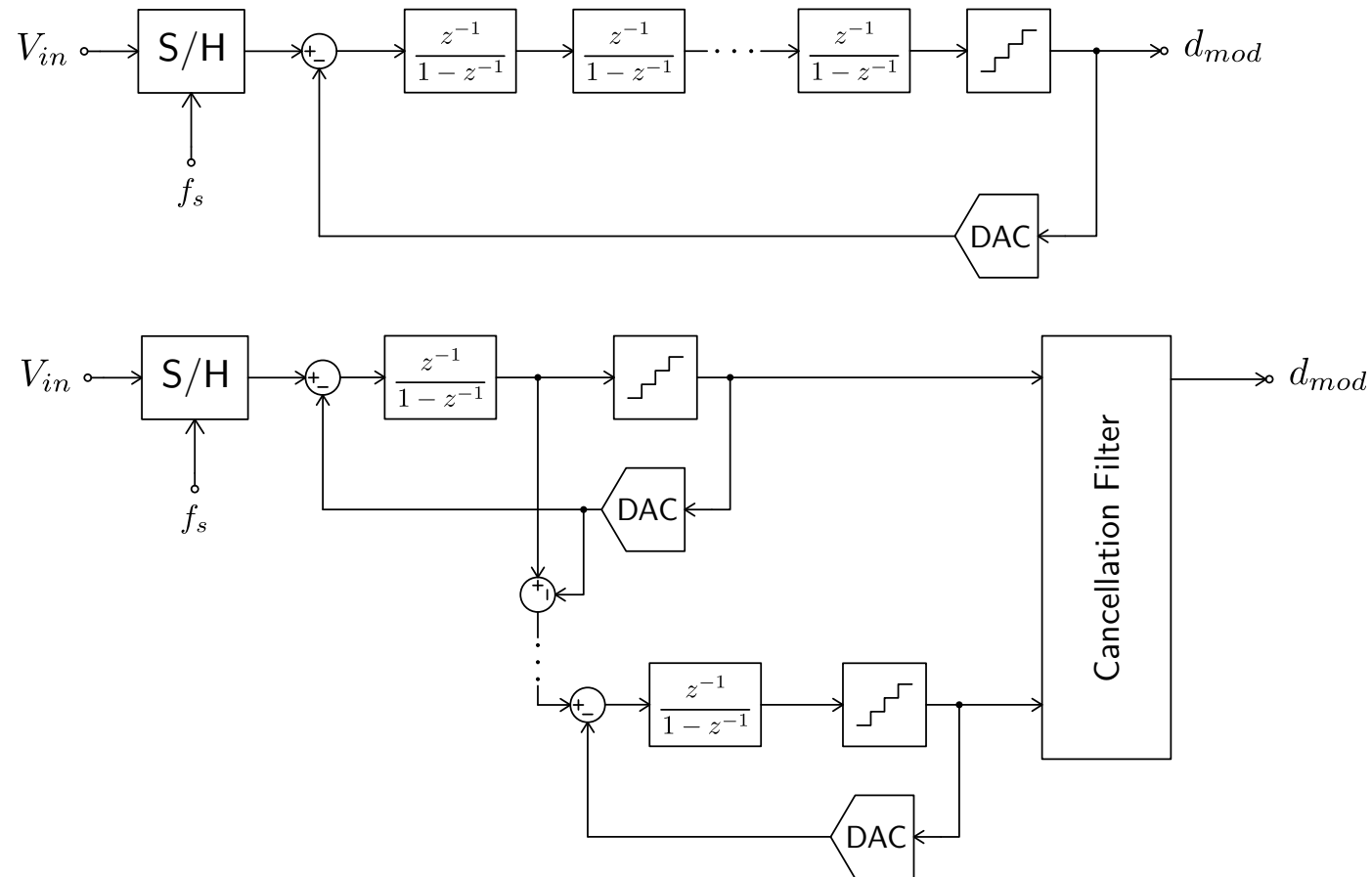
# Single-Loop vs MASH

- High-order **feedback** or **feedforward** DSM architectures:


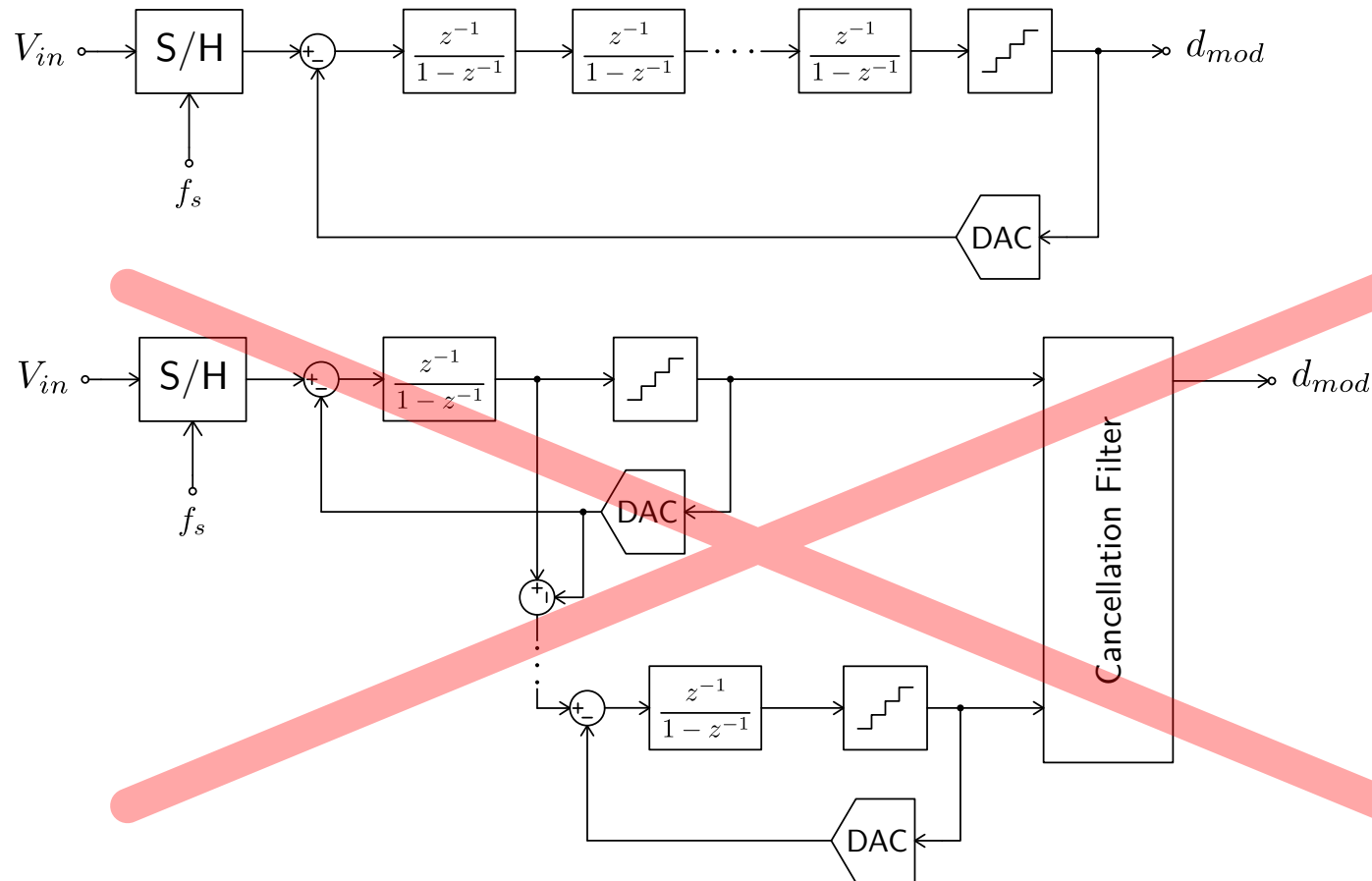
## Single-Loop vs MASH

- High-order **feedback** or **feedforward** DSM architectures:




▼ **Unstability** issues

▼ **Mismatching** sensitivity

► More suitable for DSM **DACs**!
 
# Order Selection

► Simplest DSM architecture: **first order**




$$H(z) = \frac{z^{-1}}{1 - z^{-1}} \begin{cases} STF = \frac{H}{1 + H} \equiv z^{-1} \\ NTF = \frac{1}{1 + H} \equiv 1 - z^{-1} \end{cases}$$

▲ Intrinsically **stable**


▼ **Large OSR** needed

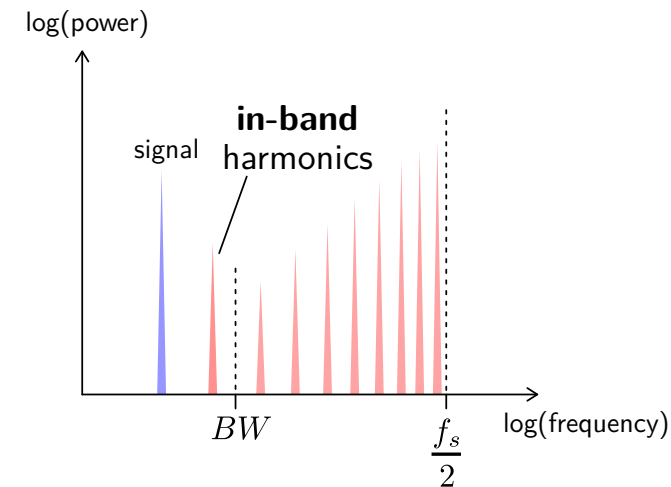▼ **Tonal** spectrum caused by signal to quantization noise correlation!


 
# Order Selection

- Next architecture step: **second order**




$$\begin{cases} STF = \frac{1}{\left(\frac{1-z^{-1}}{z^{-1}} + 1\right)(1-z^{-1}) + 1} \equiv z^{-1} \\ NTF = \frac{1}{1 + \left(\frac{1}{1-z^{-1}} + 1\right)\frac{z^{-1}}{1-z^{-1}}} \equiv (1-z^{-1})^2 \end{cases}$$

second-order high-pass

- ▲ Intrinsically **stable** for limited input range


- ▲ Signal to quantization noise **uncorrelation** (continuous spectrum)

- Moderate **OSR** requirements

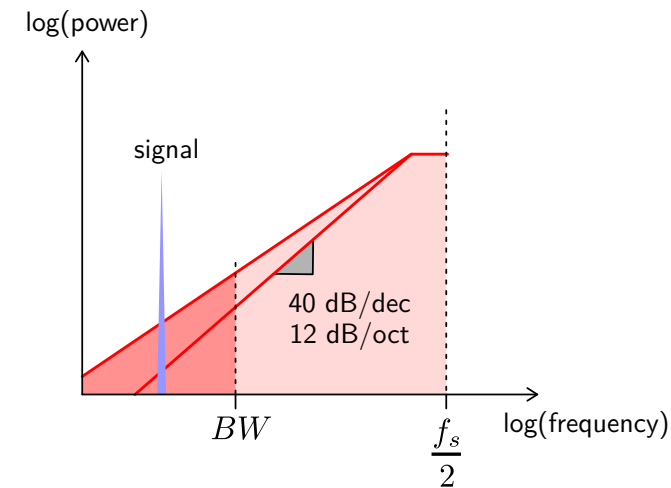

# Delta-Sigma Noise Shaping


## ► Higher-order general architecture:

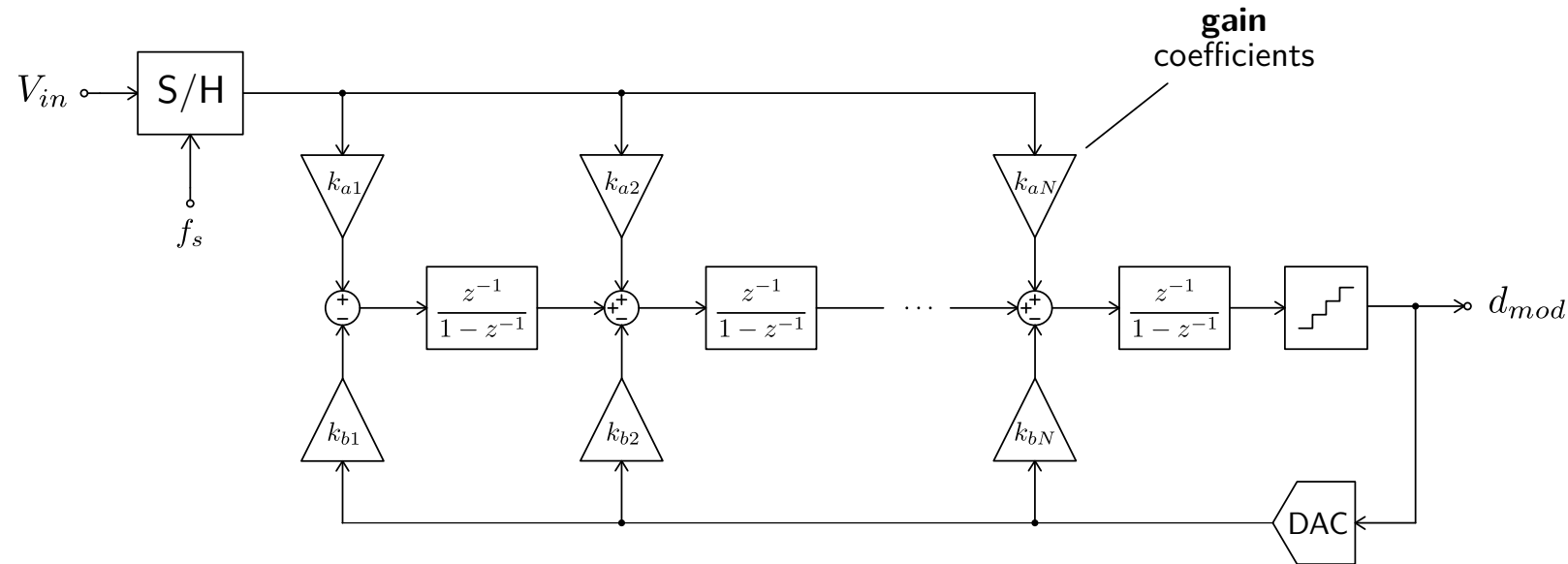

▲ Sharper noise shaping


▼ Possibility of loop instability for  $N > 2$

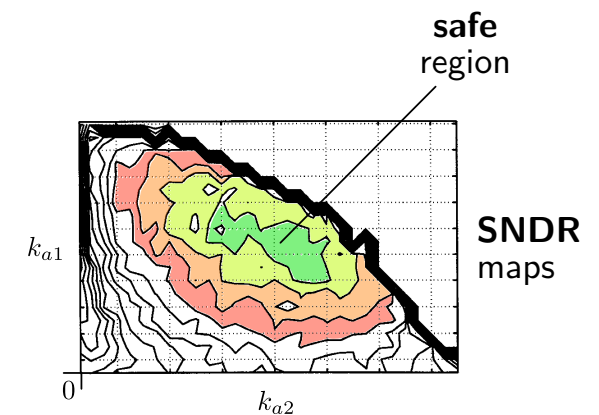► Coefficients optimization against mismatching



## Commonly Used Architectures



### ► Feedforward cancellation:

 

▲ **Internal full scale**  
low occupancy

▼ **Additional adder stage**  
in front of quantizer

### ► Resonator attenuation:

 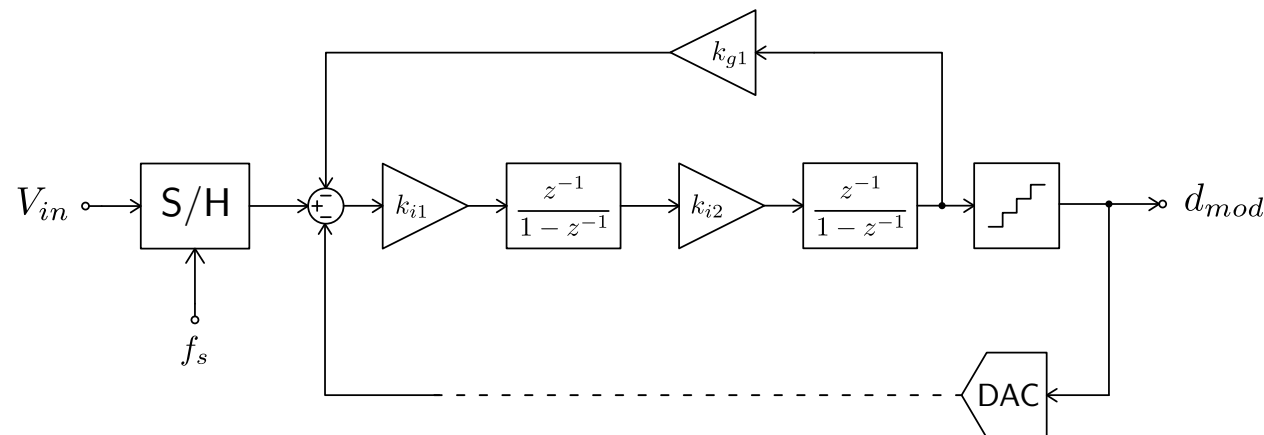


▲ Extra noise shaping  
at **band edge**

▼ Zero sensitivity to  
coefficient **matching**

- 1 Oversampling and Noise Shaping Principles
- 2 Architecture Selection Based on Quantization Error
- 3 Switched-Capacitor CMOS Implementations
- 4 Modeling Circuit Second Order Effects
- 5 Digitally Assisted Techniques
- 6 Low-Power Circuit Topologies

 
# SC Integrator

- Shaping filter basic building **block**:





Analog circuit realization (ADC)

Digital circuit realization (DAC)

 




- SC-OpAmp **compact** implementation:

 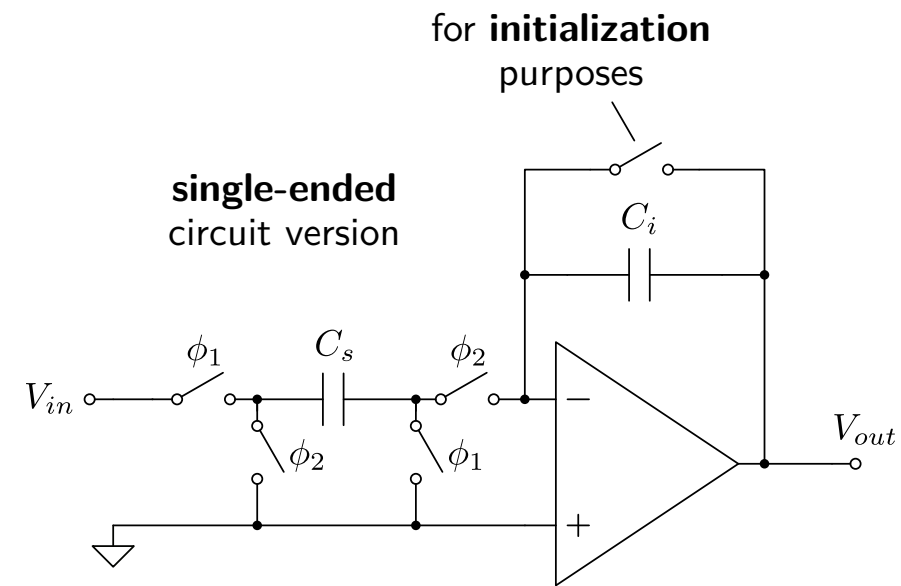







## SC Integrator

► SC-OpAmp **compact** implementation:

  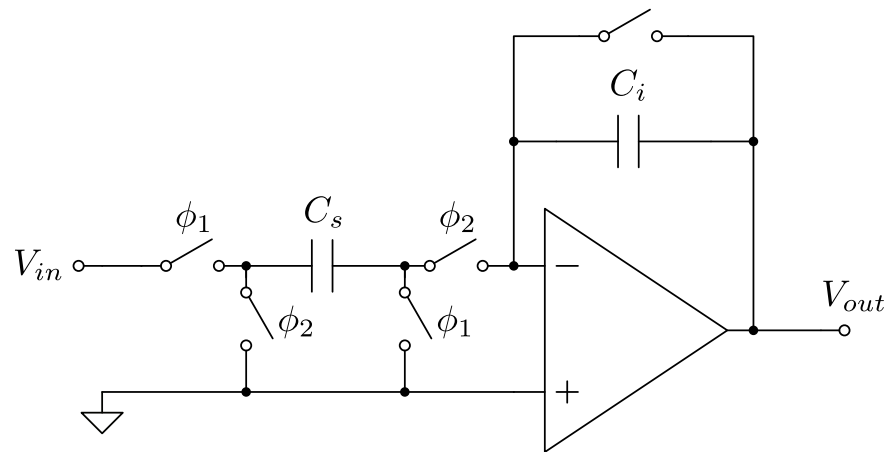

# SC Integrator



► SC-OpAmp **compact** implementation:

    



$$V_{out}(n) = V_{out}(n-1) + \frac{C_s}{C_i} V_{in}(n-1)$$

## SC Integrator

► SC-OpAmp **compact** implementation:

 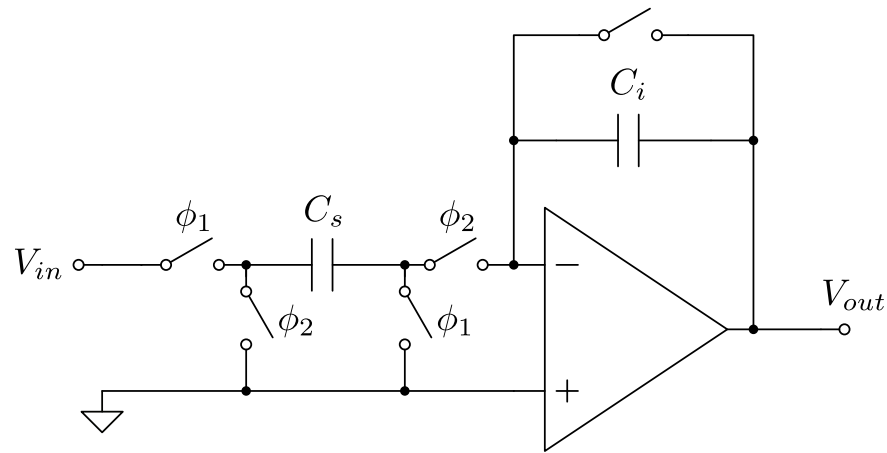
  
$$\frac{V_{out}(z)}{V_{in}(z)} = k \frac{z^{-1}}{1 - z^{-1}} \quad k \doteq \frac{C_s}{C_i}$$




$$V_{out}(n) = V_{out}(n-1) + \frac{C_s}{C_i} V_{in}(n-1)$$

$$V_{out}(z) = z^{-1} V_{out}(z) + \frac{C_s}{C_i} z^{-1} V_{in}(z)$$

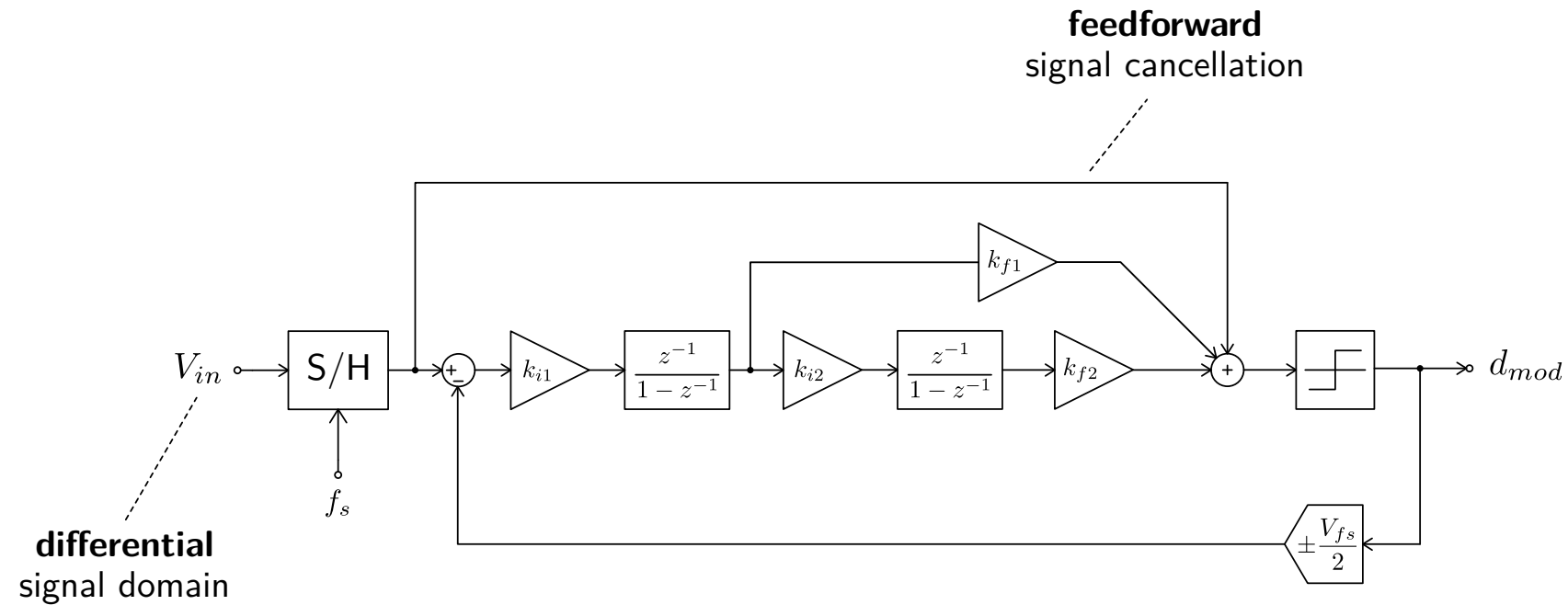
# SC Noise Shaper

- **Fully-differential** 2nd-order single-bit DSM example:


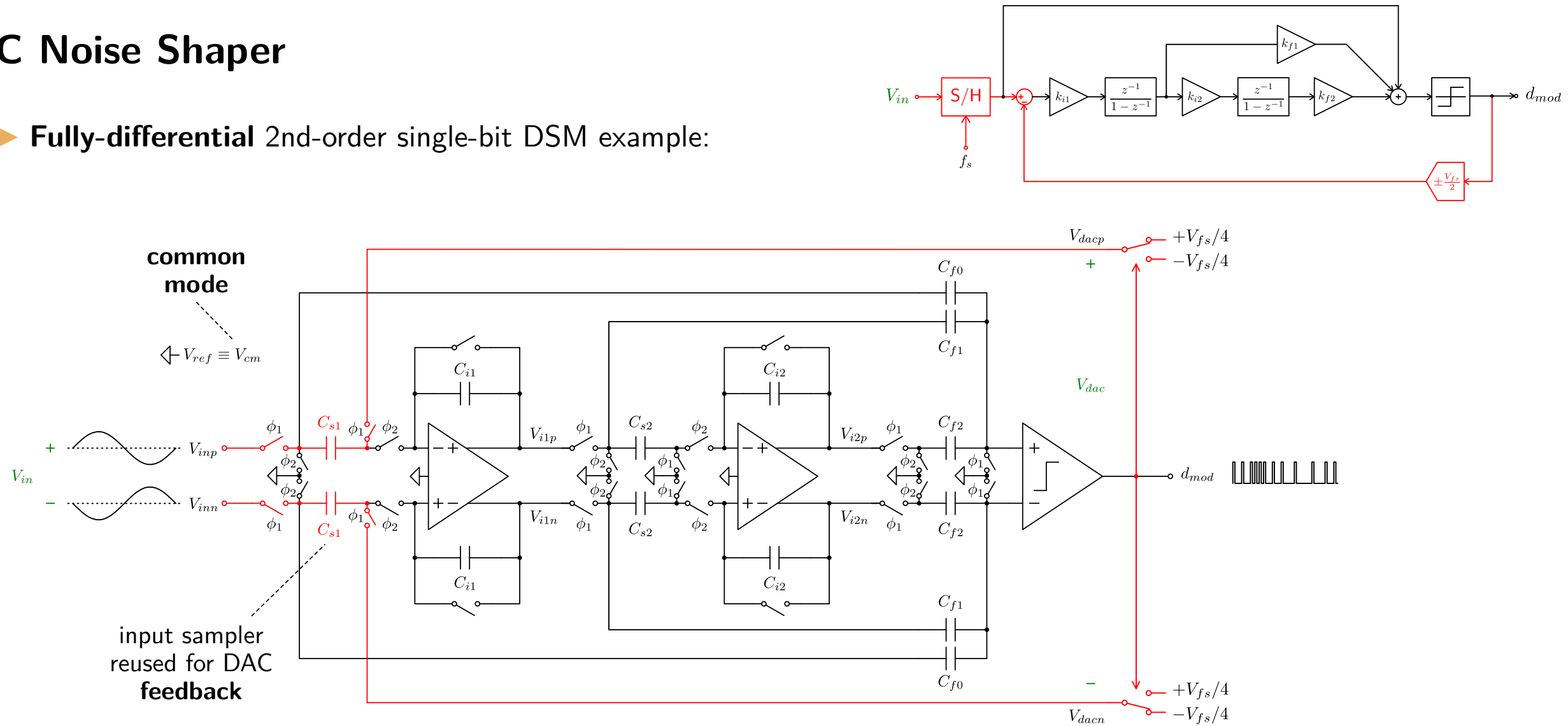
# SC Noise Shaper


- Fully-differential 2nd-order single-bit DSM example:



$$\phi_1 \quad Q_{s1}(n-1) = C_{s1} [V_{in}(n-1) - V_{dac}(n-1)]$$

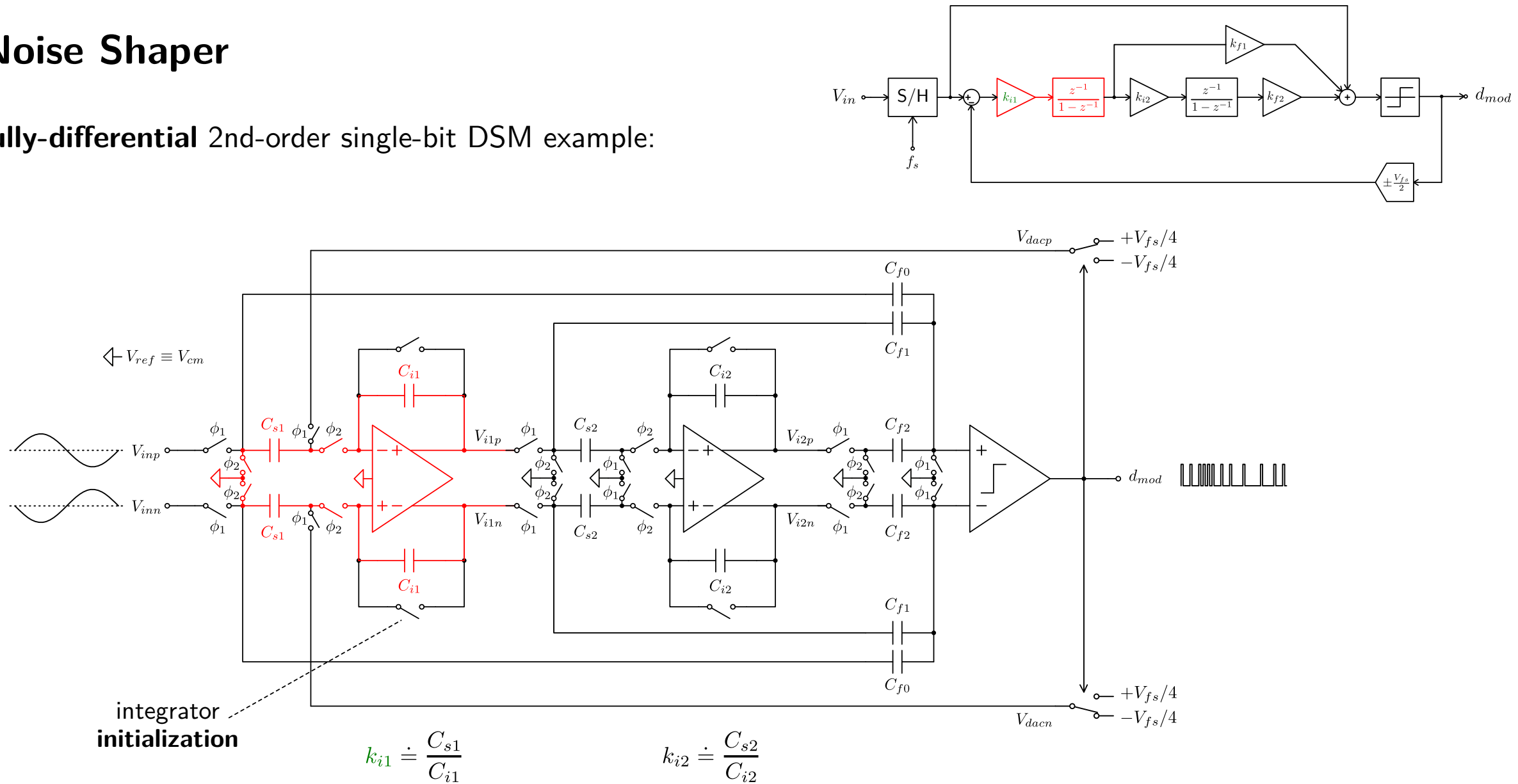
# SC Noise Shaper

- Fully-differential 2nd-order single-bit DSM example:


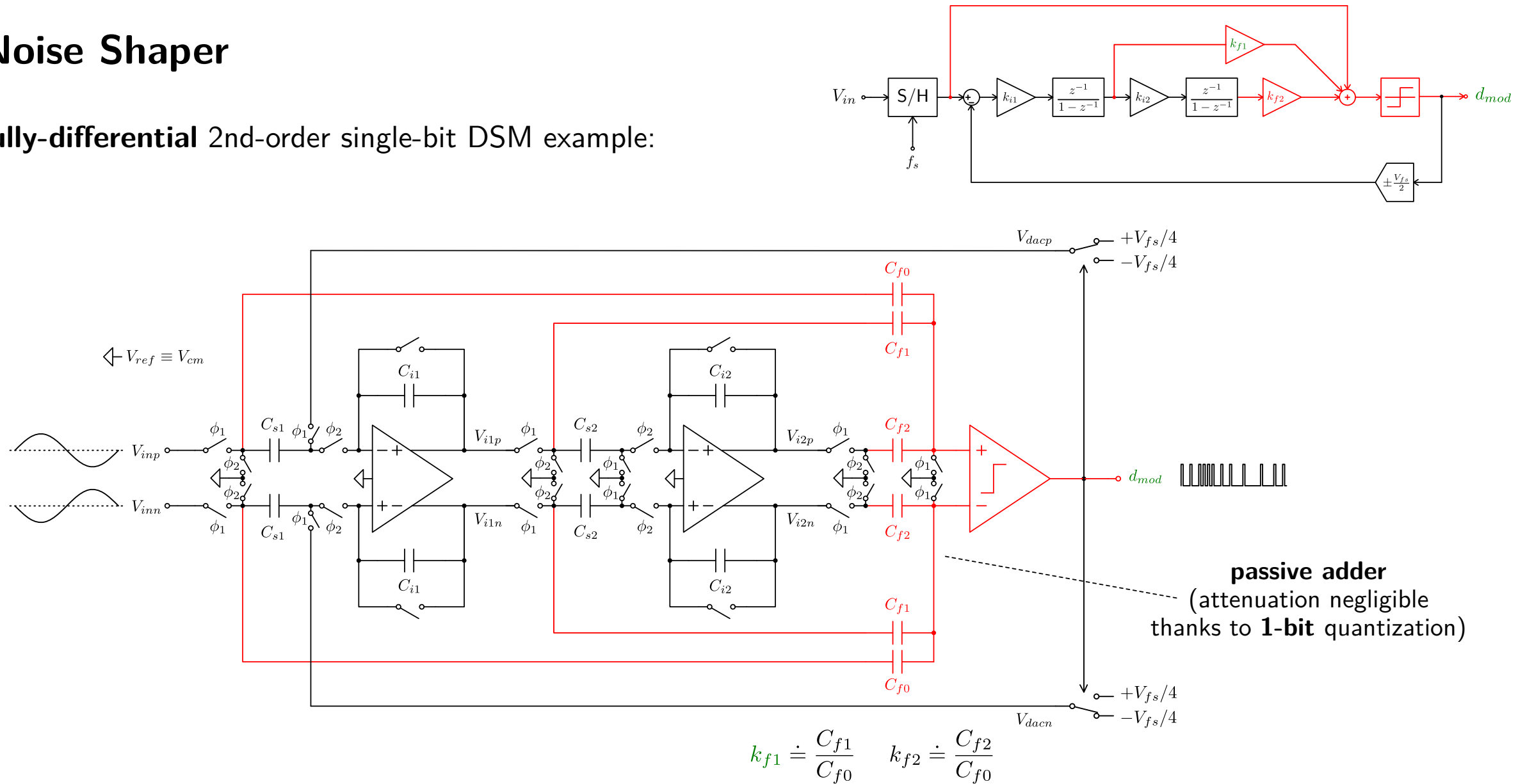
# SC Noise Shaper

- **Fully-differential** 2nd-order single-bit DSM example:




- 1 Oversampling and Noise Shaping Principles
- 2 Architecture Selection Based on Quantization Error
- 3 Switched-Capacitor CMOS Implementations
- 4 Modeling Circuit Second Order Effects
- 5 Digitally Assisted Techniques
- 6 Low-Power Circuit Topologies





# Switch Thermal Noise

- Added to signal at **input sampler**:

 


switch  
on-resistance

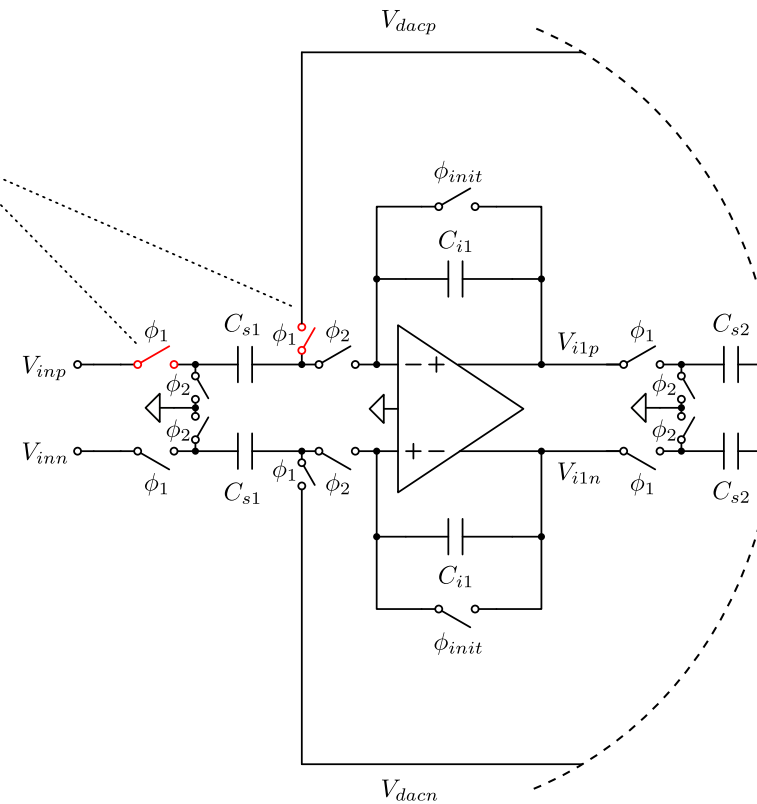 

# Switch Thermal Noise



- Added to signal at **input sampler**:

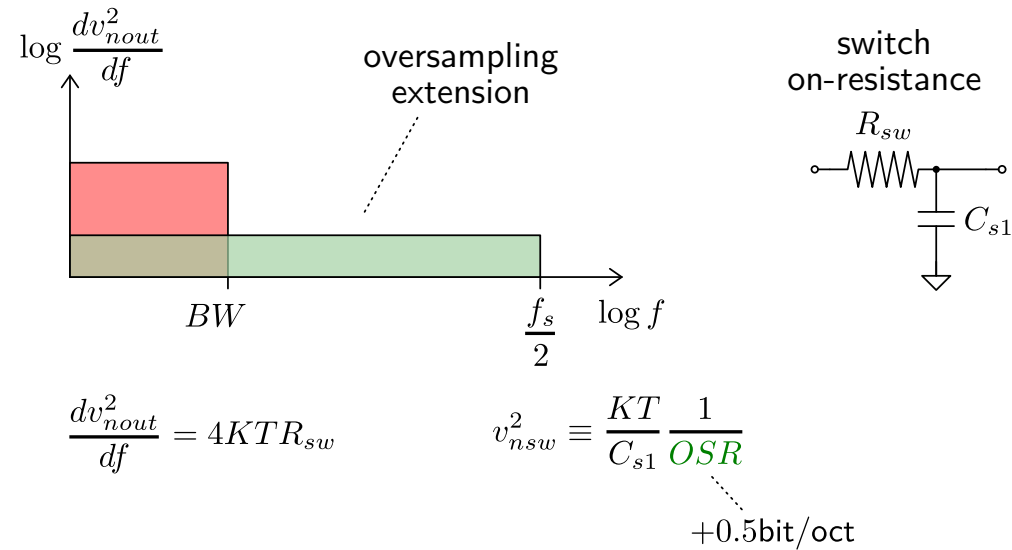

- Fully differential contributions:  $v_{nswtot}^2 \equiv 2 \frac{KT}{C_{s1}} \frac{1}{OSR}$



$$DR_{diff} = DR_{sing} - \underbrace{3\text{dB}}_{\text{switches} \times 2} + \underbrace{6\text{dB}}_{\text{full-scale} \times 2} = DR_{sing} + 3\text{dB}(+0.5\text{bit})$$

 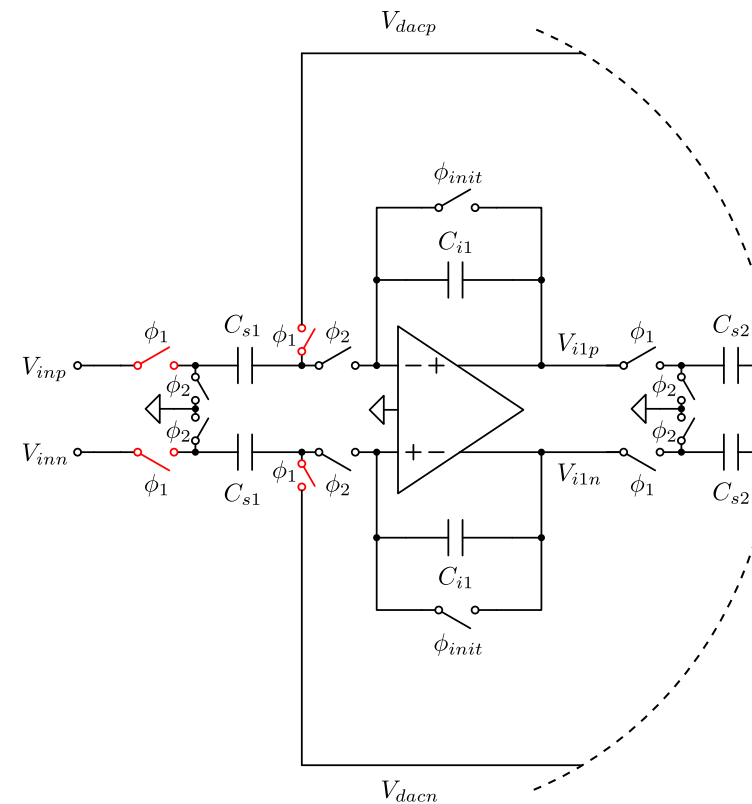- Large **capacitor area** and low **input impedance** values!


  
# Clock Jitter


- Critical at **input sampler** due to its continuous (**CT**) to discrete time (**DT**) conversion:





# OpAmp Finite Gain

- SC integrator transfer function when OpAmp **open loop gain** is limited:

equivalent **single ended** half circuit

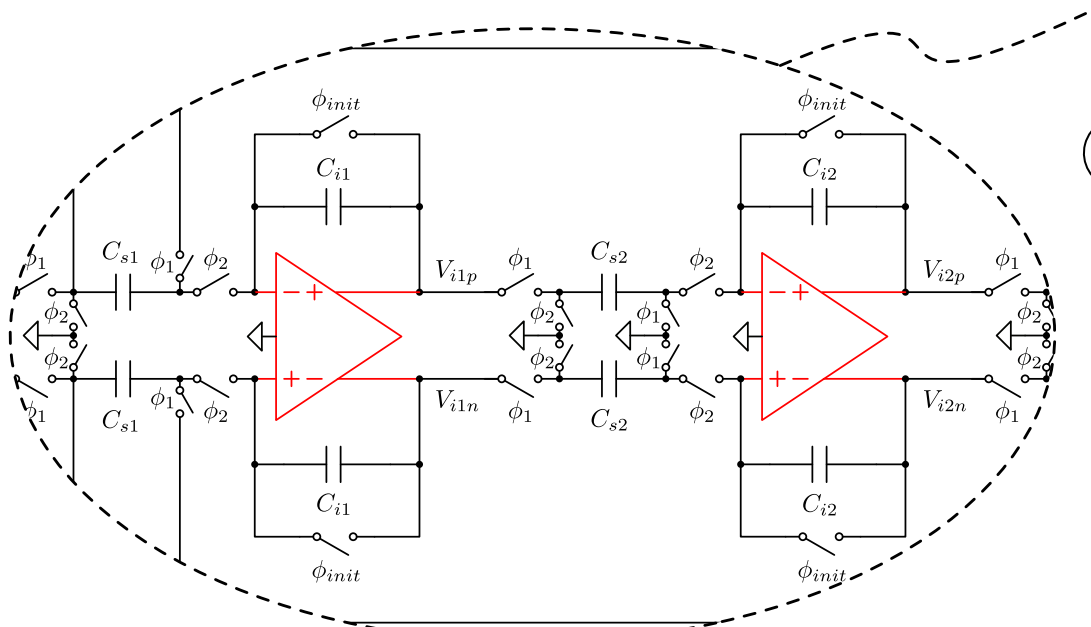

more relevant in  
first stages

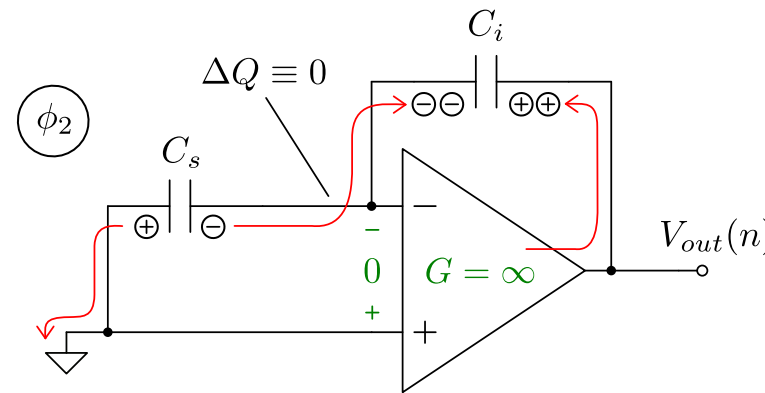 

$$V_{out}(n) = V_{out}(n-1) + \frac{C_s}{C_i} V_{in}(n-1)$$

$$\frac{V_{out}}{V_{in}}(z) = k \frac{z^{-1}}{1 - z^{-1}} \quad k \doteq \frac{C_s}{C_i}$$

## OpAmp Finite Gain



- SC **integrator** transfer function when OpAmp **open loop gain** is limited:

$$Q_x(n) \equiv Q_x(n-1)$$

$$\begin{aligned} C_s V_x(n) + C_i [V_x(n) - V_{out}(n)] &= \\ &= -C_s V_{in}(n-1) + C_i [V_x(n-1) - V_{out}(n-1)] \end{aligned}$$

$$V_x \doteq -\frac{V_{out}}{G}$$
  
$$\begin{aligned} +C_s \frac{V_{out}(n)}{G} + C_i \left(1 + \frac{1}{G}\right) V_{out}(n) &= \\ &= +C_s V_{in}(n-1) + C_i \left(1 + \frac{1}{G}\right) V_{out}(n-1) \end{aligned}$$



integration leakage

gain mismatch

$$k \doteq \frac{C_s}{C_i}$$

$$V_{out}(n) = \frac{V_{out}(n-1)}{1 + \frac{k}{1+G}} + \frac{k V_{in}(n-1)}{1 + \frac{1}{G}(k+1)}$$

## OpAmp Finite Gain



- SC integrator transfer function when OpAmp **open loop gain** is limited:

$$Q_x(n) \equiv Q_x(n-1)$$

$$\begin{aligned} C_s V_x(n) + C_i [V_x(n) - V_{out}(n)] &= \\ &= -C_s V_{in}(n-1) + C_i [V_x(n-1) - V_{out}(n-1)] \end{aligned}$$

$$V_x \doteq -\frac{V_{out}}{G}$$
  
$$\begin{aligned} +C_s \frac{V_{out}(n)}{G} + C_i \left(1 + \frac{1}{G}\right) V_{out}(n) &= \\ &= +C_s V_{in}(n-1) + C_i \left(1 + \frac{1}{G}\right) V_{out}(n-1) \end{aligned}$$



integration leakage

gain mismatch

$$k \doteq \frac{C_s}{C_i}$$

$$V_{out}(n) = \frac{V_{out}(n-1)}{1 + \frac{k}{1+G}} + \frac{k V_{in}(n-1)}{1 + \frac{1}{G}(k+1)}$$

▼ **Signal dependent** gain generates output **distortion**

$$G \rightarrow \infty$$


$$V_{out}(n) = V_{out}(n-1) + k V_{in}(n-1)$$

# OpAmp Slew-Rate and GBW
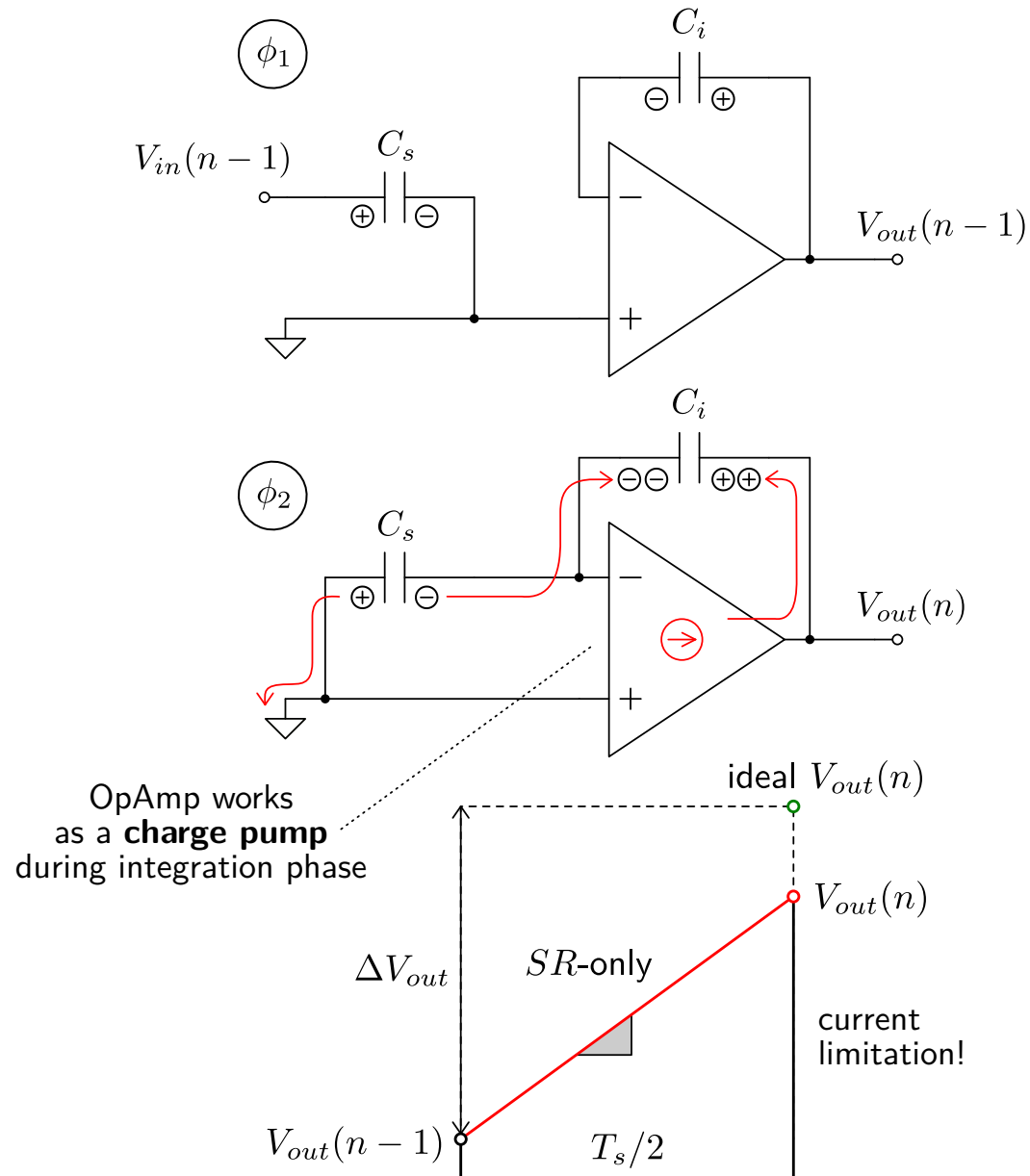
## ► Qualitative case studies:

- if  $SR < \frac{\Delta V_{out}}{T_s/2}$  : **slewing** only

$$V_{out}(n) = V_{out}(n-1) \pm SR \frac{T_s}{2}$$



# OpAmp Slew-Rate and GBW


## ► Qualitative case studies:

- if  $SR < \frac{\Delta V_{out}}{T_s/2}$  : **slewing** only

$$V_{out}(n) = V_{out}(n-1) \pm SR \frac{T_s}{2}$$

- if  $\left| \frac{\Delta V_{out}}{\tau} \right| < SR$  : **settling** only
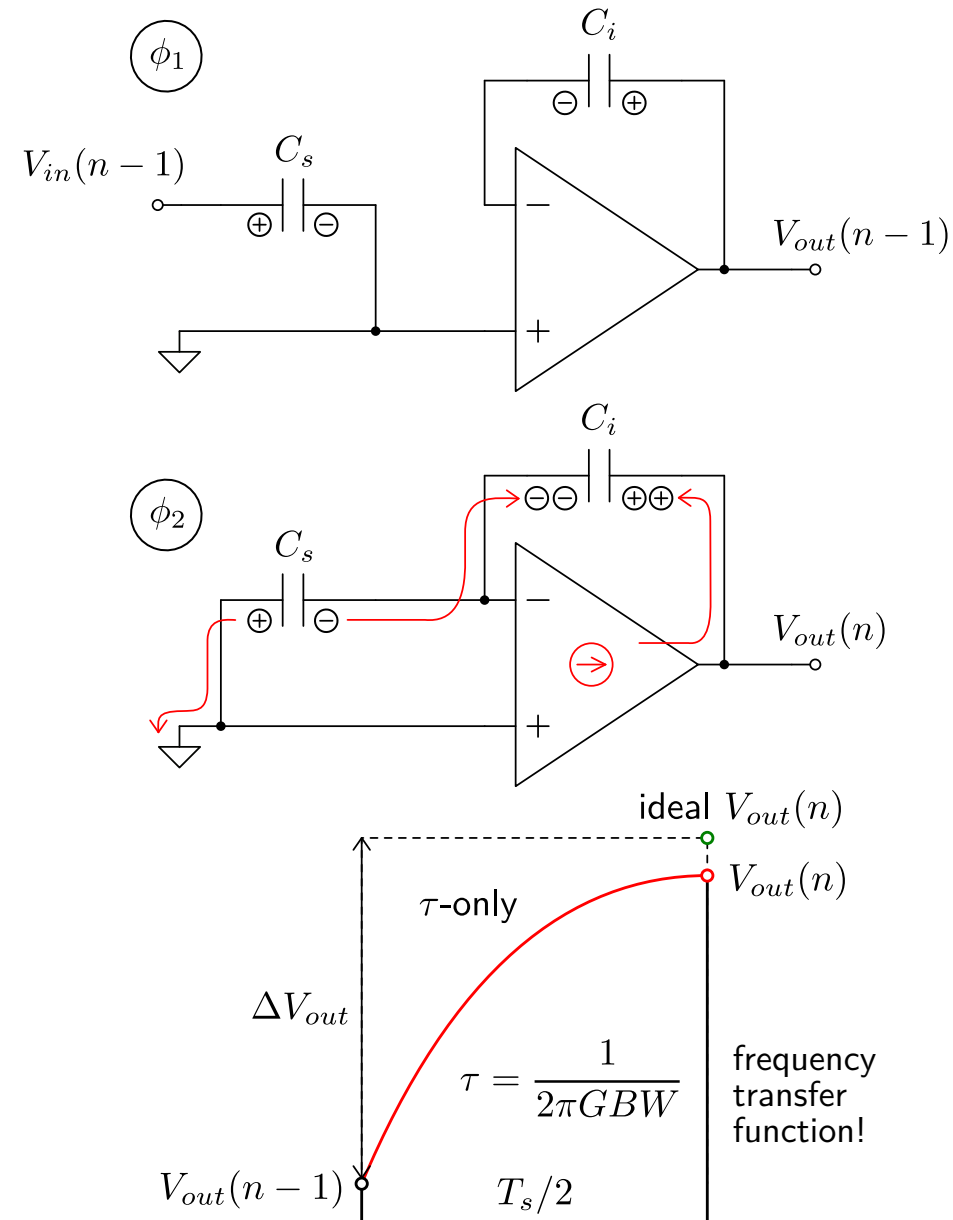
$$V_{out}(n) = V_{out}(n-1) + \Delta V_{out} \left( 1 - e^{-\frac{T_s}{2\tau}} \right)$$





# OpAmp Slew-Rate and GBW

## ► Qualitative case studies:

- if  $SR < \frac{\Delta V_{out}}{T_s/2}$  : **slewing** only

$$V_{out}(n) = V_{out}(n-1) \pm SR \frac{T_s}{2}$$


- if  $\left| \frac{\Delta V_{out}}{\tau} \right| < SR$  : **settling** only

$$V_{out}(n) = V_{out}(n-1) + \Delta V_{out} \left( 1 - e^{-\frac{T_s}{2\tau}} \right)$$

- else : **slewing+settling**


$$V_{out}(n) = V_{out}(n-1) + \Delta V_{out} - SR\tau e^{-\left(\frac{T_s}{2\tau} - \frac{\Delta V_{out}}{\tau SR} + 1\right)}$$
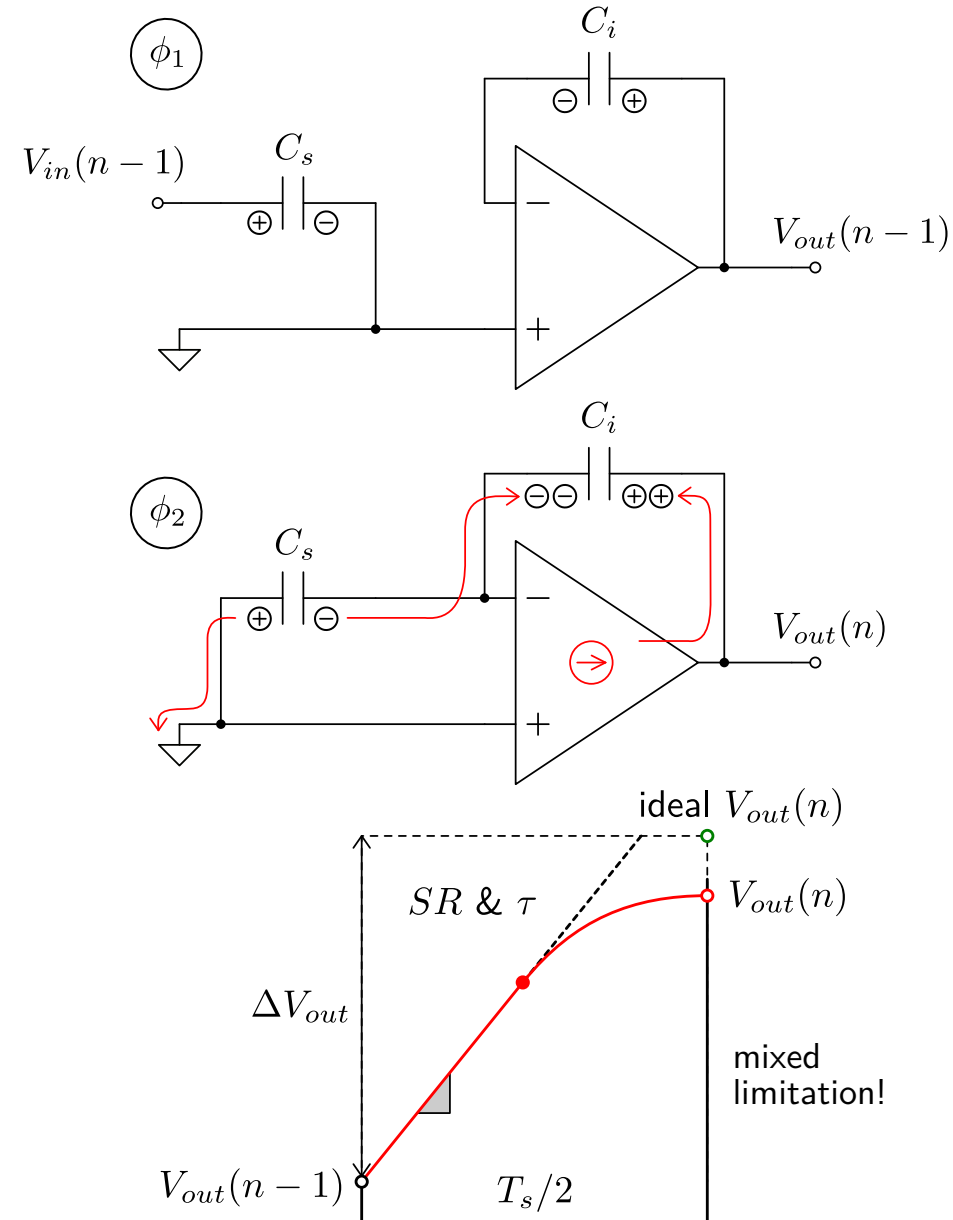
## ▼ Non-linear errors = signal distortion


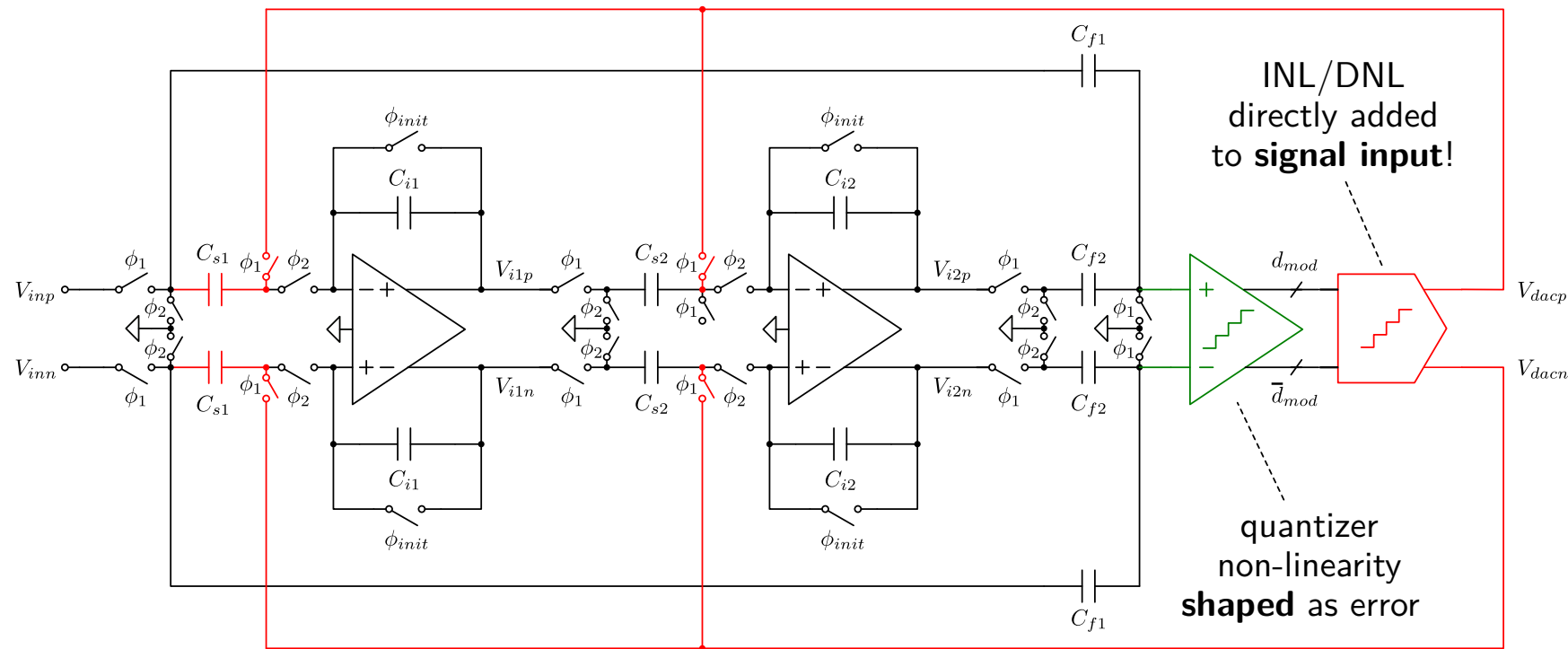
## Feedback DAC Non-Linearity

- Only for **multi-bit** DSM architectures:




▼ How to get rid of feedback **flash DAC** non-linearity effects?

- 1 Oversampling and Noise Shaping Principles
- 2 Architecture Selection Based on Quantization Error
- 3 Switched-Capacitor CMOS Implementations
- 4 Modeling Circuit Second Order Effects
- 5 Digitally Assisted Techniques
- 6 Low-Power Circuit Topologies

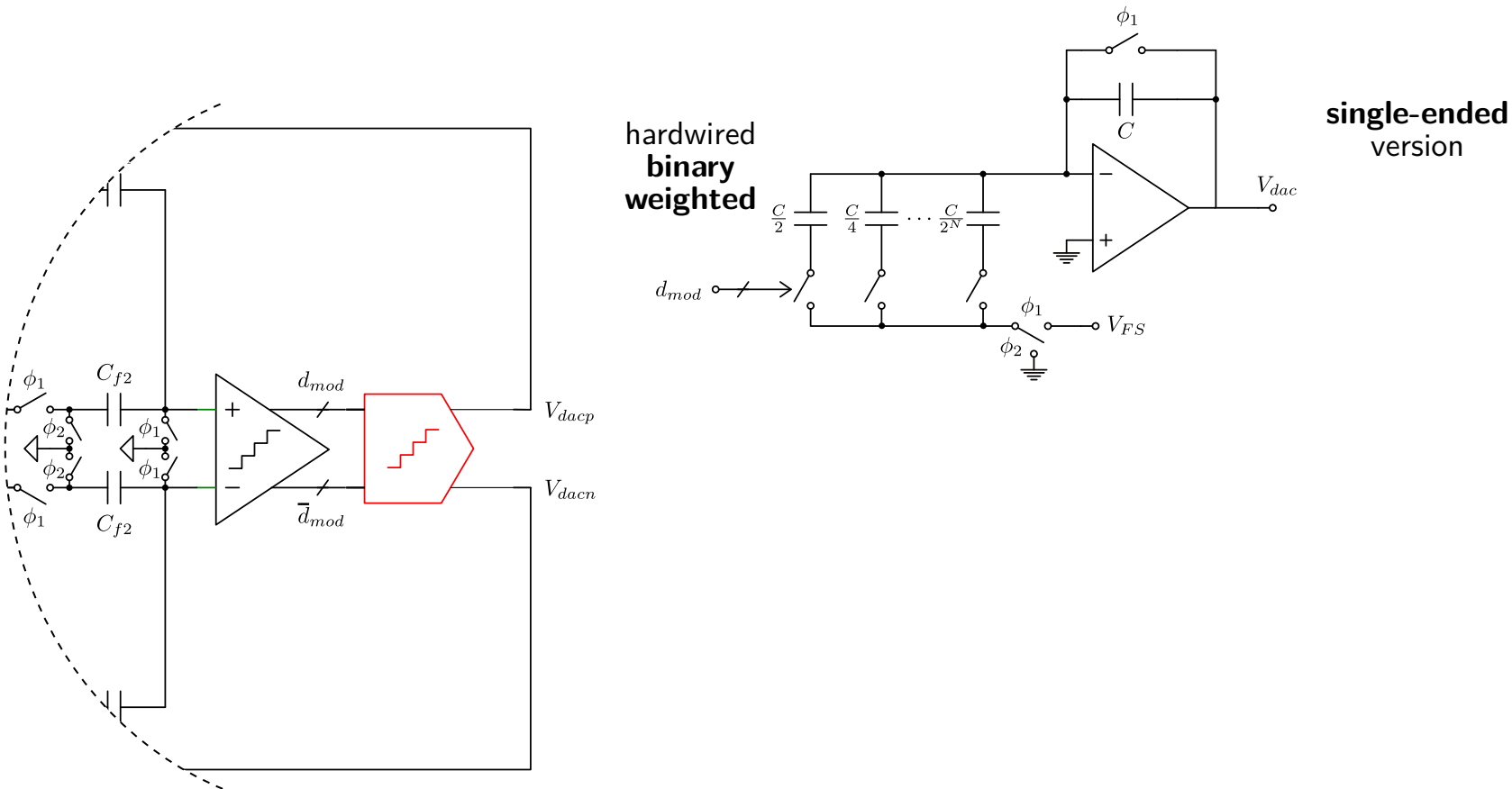
# Feedback DAC Mismatching

- Single-stage **multi-bit SC flash** architecture example:


 
# Feedback DAC Mismatching


► Single-stage **multi-bit SC flash** architecture example:



▲ Simple digital control
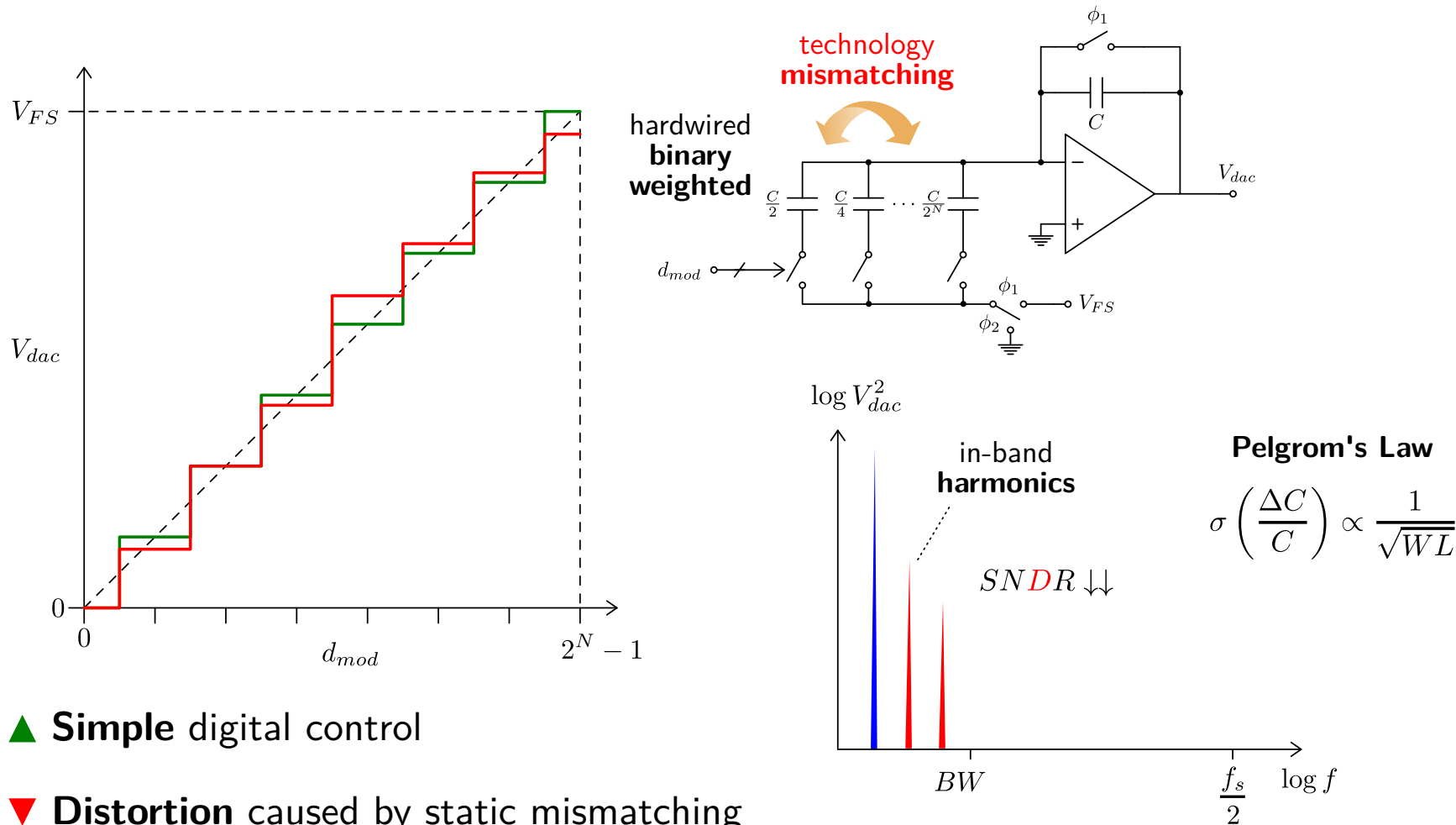
# Feedback DAC Mismatching

► Single-stage **multi-bit SC flash** architecture example:




▲ Simple digital control

▼ Distortion caused by static mismatching
 
# Feedback DAC Mismatching

► Single-stage **multi-bit SC flash** architecture example:




▼ **Complex digital control**

▲ **Low in-band noise by thermometric scrambling**
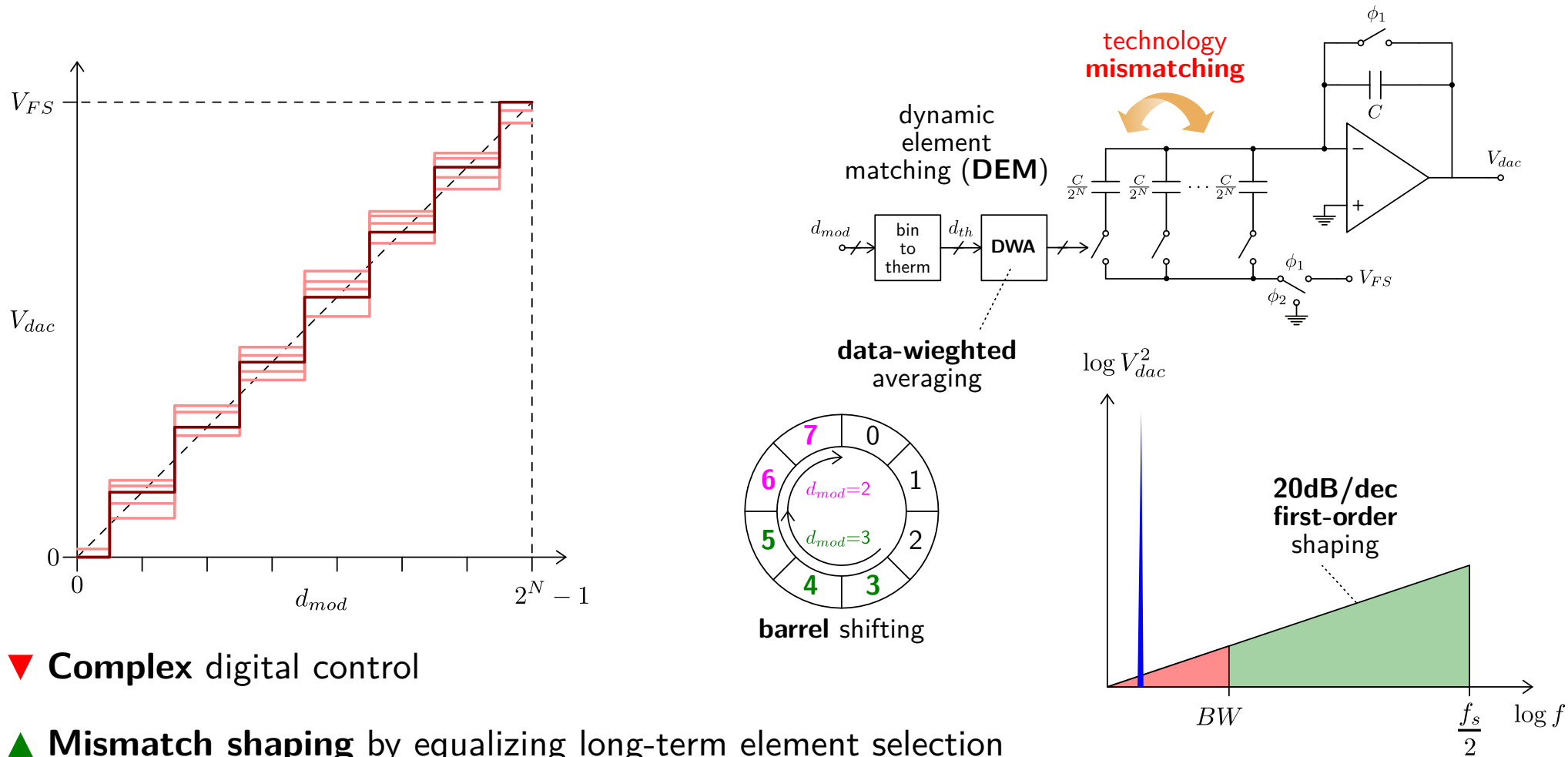
# Feedback DAC Mismatching

- Single-stage **multi-bit SC flash** architecture example:



▼ **Complex** digital control


▲ **Mismatch shaping** by equalizing long-term element selection



- 1 Oversampling and Noise Shaping Principles
- 2 Architecture Selection Based on Quantization Error
- 3 Switched-Capacitor CMOS Implementations
- 4 Modeling Circuit Second Order Effects
- 5 Digitally Assisted Techniques
- 6 Low-Power Circuit Topologies
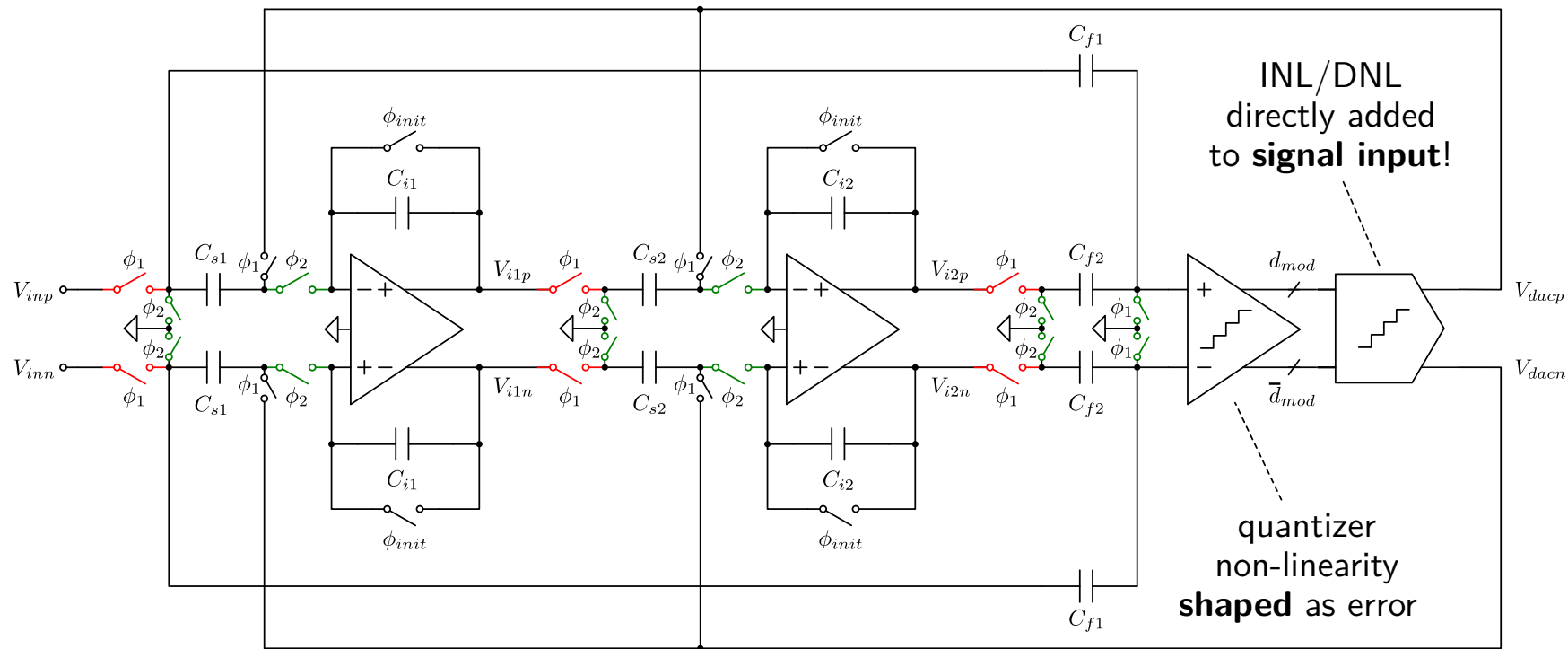
## Switched OpAmp (SOA)



- **Distortion** caused by signal-dependent switch on-resistance:



- ▼ How to make **on-resistance independent from signal** for these particular switches?
 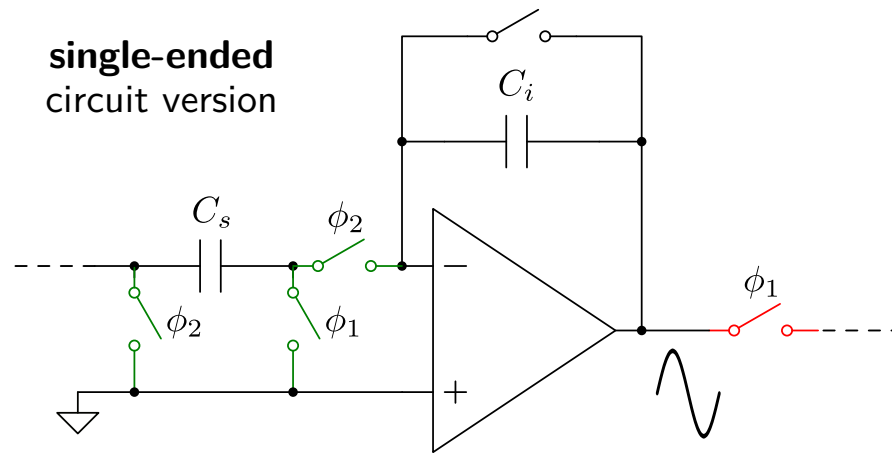
# Switched OpAmp (SOA)

- Moving output switches into **OpAmp** blocks:



# Switched OpAmp (SOA)


- Moving output switches into **OpAmp** blocks:

► J. Crols and M. Steyaert

*Switched-OpAmp: An Approach to Realize Full CMOS Switched-Capacitor Circuits at Very Low Power Supply Voltages*

IEEE Journal of Solid-State Circuits 29(8):936–942, Aug 1994

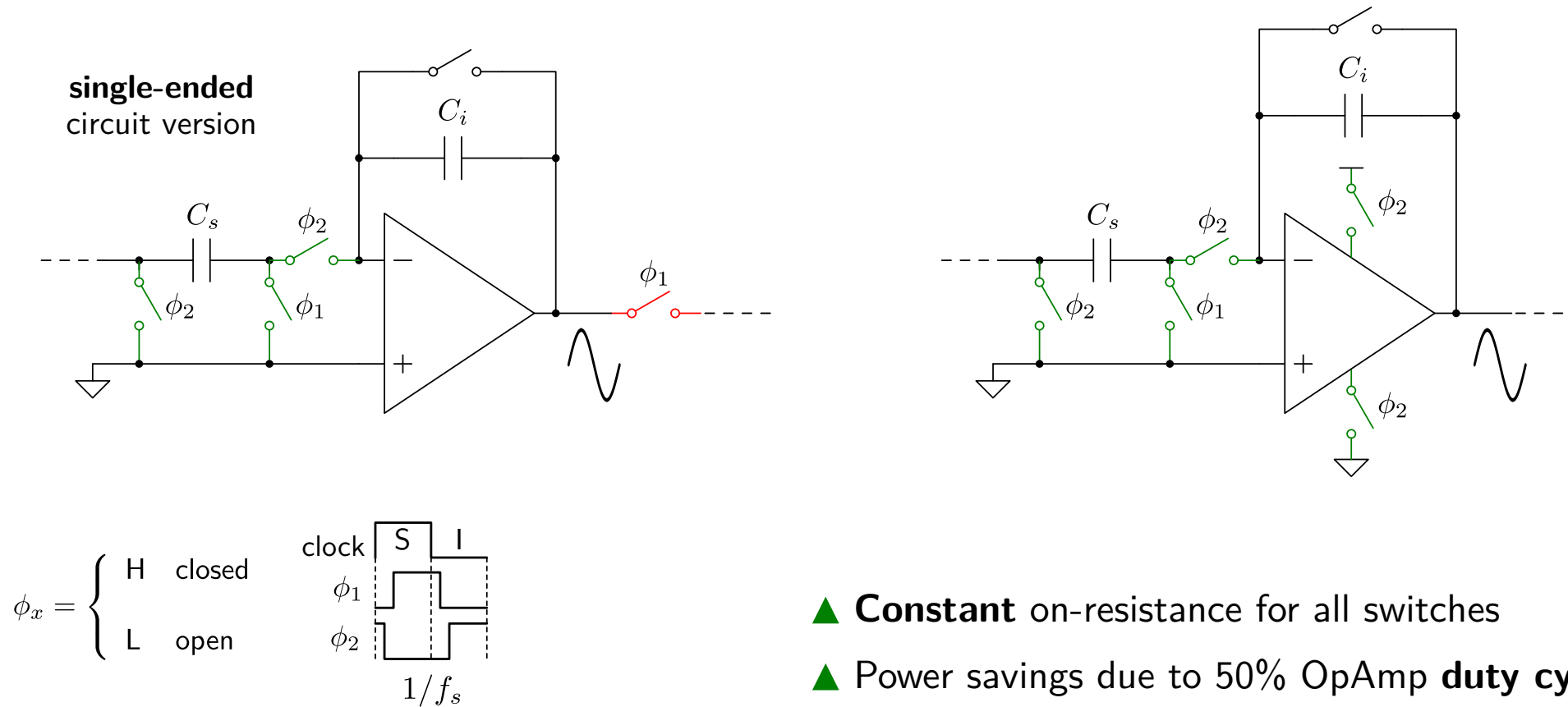
[doi.org/10.1109/4.297698](https://doi.org/10.1109/4.297698)



- ▲ **Constant** on-resistance for all switches
- ▲ Power savings due to 50% OpAmp **duty cycle**
- ▼ Each integrator stage operates in **alternative phases**
 
# Switched OpAmp (SOA)

- Moving output switches into **OpAmp** blocks:




**Example:** single-ended single-stage folded OpAmp

► J. Crols and M. Steyaert

*Switched-OpAmp: An Approach to Realize Full CMOS Switched-Capacitor Circuits at Very Low Power Supply Voltages*

IEEE Journal of Solid-State Circuits 29(8):936–942, Aug 1994




 
[doi.org/10.1109/4.297698](https://doi.org/10.1109/4.297698)



- ▲ **Constant** on-resistance for all switches
- ▲ Power savings due to 50% OpAmp **duty cycle**
- ▼ Each integrator stage operates in **alternative phases**

# OpAmp Dynamic Biasing






## ► Discrete time dynamic biasing:

   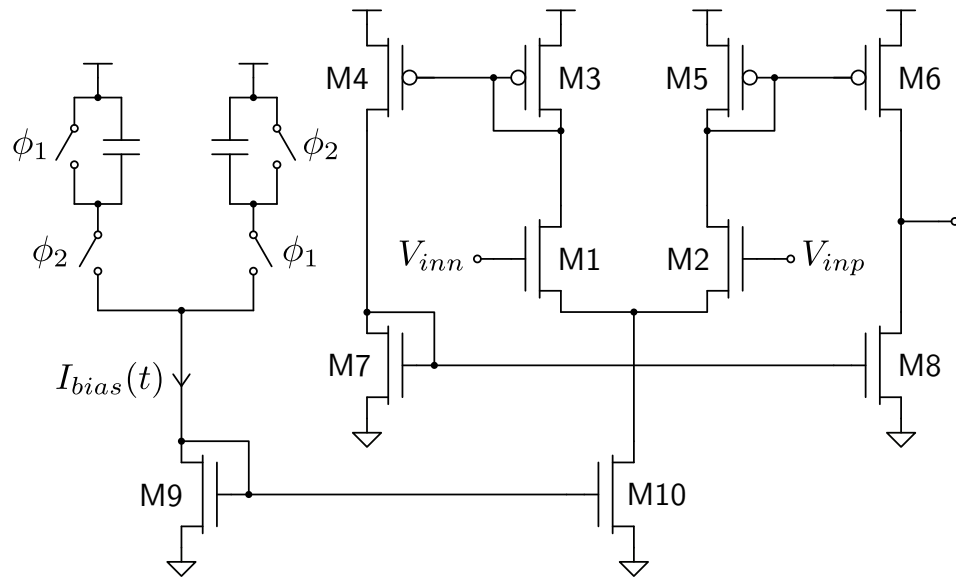

► B. J. Hosticka  
*Dynamic CMOS amplifiers*  
 IEEE Journal of Solid-State Circuits 15(5):881–886, Oct 1980  
[doi.org/10.1109/JSSC.1980.1051488](https://doi.org/10.1109/JSSC.1980.1051488)

# OpAmp Dynamic Biasing

## ► Discrete time dynamic biasing:

    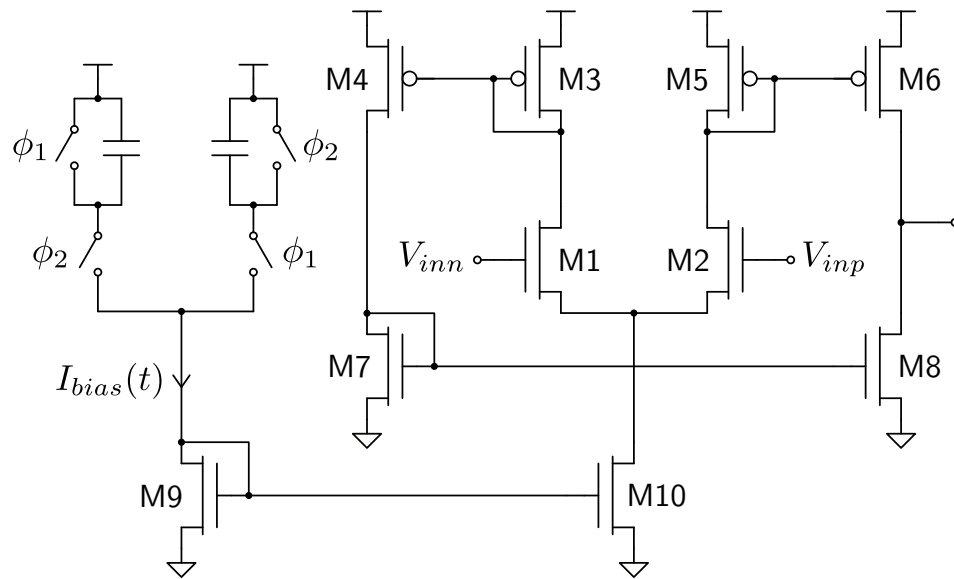

$$\phi_x = \begin{cases} \text{H} & \text{closed} \\ \text{L} & \text{open} \end{cases}$$

▲ Synchronous **Class-AB** operation

▲ Static **power** savings

▼ OpAmp fast on/off **recovery** time required

▼ Biasing **peak** value is technology dependent

▼ **Ripple** induced in the power rails (digital-like)

► B. J. Hosticka  
*Dynamic CMOS amplifiers*  
 IEEE Journal of Solid-State Circuits 15(5):881–886, Oct 1980  
[doi.org/10.1109/JSSC.1980.1051488](https://doi.org/10.1109/JSSC.1980.1051488)