

7. Application Specific ROICs for Smart Sensors

Francesc Serra Graells

francesc.serra.graells@uab.cat

Departament de Microelectrònica i Sistemes Electrònics
Universitat Autònoma de Barcelona

paco.serra@imb-cnm.csic.es

Integrated Circuits and Systems
IMB-CNM(CSIC)


- 1 High-Resolution SC Delta-Sigma ADC
for Space Applications
- 2 Compact Pixel Integrating ADC
for X-Ray Imagers
- 3 Low-Power Potentiostatic CT Delta-Sigma ADC
for Electrochemical Integrated Sensors

- 1 High-Resolution SC Delta-Sigma ADC
for Space Applications
- 2 Compact Pixel Integrating ADC
for X-Ray Imagers
- 3 Low-Power Potentiostatic CT Delta-Sigma ADC
for Electrochemical Integrated Sensors

ESA Cosmic Vision JUICE




- ▶ **Cosmic Vision** is ESA 2015-2025 planning for space science missions
- ▶ **Jupiter Icy Moons Explorer (JUICE)**
L-class mission launched in 2023
(7.6y cruise & 3.5y in the Jovian system)
- ▶ Primary mission themes:
 - Emergence of **habitable worlds** around gas giants
 - **Jupiter** system as an archetype for gas giants
- ▶ Science instrument payload:
 - **JANUS** - Optical camera system
 - **MAJIS** - Moons and Jupiter Imaging Spectrometer
 - **GALA** - GAnymede Laser Altimeter
 - **RIME** - Radar for Icy Moons Exploration
 - **J-MAG** - A magnetometer for JUICE
 - **RPWI** - Radio & Plasma Wave Investigation
 - **PRIDE** - Planetary Radio Interferometer & Doppler Experiment
 - ...

 


➤ sci.esa.int/web/juice

 ▼ Next generation of **read-out electronics** is needed!



Low-Power High-Res ADC

► Low-voltage vs **low-current** design?

 


$$P_{DD} = V_{DD} \times I_{DD}$$



- Alternative supply **sources**
(battery, solar cell, scavenging)
- **Poor** power scaling
- Limited by **technology**
- **Circuit techniques**: rail-to-rail, inverter-base, supply multipliers, back gate...
- **Strong** power savings
- Limited by **noise** and **bandwidth**
- **Circuit techniques**: subthreshold operation, Class-AB, dynamic biasing, low duty cycle...

Low-Power High-Res ADC

► Low-voltage vs **low-current** design?

 

$$P_{DD} = V_{DD} \times I_{DD}$$



- Alternative supply **sources** (battery, solar cell, scavenging)
- **Poor** power scaling
- Limited by **technology**
- **Circuit techniques**: rail-to-rail, inverter-base, supply multipliers, back gate...
- **Strong** power savings
- Limited by **noise** and **bandwidth**
- **Circuit techniques**: subthreshold operation, Class-AB, dynamic biasing, low duty cycle...


► State-of-art **extended-DR** SC circuits for DSM ADCs [1-6]:

- **Clock bootstrapping** to reduce switch non-linearity [3-5]
- **High-voltage devices** at input sampler to increase signal full scale [1,6]
- **Multi-bit quantization** with analog calibration or digital post-processing due to mismatching [6]

► **Rad-Hard** 1.8V 0.18μm 1P6M CMOS technology

DSM Architecture

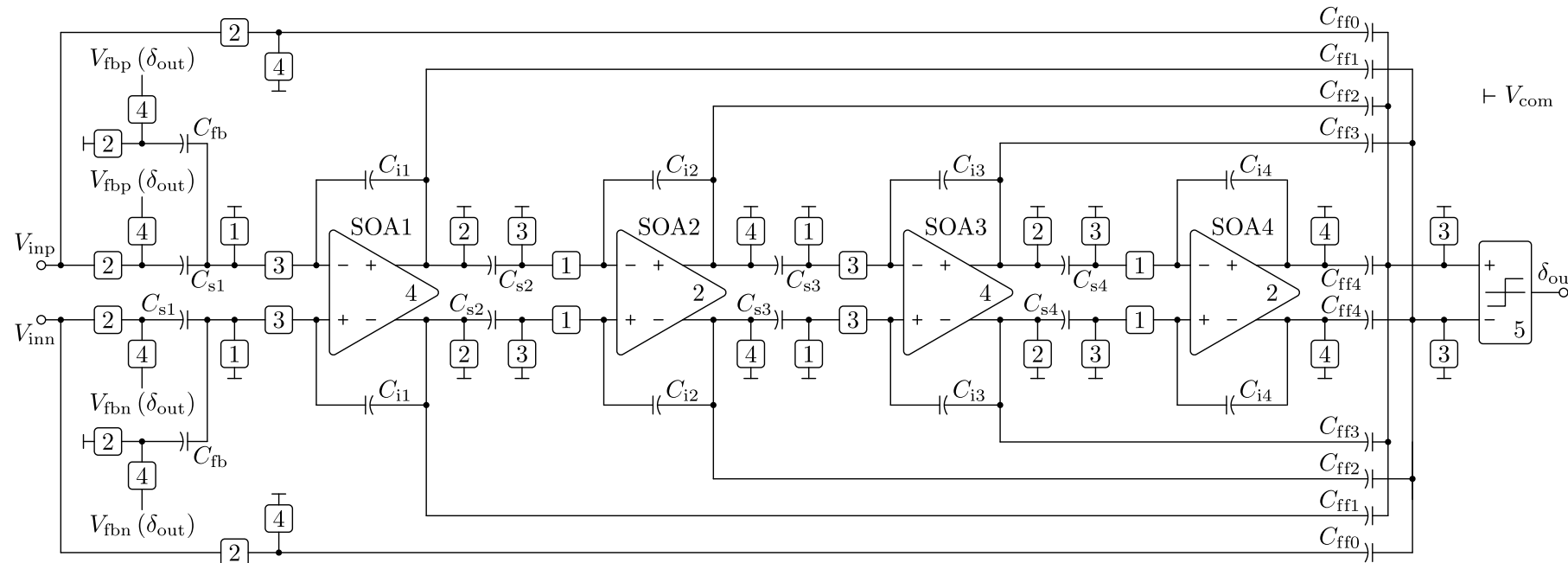
- **4th-order** single-loop 1-bit topology for **>90dB-SNDR** and **50kHz-bandwidth**:



- ▲ **Multiple feedforward paths** to relax signal headroom at OpAmps output [7]
- ▲ **Two-level quantization** is intrinsically linear and allows passive adder [5]
- ▲ High shaping order to compensate **oversampling**: $OSR = 136$ $f_s = 13.6\text{MS/s}$

DSM Architecture

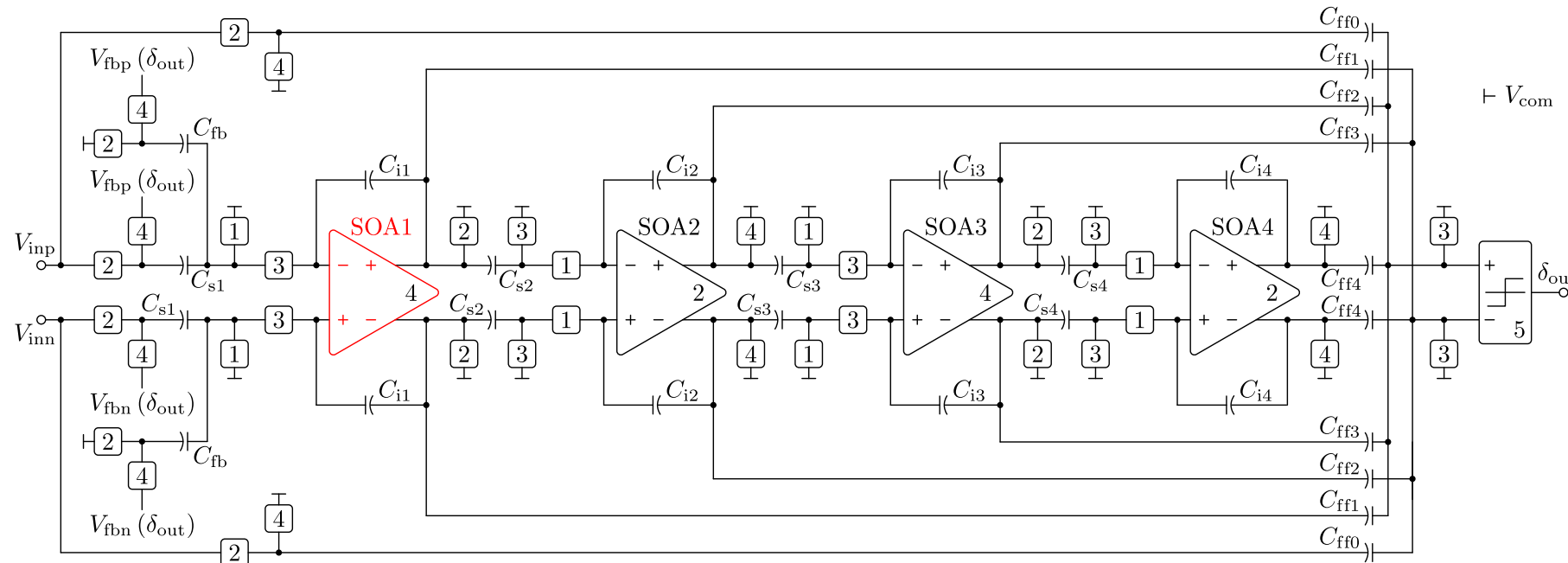- **4th-order** single-loop 1-bit topology for **>90dB-SNDR** and **50kHz-bandwidth**:




- ▼ **Large capacitor sizing** [pF]
according to kT/C specs
and optimal coefficients [8]:

Capacitance	Value	Capacitance	Value	Capacitance	Value
C_{ff0}	0.92	C_{fb}	21.16		
C_{ff1}	0.92	C_{s1}	42.32	C_{i1}	211.6
C_{ff2}	0.92	C_{s2}	3.68	C_{i2}	9.2
C_{ff3}	0.92	C_{s3}	0.92	C_{i3}	9.2
C_{ff4}	1.84	C_{s4}	0.92	C_{i4}	9.2

DSM Architecture


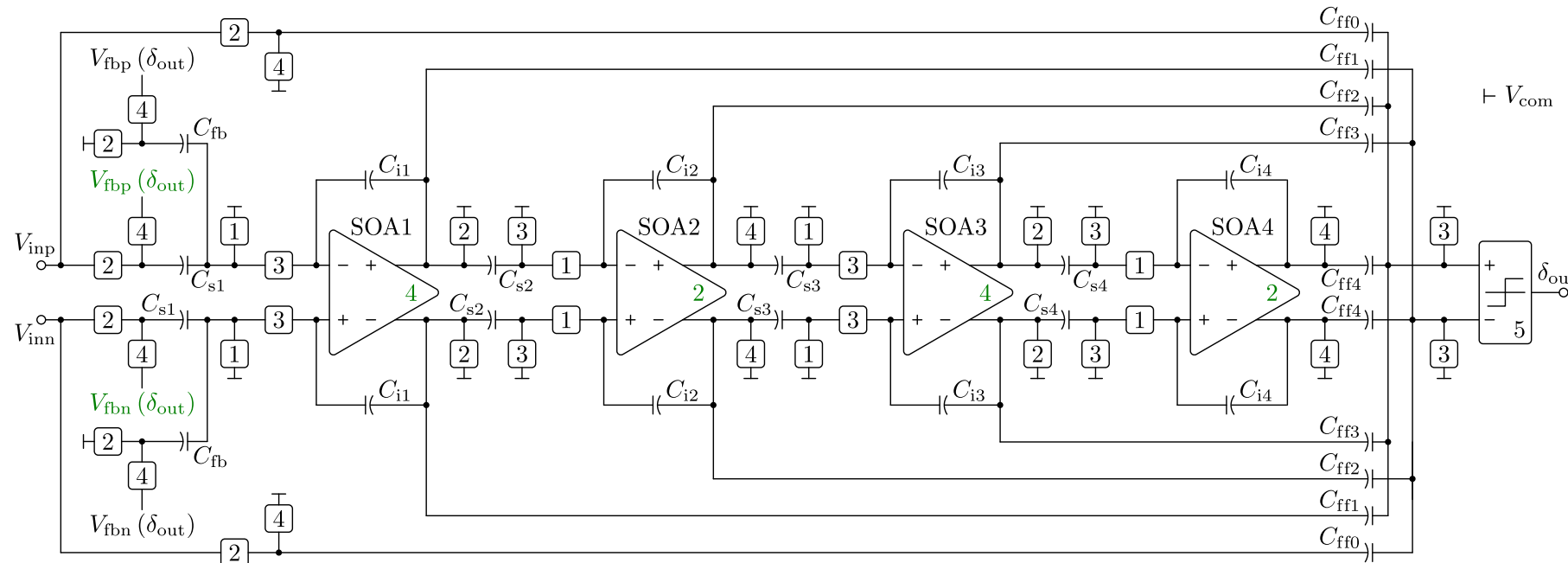
- **4th-order** single-loop 1-bit topology for **>90dB-SNDR** and **50kHz-bandwidth**:



- ▲ Feedback DAC **shares** capacitor with input sampler to reduce overall area
- ▲ **Switched-OpAmp** (SOA) for replacing critical switches and 50% duty cycle [9]

DSM Architecture

 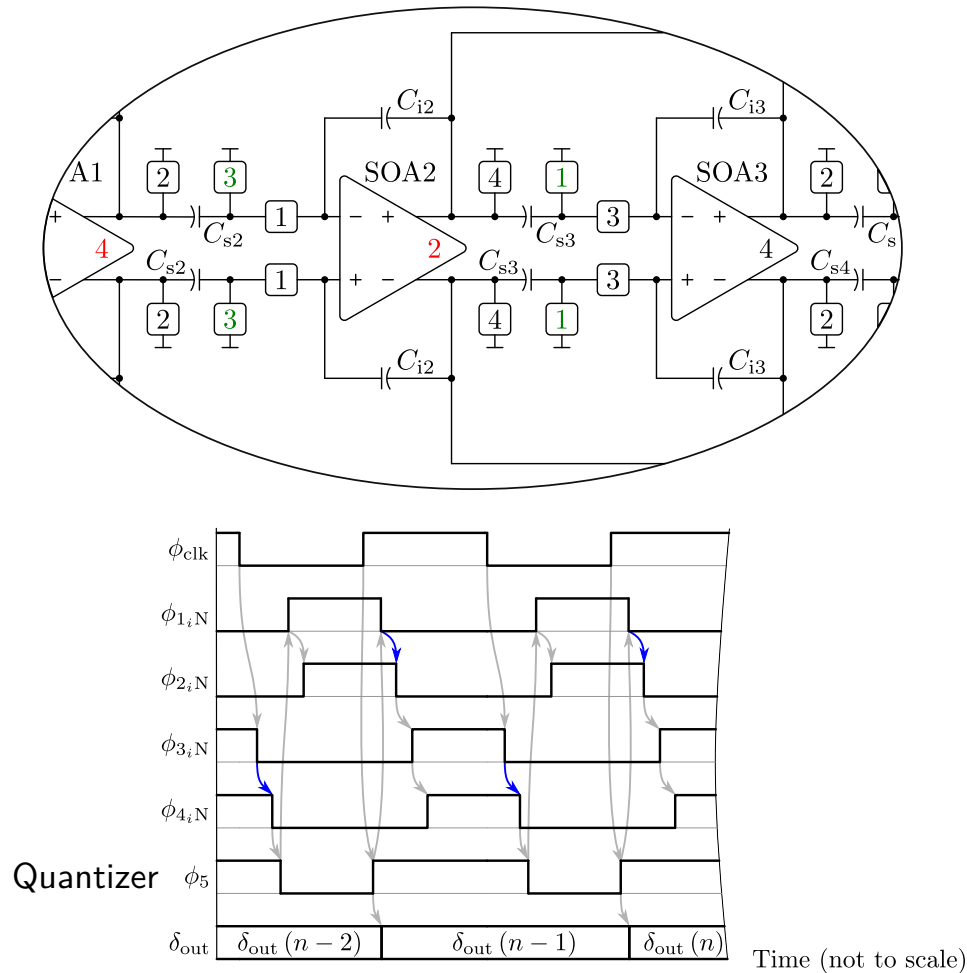
- **4th-order** single-loop 1-bit topology for **>90dB-SNDR** and **50kHz-bandwidth**:



- ▲ **(4+1)-phase** switching scheme to avoid signal-dependent charge injections that would cause distortion [8]



Switched-OpAmp Circuit

 - ▶ Low-power **Class-AB** single-stage design
- ▶ Complementary non-linear current mirrors with **partial positive** feedback
- ▲ Class-AB current in output transistors **only**
- ▲ No-need for Miller **compensation** capacitor
- ▲ Fast switched-OpAmp **on/off-power** operation





Switched-OpAmp Circuit

 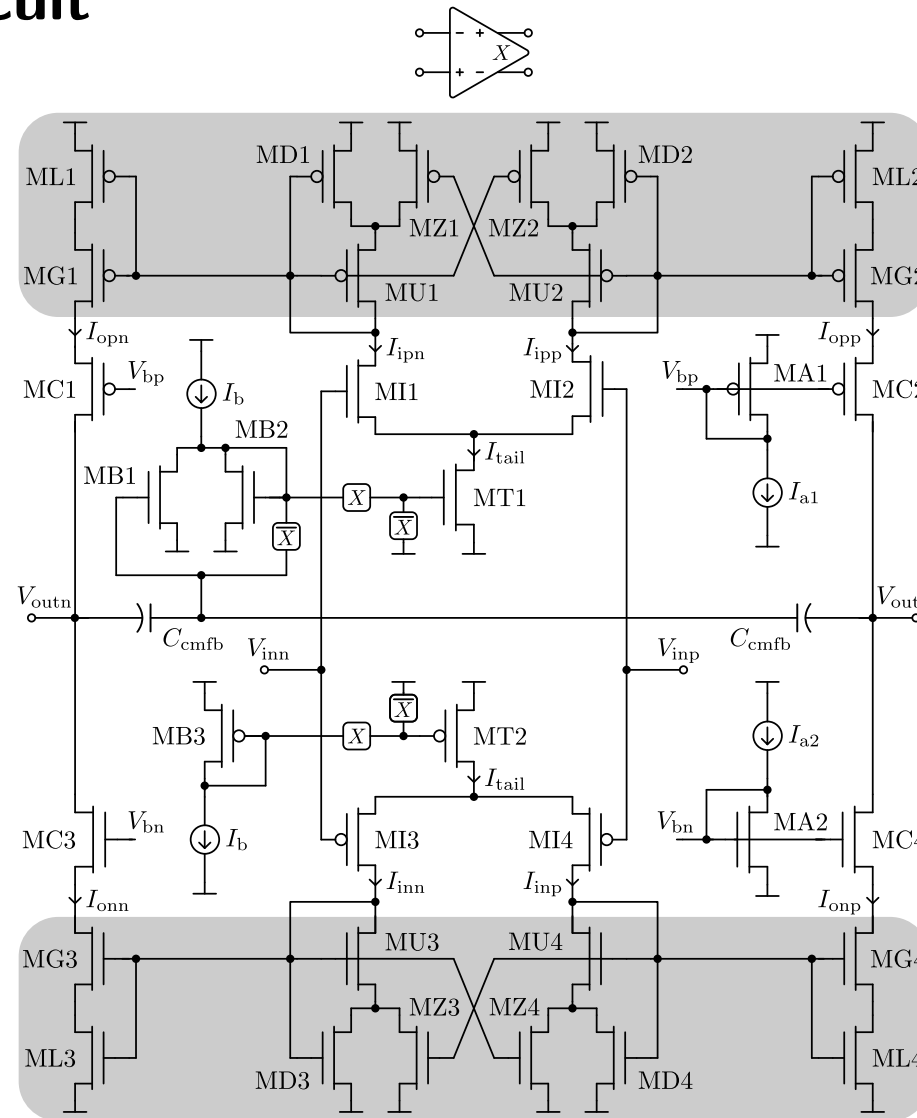- ▶ Low-power **Class-AB** single-stage design
- ▶ Complementary non-linear current mirrors with **partial positive feedback**
- ▲ Class-AB current in output transistors **only**
- ▲ No-need for Miller **compensation** capacitor
- ▲ Fast switched-OpAmp **on/off-power** operation
- ▲ Simple analytic design based on **matching ratios**




Switched-OpAmp Circuit

  - ▶ Low-power **Class-AB** single-stage design
- ▶ Complementary non-linear current mirrors with **partial positive feedback**
- ▲ Class-AB current in output transistors **only**
- ▲ No-need for Miller **compensation** capacitor
- ▲ Fast switched-OpAmp **on/off-power** operation
- ▲ Simple analytic design based on **matching ratios**
- ▲ **Low sensitivity** to CMOS technology deviations




DSM CMOS Integration

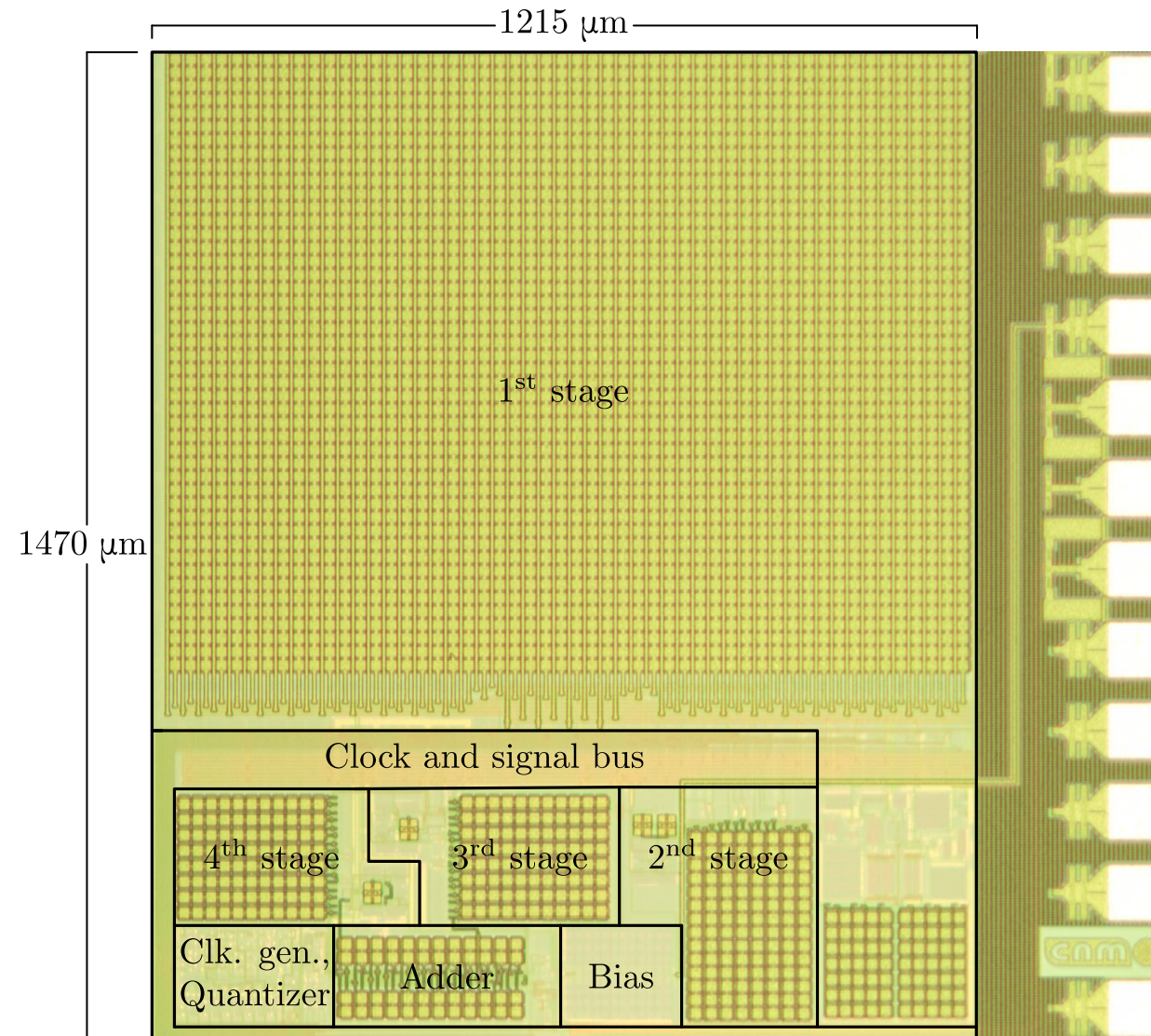- ▶ **Rad-Hard** 1.8V 0.18 μm 1P6M CMOS technology
- ▶ Metal-insulator-metal (**MIM**) capacitors
- ▶ **1.8mm²** overall area




Experimental Results

 - ▶ Power spectral density at **-2dB** full scale



Experimental Results

 - ▶ Power spectral density at **-2dB** full scale
- ▲ **$\text{SNDR}_{\text{max}}=96.6\text{dB}$** ,
 $\text{SFDR}_{\text{max}}=105.3\text{dB}$,
and **$\text{DR}=97\text{dB}$**
at 13.28kHz
- ▲ **2.4V_{pp}** input full-scale
- ▲ **7.9mW** at 1.8V
- ▲ **Non-bootstrapped** supply
to avoid device stress
- ▲ **Calibration-free** operation
to increase ADC robustness



Comparison with High-Res ADCs

► Schreier **FOM** comparison:

$$FOM_S[\text{dB}] \doteq SNDR[\text{dB}] + 10 \log(BW/P)$$

	[1]	[2]	[3]	[4]	[5]	[6]	This work	
Architecture	$\Delta\Sigma$ SC	$\Delta\Sigma$ CT+SC	$\Delta\Sigma$ SC	$\Delta\Sigma$ SC	$\Delta\Sigma$ SC	Pipe+ SAR	$\Delta\Sigma$ SC	
Technology	0.25	0.18	0.18	0.18	0.35	0.18	0.18	μm
Supply voltage		3.3	1.8	0.7	1.5	5, 1.8	1.8	V
Diff. full scale	6.6	5.7				10	2.4	V_{pp}
Sampling rate	20	6.14	45.2	5	2.4	5	13.6	MS/s
Bandwidth	1000	20	500	25	20	2500	50	kHz
Supply power	475	37	38	0.87	0.14	30.5	7.9	mW
Area	20.2	0.65	3.5	2.16	0.21	5.74	1.8	mm^2
DR	103	102	90.1	100	92.6	100.2	97	dB
SFDR _{max}			97				105.3	dB
SNDR _{max}		95	86.3	95	87.9	98.6	96.6	dB
FOM	(166.2)	152.3	157.5	169.6	169.5	177.7	164.6	dB
Bootstrap-free	Yes	Yes	No	No	No	Yes	Yes	
Calibration-free	Yes	Yes	Yes	Yes	Yes	No	Yes	

► S. Sutula, et al.

A Calibration-Free 96.6-dB-SNDR Non-Bootstrapped 1.8-V 7.9-mW Delta-Sigma Modulator with Class-AB Single-Stage Switched VMAs

IEEE International Symposium on Circuits and Systems (ISCAS), Montreal, Canada, May 2016

doi.org/10.1109/ISCAS.2016.7527170


References

- [1] R. Brewer, J. Gorbald, P. Hurrell, C. Lyden, R. Maurino, and M. Vickery, "A 100dB SNR 2.5MS/s Output Data Rate $\Delta\Sigma$ ADC," in Proceedings of the IEEE International Solid-State Circuits Conference, 2005, pp. 172–173.
- [2] P. Morrow, M. Chamarro, C. Lyden, P. Ventura, A. Abo, A. Matamura, M. Keane, R. O'Brien, P. Minogue, J. Mansson, N. McGuinness, M. McGranaghan, and I. Ryan, "A 0.18 μm 102dB-SNR Mixed CT SC Audio-Band $\Delta\Sigma$ ADC," in Proceedings of the IEEE International Solid-State Circuits Conference, 2005, pp. 178–592.
- [3] A. Agah, K. Vleugels, P. Griffin, M. Ronaghi, J. Plummer, and B. Wooley, "A High-Resolution Low-Power Oversampling ADC with Extended-Range for Bio-Sensor Arrays," in Symposium on VLSI Circuits Digest of Technical Papers, 2007, pp. 244–245.
- [4] H. Park, K. Nam, D. K. Su, K. Vleugels, and B. A. Wooley, "A 0.7-V 100-dB 870- μW Digital Audio $\Delta\Sigma$ Modulator," in Symposium on VLSI Circuits Digest of Technical Papers, 2008, pp. 178–179.
- [5] T. Christen, "A 15bit 140 μW Scalable-Bandwidth Inverter-Based Audio $\Delta\Sigma$ Modulator with >78dB PSRR," in Proceedings of the European Solid-State Circuits Conference, 2012, pp. 209–212.
- [6] A. Bannon, C. Hurrell, D. Hummerston, and C. Lyden, "An 18 b 5 MS/s SAR ADC with 100.2 dB Dynamic Range," in Symposium on VLSI Circuits Digest of Technical Papers, 2014, pp. 1–2.
- [7] J. Silva, U. Moon, J. Steensgaard, and G. C. Temes, "A wideband low-distortion Delta-Sigma ADC topology," IEEE Electronics Letters, vol. 37, pp. 737–738, 2001.
- [8] L. Yao, M. Steyaert, and W. Sansen, "A 1-V, 1-MSs, 88-dB Sigma-Delta Modulator in 0.13- μm Digital CMOS Technology," in Symposium on VLSI Circuits Digest of Technical Papers, 2005, pp. 180–183.
- [9] J. Crols and M. Steyaert, "Switched-OpAmp: An Approach to Realize Full CMOS Switched-Capacitor Circuits at Very Low Power Supply Voltages," IEEE J. Solid-State Circuits, vol. 29, no. 8, pp. 936–942, Aug 1994.
- [10] P. Aguirre and F. Silveira, "Bias Circuit Design for Low-Voltage Cascode Transistors," in Proceedings of the 19th Annual Symposium on Integrated Circuits and Systems Design, 2006, pp. 94–97.

- 1 High-Resolution SC Delta-Sigma ADC
for Space Applications
- 2 Compact Pixel Integrating ADC
for X-Ray Imagers
- 3 Low-Power Potentiostatic CT Delta-Sigma ADC
for Electrochemical Integrated Sensors

Direct X-Ray Digital Imagers

 - ▶ Low-energy ($<20\text{keV}$) medical applications: e.g. **Mammography**




- High **dynamic range** (e.g. 10-bit) and high **spatial resolution** (e.g. $50\mu\text{m}$ -pitch) to identify microcalcifications
- **High-speed** A/D conversion for low-dose X-ray exposure
- **Low-power** circuit consumption to prevent heating X-ray detector

Direct X-Ray Digital Imagers




 - ▶ Low-energy (<20keV) medical applications: e.g. **Mammography**



- High **dynamic range** (e.g. 10-bit) and high **spatial resolution** (e.g. 50 μ m-pitch) to identify microcalcifications
- **High-speed** A/D conversion for low-dose X-ray exposure
- **Low-power** circuit consumption to prevent heating X-ray detector


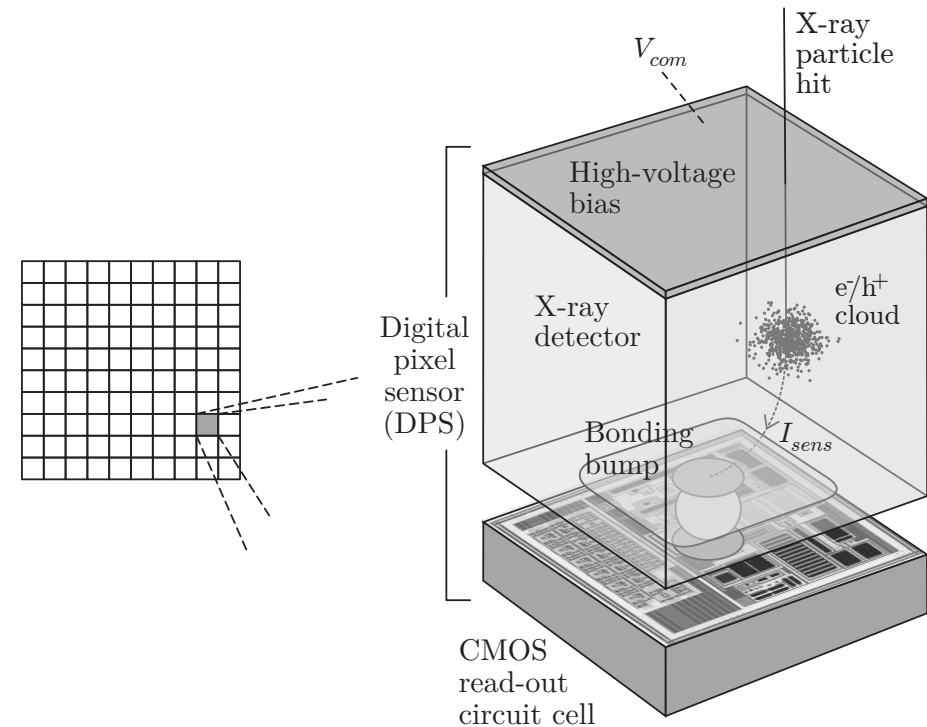
- ▶ **Digital pixel sensor (DPS)** = X-ray detector (e.g. CdTe or Si) + CMOS read-out circuit



- ▶ Pixel-by-pixel **bump-bonding** (bump-growing + flip-chip):

- High **filling** factors
- **Expensive** packaging

Photon Counting vs Charge Integration

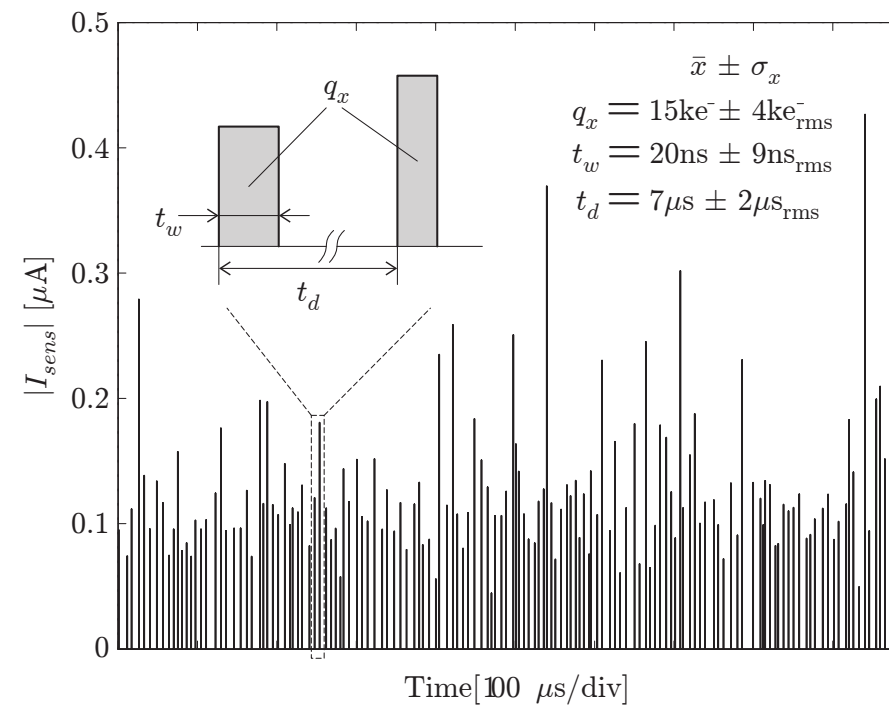 


► Single particle detection:

- Less sensitive to circuit **noise**
- Possibility of photon **classification**
- Transient **pile-up** effects
- **Charge-sharing** between pixels

► Overall charge integration:

- Less sensitive to **pile-up** effects
- **Charge-sharing** can be compensated by digital post-processing
- Circuit **noise** can corrupt data

Proposed DPS Architecture

 

► **Charge integration** method

▲ Self-biasing for **digital-only I/O** and inter-pixel **low crosstalk**

▲ **Linear ADC** for high-flux X-rays


▲ Fixed-pattern noise (**FPN**) cancellation for image equalization

▲ **Built-in test** for pre-packaging screening


▼ All with **reduced pitch** and **low power**

Loss-Less A/D Conversion

 - **Classic** asynchronous integrate-and-fire (IAF) modulator:



 
- ▼ **Saturation** due to event reset time!



e.g. $C_{int}=100\text{fF}$, $V_{th}=200\text{mV}$, $T_{caq}=2\text{ms}$ and 10bit output

Loss-Less A/D Conversion

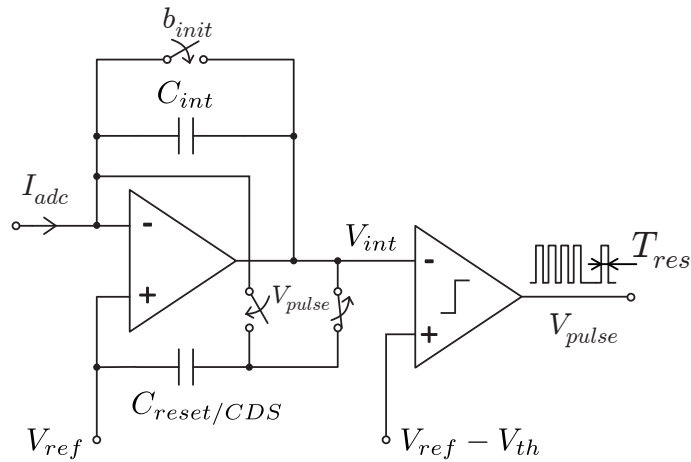
► **Classic** asynchronous integrate-and-fire (IAF) modulator:



▲ Reset-time **independent**


▲ Max f_{pdm} close to $1/T_{res}$

▼ **Double**-capacitor area

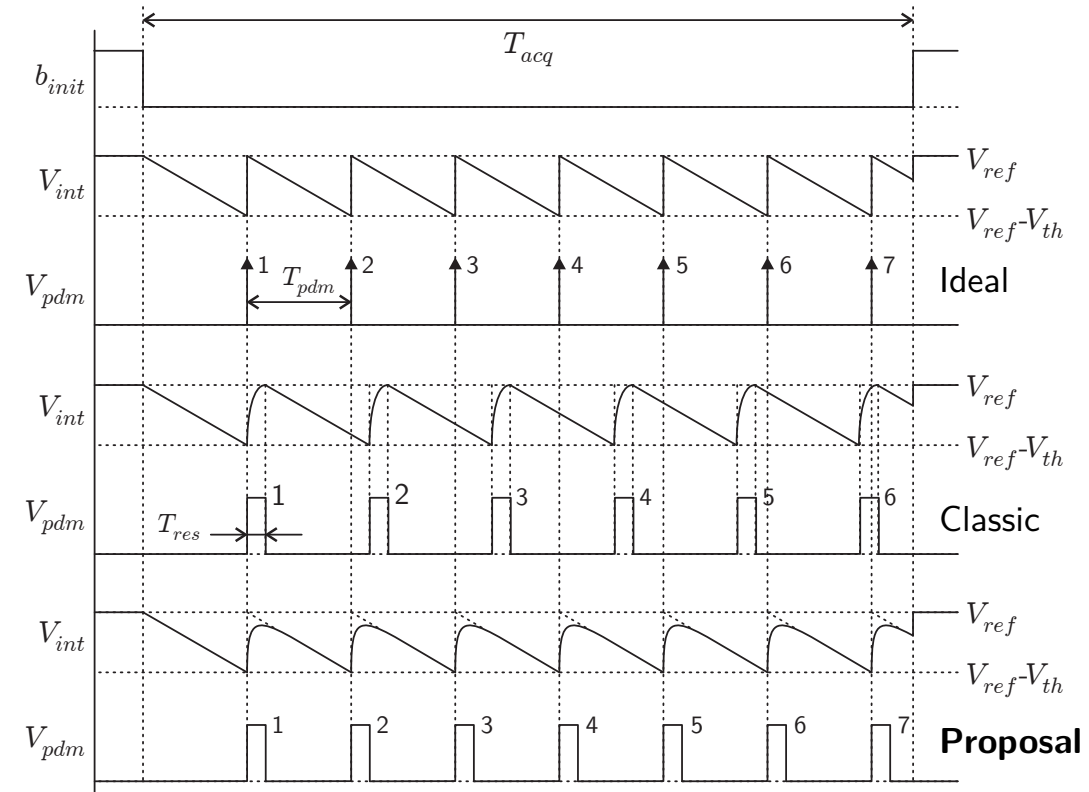


Loss-Less A/D Conversion

 ► **Compact** CMOS circuit implementation:




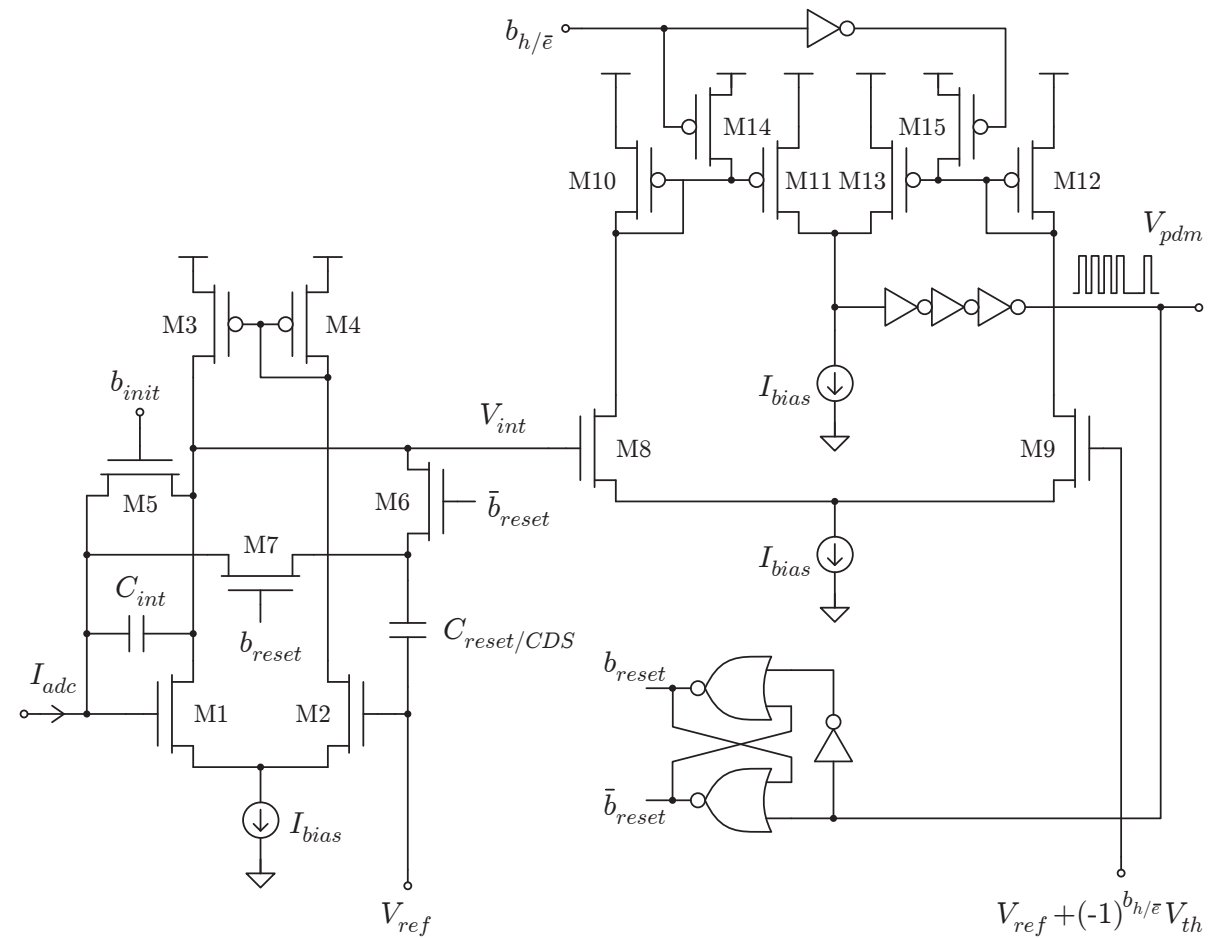▲ **Bidirectional e^-/h^+ charge collection**



Dark-Current Cancellation


► Based on **current-copiers**:

 

▲ **Auto-calibration**

▲ **Coarse + fine** for charge-injection compensation

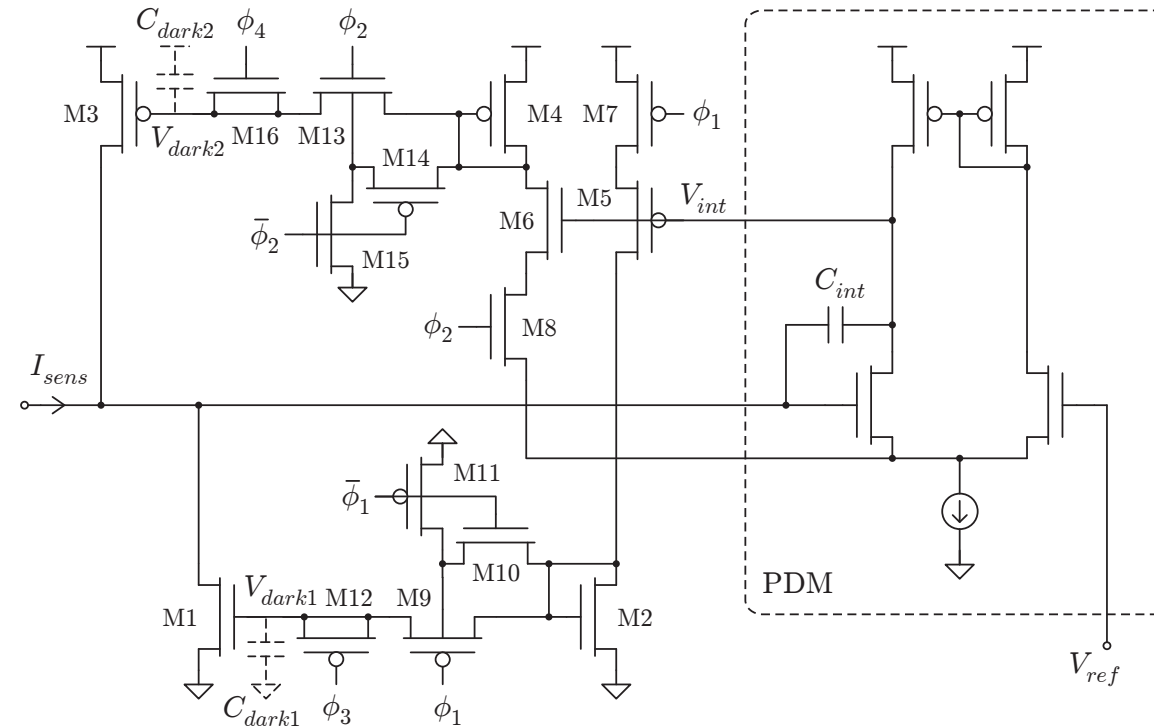
▲ **Reuse of ADC CMOS circuit** for compact area




▲ Composite switches for **long retention** times

Individual-Pixel Gain Programmability

► In-pixel SC DAC circuit:

 

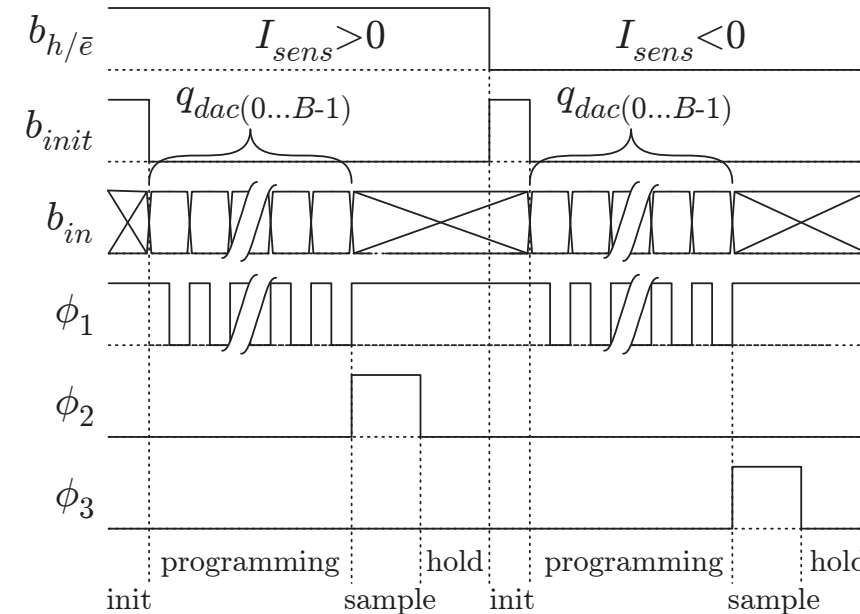▲ Reuse of ADC CMOS circuit for compact area





▲ Serially **program-in** during read-out (no speed reduction)

▲ Gain **FPN** compensation

▲ Also for **built-in test** through input charge injection...

Individual-Pixel Gain Programmability


► In-pixel SC DAC circuit:

 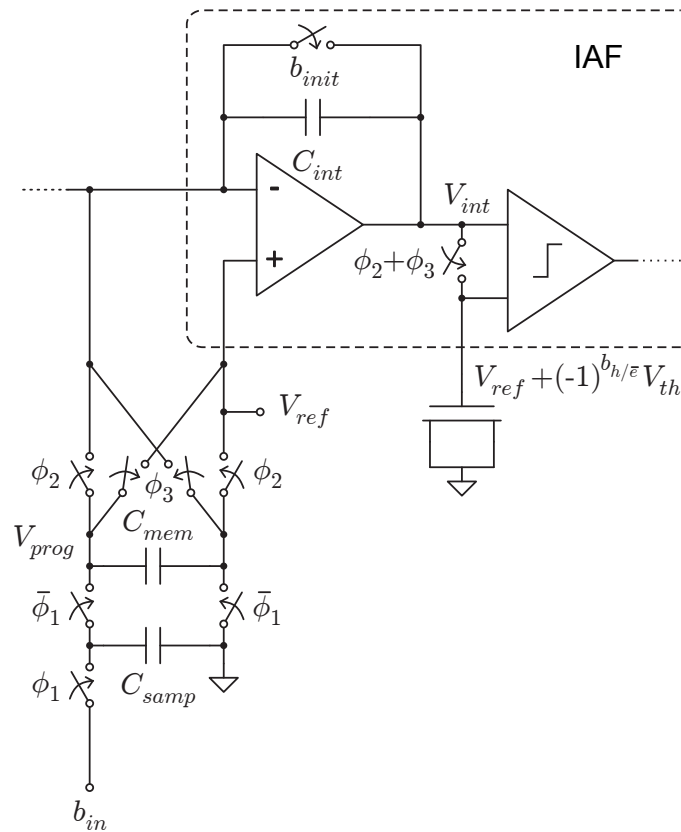

DPS CMOS Integration

- ▶ 1.8V 0.18 μm 1P6M CMOS technology
- ▶ **Pitch** evolution:
100 μm (Gen-1),
70 μm (Gen-2)
and 55 μm (Gen-3)


Parameter	Value	Units
I_{bias}	450	nA
V_{ref}	760	mV
C_{int}	85	fF
$C_{reset/CDS}$	85	fF
C_{mem}	85	fF
C_{samp}	85	fF
V_{th}	40 to 400	mV
T_{reset}	0.5	μs
N	10 to 12	bit

 

DPS CMOS Integration

- ▶ 1.8V 0.18 μm 1P6M CMOS technology
- ▶ **Pitch** evolution:
100 μm (Gen-1),
70 μm (Gen-2)
and 55 μm (Gen-3)

Parameter	Value	Units
I_{bias}	450	nA
V_{ref}	760	mV
C_{int}	85	fF
$C_{reset/CDS}$	85	fF
C_{mem}	85	fF
C_{samp}	85	fF
V_{th}	40 to 400	mV
T_{reset}	0.5	μs
N	10 to 12	bit

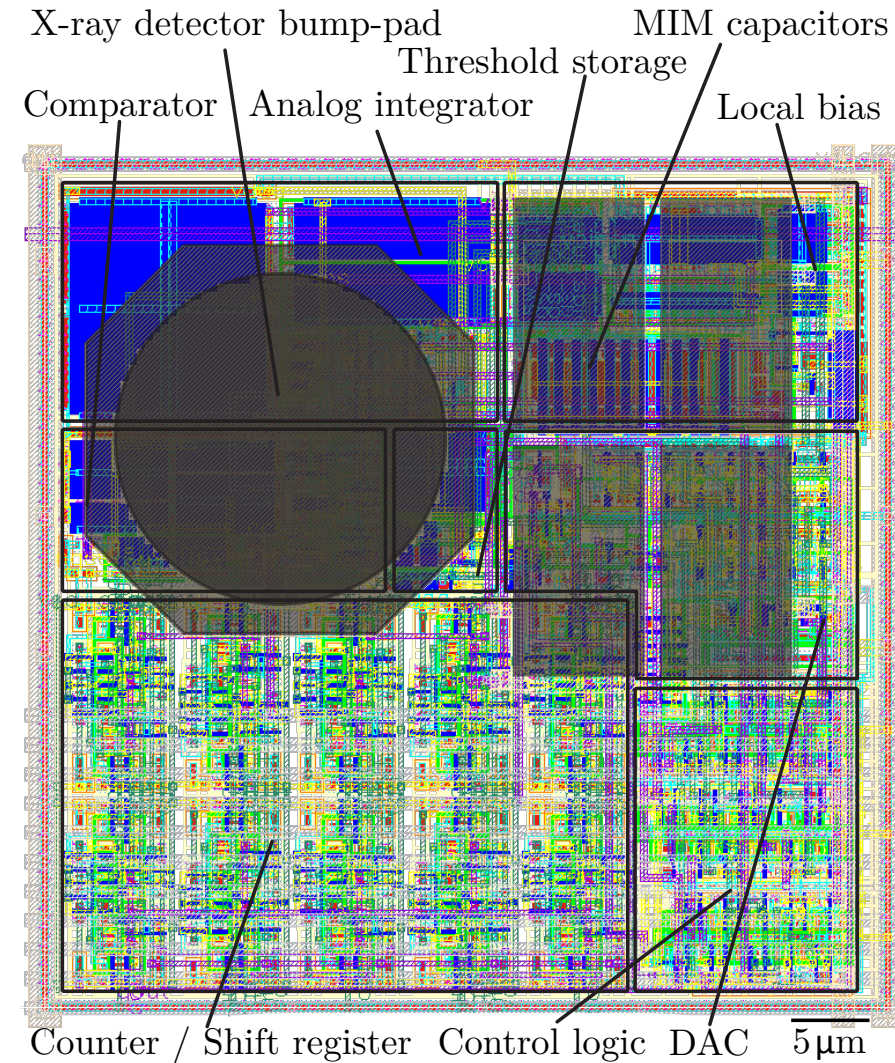




DPS CMOS Integration

- ▶ 1.8V 0.18 μm 1P6M CMOS technology
- ▶ **Pitch** evolution:
100 μm (Gen-1),
70 μm (Gen-2)
and 55 μm (Gen-3)

Parameter	Gen-1	Gen-2	Gen-3	Units
Supply voltage	1.8	1.8	1.8	V
Reference voltage	650	815	830	mV
Biasing current	270	550	500	nA
Bias mismatching	< 10	< 10	< 15	%
Typical transfer gain	1/50	1/50	1/50	LSB/ ke^-
Full scale	> 10	> 10	> 10	nA
Integration time	1 to 1000	1 to 1000	1 to 1000	ms
Output dynamic range	10	10	12	bit
Digital I/O speed	> 50	> 60	100	Mbps
PDM pulses frequency	600	600	800	kHz
Dark current range	up to 20	up to 20	N.A.	nA
Compensated dark current	95	95	N.A.	%
Equivalent noise charge	< 2	< 2	< 2	ke^-_{rms}
Crosstalk	no	no	no	
Static power consumption	5	8	6	μW
Integrating capacitor	100	100	100	fF
Silicon area	100 \times 100	70 \times 70	55 \times 55	$\mu\text{m} \times \mu\text{m}$



X-Ray Test ICs

   - ▶ **Small arrays** of DPS cells in standard UMC 0.18 μm 1P6M MIM CMOS technology
- ▶ **Si pixelated detectors** in inexpensive IMB-CNM(CSIC) 2.5 μm 2P1M PIP CMOS technology




X-Ray Test ICs

  ▲ **Good DPS** results in terms of maximum SNDR, FPN reduction, spatial resolution, crosstalk...



True 2D Modular X-Ray Imagers


 
- ▶ Array of read-out ICs attached to **seamless** pixelated detector substrate:



- ▲ Final goal is to reduce **CMOS costs** for large area imagers...

True 2D Modular X-Ray Imagers

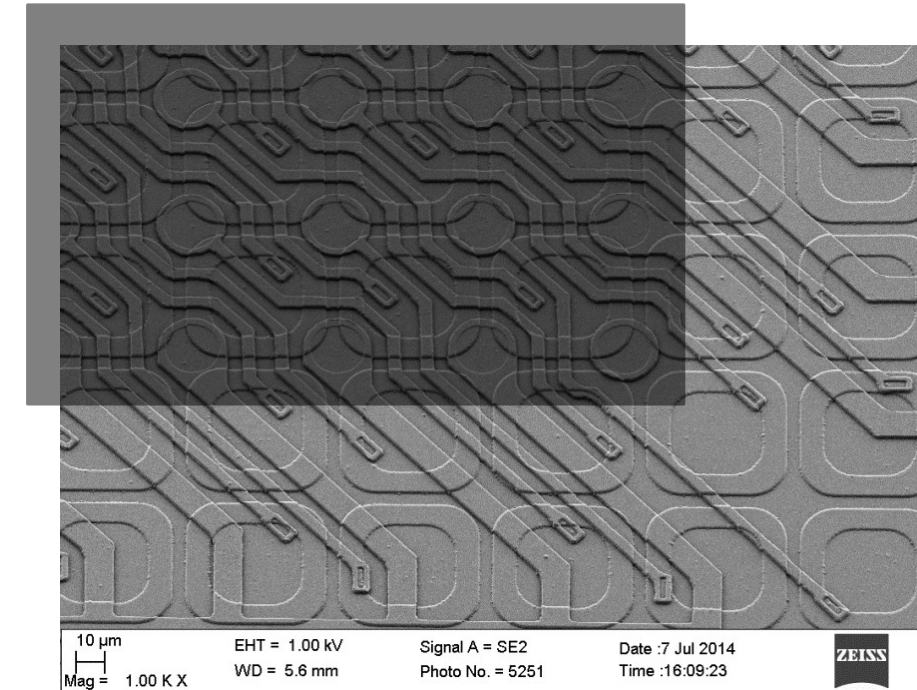 - Array of read-out ICs attached to **seamless** pixelated detector substrate:




▲ Pixel detector-to-circuit **rerouting**

▼ Inter-pixel **crosstalk?**

True 2D Modular X-Ray Imagers



► CMOS ROIC module

 - 94x94 pixel (5mmx 5mm)
- 52 μ m-pitch
- 6 μ W/pix at 1.8V



True 2D Modular X-Ray Imagers

  - ▶ 55 μm -pitch **seamless arrays** of pixelated Si detectors in 4-inch wafers:



- R. Figueras et al.
A 70- μm Pitch 8- μW Self-Biased Charge-Integration Active Pixel for Digital Mammography
IEEE Transactions on Biomedical Circuits and Systems, 5:5(481-489), Oct 2011
doi.org/10.1109/TBCAS.2011.2151192
- R. Figueras et al.
Experimental Characterization of a 10 μW 55 μm -pitch FPN-Compensated CMOS Digital Pixel Sensor for X-ray Imagers, Elsevier Nuclear Instruments and Methods in Physics Research A, 761(19-27), Oct 2014
doi.org/10.1016/j.nima.2014.05.085

- 1 High-Resolution SC Delta-Sigma ADC
for Space Applications
- 2 Compact Pixel Integrating ADC
for X-Ray Imagers
- 3 Low-Power Potentiostatic CT Delta-Sigma ADC
for Electrochemical Integrated Sensors

Smart Electrochemical Sensors



► Integrated chemical sensors:



- Interaction with microorganisms
- Selectivity by functionalization
- Speed limitation
- Reduced life time
- Packaging costs

► Electrochemical family:

- CMOS compatible
- **Potentiostatic** biasing
- **Amperometric** reading




▼ **Classic** circuit interfaces require multiple OpAmps + resistors + ADC

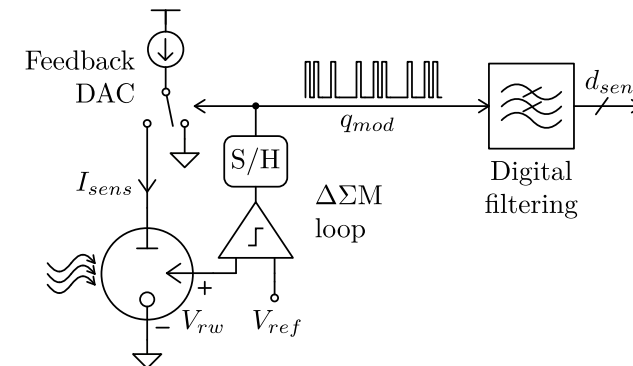 ▲ **Low-power MOS-only** circuit proposal based on mixed electronic and chemical domain potentiostatic $\Delta\Sigma$ modulator




Sensor Modeling

- ▶ Reuse of **sensor dynamics** for circuit design needs accurate device modeling!
- ▶ **Reference**, **Working** and **Counter** planar microelectrodes
- ▶ Non-linear electrical impedance model under **potentiostatic** operation:
 - R_s = electrolyte solution resistance
 - R_{ctx} = charge-transfer resistance
 - C_{dlx} = double-layer capacitance
- ▲ **Solution resistance** smaller than electrode-solution counterparts ($10^2 k\Omega$)
- ▲ Similar impedance results with internal (micro) and external (macro) **counter microelectrodes**
- ▲ Simplified linear **dynamic model**

   

$\Delta\Sigma$ Modulator Architecture

- ▶ Behavior similar to **low-pass first-order single-bit CT $\Delta\Sigma$ A/D modulator**
- ▶ Error current is converted into voltage and shaped in frequency by the **electrochemical sensor** itself
- ▶ Quantization, S/H and DAC feedback in **electronic domain**
- ▲ **Amperometric** read-out through the $\Delta\Sigma$ modulation of output bit stream q_{mod} by chemical input I_{in}
- ▲ Overall negative feedback ensures **potentiostatic** operation by keeping V_{rw} biased closed to V_{ref} potential
- ▲ High oversampling ratios (**OSR > 100**) can be easily obtained with kHz-range clock frequencies f_s



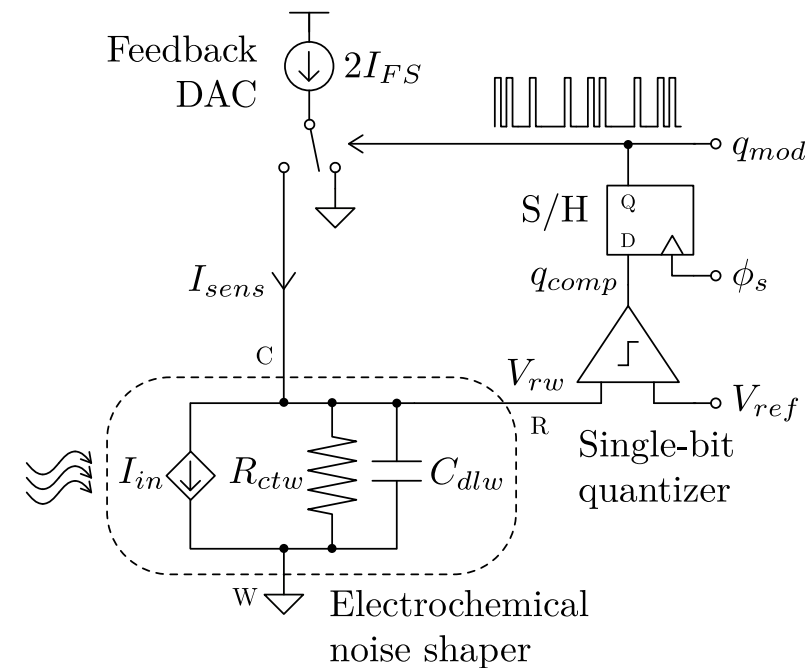


Class-A full scale:
$$I_{FS} = \frac{V_{ref}}{R_{ctw}}$$

Electrochemical time constant:
$$\tau_{ch} = R_{ctw}C_{dlw} \sim 10^{-1}s$$

$\Delta\Sigma$ Modulator Optimization

  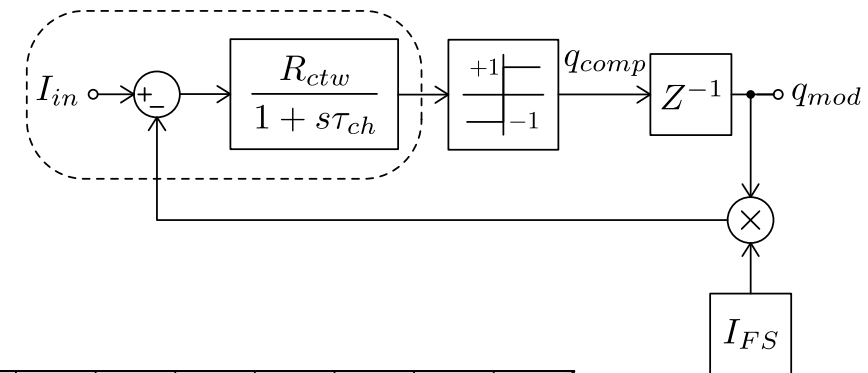- ▼ Typical **tonal components** of first-order $\Delta\Sigma$ modulation are attenuated through **thermal noise dithering** at DAC
- ▼ Fractal **staircase** DC transfer function due to DT losses of CT electrochemical integrator is improved by **increasing OSR**




e.g. $\Delta\Sigma$ M behavioral simulation for $R_{ctw}=500\text{k}\Omega$, $\tau_{ch}=0.16\text{s}$, $V_{ref}=1\text{V}$ and $I_{FS}=2\mu\text{A}$


Low-Power MOS-Only Circuits

▲ Two analog blocks only

 ► Latched comparator for 1-bit quantization:



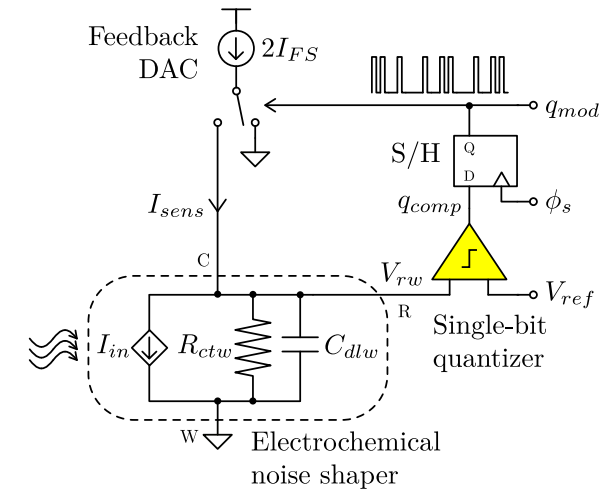
- **Technology mismatching** does not cause distortion but DC offset at V_{rw}
- If V_{ref} is chosen higher than redox potential, electrochemical signals can tolerate comparator **offsets** as large as $\pm 10\text{mV}$



Low-Power MOS-Only Circuits




▲ Two analog blocks only

 ► Latched comparator for 1-bit quantization:



- **Technology mismatching** does not cause distortion but DC offset at V_{rw}
- If V_{ref} is chosen higher than redox potential, electrochemical signals can tolerate comparator **offsets** as large as $\pm 10\text{mV}$

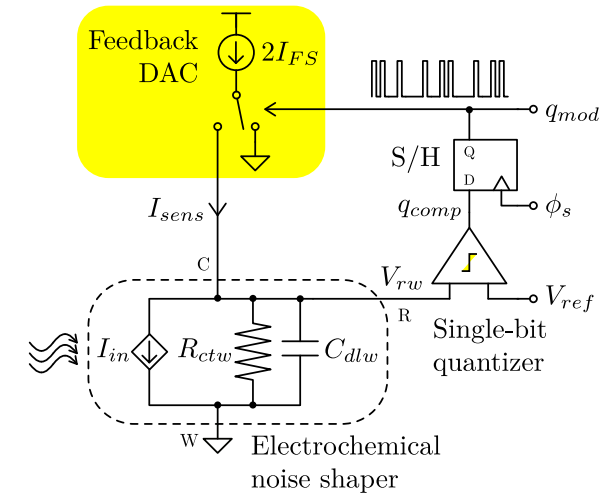  ► Compact reference generator for current DAC:




- **Programmable full scale** for different integrated sensor designs
- **Power in/off** instead of current steering operation to reset all MOSFETs and reduce **flicker noise**
- **RTZ** signaling in order to avoid typical waveform asymmetries issues of CT $\Delta\Sigma$ Ms

➤ F. Serra-Graells and J. L. Huertas
Sub-1V CMOS Proportional-to-Absolute-Temperature References
 IEEE J. Solid-State Circuits, 38:1(84-88), Jan 2003
doi.org/10.1109/JSSC.2002.806258



Monolithic CMOS Integration

- ▶ Inexpensive 2.5 μm 1M CMOS technology (**CNM25**)
- ▶ In-house **sensor post-processing** at wafer level consisting on sputtering of Ti(15nm)+Au(150nm) thin films and lithographic patterning by lift-off
- ▶ **Sensor layout** design: $D_{\text{in}}=390\mu\text{m}$, $D_{\text{out}}=830\mu\text{m}$ and $S=30\mu\text{m}$
- ▶ **Sensor electrical** model: $R_{\text{ctw}}=500\text{k}\Omega$ and $\tau_{\text{ch}}=0.16\text{s}$
- ▶ **$\Delta\Sigma\text{M}$** design parameters: $V_{\text{ref}}=1\text{V}$, $I_{\text{FS}}=2\mu\text{A}$ and $f_{\text{S}}=1024\text{Hz}$ (OSR=512)
- ▲ **Low-area** overhead of proposed $\Delta\Sigma\text{M}$
- ▲ **Digital-only interface** for low-pass filtering + V_{ref} and I_{FS} programming

 





Electrical Tests

  - ▶ **Sensor emulation** with external network ($R_{ctw}=500\text{k}\Omega$, $C_{dlw}=330\text{nF}$) and SRS DS360 generator in equivalent Thévenin configuration
- ▲ Although dithering noise at DAC should be increased, PSD returns good **robustness** against tones





Electrical Tests

- ▶ **Sensor emulation** with external network ($R_{ctw}=500k\Omega$, $C_{dlw}=330nF$) and SRS DS360 generator in equivalent Thévenin configuration
- ▲ Although dithering noise at DAC should be increased, PSD returns good **robustness** against tones
- ▲ Quasi-static response shows high enough **SNDR** to not limit electrochemical sensor resolution
- ▲ **Statistical analysis** on 9 samples returns DR deviations below $\pm 0.5\text{bit}$
- ▲ Experimental comparison between **power-on/off** and current steering DAC operation points to 3dB flicker noise reduction

    

Electrochemical Tests

  - ▶ **Standard experiment** based on ferrocyanide ion oxidation into ferricyanide:
- ▶ **10 μ L reservoir** with ferrocyanide dissolved in Phosphate buffer solution (PBS) at pH=7
- ▶ **Ion concentration** swept from 0.1mM to 1mM and **potentiostatic** $V_{\text{ref}}=0.7\text{V}$
- ▲ Electrochemical **time constant** as expected...



Electrochemical Tests

- ▲ Remarkable **linearity** below 1mM
- ▲ Comparable to lab **desktop equipment**
- ▲ Good **performance** for sensing applications
- ▲ Very **low-power** operation compared to sensor consumption itself (can improve with low-voltage CMOS technologies)

Parameter	Value	Units
Full scale range	2 to 32	μA
Potential range	0 to 5	V
Sampling frequency	1	kHz
Oversampling ratio	≥ 256	
Electrical dynamic range	> 10	ENOB
Residual standard deviation ($n=6$)	< 15	%
Coefficient of determination (R^2)	0.9985	
Supply voltage	5	V
Power consumption at $2\mu\text{A}_{\text{FS}}$	25	μW
Die size	2.3×2.8	mm^2

S. Sutula, et al.
 A 25- μW All-MOS Potentiostatic Delta-Sigma ADC
 for Smart Electrochemical Sensors
 IEEE Transactions on Circuits and Systems-I, 61:3(671-679), Mar 2014
doi.org/10.1109/TCSI.2013.2284179

